

Circuit Analysis with Phasors

With phasors, you can also analyze electrical circuits. For a resistor

$$V = IR$$

For an inductor

$$V = L \frac{dI}{dt}$$

Using phasors, differentiation becomes multiplication by $j\omega$

$$V = (j\omega L)I$$

so inductors look like resistors with an impedance of $j\omega L$. For a capacitor

$$I = C \frac{dV}{dt}$$


$$I = Cj\omega V$$

$$V = \left(\frac{1}{j\omega C} \right) I$$

Capacitors look like resistors with an impedance of $\left(\frac{1}{j\omega C} \right)$. Using this we can analyze AC circuits just like we analyze DC circuits, only with complex numbers. In summary

Component	Impedance	Impedance
Input	e^{st}	$e^{j\omega t}$
R	R	R
L	Ls	$j\omega L$
C	$1 / Cs$	$1 / j\omega C$

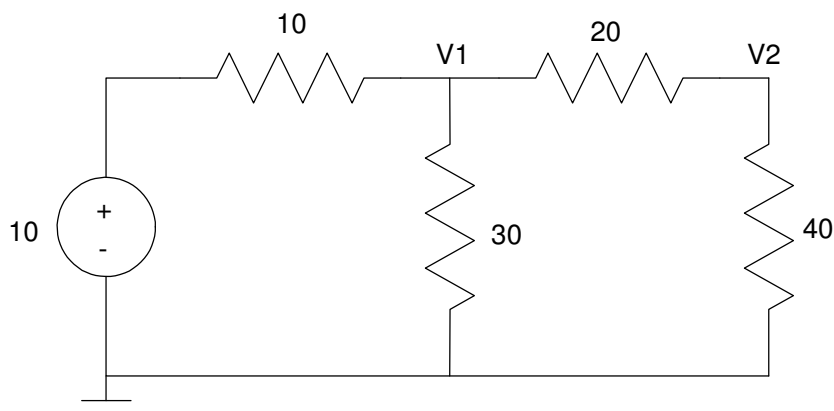For example, find the voltages for the following circuit (EE 206 example: DC circuit)



Using voltage nodes, the nodal equations would be

$$\left(\frac{V_1-10}{10}\right) + \left(\frac{V_1}{30}\right) + \left(\frac{V_1-V_2}{20}\right) = 0$$

$$\left(\frac{V_2-V_1}{20}\right) + \left(\frac{V_2}{40}\right) = 0$$

Grouping terms

$$\left(\frac{1}{10} + \frac{1}{30} + \frac{1}{20}\right) V_1 - \left(\frac{1}{20}\right) V_2 = \left(\frac{1}{10}\right) 10$$

$$\left(\frac{1}{20} + \frac{1}{40}\right) V_2 - \left(\frac{1}{20}\right) V_1 = 0$$

Placing in matrix form

$$\begin{bmatrix} \left(\frac{1}{10} + \frac{1}{30} + \frac{1}{20}\right) & \left(\frac{-1}{20}\right) \\ \left(\frac{1}{20}\right) & \left(\frac{1}{20} + \frac{1}{40}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \left(\frac{10}{10}\right) \\ 0 \end{bmatrix}$$

Solving 2 equations for 2 unknowns in Matlab:

```
-->A = [1/10+1/30+1/20, -1/20 ; -1/20, 1/20+1/40]
```

```
    0.18333333   - 0.05
   - 0.05         0.075
```


```
-->B = [1;0]
```

```
    1.
    0.
```

```
-->inv(A) *B
```

```
V1    6.6666667
V2    4.4444444
```

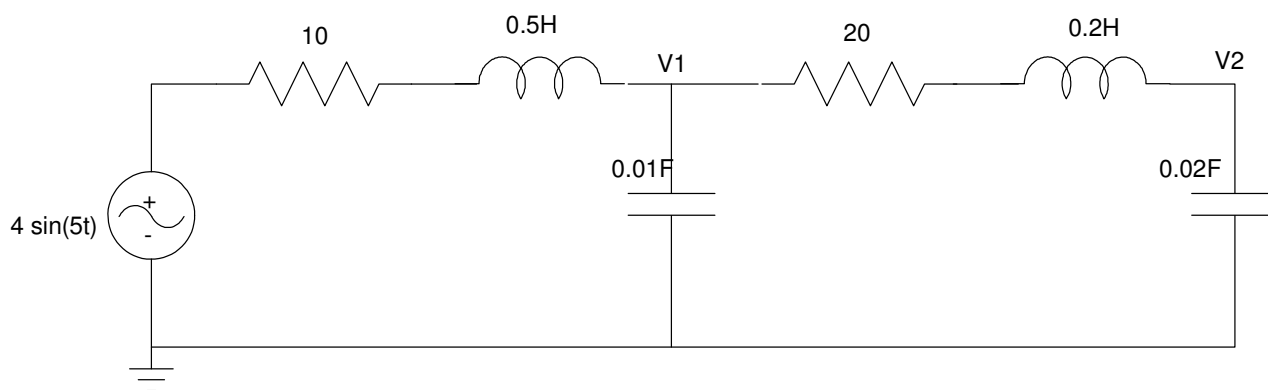Now find the voltages for the following circuit



Step 1: Convert to phasor notation. The input becomes

$$4 \sin(5t) \rightarrow 0 - j4$$


The resistors remain unchanged. The inductors become

$$L \rightarrow j\omega L$$

where ω is 5 rad/sec. The capacitors become

$$C \rightarrow \frac{1}{j\omega C}$$

This results in

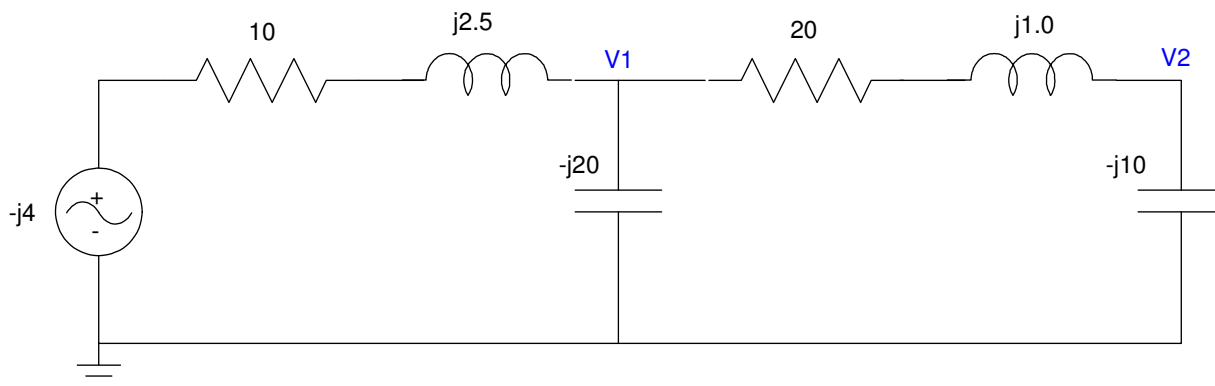

Now write the voltage node equations just like before

$$\left(\frac{V_1 - (-j4)}{10 + j2.5} \right) + \left(\frac{V_1}{-j20} \right) + \left(\frac{V_1 - V_2}{20 + j1} \right) = 0$$

$$\left(\frac{V_2 - V_1}{20 + j1.0} \right) + \left(\frac{V_2}{-j10} \right) = 0$$

Group terms

$$\left(\frac{1}{10 + j2.5} + \frac{1}{-j20} + \frac{1}{20 + j1} \right) V_1 - \left(\frac{1}{20 + j1} \right) V_2 = \left(\frac{-j4}{10 + j2.5} \right)$$

$$\left(\frac{-1}{20 + j} \right) V_1 + \left(\frac{1}{20 + j} + \frac{1}{-j10} \right) V_2 = 0$$

Place in matrix form

$$\begin{bmatrix} \left(\frac{1}{10 + j2.5} + \frac{1}{-j20} + \frac{1}{20 + j1} \right) & \left(\frac{-1}{20 + j1} \right) \\ \left(\frac{-1}{20 + j1} \right) & \left(\frac{1}{20 + j} + \frac{1}{-j10} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \left(\frac{-j4}{10 + j2.5} \right) \\ 0 \end{bmatrix}$$

Solve in Matlab

```
-->a11 = 1/(10+j*2.5)-1/(j*20)+1/(20+j);
-->a12 = -1/(20+j);
-->a21 = -1/(20+j);
-->a22 = 1/(20+j) + 1/(-j*10);
```

```

-->A = [a11, a12 ; a21, a22]
      0.1439930 + 0.0239768i  - 0.0498753 + 0.0024938i
      - 0.0498753 + 0.0024938i  0.0498753 + 0.0975062i

-->B = [-j*4/(10+j*2.5) ; 0]
      - 0.0941176 - 0.3764706i
      0

-->V = inv(A)*B

V1 - 1.4559151 - 2.2895748i
V2 - 1.2244227 + 0.1769673i

```


meaning

$$V_1(t) = -1.4559 \cos(5t) + 2.289 \sin(5t)$$

$$V_2(t) = -1.224 \cos(5t) - 0.176 \sin(5t)$$

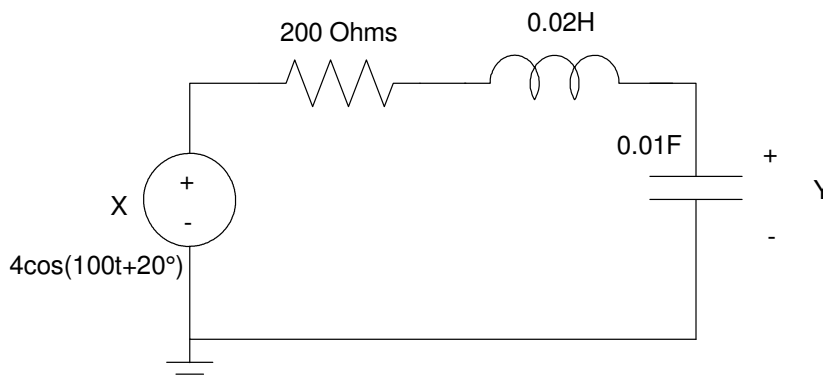Example 3) Voltage Division

Everything we did in EE 206 for DC analysis also works for AC circuits - only with complex numbers. For example, use voltage division to find $y(t)$:



First, convert to phaser notation. For this forcing function, $x(t)$,

$$s = j100$$

Change the input to phaser notation:


$$X = 4\angle 20^\circ$$

Change RLC to phaser impedances:

$$R \rightarrow R = 200\Omega$$

$$L \rightarrow Ls = j2\Omega$$
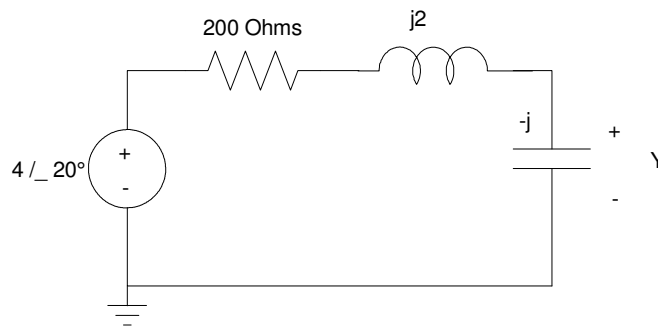
$$C \rightarrow \frac{1}{Cs} = -j\Omega$$



Now, solve using voltage division:

$$Y = \left(\frac{-j}{200 + 2j - j} \right) \cdot 4 \angle 20^\circ$$


$$Y = 0.02 \angle -70.3^\circ$$

$$y(t) = 0.02 \cos(100t - 70.3^\circ)$$


Note that these answers were *much* easier to obtain than before.

Example 4: Op-Amp Circuits

Find $y(t)$:

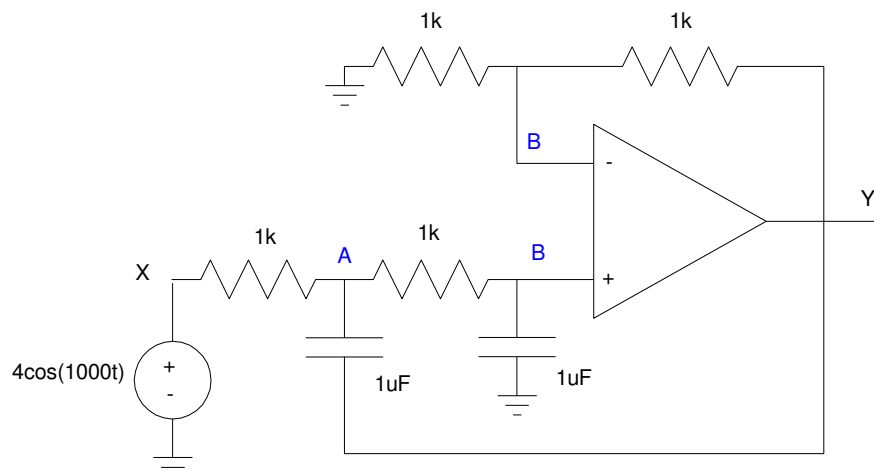

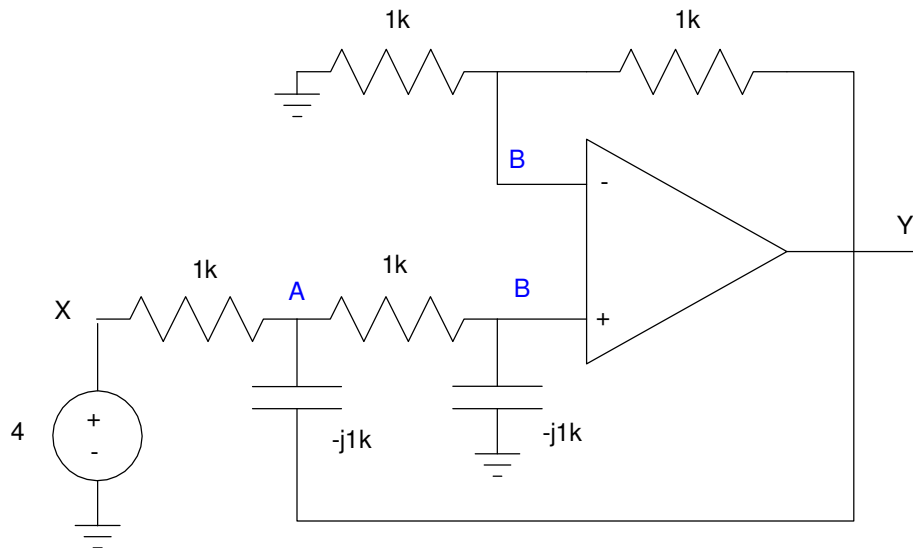First, convert to phasor notation. In this case, $s = j1000$



Next, write the voltage node equations:

$$A \quad \left(\frac{A-4}{1000} \right) + \left(\frac{A-Y}{-j1000} \right) + \left(\frac{A-B}{1000} \right) = 0$$

$$V- \quad \left(\frac{B-A}{1000} \right) + \left(\frac{B-0}{-j1000} \right) = 0$$

$$V+ \quad \left(\frac{B-0}{1000} \right) + \left(\frac{B-Y}{1000} \right) = 0$$

Note that you can't write a voltage node equation at Y. The op-amp puts out whatever current it takes to force $V- = V+$. Since you don't know this current, you can't sum the currents to zero. The fourth equation already incorporated in the above three is

$$V^+ = V^-$$

To make the numbers nicer, lets scale all three equations by 1000 and group terms:

$$A \quad (2+j)A + (-j)Y + (-1)B = 4$$

$$V- \quad (-1)A + (0)Y + (1+j)B = 0$$

$$V+ \quad (0)A + (-1)Y + (2)B = 0$$

Solving three equations for three unknowns (again using MATLAB):

$$\begin{aligned} \text{-->W} &= [2+j, -j, -1; -1, 0, 1+j; 0, -1, 2] \\ \bar{W} &= \end{aligned}$$

$$\begin{array}{ccc} 2. + i & - i & - 1. \\ - 1. & 0 & 1. + i \\ 0 & - 1. & 2. \end{array}$$

```
-->inv(W)*[4;0;0]
ans =
```

$$\begin{array}{l} V_a \quad 4. - 4.i \\ V_y \quad - 8.i \\ V_b \quad - 4.i \end{array}$$

The way I set up the problem, Y was the second column in the 3x3 matrix. Likewise, Y will be the second entry in the answer:

$$Y = -j8$$

and

$$y(t) = 8 \sin(1000t)$$