

## Circuit Analysis with LaPlace Transforms

### Background

Phasors allow you to analyze circuits with inductors and capacitors just like you analyze resistor circuits - the only difference is you need to use complex numbers. With phasor analysis, the basic assumption is that all functions are in the form of

$$x = a \cdot e^{j\omega t}$$

resulting in the phasor impedance for an inductor and capacitor being:

$$L \rightarrow j\omega L$$

$$C \rightarrow \frac{1}{j\omega C}$$

In contrast, LaPlace transforms assume all functions are in the form of

$$x(t) = a \cdot e^{st}$$

resulting in the LaPlace impedance being:

$$L \rightarrow Ls$$

$$C \rightarrow \frac{1}{Cs}$$

Component	Phasor Impedance	LaPlace Impedance
R	R	R
L	$j\omega L$	$Ls$
C	$1 / j\omega C$	$1 / Cs$

With LaPlace impedance's, everything that worked in Circuits I and II still apply:

- Impedance's in series add: A resistor, inductor, and capacitor in series have an impedance of:

$$Z = R + Ls + \frac{1}{Cs}$$

- Impedance's in parallel add as the sum of the inverses, inverted. A resistor, inductor, and capacitor in parallel have a total impedance of

$$Z = \left( \frac{1}{R} + \frac{1}{Ls} + \frac{1}{1/Cs} \right)^{-1}$$

- Current loops still work: The sum of the voltages around any closed path has to add to zero.
- Voltage nodes still work: The sum of the current from a node must add to zero.

There is a short-cut for analyzing electrical circuits using LaPlace transforms, however. This is to use a formulation called *state space*.

## State Space

One way to describe a dynamic system is with a transfer function:

$$Y = G(s) \cdot U$$

Another way is to put the system in matrix form (called state space). If the energy in the system is defined by vector  $X$  (think of  $X$  as the voltages on capacitors and current in inductors: things that define the energy in the system), then the change in energy along with the output as function of the system state can be written as

$$X' = AX + BU$$

$$Y = CX + DU$$


With state-space, there is a third way to input a dynamic system into Matlab:

$$G = ss(A, B, C, D);$$

It's probably easiest to explain this with examples.

## State-Space and Natural Responses

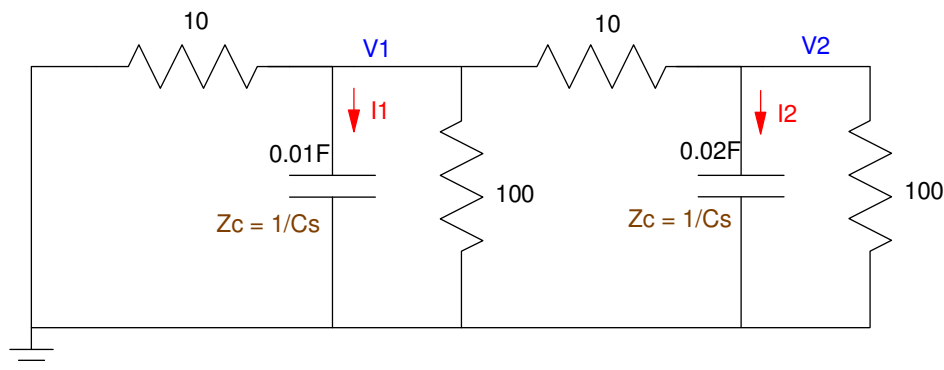**Example 1:** For the following circuit, find the voltage,  $y(t) = v_4(t)$  assuming  $v_1(0) = v_2(0) = 10$ .



2nd-Order System: (there are two energy storage elements)

Step 1: Define the system states.

This is the voltage across the capacitors and the current through inductors. This defines the energy in the system.

$$X = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Step 2: Define the change in energy in terms of the input (none here) and the system states

From the equations for a capacitor

$$i_c = C \frac{dv}{dt}$$

In the LaPlace domain:

$$I_c = C(sV - v(0))$$

Defining the current to each capacitor in terms of the states

$$I_1 = 0.01(sV_1 - v_1(0)) = \left(\frac{0-V_1}{10}\right) + \left(\frac{V_2-V_1}{10}\right) + \left(\frac{0-V_1}{100}\right)$$

$$I_2 = 0.02(sV_2 - v_2(0)) = \left(\frac{0-V_2}{100}\right) + \left(\frac{V_1-V_2}{10}\right)$$

Group terms:

$$sV_1 = -21V_1 + 10V_2 + v_1(0) \quad * 21$$

$$sV_2 = 5V_1 - 5.5V_2 + v_2(0) \quad * 5$$

Step 3: Solve for  $y = V_2$ . Place this in matrix (state-space form)

$$s \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -21 & 10 \\ 5 & -5.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + \begin{bmatrix} v_1(0) \\ v_2(0) \end{bmatrix}$$

$$Y = V_2 = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} + [0]$$

In Matlab:

```
>> A = [-21, 10 ; 5, -5.5]
```

```
   -21.0000    10.0000
     5.0000    -5.5000
```

```
>> B = [10 ; 10]
```

```
    10
    10
```

```
>> C = [0, 1];
```

```
>> D = 0;
```

```
>> Y = ss(A,B,C,D);
```


At this point you can solve for  $Y(s)$ :

```
>> zpk(Y)
```

$$Y(s) = \frac{10 (s+26)}{(s+23.74) (s+2.759)}$$

$y(t)$  is found using the impulse response function for  $Y(s)$
 
```
t = [0:0.01:5]';
y = impulse(Y, t);
plot(t, y)
```



$y(t)$  for initial conditions of  $v_1(0) = v_2(0) = 10$

**Eigenvalues and Eigenvectors:** The eigenvalues of matrix  $X$  are the poles of the system. This tells you how the system behaves

```
>> eig(A)

-23.7411
 -2.7589
```

The eigenvectors of  $A$  tell you what behaves each way:

```
>> [a,b] = eig(A)

a =
 -0.9644  -0.4807
  0.2644  -0.8769

b =
 -23.7411  0
  0       -2.7589
```


If the initial condition was  $\begin{bmatrix} -0.9644 \\ 0.2644 \end{bmatrix}$  (or a scalar multiple of this), then  $y(t)$  decays as  $e^{-23.74t}$

If the initial condition was  $\begin{bmatrix} -0.4807 \\ -0.8679 \end{bmatrix}$  (or a scalar multiple of this), then  $y(t)$  decays as  $e^{-2.7589t}$

To illustrate this, using the fast (first) eigenvector:

```
>> B = a(:,1)
-0.9644
 0.2644
 
>> Y = ss(A,B,C,D);
>> y = impulse(Y, t);
>> plot(t,y)
```




y(t) when the initial conditions are equal to the fast eigenvector

Using the slow (second) eigenvector:

```
>> B = -a(:,2)
 0.4807
 0.8769

 
>> Y = ss(A,B,C,D);
>> y = impulse(Y, t);
>> plot(t,y)
```



y(t) when the initial conditions are equal to the slow eigenvector

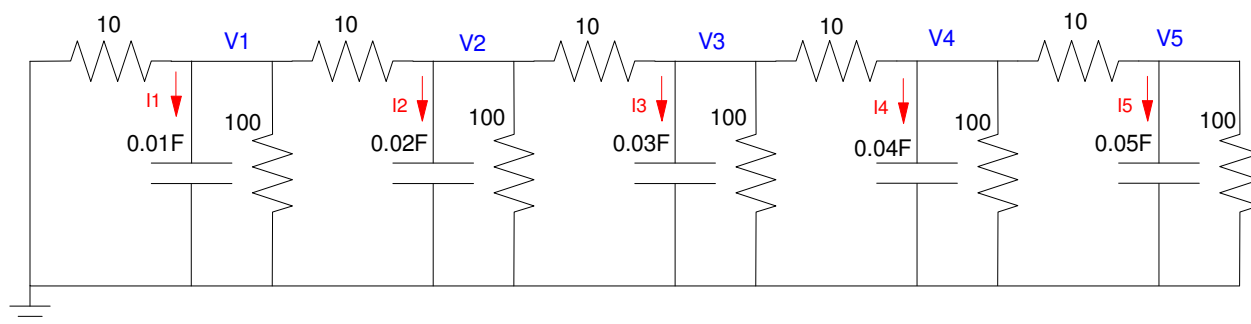**Example 2: 5-stage RC filter.**

Find  $V_5(t)$  if the initial condition is  $v_1(0) = v_2(0) = v_3(0) = v_4(0) = v_5(0) = 10V$



This is where state-space really shines. You could use voltage nodes or current loops and solve for  $V_5$ . That will take about two hours. It's much easier with state space.

Step 1: Define the state variables. The energy in the system is defined by

$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix}$$

Step 2: Define the change in the state variables in terms of the other states

$$I_1 = 0.01 \frac{dV_1}{dt} = 0.01(sV_1 - v_1(0)) = \left( \frac{0-V_1}{10} \right) + \left( \frac{0-V_1}{100} \right) + \left( \frac{V_2-V_1}{10} \right)$$

$$I_2 = 0.02 \frac{dV_2}{dt} = 0.02(sV_2 - v_2(0)) = \left( \frac{V_1-V_2}{10} \right) + \left( \frac{0-V_2}{100} \right) + \left( \frac{V_3-V_2}{10} \right)$$

$$I_3 = 0.03 \frac{dV_3}{dt} = 0.03(sV_3 - v_3(0)) = \left( \frac{V_2-V_3}{10} \right) + \left( \frac{0-V_3}{100} \right) + \left( \frac{V_4-V_3}{10} \right)$$

$$I_4 = 0.04 \frac{dV_4}{dt} = 0.04(sV_4 - v_4(0)) = \left( \frac{V_3-V_4}{10} \right) + \left( \frac{0-V_4}{100} \right) + \left( \frac{V_5-V_4}{10} \right)$$

$$I_5 = 0.05 \frac{dV_5}{dt} = 0.05(sV_5 - v_5(0)) = \left( \frac{V_4-V_5}{10} \right) + \left( \frac{0-V_5}{100} \right)$$

Solve for the derivative

$$sV_1 = -21V_1 + 10V_2 + v_1(0)$$

$$sV_2 = 5V_1 - 10.5V_2 + 5V_3 + v_2(0)$$

$$sV_3 = 3.33V_2 - 7V_3 + 3.33V_4 + v_3(0)$$

$$sV_4 = 2.5V_3 - 5.25V_4 + 2.5V_5 + v_4(0)$$

$$sV_5 = 2V_4 - 2.2V_5 + v_5(0)$$

Place in matrix form

$$s \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} -21 & 10 & 0 & 0 & 0 \\ 5 & -10.5 & 5 & 0 & 0 \\ 0 & 3.33 & -7 & 3.33 & 0 \\ 0 & 0 & 2.5 & -5.25 & 2.5 \\ 0 & 0 & 0 & 2 & -2.2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} v_1(0) \\ v_2(0) \\ v_3(0) \\ v_4(0) \\ v_5(0) \end{bmatrix}$$

$$Y = V_5 = \begin{bmatrix} 0 & 0 & 0 & 0 & 1 \end{bmatrix} V_{1..5} + [0]$$

Step 3: Find Y(s)

$$A = [-21, 10, 0, 0, 0 ; 5, -10.5, 5, 0, 0 ; 0, 3.333, -7, 3.333, 0 ; 0, 0, 2.5, -5.25, 2.5 ; 0, 0, 0, 2, -2.2]$$

$$\begin{array}{ccccc} -21.0000 & 10.0000 & 0 & 0 & 0 \\ 5.0000 & -10.5000 & 5.0000 & 0 & 0 \\ 0 & 3.3330 & -7.0000 & 3.3330 & 0 \\ 0 & 0 & 2.5000 & -5.2500 & 2.5000 \\ 0 & 0 & 0 & 2.0000 & -2.2000 \end{array}$$

$$B = [10; 10; 10; 10; 10]$$

$$\begin{array}{c} 10 \\ 10 \\ 10 \\ 10 \\ 10 \end{array}$$

$$C = [0, 0, 0, 0, 1];$$

$$D = 0;$$


$$Y = ss(A, B, C, D);$$

$$zpk(Y)$$

$$Y(s) = \frac{10 (s+24.75) (s+11.46) (s+6.061) (s+3.48)}{(s+24.76) (s+11.31) (s+6.601) (s+2.822) (s+0.4601)}$$

Step 4: Find  $y(t)$ .
 
```
t = [0:0.01:10]';
y = impulse(G,t);
plot(t,y)
```



Natural Response  $v_5(t)$  for initial condition of  $\{10, 10, 10, 10, 10\}$

Sidelight:

- Find the initial condition which decays as slow as possible.
- Find the initial condition which decays as slow as possible.

Solution: This is asking for the fast and slow eigenvector.

```
>> [a,b] = eig(A)
```

```
a =
-0.9339   -0.5296   -0.4249   -0.3229    0.1366
 0.3511   -0.5133   -0.6118   -0.5870    0.2807
-0.0675    0.6124   -0.0521   -0.5785    0.4269
 0.0088   -0.2780    0.6056   -0.1382    0.5570
-0.0008    0.0610   -0.2752    0.4443    0.6403
```

```
b =
-24.7599    0    0    0    0
 0 -11.3067    0    0    0
 0    0 -6.6013    0    0
 0    0    0 -2.8219    0
 0    0    0    0 -0.4601
```


- The slow eigenvector is in red. This mode decays as  $\exp(-0.46t)$
- The fast eigenvector is in blue. This mode decays as  $\exp(-24.76t)$



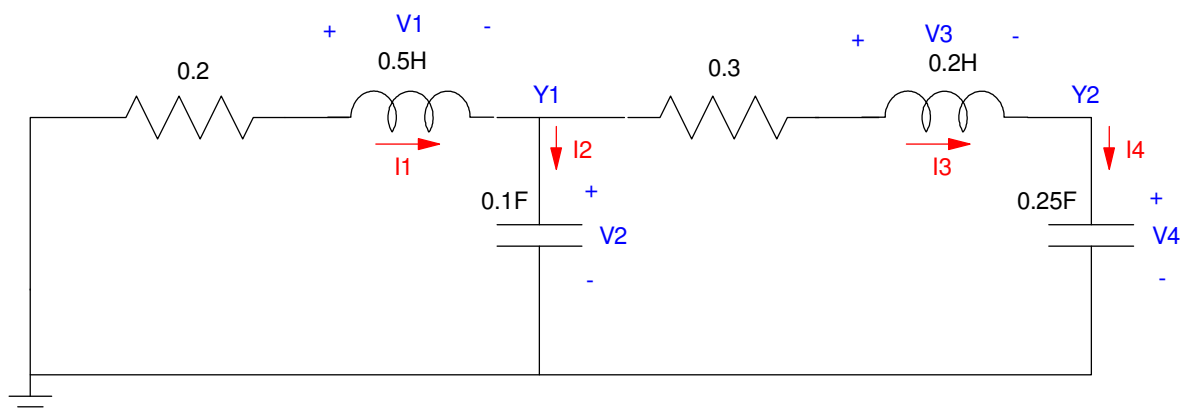**Example 3: RLC Circuit**

Find  $V_4(t)$  assuming

- $v_2(0) = v_4(0) = 10V$
- $i_1(0) = i_3(0) = 2A$



Solution: Use state-space (current loops or voltage nodes also work but state-space is easier if you have access to Matlab)

Step 1: Define the state variables. These define the energy in the system

$$X = \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix}$$

Step 2: Define the change in the states. This comes from

$$v = L \frac{di}{dt}$$

$$i = C \frac{dv}{dt}$$

which leads to

$$v_1 = 0.5 \frac{di_1}{dt} = 0.5(sI_1 - i_1(0)) = (0 - 0.2I_1) - V_2$$

$$i_2 = 0.1 \frac{dv_2}{dt} = 0.1(sV_2 - v_2(0)) = I_1 - I_3$$

$$v_3 = 0.2 \frac{di_3}{dt} = 0.2(sI_3 - i_3(0)) = V_2 - 0.3I_3 - V_4$$

$$i_4 = 0.25 \frac{dv_4}{dt} = 0.25(sV_4 - v_4(0)) = I_3$$

Step 3: Rewrite these equations as

$$sI_1 = -0.4I_1 - 2V_2 + i_1(0)$$

$$sV_2 = 10I_1 - 10I_3 + v_2(0)$$

$$sI_3 = 5V_2 - 1.5I_3 - 5V_4 + i_3(0)$$

$$sV_4 = 4I_3 + v_4(0)$$

Place in matrix form

$$s \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} -0.4 & -2 & 0 & 0 \\ 10 & 0 & -10 & 0 \\ 0 & 5 & -1.5 & -5 \\ 0 & 0 & 4 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix} + \begin{bmatrix} i_1(0) \\ v_2(0) \\ i_3(0) \\ v_4(0) \end{bmatrix}$$

$$Y = V_4 = \begin{bmatrix} 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ I_3 \\ V_4 \end{bmatrix} + [0]$$

Solve in Matlab

```
>> A = [-0.4,-2,0,0 ; 10,0,-10,0 ; 0,5,-1.5,-5 ; 0,0,4,0]
```

```

-0.4000    -2.0000         0         0
10.0000         0   -10.0000         0
         0     5.0000    -1.5000   -5.0000
         0         0     4.0000         0

```

```
>> B = [2 ; 10 ; 2 ; 10]
```

```

 2
10
 2
10

```

```
>> C = [0,0,0,1];
```

```
>> D = 0;
```


```
>> Y = ss(A,B,C,D);
```

```
>> zpk(Y)
```

$$Y(s) = \frac{10 (s+1.279) (s^2 + 1.421s + 89.1)}{(s^2 + 0.6102s + 4.7) (s^2 + 1.29s + 85.11)}$$

```
>> t = [0:0.01:10]';
```

```
>> plot(t,y)
```

 

$$y(t) = v4(t)$$

Just for fun,

- Find the initial conditions which make this system decay as slow as possible.
- Find the initial conditions which make this system decay as slow as possible.

Solution: Find the eigenvalues and eigenvectors

```
>> [m,v] = eig(A)
```

m =

```

0.0045 + 0.1696i    0.0045 - 0.1696i    0.0778 - 0.4519i    0.0778 + 0.4519i
0.7808              0.7808              -0.4887 - 0.0621i   -0.4887 + 0.0621i
0.0549 - 0.5490i   0.0549 + 0.5490i   0.0496 - 0.3489i   0.0496 + 0.3489i
-0.2391 - 0.0071i  -0.2391 + 0.0071i  -0.6503            -0.6503
```

v =

```

-0.6449 + 9.2031i    0          0          0
0                   -0.6449 - 9.2031i    0          0
0                   0          -0.3051 + 2.1463i    0
0                   0          0          -0.3051 - 2.1463i
```

Slow: Make the initial conditions equal to the slow eigenvector. This is complex, so you can use the real part (to get cosine) or imaginary part (to get sine).


```
X0 = imag(m(:,4))
```

```

 0.4519
0.0621
0.3489
0
```

```

Y = ss(A,X0,C,D);
y = impulse(Y, t);
plot(t,y)
```



$V_4(t)$  when the initial condition is equal to the slow eigenvector


**Fast:** Make the initial condition equal to the fast eigenvector. Again, use the real part for cosine, imaginary part for sine.

```
>> X0 = real( m(:,1) )
```

```
X0 =
```

```
0.0045  
0.7808  
0.0549  
-0.2391
```
 
```
>> Y = ss(A,X0,C,D);  
>> y = impulse(Y, t);  
>> plot(t,y)
```



$V_4(t)$  when the initial condition is equal to the fast eigenvector