

# ECE 376 - Homework #3

Binary Inputs, Outputs, and Timing. Due Monday, January 31st

Please make the subject "ECE 376 HW#3" if submitting homework electronically to Jacob\_Glower@yahoo.com (or on blackboard)

## Assembler Coding

1) Determine the content of the W register and memory locations A and B after each operation:

Command	W	A	B
<code>; Start</code>	7	8	9
<code>addwf B,F</code>	7	8	16
<code>incf A,W</code>	9	8	16
<code>subwf A,F</code>	9	255	16
<code>sublw 9</code>	0	255	16
<code>movlw 3</code>	3	255	16
<code>andwf A,F</code>	3	3	16
<code>iorwf B,W</code>	19	3	16

## Binary Inputs

Assume the resistance - voltage relationship for a thermistor is (T is temperature in Celsius)

$$R = 1000 \cdot \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

2) Design a circuit that output

- 0V for temperatures less than 35C
- 5V for temperatures more than 35C

Assume a 1k resistor in a voltage divider



At 35C:

- $R = 653 \text{ Ohms}$
- $V_x = 1.976V$

When the temperature goes up...

- R goes down
- $V_x$  goes down
- $V_y$  goes up to +5V

Connect to the minus input

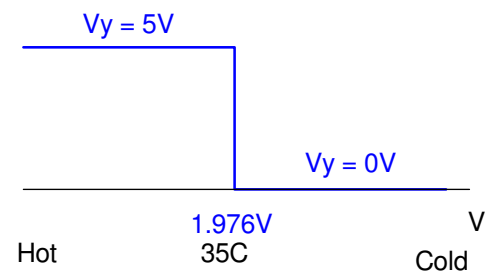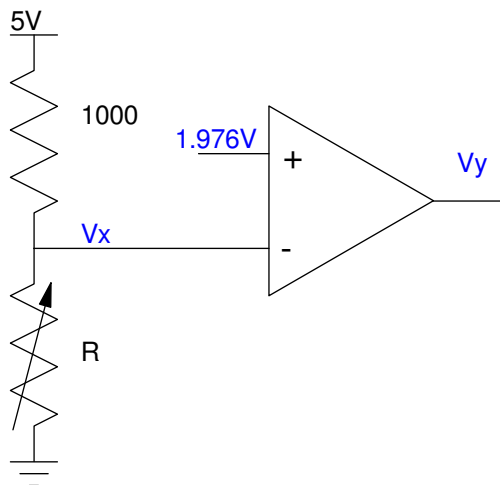

3) Design a circuit with hysteresis that outputs

- 0V when the temperature is less than 35C
- 5V when the temperature is more than 40C
- No change (0V or 5V) for temperatures inbetween 35C and 40C

At 35C:

- $R = 653 \text{ Ohms}$
- $V_x = 1.976V$
- $V_y = 0V$

At 40C



- $R = 533.66 \text{ Ohms}$
- $V_x = 1.740V$
- $V_y = 5V$

As  $V_x$  goes down,  $V_y$  goes up. Connect to the minus input.

$V_y$  becomes 5V when  $V_x$  is 1.740V. Make the offset 1.740V

The gain needed is
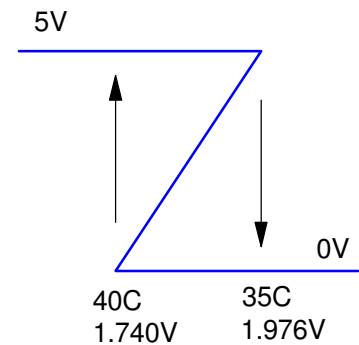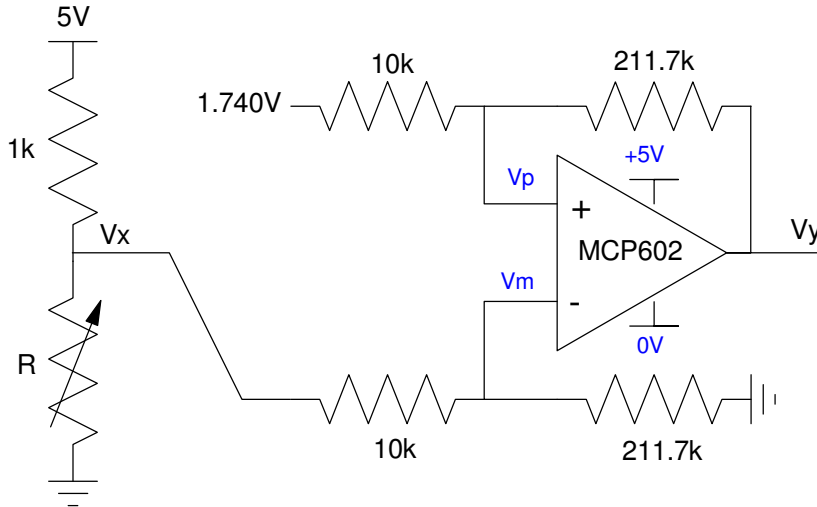
$$gain = \left( \frac{\text{change in } V_y}{\text{change in } V_x} \right) = \left( \frac{5V - 0V}{1.976V - 1.740V} \right) = 21.17$$



## Binary Outputs

4) Design a circuit which allows your PIC board to turn on and off an RGB Piranha LED at 0mA (off) and 20mA (on). Assume the specifications for the LEDs are:

Color	V <sub>f</sub> @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

Since the PIC is driving a load that needs


- Less than 5V and
- Less than 25mA

a PIC can drive the load directly using only a resistor to limit the current:

$$R_r = \left( \frac{5V - 2.0V}{20mA} \right) = 150\Omega$$

$$R_g = \left( \frac{5V - 3.2V}{20mA} \right) = 90\Omega$$
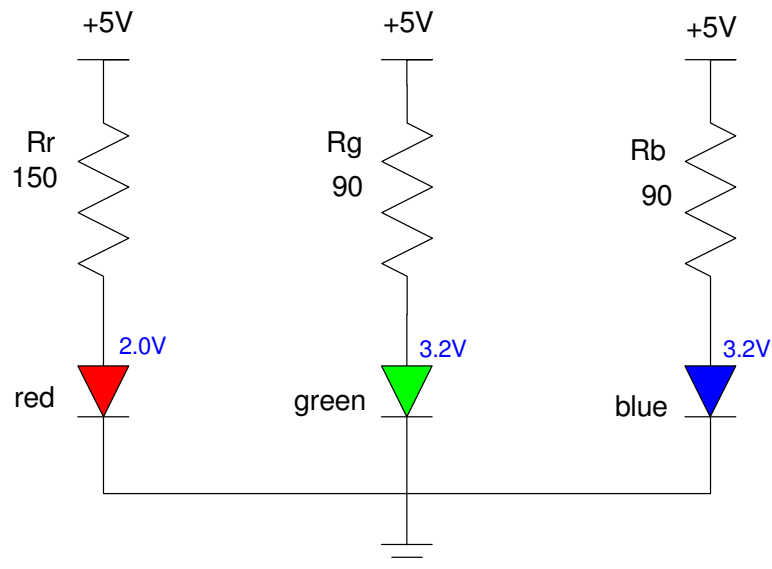
$$R_b = \left( \frac{5V - 3.2V}{20mA} \right) = 90\Omega$$



5) Design a circuit which allows your PIC board to turn on and off a 1W LED. The specs for the LED are:

- $V_f = 3.2 - 3.6V$
- Current = 350mA
- 100 Lumens (equivalent to a 10W light bulb).

<https://www.ebay.com/itm/1W-3W-5W-10W-50W-100W-High-power-SMD-Chip-LED-COB-White-Blue-Red-Light-Beads/124011607823>

In this case, you need a transistor since the current is more than a PIC can output. Assume a 6144 NPN transistor.


- $\beta = 100$  *worst case*
- $V_{ce}(sat) = 0.2V$

$$R_c = \left( \frac{5V - 3.4V}{350mA} \right) = 4.57\Omega$$

$$I_b > \frac{I_c}{\beta} = \frac{350mA}{100} = 3.5mA$$

Let  $I_b = 10mA$
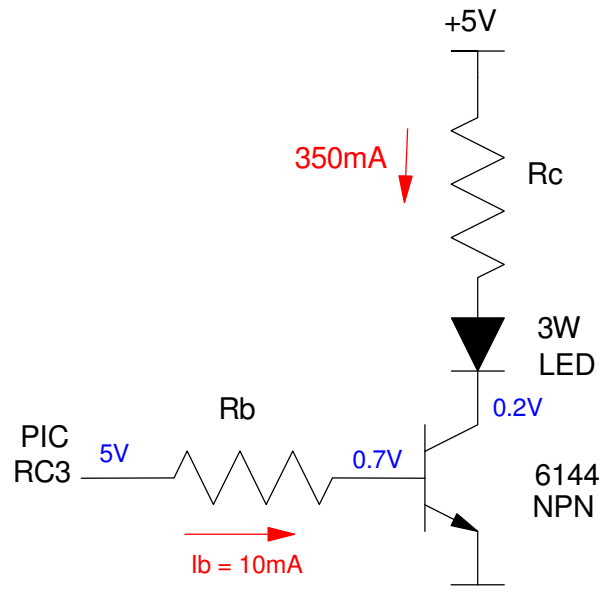
$$R_b = \left( \frac{5V - 0.7V}{10mA} \right) = 430\Omega$$



## Timing:

6) Write a program which outputs the music note D3# (155.56 Hz)

- Verify the frequency of the square wave you generate
- (Pano Tuner app on you cell phone works well for this)

The number of clocks per toggle (the timing for the wait loop) is

$$N = \left( \frac{10,000,000}{2 \cdot Hz} \right) = 32,141.939$$

Come up with a wait loop that burns 32,141 clocks:

$$N = 10 \cdot A \cdot B + 5 \cdot A + 9 = 32,141$$

$$A = 13, B = 247 \text{ results in } N = 32,184 \text{ (off by 0.131\%)}$$

```
#include <p18f4620.inc>

; Variables
CNT0 EQU 1
CNT1 EQU 2

; Program
    org 0x800
    call Init
Loop:
    incf PORTC,F
    call Wait      ; Play note D#2
    goto Loop

; --- Subroutines ---

Init:
    clrf TRISA
    clrf TRISB
    clrf TRISC
    clrf TRISD
    clrf TRISE
    movlw 0x0F
    movwf ADCON1 ;everyone is binary
    return

; Wait 32,141 clocks (actual wait = 32,184)
Wait:
    movlw 13      ; A
    movwf CNT1
W1:
    movlw 247     ; B
    movwf CNT0
W0:
    nop          ; 10 clocks
    nop
    nop
    nop
    nop
    nop
    nop
    decfsz CNT0, F
    goto W0
    decfsz CNT1, F
    goto W1
    return
```

## Lab:

### 7) Requirements:

- Inputs: Buttons on RB0 / RB1 / RB2 / RB3
- Outputs: RC0
- Relationship: Output a square wave on RC0 based upon the button pressed:
  - RB0: 261 Hz (C4)
  - RB1: 293 Hz (D4)
  - RB2: 329 Hz (E4)
  - RB3: 349 Hz (F4)

8) Analysis, Code, and Flow Chart. Give computations for resistor values (if any), timing, assembler code, and a flow chart for your code

The number of clocks needed for each note are:

$$N = \left( \frac{10,000,000}{2 \cdot \text{Hz}} \right)$$

N is created using a series of loops:

$$N = 100AB + 5B + 5$$

261Hz:

- $N = 19,157$
- $A = 100, B = 19$

293 Hz:

- $N = 17,026$
- $A = 100, B = 17$

329 Hz

- $N = 15,167$
- $A = 100, B = 15$

349 Hz

- $N = 14,317$
- $A = 100, B = 14$

```

; --- Piano4.asm ---
; When you press button RB0..RB3, you play a note
; on RC0:
;   RB0:  291 Hz (C4)
;   RB1:  293 Hz (D4)
;   RB2:  329 Hz (E4)
;   RB3:  349 Hz (F4)

```

```

#include <p18f4620.inc>

```

```

; Variables
CNT0 EQU 1
CNT1 EQU 2

```

```

; Program
org 0x800
call Init
Loop:
    movlw 0
    cpfseq PORTB ; if any button is pressed
    btg    PORTC,0

    btfsc PORTB,0
    call  C4
    btfsc PORTB,1
    call  D4
    btfsc PORTB,2
    call  E4
    btfsc PORTB,3
    call  F4

    goto Loop

```

```

; --- Subroutines ---

```

```

Init:
    clrf TRISA      ;PORTA is output
    movlw 0xFF
    movwf TRISB     ;PORTB is input
    clrf TRISC      ;PORTC is output
    clrf TRISD      ;PORTD is output
    clrf TRISE      ;PORTE is output
    movlw 15
    movwf ADCON1     ;everyone is binary
    return

```

```

C4:  ; 261Hz = 19,157 clocks
    movlw 19
    movwf CNT1

```

```


C4a:
    movlw 100
    movwf CNT0

```

```

C4b:
    nop
    nop
    nop
    nop
    nop
    nop
    nop
    decfsz CNT0, F
    goto C4b
    decfsz CNT1, F
    goto C4a
    return

```

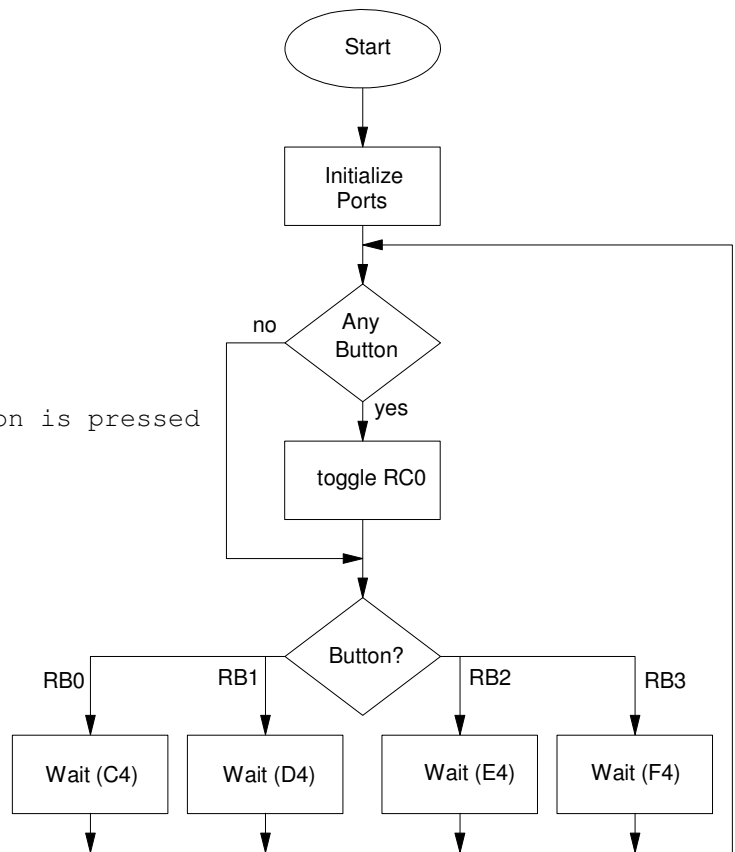



8) Validation: Collect data in the lab to verify your code works.

- For a binary clock, is it counting once per second?
- For the dice, are the results random? Is the beep 220Hz? Is it 1 second?
- For the piano, is each note correct in frequency?



9) Demonstration: Demonstrate that your embedded system works (either in person or with a video)