
## ECE 376 - Homework #1

PIC Background.

Please submit as a hard copy, submit on BlackBoard, or email

Problem	Answer
<ol> <li>How many clocks does it take to write the LCD display?</li> <li>Check Homework #9 solutions for Spring 2023</li> </ol>	6.2007ms
2) A PIC's output is limited to 25mA. Assuming V2 is 5V, what is the smallest resistance youcan connect to the output? (how small can R3 be?)	200 Ohms
A PIC can measure voltage to 4.88mV. To give an idea of how small thi	s is
3) What is the smallest change in R2 a PIC can measure if $R2 = 2000$ Ohms nominally?	8.32 Ohms
<ul> <li>How much does R2 have to change from 2000 Ohms for V1 to change by 4.88mV?</li> </ul>	
<ul> <li>4) Assume R2 is a thermistor.</li> <li>What temperature is it if R2 = 2000 Ohms?</li> <li>How much does the temperature have to change for V1 to change by 4.88mV?</li> </ul>	0.085C
A PIC can measure time to 100ns. To give an idea of how small this is	
5) The average NFL quarterback can throw a football 87 km/h. Fow far does the football travel in 100ns?	2.416um
<ul> <li>6) Assume for the 555 timer</li> <li>R1 = 1k, R2 = 2k, C = 0.1uF</li> <li>What frequency does the 555 timer output on pin #3?</li> </ul>	2885.39 Hz
7) What is the smallest change in frequency a PIC can detect?	0.83Hz
• i.e. how much does the frequency have to change for the period to change by 100ns?	
8) With this circuit, you can build an Ohm-meter (replace R2 with the resistance to be measured.) Assume $R2 = 10k$ Ohms (nominally). How much does R2 have to change for the period to change by 100ns?	0.72 Ohms
• i.e. What is the resolution of this circuit when used as an Ohm-meter?	
<ul> <li>9) Replace R2 with a thermistor which reads 2k Ohms nominally. How much does the temperature have to change for the period to increase by 100ns?</li> <li>i.e. what is the resolution in degrees C?</li> </ul>	0.0074C

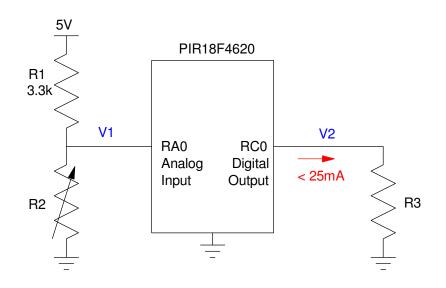

Problem #1 to #3

2) A PIC's output is limited to 25mA. Assuming V2 is 5V, what is the smallest resistance youcan connect to the output? (how small can R3 be?)

$$R = \left(\frac{5V}{25mA}\right) = 200\Omega$$

3) What is the smallest change in R2 a PIC can measure if R2 = 2000 Ohms nominally?

• How much does R2 have to change from 2000 Ohms for V1 to change by 4.88mV?

If R2 = 2000 Ohms

$$V_1 = \left(\frac{R_2}{R_2 + R_1}\right) 5V = 1.887V$$

If V1 is 4.88mV more, then

$$V_1 + 4.88mV = 1.89167V = \left(\frac{R_2}{R_2 + 3300}\right)5V$$
$$R_2 = 2008.32V$$

The change in R2 required to produce a 4.88mV change in V1 is 8.32 Ohms

- 4) Assume R2 is a thermistor.
  - What temperature is it if R2 = 2000 Ohms?
  - How much does the temperature have to change for V1 to change by 4.88mV?

• 
$$R_2 = 1000 \cdot \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

2000 Ohms corresponds to a temperature of

T = 10.02897C

2008.32 Ohms corresponds to a temperature of

T = 9.94383C


The difference is -0.08514C

A PIC can detect a change in temperature of 0.085C

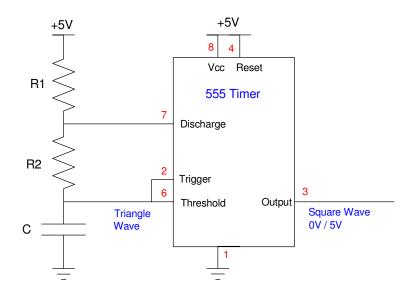5) The average NFL quarterback can throw a football 87 km/h. Fow far does the football travel in 100ns?

$$d = v \cdot t$$
  
$$d = 87 \left(\frac{km}{h}\right) \left(\frac{1000m}{km}\right) \left(\frac{1h}{3600s}\right) \cdot 100ns = 2.416\mu m$$

An average NFL quarterback's pass travels 2.4 micons in one clock



Astable 555 Timer: Problems 5-8 The square wave at the Output has a period of  $T=(R_1+2R_2)\cdot C\cdot \ln(2)$  seconds

6) Assume for the 555 timer

- R1 = 1k, R2 = 2k, C = 0.1uF
- What frequency does the 555 timer output on pin #3?

 $T = (R_1 + 2R_2) \cdot C \cdot \ln(2)$   $T = 346.6 \mu s$  $f = \frac{1}{T} = 2885.3901 Hz$ 

- 7) What is the smallest change in frequency a PIC can detect?
  - i.e. how much does the frequency have to change for the period to change by 100ns?

$$f_2 = \frac{1}{T + 100ns} = 2884.5578Hz$$
$$\delta f = f_1 - f_2 = 0.8323Hz$$

8) With this circuit, you can build an Ohm-meter (replace R2 with the resistance to be measured.) Assume R2 = 2000 Ohms (nominally). How much does R2 have to change for the period to change by 100ns?

i.e. What is the resolution of this circuit when used as an Ohm-meter?

$$T + 100ns = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$
$$R_2 = 2000.7213\Omega$$
$$\delta R = 0.72135\Omega$$

9) Replace R2 with a thermistor which reads 2k Ohms nominally. How much does the temperature have to change for the period to increase by 100ns? i.e. what is the resolution in degrees C?

 $P = 1000 \text{ avg} \begin{pmatrix} 3905 & 3905 \end{pmatrix} O$ 

$$R_2 = 1000 \cdot \exp\left(\frac{3905}{T + 273} - \frac{3905}{298}\right) \Omega$$

2000 Ohms corresponds to a temperature of

$$T = 10.02897C$$

2000.7213 Ohms corresponds to a temperature of

T = 10.0216C

with a difference of 0.0074C