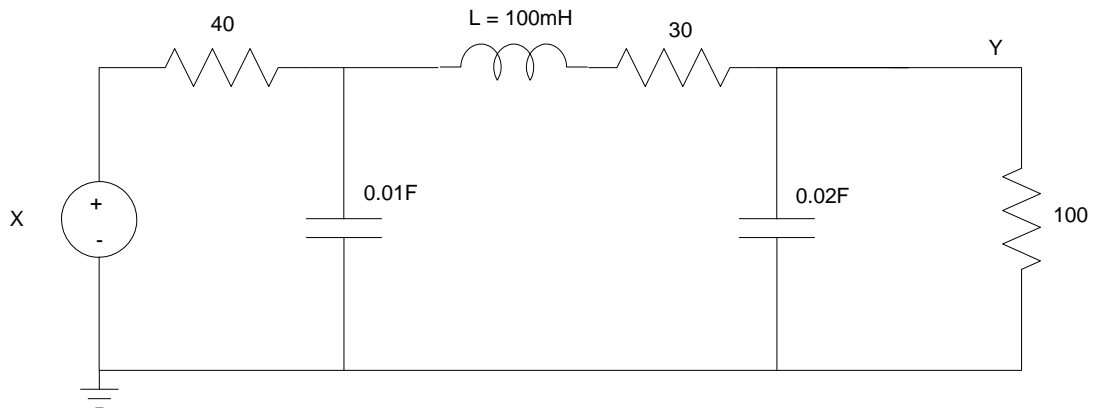


Homework #5: ECE 461

State Space, Canonical Forms, Heat Equation. Due Monday, October 2nd


- 1a) Write the differential equations which describe the following circuit
- 1b) Express these dynamics in state-space form
- 1c) Find the transfer function from X to Y
- 1d) From the dominant poles, predict what the step response will be like:
 - DC gain
 - 2% settling time
 - % overshoot for a step input
- 1e) Find the step response for this system in Matlab and compare the actual response to what you predicted with the 1st or 2nd-order approximation.



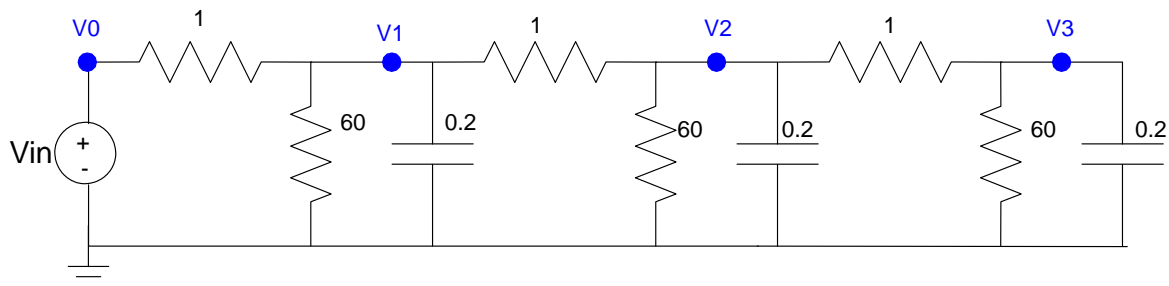Problem 1-5

3-Stage RC Filter

- 2a) Write the differential equations which describe the following circuit
- 2b) Express these dynamics in state-space form
- 2c) Find the transfer function from V_{in} to V_3
- 2d) From the dominant pole, predict what the step response will be like:
 - DC gain
 - 2% settling time
 - % overshoot for a step input
- 2e) Find the step response for this system in Matlab and compare the actual response to what you predicted with the 1st-order approximation.



10-Stage RC Filter


3a) Give the state-space model for the 10th-order RC filter shown below (Matlab printout of A,B,C,D preferred)

3b) Find the transfer function from V_{in} to V_{10}

3c) From the dominant pole, predict what the step response will be like:

- DC gain
- 2% settling time
- % overshoot for a step input

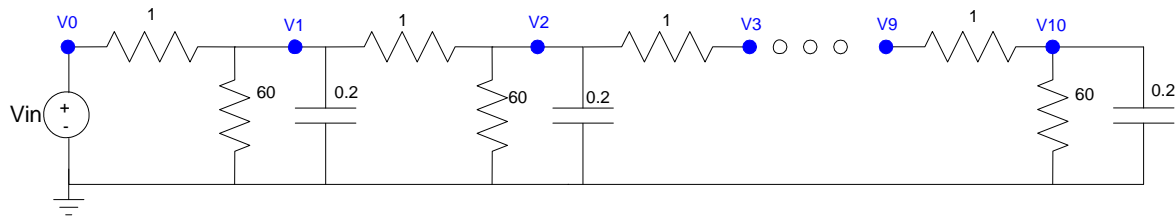3d) Find the step response for the 10th-order system in Matlab and compare the actual response to what you predicted with the 1st-order approximation.



4) Modify the program Heat.m to simulate the above 10th-order RC filter. Give a printout of the resulting code

note: We'll be using this simulation later on to check the controllers we design