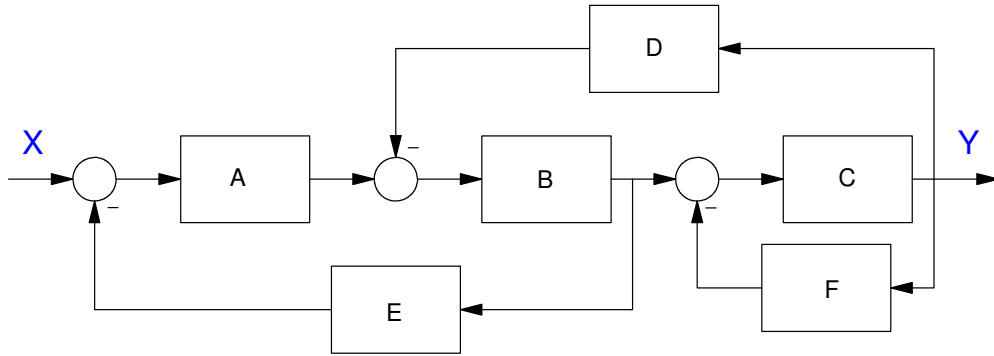


Homework #4: ECE 461/661


Block Diagrams, Canonical Forms, Electrical Circuits. Due Monday, September 20th

Block Diagrams

1) Determine the transfer function from X to Y



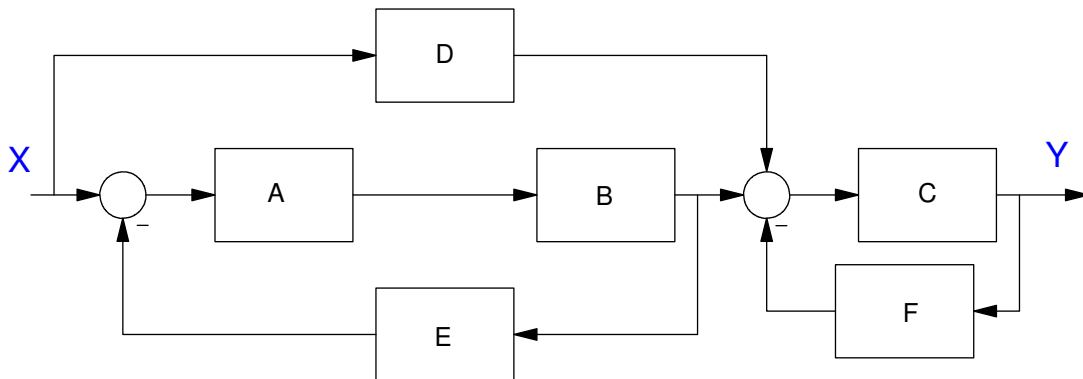2) Determine the transfer function from X to Y



Canonical Forms


3) Give two different state-space models that produce the following transfer function

$$Y = \left(\frac{30}{(s+2)(s+3)(s+4)} \right) U$$

Electrical Circuits


4) Using state-space methods, find the transfer function from V_{in} to V_3

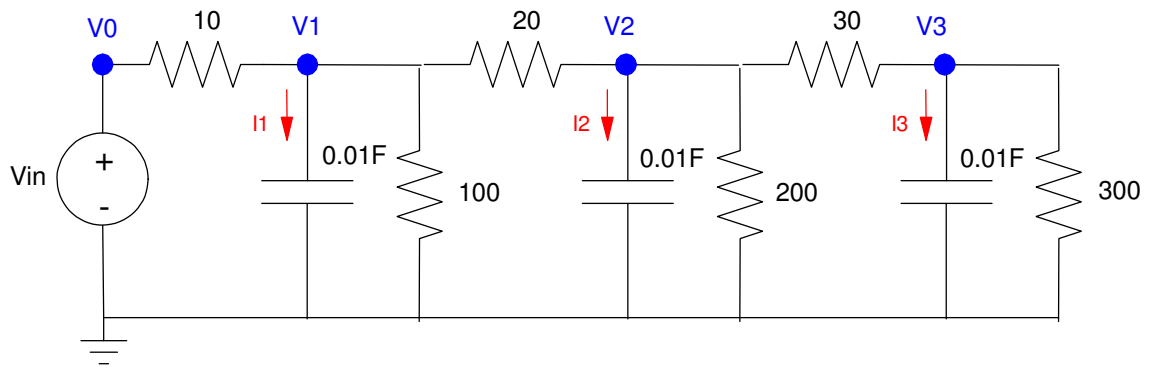5) Using state-space methods, find the transfer function from V_{in} to V_2



Problem 4 & 5

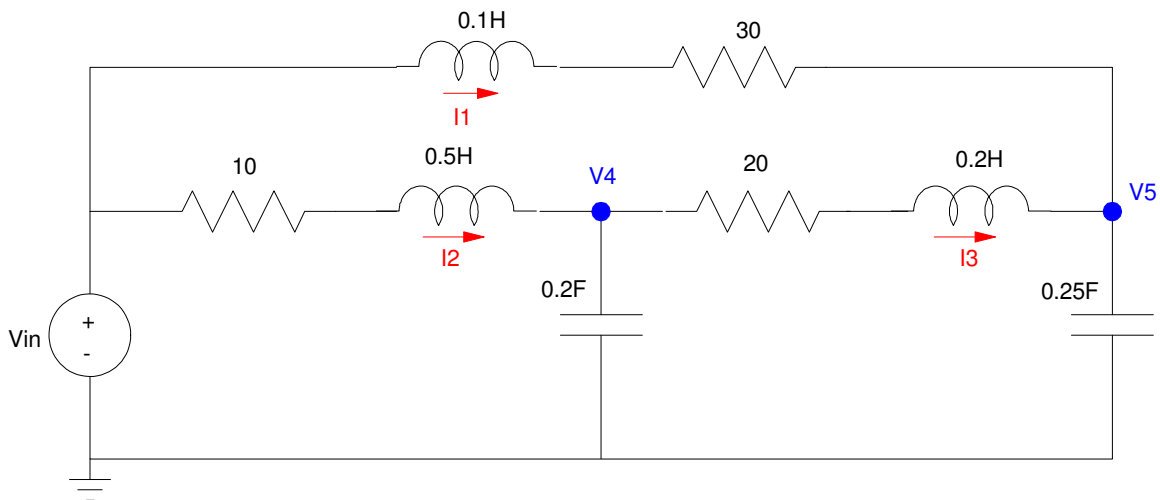- 6) Express the dynamics for the following RLC circuit in state-space form.
- Find the transfer function from V_{in} to V_5
- 7) Assume $V_{in} = 0$. Specify the initial conditions so that the total energy at $t = 0$ is 1.0 Joules and
- The transients decay as slow as possible
 - The transients decay as fast as possible



Problem 6 & 7