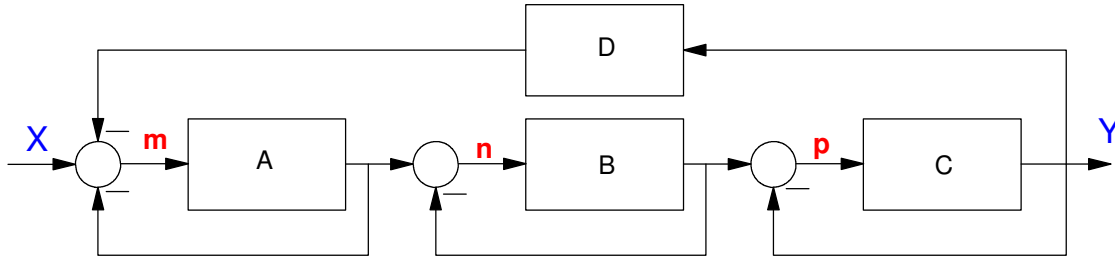


Homework #5: ECE 461/661

Block Diagrams, Canonical Forms, Electrical Circuits. Due Monday, September 19th

Block Diagrams

1) Determine the transfer function from X to Y



Shortcut (not quite right)

$$Y = \left(\frac{ABC}{1+A+B+C+ABCD} \right) X$$

Shortcut (right)

$$Y = \left(\frac{\left(\frac{A}{1+A} \right) \left(\frac{B}{1+B} \right) \left(\frac{C}{1+C} \right)}{1 + \left(\frac{A}{1+A} \right) \left(\frac{B}{1+B} \right) \left(\frac{C}{1+C} \right) D} \right) X$$

$$Y = \left(\frac{ABC}{(1+A)(1+B)(1+C)+ABCD} \right) X$$

Long Way

$$m = X - DCp - Am$$

$$n = Am - Bn$$

$$p = Bn - Cp$$

$$Y = Cp$$

Simplify

$$m = \left(\frac{1}{1+A} \right) X + \left(\frac{DC}{1+A} \right) p$$

$$n = \left(\frac{A}{1+B} \right) m$$

$$p = \left(\frac{B}{1+C} \right) p$$

$$p = \left(\frac{B}{1+C}\right)\left(\frac{A}{1+B}\right)\left(\left(\frac{1}{1+A}\right)X + \left(\frac{DC}{1+A}\right)p\right)$$


$$(1+A)(1+B)(1+C)p = ABX + BAD Cp$$

$$p = \left(\frac{AB}{(1+A)(1+B)(1+C)+ABCD}\right)X$$

$$Y = \left(\frac{ABC}{(1+A)(1+B)(1+C)+ABCD}\right)X$$

which matches

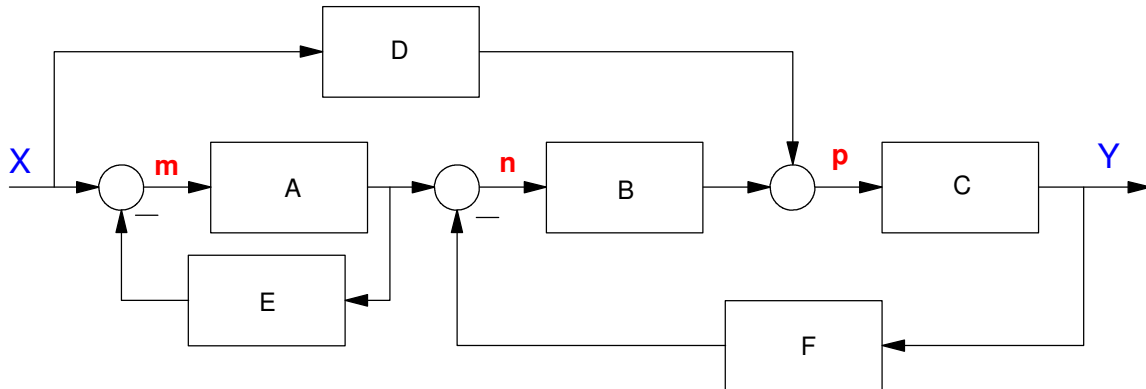2) Determine the transfer function from X to Y



Shortcut: This is actually two systems cascaded

$$Y = \left(\frac{A}{1+AE} \right) \left(\frac{BC}{1+BCF} \right) X + \left(\frac{DC}{1+BCF} \right) X$$

Long Way

$$m = X - EAm$$

$$n = Am - FCp$$

$$p = Bn + DX$$

$$Y = Cp$$

Simplify

$$m = \left(\frac{1}{1+EA} \right) X$$

$$n = Am - FC(Bn + DX)$$

$$(1 + FCB)n = A \left(\frac{1}{1+EA} \right) X - FCDX$$

$$(1 + FCB)(1 + EA)n = AX - (1 + EA)FCDX$$

$$(1 + FCB)(1 + EA)n = (A - FCD - EAFCD)X$$

$$n = \left(\frac{A - CDF - ACDEF}{(1+FCB)(1+EA)} \right) X$$

$$p = Bn + DX = B \left(\frac{A - CDF - ACDEF}{(1+FCB)(1+EA)} \right) X + DX$$

$$Y = Cp = CB \left(\frac{A - CDF - ACDEF}{(1+FCB)(1+EA)} \right) X + CDX$$

$$(1 + FCB)(1 + EA)Y = (CBA - CBCDF - CBACDEF + CD(1 + FCB)(1 + EA))X$$

$$= (CBA - CBCDF - CBACDEF + CD + CDFCB + CDEA + CDFCBEA)X$$

$$(1 + FCB)(1 + EA)Y = (CBA + CD + CDEA)X$$

$$Y = \left(\frac{CBA + CD + CDEA}{(1 + FCB)(1 + EA)} \right) X$$

$$Y = \left(\frac{CBA + CD(1 + EA)}{(1 + FCB)(1 + EA)} \right) X$$

$$Y = \left(\left(\frac{CBA}{(1 + FCB)(1 + EA)} \right) + \left(\frac{CD}{(1 + FCB)} \right) \right) X$$

which matches

Canonical Forms

3) Give two different state-space models that produce the following transfer function

$$Y = \left(\frac{30s+30}{(s+2)(s+3)(s+4)} \right) U$$

Multiply out and use controller canonical form

$$Y = \left(\frac{30s+30}{s^3+9s^2+26s+24} \right) U$$

$$sX = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -24 & -26 & -9 \end{bmatrix} X + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} U$$

$$Y = \begin{bmatrix} 30 & 30 & 0 \end{bmatrix} X$$

Transpose to get observer canonical form

$$sX = \begin{bmatrix} 0 & 0 & -24 \\ 1 & 0 & -26 \\ 0 & 1 & -9 \end{bmatrix} X + \begin{bmatrix} 30 \\ 30 \\ 0 \end{bmatrix} U$$

$$Y = \begin{bmatrix} 0 & 0 & 1 \end{bmatrix} X$$

Do partial fractions to get Jordan form


$$Y = \left(\left(\frac{-15}{s+2} \right) + \left(\frac{60}{s+3} \right) + \left(\frac{-45}{s+4} \right) \right) U$$

$$sX = \begin{bmatrix} -2 & 0 & 0 \\ 0 & -3 & 0 \\ 0 & 0 & -4 \end{bmatrix} X + \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} U$$

$$Y = \begin{bmatrix} -15 & 60 & -45 \end{bmatrix} X$$

Electrical Circuits

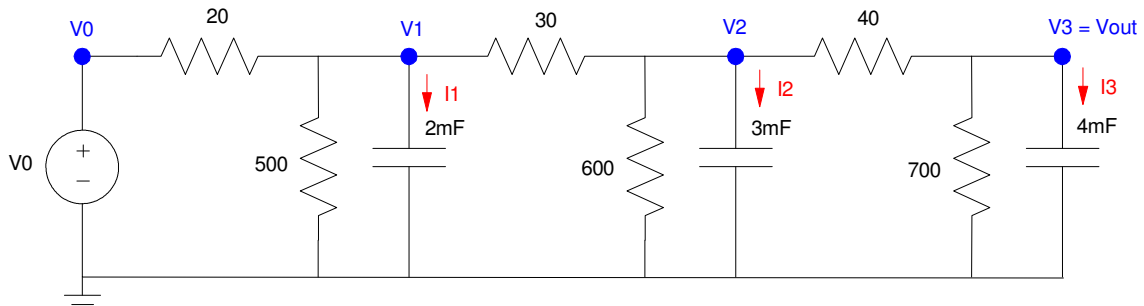4) Using state-space methods, find the transfer function from V_0 to V_3



$$I_1 = 0.002\dot{V}_1 = \left(\frac{V_0 - V_1}{20}\right) + \left(\frac{-V_1}{500}\right) + \left(\frac{V_2 - V_1}{30}\right)$$

$$I_2 = 0.003\dot{V}_2 = \left(\frac{V_1 - V_2}{30}\right) + \left(\frac{-V_2}{600}\right) + \left(\frac{V_3 - V_2}{40}\right)$$

$$I_3 = 0.004\dot{V}_3 = \left(\frac{V_2 - V_3}{40}\right) + \left(\frac{-V_3}{700}\right)$$

Simplify

$$\dot{V}_1 = 25V_0 - 42.667V_1 + 16.667V_2$$

$$\dot{V}_2 = 11.111V_1 - 20V_2 + 8.333V_3$$

$$\dot{V}_3 = 6.25V_2 - 6.607V_3$$

Place in matrix (state-space) form

$$\begin{bmatrix} sV_1 \\ sV_2 \\ sV_3 \end{bmatrix} = \begin{bmatrix} -42.667 & 16.667 & 0 \\ 11.111 & -20 & 8.333 \\ 0 & 6.25 & -6.607 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} + \begin{bmatrix} 25 \\ 0 \\ 0 \end{bmatrix} V_0$$

$$Y = V_3 = \begin{bmatrix} 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

Place in Matlab and find the transfer function

```
>> A = [-42.667,16.667,0 ; 11.111,-20,8.333 ; 0,6.25,-6.607]
```

```
A =
```

```
-42.6670    16.6670         0
 11.1110   -20.0000    8.3330
         0     6.2500   -6.6070
```

```
>> B = [25;0;0];
```

```
>> C = [0,0,1];
```

```
>> D = 0;
```

```
>> G = ss(A,B,C,D);
```

```
>> zpk(G)
```

1736.0938

(s+49.27) (s+17.46) (s+2.549)

5) Using state-space methods, find the transfer function from V0 to V2

Just change the C matrix

$$Y = V_2 = \begin{bmatrix} 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

```
>> C = [0,1,0];
```

```
>> D = 0;
```

```
>> G = ss(A,B,C,D);
```

```
>> zpk(G)
```

277.775 (s+6.607)


(s+49.27) (s+17.46) (s+2.549)

Note that when you change the output

- The zeros change, but
- The poles are unchanged

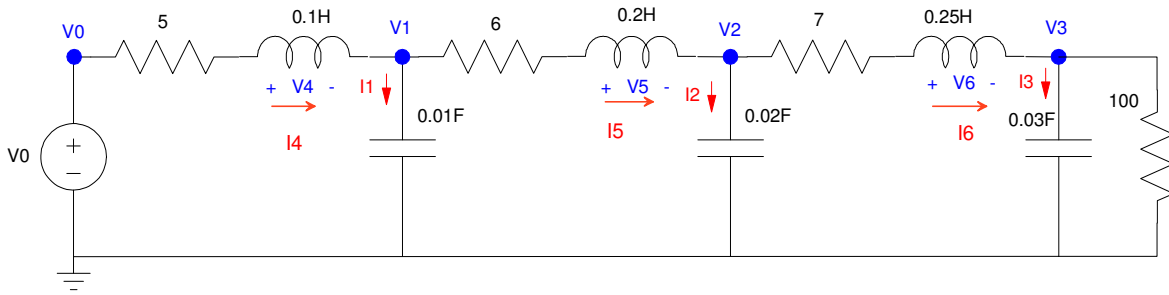6) Express the dynamics for the following RLC circuit in state-space form.

- Find the transfer function from V_0 to V_3



$$I_1 = 0.01sV_1 = I_4 - I_5$$

$$I_2 = 0.02sV_2 = I_5 - I_6$$

$$I_3 = 0.03sV_3 = I_6 - \left(\frac{V_3}{100}\right)$$

$$V_4 = 0.1sI_4 = V_0 - 5I_4 - V_1$$

$$V_5 = 0.2sI_5 = V_1 - 6I_5 - V_2$$

$$V_6 = 0.25sI_6 = V_2 - 7I_6 - V_3$$

Solving for the derivative of the states

$$sV_1 = 100I_4 - 100I_5$$

$$sV_2 = 50I_5 - 50I_6$$

$$sV_3 = 33.33I_6 - 0.333V_3$$

$$sI_4 = 10V_0 - 50I_4 - 10V_1$$

$$sI_5 = 5V_1 - 30I_5 - 5V_2$$

$$sI_6 = 4V_2 - 28I_6 - 4V_3$$

Place in matrix form

$$\begin{bmatrix} sV_1 \\ sV_2 \\ sV_3 \\ sI_4 \\ sI_5 \\ sI_6 \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 100 & -100 & 0 \\ 0 & 0 & 0 & 0 & 50 & -50 \\ 0 & 0 & -0.333 & 0 & 0 & 33.33 \\ -10 & 0 & 0 & -50 & 0 & 0 \\ 5 & -5 & 0 & 0 & -30 & 0 \\ 0 & 4 & -4 & 0 & 0 & -28 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 10 \\ 0 \\ 0 \end{bmatrix} V_0$$

Solve for the transfer function to V3 using Matlab

```
>> a1 = [0,0,0,100,-100,0];  
>> a2 = [0,0,0,0,50,-50];  
>> a3 = [0,0,-0.333,0,0,33.33];  
>> a4 = [-10,0,0,-50,0,0];  
>> a5 = [5,-5,0,0,-30,0];  
>> a6 = [0,4,-4,0,0,-28];  
>> A = [a1;a2;a3;a4;a5;a6]
```

A =

```
      0      0      0 100.0000 -100.0000      0  
      0      0      0      0      50.0000 -50.0000  
      0      0 -0.3330      0      0      33.3300  
 -10.0000      0      0 -50.0000      0      0  
   5.0000 -5.0000      0      0 -30.0000      0  
      0   4.0000 -4.0000      0      0 -28.0000
```

```
>> eig(A)
```

ans =

```
-19.1447 +33.5430i  
-19.1447 -33.5430i  
-37.3121  
-15.5065 +13.0642i  
-15.5065 -13.0642i  
-1.7186
```

```
>> B = [0;0;0;10;0;0];  
>> C = [0,0,1,0,0,0];  
>> D = 0;  
>> G = ss(A,B,C,D);  
>> zpk(G)
```

33330000

(s+37.31) (s+1.719) (s^2 + 31.01s + 411.1) (s^2 + 38.29s + 1492)

```
>>
```

7) Assume $V_0 = 0$. Specify the initial conditions so that the total energy at $t = 0$ is 1.0 Joules and

- The transients decay as slow as possible
- The transients decay as fast as possible

This is an eigenvector problem. The eigenvalues and eigenvectors are:

```
>> [M,V] = eig(A)

M (eigenvector)

-0.9292          -0.9292          -0.7116
 0.2417 - 0.0835i  0.2417 + 0.0835i -0.2797
-0.0231 + 0.0163i -0.0231 - 0.0163i -0.0781
 0.1380 - 0.1501i  0.1380 + 0.1501i  0.5609
-0.0399 + 0.1616i -0.0399 - 0.1616i  0.2953
-0.0033 - 0.0325i -0.0033 + 0.0325i  0.0866

V (eigenvalue)

-19.1447 -33.5430i -19.1447 +33.5430i -37.3121
```

```
M (eigenvector)

 0.5231 - 0.1566i  0.5231 + 0.1566i -0.2718
 0.6811           0.6811           -0.5637
-0.3908 + 0.0603i -0.3908 - 0.0603i -0.7756
-0.1176 + 0.0899i -0.1176 - 0.0899i  0.0563
-0.0569 - 0.0027i -0.0569 + 0.0027i  0.0516
 0.1543 - 0.1806i  0.1543 + 0.1806i  0.0322

V (eigenvalues)

-15.5065 -13.0642i -15.5065 +13.0642i -1.7186
```

The fast mode (blue) decays as $\exp(-37.31t)$. Using these values, the energy in the initial condition is

$$E = \sum \frac{1}{2} CV^2 + \sum \frac{1}{2} LI^2$$

Using this initial condition, the initial energy is 290mJ

```
X0 = M(:, 3);

>> LC = [0.01, 0.02, 0.03, 0.1, 0.2, 0.3]

LC =    0.0100    0.0200    0.0300    0.1000    0.2000    0.3000

>> J = 0.5 * LC * (X0 .^ 2)

J =    0.0290
```

Scale X0 so that the initial energy is 1.00J

```
>> X0 / sqrt(J)
```

```
V1  -4.1801  
V2  -1.6430  
V3  -0.4586  
I4   3.2945  
I5   1.7348  
I6   0.5088
```

Slow Mode

```
>> X0 = M(:,6);  
>> J = 0.5 * LC * (X0 .^ 2)
```

```
J =    0.0132
```

```
>> X0 / sqrt(J)
```

```
V1  -2.3699  
V2  -4.9159  
V3  -6.7631  
I4   0.4908  
I5   0.4501  
I6   0.2812
```

```
>>
```