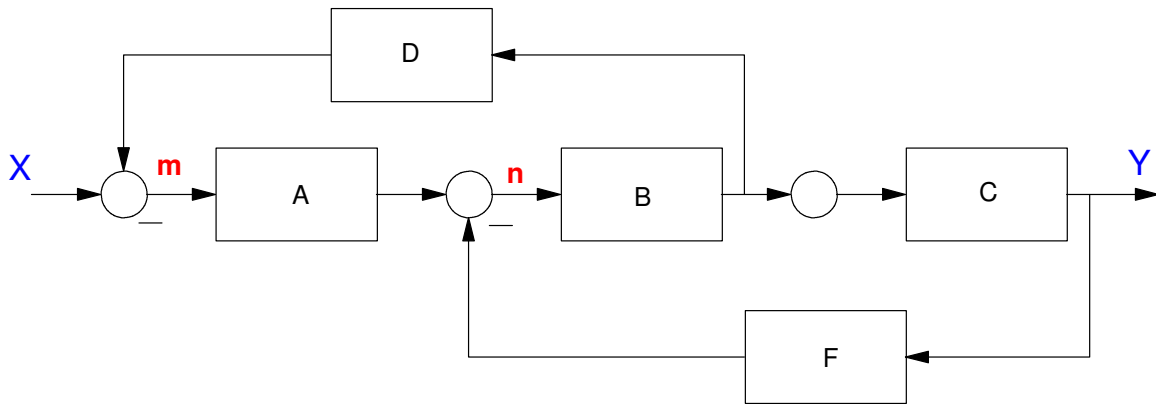


Homework #5: ECE 461/661

Block Diagrams, Canonical Forms, Electrical Circuits. Due Monday, September 18th

Block Diagrams

1) Determine the transfer function from X to Y



Shortcut

$$Y = \left(\frac{ABC}{1+ABD+BCF} \right) X$$

Long Way

$$m = X - DBn$$

$$n = Am - FY$$

$$Y = CBn$$

Substitute and do some algebra

$$n = A(X - DBn) - FY$$

$$(1 + ADB)n = AX - FY$$

$$n = \left(\frac{AX - FY}{1 + ADB} \right)$$

$$Y = CBn = CB \left(\frac{AX - FY}{1 + ADB} \right)$$


$$(1 + ADB)Y = CB(AX - FY)$$

$$(1 + ADB + CBF)Y = CBAX$$

$$Y = \left(\frac{CBA}{1 + ADB + CBF} \right) X$$

same answer

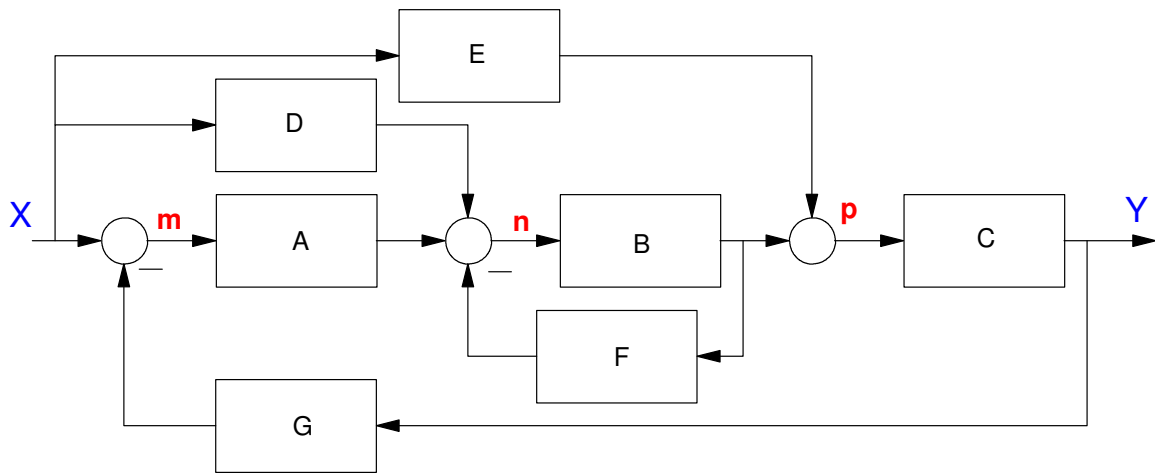2) Determine the transfer function from X to Y



Shortcut

$$Y = \left(\frac{EC+DBC+ABC}{1+BF+ABCG} \right) X$$

Long Way

$$m = X - GY$$

$$n = Am + DX - FBn$$

$$p = Bn + EX$$

$$Y = Cp$$

Substituting and doing some algebra

$$(1 + FB)n = A(X - GY) + DX$$

$$n = \frac{AX - AGY + DX}{(1 + FB)}$$

$$p = Bn + EX = B \left(\frac{AX - AGY + DX}{(1 + FB)} \right) + EX$$

$$Y = Cp = C \left(B \left(\frac{AX - AGY + DX}{(1 + FB)} \right) + EX \right)$$

$$(1 + FB)Y = CB(AX - AGY + DX) + (1 + FB)CEX$$

$$(1 + FB + CBAG)Y = (CBA + CBD + CE + FBCE)X$$

$$Y = \left(\frac{CBA + CBD + CE + FBCE}{1 + FB + CBAG} \right) X$$

Almost the same, but there's an extra term in the numerator (FBCE). The shortcut method missed this term.

Canonical Forms

3) Give two different state-space models that produce the following transfer function

$$Y = \left(\frac{2s+20}{(s+1)(s+3)(s+5)+10} \right) U$$

Controller Form: Multiply out

$$Y = \left(\frac{2s+20}{s^3+9s^2+23s+25} \right) U$$

By inspection (controller form)

$$sX = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -25 & -23 & -9 \end{bmatrix} X + \begin{bmatrix} 0 \\ 0 \\ 1 \end{bmatrix} U$$

$$Y = [20 \ 2 \ 0] X + [0] U$$

Observer form:

$$sX = \begin{bmatrix} 0 & 0 & -25 \\ 1 & 0 & -23 \\ 0 & 1 & -9 \end{bmatrix} X + \begin{bmatrix} 20 \\ 2 \\ 0 \end{bmatrix} U$$

$$Y = [0 \ 0 \ 1] X + [0] U$$

The roots are complex, so cascade and Jordan form are a little trickier. Keep the complex poles together creating a 2x2 block

Cascade:


$$\left(\frac{2}{s+5.7608} \right) \left(\frac{s+10}{s^2+3.2392s+4.3397} \right)$$

$$sX = \begin{bmatrix} -5.7608 & \vdots & 0 & 0 \\ \cdots & & \cdots & \cdots \\ 0 & \vdots & 0 & 1 \\ 2 & \vdots & -4.3397 & -3.2392 \end{bmatrix} X + \begin{bmatrix} 1 \\ \cdots \\ 0 \\ 0 \end{bmatrix} U$$

$$Y = [0 \ \vdots \ 10 \ 1] X + [0] U$$

Electrical Circuits

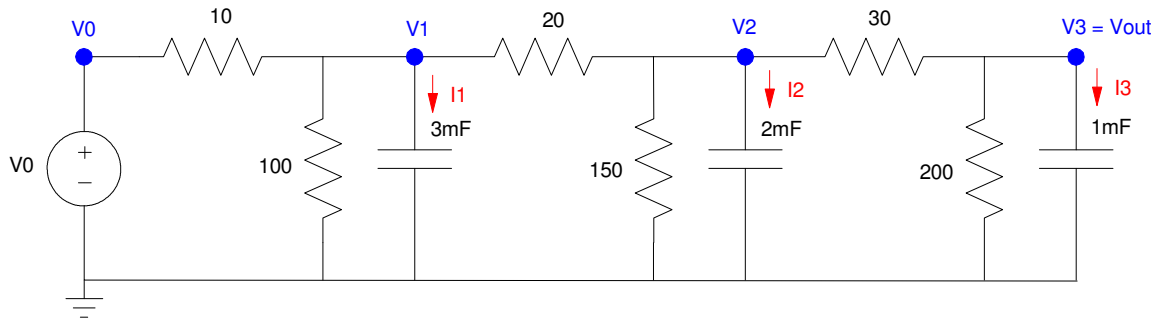4) Using state-space methods, find the transfer function from V_0 to V_3



$$I_1 = C_1 s V_1 = \left(\frac{V_0 - V_1}{10} \right) + \left(\frac{V_2 - V_1}{20} \right) + \left(\frac{0 - V_1}{100} \right)$$

$$I_2 = C_2 s V_2 = \left(\frac{V_1 - V_2}{20} \right) + \left(\frac{V_3 - V_2}{30} \right) + \left(\frac{0 - V_2}{150} \right)$$

$$I_3 = C_3 s V_3 = \left(\frac{V_2 - V_3}{30} \right) + \left(\frac{0 - V_3}{200} \right)$$

Plugging in C_1 , C_2 , and C_3 , then simplifying

$$sV_1 = 33.33V_0 - 53.33V_1 + 16.67V_2$$

$$sV_2 = 25V_1 - 45V_2 + 16.67V_3$$

$$sV_3 = 33.33V_2 - 38.33V_3$$

Putting in state-space form

$$\begin{bmatrix} sV_1 \\ sV_2 \\ sV_3 \end{bmatrix} = \begin{bmatrix} -53.33 & 16.67 & 0 \\ 25 & -45 & 16.67 \\ 0 & 33.33 & -38.33 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} + \begin{bmatrix} 33.33 \\ 0 \\ 0 \end{bmatrix} V_0$$

$$Y = V_3 = \begin{bmatrix} 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} + [0]V_0$$

Use Matlab to find the transfer function

```

>> A = [-53.33, 16.67, 0; 25, -45, 16.67; 0, 33.33, -38.33]

-53.3300    16.6700         0
 25.0000   -45.0000    16.6700
         0    33.3300   -38.3300

>> B = [33.33; 0; 0]

 33.3300
         0
         0

>> C = [0, 0, 1];
>> D = 0;
>> G = ss(A, B, C, D);
>> zpk(G)

```

27772.2225

(s+76.99) (s+46.8) (s+12.87)

>>

5) Using state-space methods, find the transfer function from V0 to V1

Just change the C matrix

```

>> C = [1, 0, 0];
>> G = ss(A, B, C, D);
>> zpk(G)

```

33.33 (s+65.47) (s+17.86)


(s+76.99) (s+46.8) (s+12.87)

Note: When you change what you're measuring

- The poles remain the same
- The zeros change

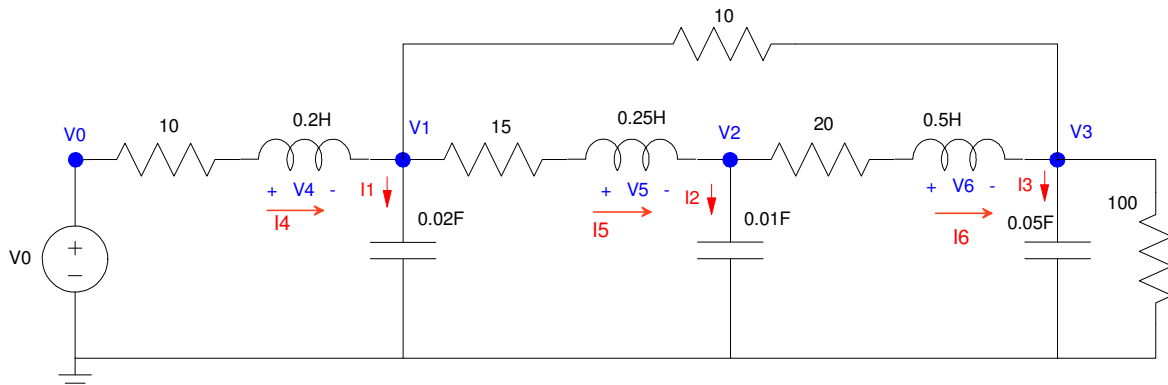6) Express the dynamics for the following RLC circuit in state-space form.

- Find the transfer function from V_0 to V_3



Use the currents in the inductors and voltages across the resistors as the energy states

$$I_1 = 0.02sV_1 = I_4 - I_5 - \left(\frac{V_1 - V_3}{10}\right)$$

$$I_2 = 0.01sV_2 = I_5 - I_6$$

$$I_3 = 0.05sV_3 = I_6 + \left(\frac{V_1 - V_3}{10}\right) - \left(\frac{V_3}{100}\right)$$

$$V_4 = 0.2sI_4 = V_0 - 10I_4 - V_1$$

$$V_5 = 0.25sI_5 = V_1 - 15I_5 - V_2$$

$$V_6 = 0.5sI_6 = V_2 - 20I_6 - V_3$$

Simplify

$$sV_1 = 50I_4 - 50I_5 - 5V_1 + 5V_3$$

$$sV_2 = 100I_5 - 100I_6$$

$$sV_3 = 20I_6 + 2V_1 - 2.2V_3$$

$$sI_4 = 5V_0 - 50I_4 - 5V_1$$

$$sI_5 = 4V_1 - 60I_5 - 4V_2$$

$$sI_6 = 2V_2 - 40I_6 - 2V_3$$

Place in state-space form

$$s \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} -5 & 0 & 5 & 50 & -50 & 0 \\ 0 & 0 & 0 & 0 & 100 & -100 \\ 2 & 0 & -2.2 & 0 & 0 & 20 \\ -5 & 0 & 0 & -50 & 0 & 0 \\ 4 & -4 & 0 & 0 & -60 & 0 \\ 0 & 2 & -2 & 0 & 0 & -40 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_4 \\ I_5 \\ I_6 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 5 \\ 0 \\ 0 \end{bmatrix} V_0$$

Use Matlab to find the transfer function to V3

```
>> A = [-5, 0, 5, 50, -50, 0; 0, 0, 0, 0, 100, -100; 2, 0, -2.2, 0, 0, 20];  
>> A = [A; -5, 0, 0, -50, 0, 0; 4, -4, 0, 0, -60, 0; 0, 2, -2, 0, 0, -40]
```

```
-5.0000      0      5.0000     50.0000    -50.0000      0  
      0      0      0      0      100.0000    -100.0000  
      2.0000      0     -2.2000      0      0      20.0000  
-5.0000      0      0     -50.0000      0      0  
      4.0000     -4.0000      0      0     -60.0000      0  
      0      2.0000     -2.0000      0      0     -40.0000
```

```
>> B = [0; 0; 0; 5; 0; 0]
```

```
0  
0  
0  
5  
0  
0
```

```
>> C = [0, 0, 1, 0, 0, 0]
```

```
0      0      1      0      0      0
```

```
>> D = 0;
```

```
>> G = ss(A, B, C, D);
```

```
>> zpk(G)
```

$$\frac{500 (s+60) (s^2 + 40s + 600)}{(s+1.053) (s+12.14) (s+39.17) (s+52.64) (s^2 + 52.2s + 804.4)}$$

```
>>
```

7) Assume $V_0 = 0$. Specify the initial conditions so that $V_3(0) = 1V$ and

- The transients decay as slow as possible
- The transients decay as fast as possible

This is an eigenvector & eigenvalue problem

```
>> [m,n] = eig(A)
m =
-0.4337      0.5456     -0.4629 - 0.1752i  -0.4629 + 0.1752i   0.1813      0.8719
-0.5913      0.7890      0.8425      0.8425      -0.7575     -0.0667
-0.6784     -0.2616     -0.0464 + 0.0489i  -0.0464 - 0.0489i  -0.0515     -0.1305
 0.0443     -0.0720      0.0937 - 0.0068i   0.0937 + 0.0068i   0.3429     -0.4026
 0.0107     -0.0203     -0.1452 + 0.0269i  -0.1452 - 0.0269i  0.5105      0.1802
 0.0045      0.0754      0.0747 - 0.0667i   0.0747 + 0.0667i   0.1117      0.1541

n =
-1.0532      0      0      0      0      0
 0     -12.1359      0      0      0      0
 0      0     -26.0981 +11.1017i   0      0      0
 0      0      0     -26.0981 -11.1017i   0      0
 0      0      0      0     -52.6436      0
 0      0      0      0      0     -39.1711

>>
```

The slow mode is the 1st eigenvector (eigenvalue = -1.0532)

```
>> X0 = m(:,1)

-0.4337
-0.5913
-0.6784
 0.0443
 0.0107
 0.0045

>> X0 = X0 / X0(3)

V1    0.6393
V2    0.8717
V3    1.0000
I4   -0.0653
I5   -0.0158
I6   -0.0066
```

The fast mode is the 5th eigenvector (eigenvalue = -52.64)

```
>> X0 = m(:,5)

 0.1813
-0.7575
-0.0515
 0.3429
 0.5105
 0.1117

>> X0 = X0 / X0(3)

V1   -3.5222
V2   14.7180
V3    1.0000
I4   -6.6618
I5   -9.9181
I6   -2.1700
```