

ECE 463/663 - Homework #2

State-Space, Eigenvalues, Eigenvectors. Due Monday, Jan 25th

Please make the subject "ECE 463/663 HW#2" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

1) For the following RLC circuit

Specify the dynamics for the system (write N coupled differential equations)


$$V_1 = 0.5sI_1 = V_{in} - 10I_1 - V_4$$

$$V_2 = 0.2sI_2 = V_{in} - 5I_2 - V_4$$

$$V_3 = 0.25sI_3 = V_4 - 15I_3$$

$$I_4 = 0.1sV_4 = I_1 + I_2 - I_3 - \left(\frac{V_3 - V_4}{50}\right)$$
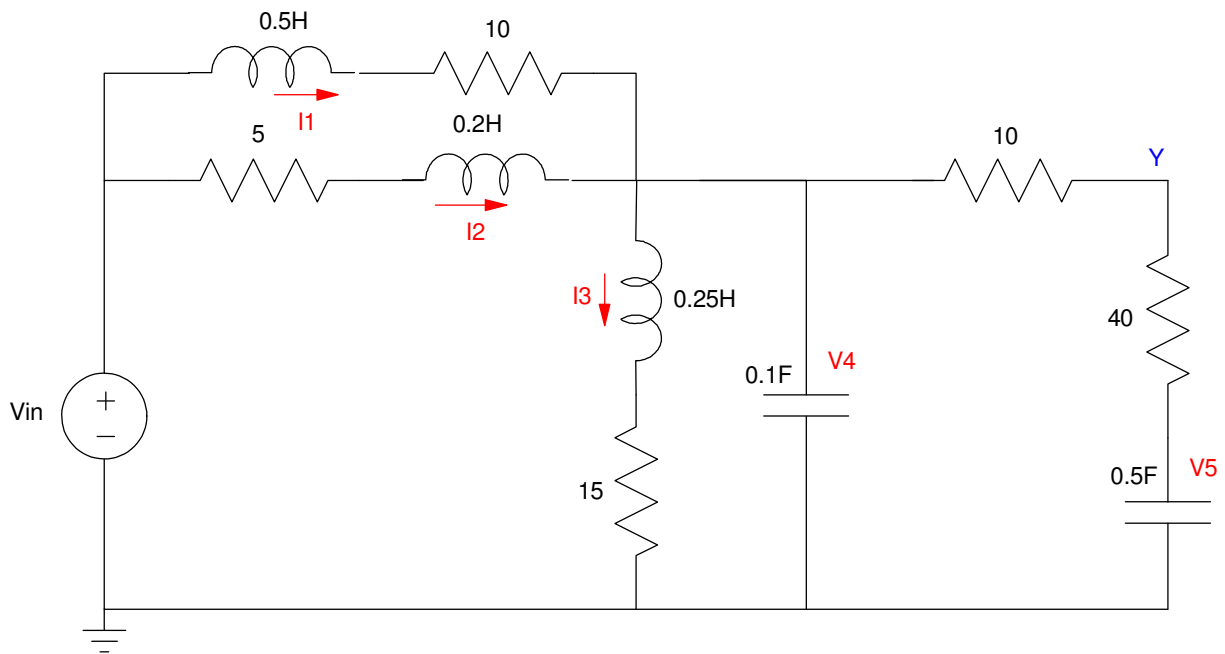
$$I_5 = 0.5sV_5 = \left(\frac{V_4 - V_5}{50}\right)$$



Simplify

$$sI_1 = 2V_{in} - 20I_1 - 2V_4$$

$$sI_2 = 5V_{in} - 25I_2 - 5V_4$$

$$sI_3 = 4V_4 - 60I_3$$

$$sV_4 = 10I_1 + 10I_2 - 10I_3 - 0.2V_3 + 0.2V_4$$

$$sV_5 = 0.04V_4 - 0.04V_5$$

Express these dynamics in state-space form

$$s \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ V_4 \\ V_5 \end{bmatrix} = \begin{bmatrix} -20 & 0 & 0 & -2 & 0 \\ 0 & -25 & 0 & -5 & 0 \\ 0 & 0 & -60 & 4 & 0 \\ 10 & 10 & -10 & -0.2 & 0.2 \\ 0 & 0 & 0 & 0.04 & -0.04 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ V_4 \\ V_5 \end{bmatrix} + \begin{bmatrix} 2 \\ 5 \\ 0 \\ 0 \\ 0 \end{bmatrix} V_{in}$$

The output equation (Y): write the voltage node equation

$$\left(\frac{Y-V_4}{10}\right) + \left(\frac{Y-V_5}{40}\right) = 0$$

$$\left(\frac{1}{10} + \frac{1}{40}\right) Y = \left(\frac{1}{10}\right) V_4 + \left(\frac{1}{40}\right) V_5$$

$$Y = 0.8V_4 + 0.2V_5$$

$$Y = \begin{bmatrix} 0 & 0 & 0 & 0.8 & 0.2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ V_4 \\ V_5 \end{bmatrix}$$

Determine the transfer function from Vin to Y

```
>> A = [-20,0,0,-2,0;0,-25,0,-5,0;0,0,-60,4,0;10,10,-10,-0.2,0.2;0,0,0,0.04,-0.04]
```

```
A =
```

```
-20.0000    0    0    -2.0000    0
    0   -25.0000    0    -5.0000    0
    0    0   -60.0000    4.0000    0
   10.0000   10.0000  -10.0000   -0.2000    0.2000
    0    0    0    0.0400   -0.0400
```

```
>> B = [2;5;0;0;0];
```

```
>> C = [0,0,0,0.8,0.2];
```

```
>> G = ss(A,B,C,0);
```

```
>> zpk(G)
```

```
56 (s+21.43) (s+60) (s+0.05)
```

```
(s+59.35) (s+23.22) (s+17.94) (s+4.694) (s+0.03791)
```

```
>>
```

2) For the transfer function from V_{in} to Y

Determine a 1st or 2nd-order approximation for this transfer function

```
>> zpk(G)
-----
      56 (s+21.43) (s+60) (s+0.05)
-----
(s+59.35) (s+23.22) (s+17.94) (s+4.694) (s+0.03791)

>> DC = evalfr(G,0)

DC =      0.8182
```

Keep

- The dominant pole at $s = -0.03791$
- The zero at $s = -0.05$ is within 10x the pole
- The DC gain is 0.8182


$$G(s) \approx \left(\frac{0.6204(s+0.05)}{s+0.03791} \right)$$

Note: This system has a non-zero D matrix

```
>> ss(G1)

a = -0.03791
b = 0.11
c = 0.06822
d = 0.6204
```

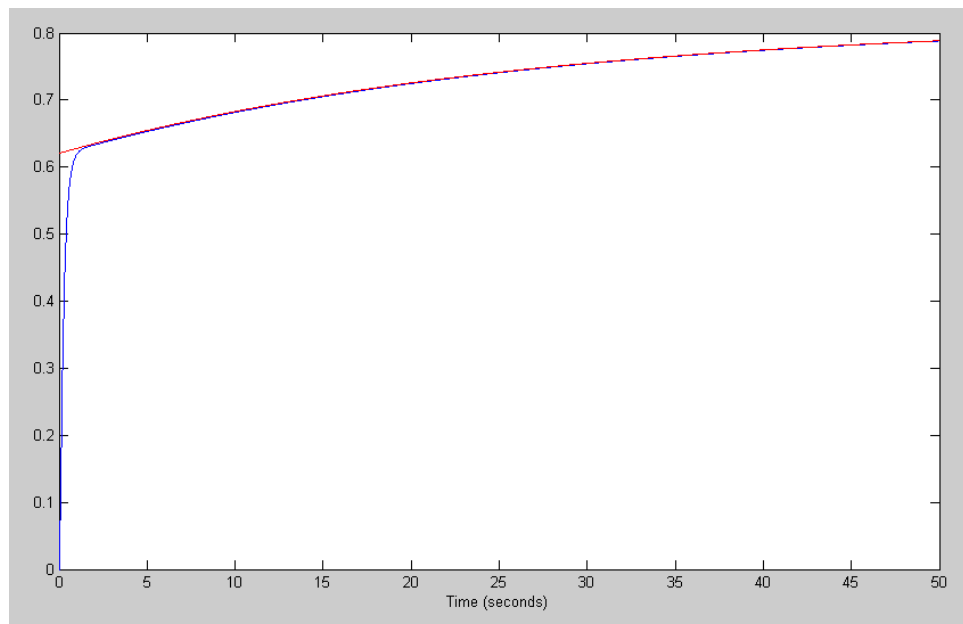Plot the step response of the actual 5th-order system and its approximation shows the two match pretty well



3) For this circuit...

- What initial condition will the energy in the system decay as slowly as possible?
- What initial condition will the energy in the system decay as fast as possible?

This is an eigenvalue / eigenvector problem

```
>> [M,V] = eig(A)
```

M =

fast				slow
-0.0082	-0.2033	0.6198	0.1256	-0.0052
-0.0235	0.9220	0.4522	0.2366	-0.0104
-0.9866	-0.0356	-0.0607	-0.0695	0.0035
-0.1614	-0.3276	-0.6385	-0.9609	0.0521
0.0001	0.0006	0.0014	0.0083	0.9986

V =


-59.3454	0	0	0	0
0	-23.2232	0	0	0
0	0	-17.9395	0	0
0	0	0	-4.6940	0
0	0	0	0	-0.0379

If the initial conditions are proportional to the fast eigenvector, the transients decay as $\exp(-59.34t)$

If the initial conditions are proportional to the slow eigenvector, the transients decay as $\exp(-0.0379t)$

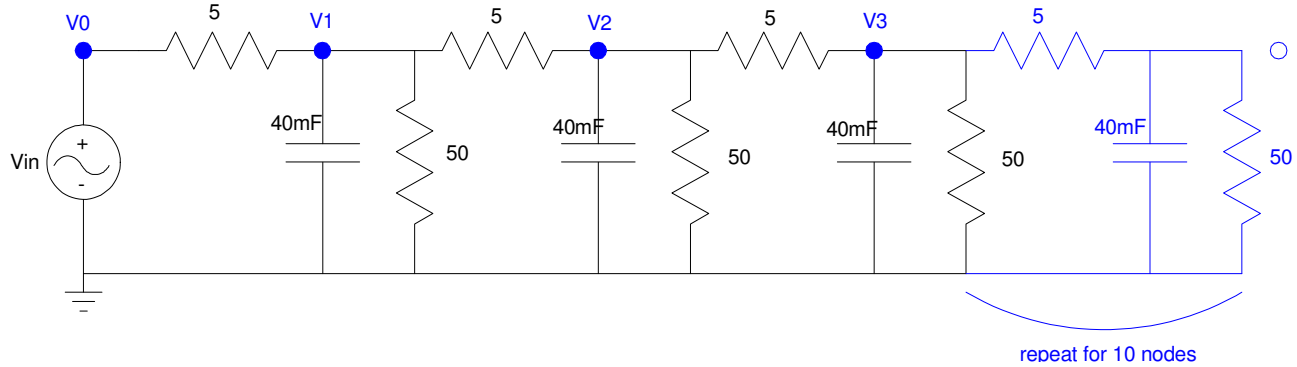4) For the following 10-stage RC circuit

- Specify the dynamics for the system (write N coupled differential equations)
 - note: Nodes 1..9 have the same form. Just write the node equation for node 1 and node 10.
- Express these dynamics in state-space form
- Determine the transfer function from V_{in} to V_{10}



Node V2:

$$0.04sV_2 = \left(\frac{V_1 - V_2}{5}\right) + \left(\frac{V_3 - V_2}{5}\right) - \left(\frac{V_2}{50}\right)$$

$$sV_2 = 5V_1 - 10.5V_2 + 5V_3$$

ditto for nodes 1..9. Node #10 is slightly different

$$0.04sV_{10} = \left(\frac{V_9 - V_{10}}{5}\right) - \left(\frac{V_{10}}{50}\right)$$

$$sV_{10} = 5V_9 - 5.5V_{10}$$

In state-space form, the {A, B, C, D} matrices and transfer function are:

```
A = zeros(10,10);
for i=1:9
    A(i,i) = -10.5;
    A(i+1,i) = 5;
    A(i,i+1) = 5;
end
A(10,10) = -5.5
```

A =

-10.5000	5.0000	0	0	0	0	0	0	0	0	0
5.0000	-10.5000	5.0000	0	0	0	0	0	0	0	0
0	5.0000	-10.5000	5.0000	0	0	0	0	0	0	0
0	0	5.0000	-10.5000	5.0000	0	0	0	0	0	0
0	0	0	5.0000	-10.5000	5.0000	0	0	0	0	0
0	0	0	0	5.0000	-10.5000	5.0000	0	0	0	0
0	0	0	0	0	5.0000	-10.5000	5.0000	0	0	0
0	0	0	0	0	0	5.0000	-10.5000	5.0000	0	0
0	0	0	0	0	0	0	5.0000	-10.5000	5.0000	0
0	0	0	0	0	0	0	0	5.0000	-10.5000	5.0000
0	0	0	0	0	0	0	0	0	5.0000	-5.5000

```
B = zeros(10,1);
B(1) = 5
```

```
5
0
0
0
0
0
0
0
0
0
```

```

0
0
0

C = zeros(1,10);
C(10) = 1

0 0 0 0 0 0 0 0 0 1

D = 0;
G = ss(A,B,C,D);
DC = evalfr(G,0)

DC = 0.0741

zpk(G)

9765625
-----
(s+20.06) (s+18.76) (s+16.73) (s+14.15) (s+11.25) (s+8.275) (s+5.5) (s+3.169) (s+1.49) (s+0.6117)

```

5) For the transfer function for problem #4

- Determine a 2nd-order approximation for this transfer function
- Plot the step response of the actual 10th-order system and its 2nd-order approximation

Keep the two most dominant poles

Match the DC gain

```

>> DC = evalfr(G,0)

DC = 0.0741

>> G2 = zpk([], [-0.6117, -1.49], DC*0.6117*1.49)


```

```

0.067522
-----
(s+0.6117) (s+1.49)

>> t = [0:0.01:10]';
>> y10 = step(G,t);
>> y2 = step(G2,t);
>> plot(t,y10,'b',t,y2,'r');
>> xlabel('Time (seconds)');

```

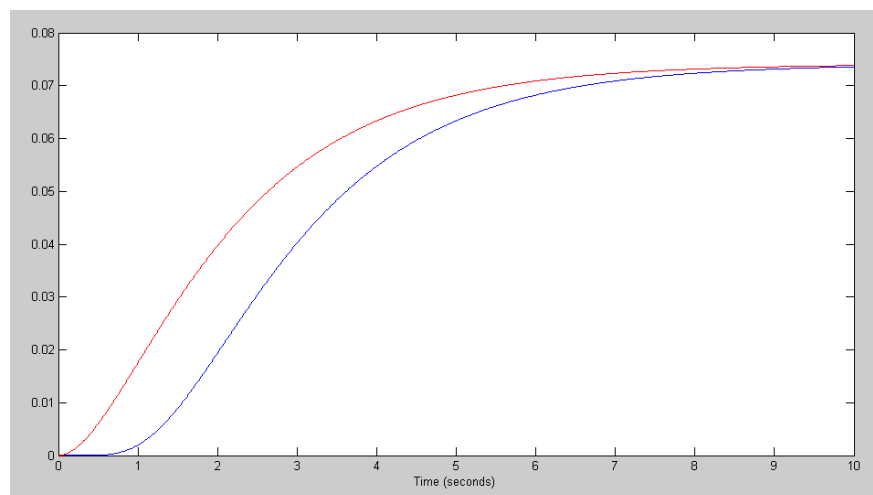

6) For the circuit for problem #4

- What initial condition will decay as slowly as possible?
- What initial condition will decay as fast as possible?

This is an eigenvector problem.

```
>> [M,V] = eig(A)
```

```
M =
```

	fast								slow
-0.1286	-0.2459	0.3412	0.4063	0.4352	0.4255	0.3780	0.2969	-0.1894	0.0650
0.2459	0.4063	-0.4255	-0.2969	-0.0650	0.1894	0.3780	0.4352	-0.3412	0.1286
-0.3412	-0.4255	0.1894	-0.1894	-0.4255	-0.3412	-0.0000	0.3412	-0.4255	0.1894
0.4063	0.2969	0.1894	0.4352	0.1286	-0.3412	-0.3780	0.0650	-0.4255	0.2459
-0.4352	-0.0650	-0.4255	-0.1286	0.4063	0.1894	-0.3780	-0.2459	-0.3412	0.2969
0.4255	-0.1894	0.3412	-0.3412	-0.1894	0.4255	0.0000	-0.4255	-0.1894	0.3412
-0.3780	0.3780	0.0000	0.3780	-0.3780	-0.0000	0.3780	-0.3780	-0.0000	0.3780
0.2969	-0.4352	-0.3412	0.0650	0.2459	-0.4255	0.3780	-0.1286	0.1894	0.4063
-0.1894	0.3412	0.4255	-0.4255	0.3412	-0.1894	-0.0000	0.1894	0.3412	0.4255
0.0650	-0.1286	-0.1894	0.2459	-0.2969	0.3412	-0.3780	0.4063	0.4255	0.4352

```
>> eig(A)'
```

```
-20.0557 -18.7624 -16.7349 -14.1534 -11.2473 -8.2748 -5.5000 -3.1695 -1.4903 -0.6117
```


```
>>
```

If the initial condition is proportional to the fast eigenvector, the transient decays as $\exp(-20.055t)$


If the initial condition is proportional to the slow eigenvector, the transient decays as $\exp(-0.6117t)$

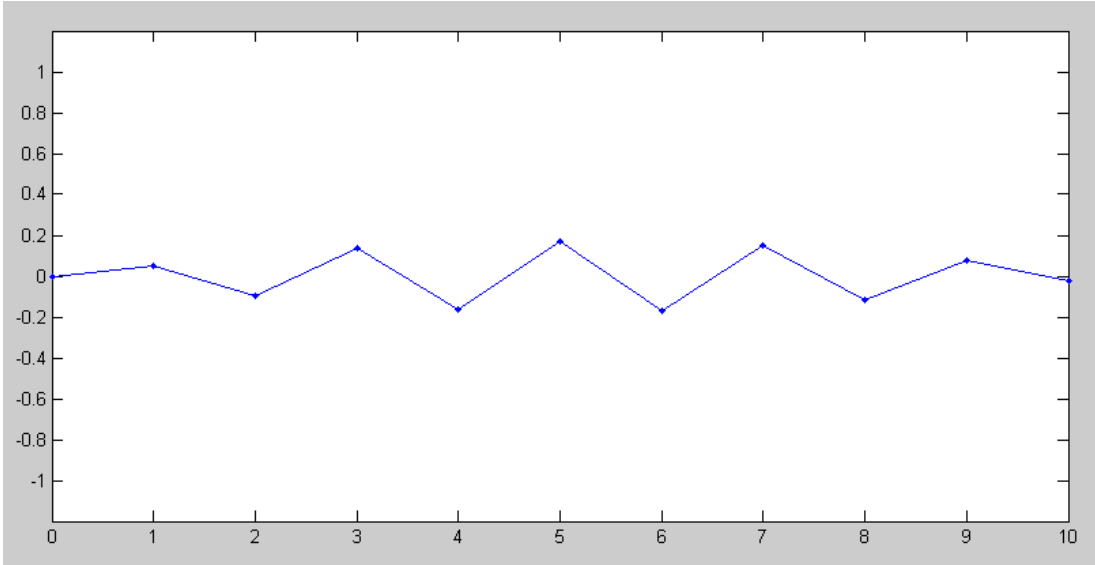7) Modify the program *heat.m* to match the dynamics you calculated for this problem.


- Give the program listing
- Give the response for $V_{in} = 0$ and the initial conditions being
 - The slowest eigenvector
 - The fastest eigenvector
 - A random set of voltages



Fast Mode: Quickly decays to zero

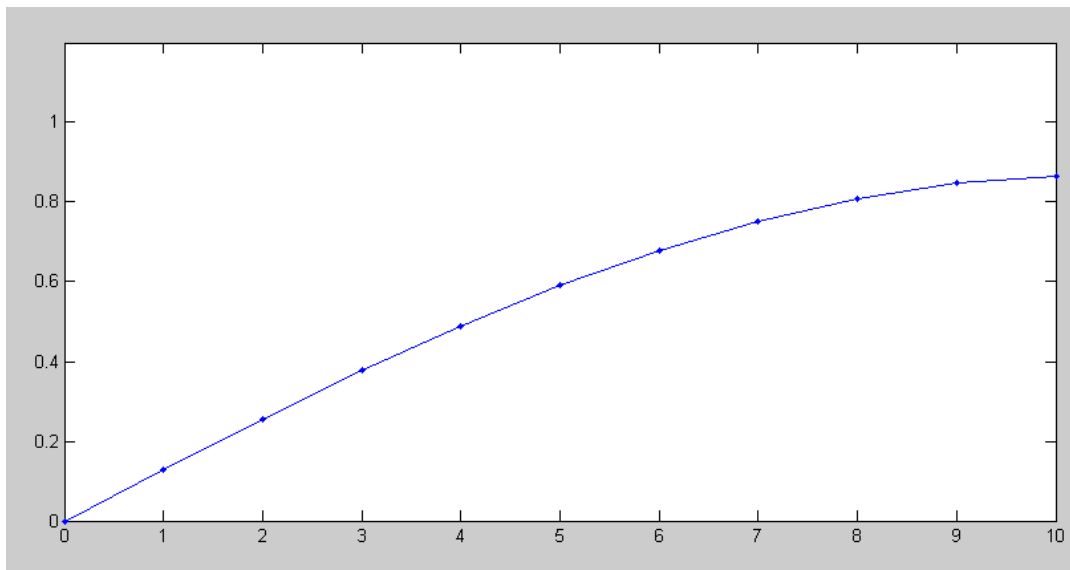

Slow Mode: Slowly decays

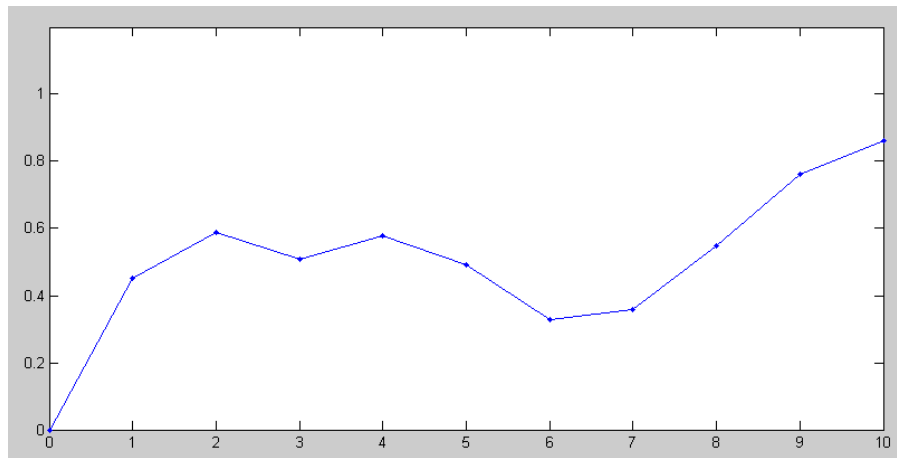

Random initial condition: quickly converges to the slow mode

Code

```

% 10-stage RC Filter

V = rand(10,1);

V0 = 0;
DATA = [V0;V];
dV = zeros(10,1);

dt = 0.001;
t = 0;

while(t < 10)

    dV(1) = 5*V0 - 10.5*V(1) + 5*V(2);
    dV(2) = 5*V(1) - 10.5*V(2) + 5*V(3);
    dV(3) = 5*V(2) - 10.5*V(3) + 5*V(4);
    dV(4) = 5*V(3) - 10.5*V(4) + 5*V(5);
    dV(5) = 5*V(4) - 10.5*V(5) + 5*V(6);
    dV(6) = 5*V(5) - 10.5*V(6) + 5*V(7);
    dV(7) = 5*V(6) - 10.5*V(7) + 5*V(8);
    dV(8) = 5*V(7) - 10.5*V(8) + 5*V(9);
    dV(9) = 5*V(8) - 10.5*V(9) + 5*V(10);
    dV(10) = 5*V(9) - 5.5*V(10);

    V = V + dV*dt;
    t = t + dt;

    plot([0:10], [V0;V], '-.');
    ylim([0,1.2]);
    pause(0.01);
end

```