


ECE 463/663 - Homework #2

State-Space, Eigenvalues, Eigenvectors. Due Monday, Jan 26th

Please make the subject "ECE 463/663 HW#2" if submitting homework electronically to Jacob_Glower@yahoo.com (or on blackboard)

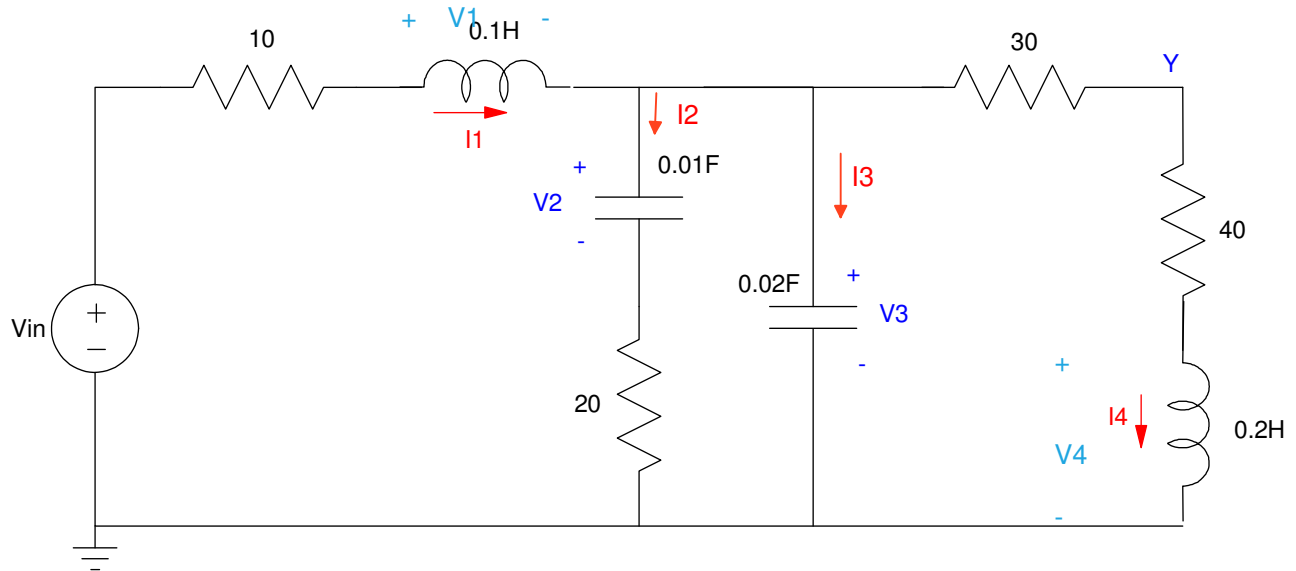1) For the following RLC circuit

- Specify the dynamics for the system (write N coupled differential equations)
- Express these dynamics in state-space form
- Determine the transfer function from V_{in} to Y



Step 1: Write the differential equations

$$V_1 = 0.1sI_1 = V_{in} - 10I_1 - V_3$$

$$I_2 = 0.01sV_2 = \left(\frac{V_3 - V_2}{20} \right)$$

$$I_3 = 0.02sV_3 = I_1 - I_4 - \left(\frac{V_3 - V_2}{20} \right)$$

$$V_4 = 0.2sI_4 = V_3 - 70I_4$$

$$Y = V_3 - 30I_4$$

Group terms and simplify

$$sI_1 = 10V_{in} - 100I_1 - 10V_3$$

$$sV_2 = 2.5V_3 - 2.5V_2$$

$$sV_3 = 50I_1 - 50I_4 - 2.5V_3 + 2.5V_2$$

$$sI_4 = 5V_3 - 350I_4$$

$$Y = V_3 - 30I_4$$

Place in state-space (matrix) form

$$\begin{bmatrix} sI_1 \\ sV_2 \\ sV_3 \\ sI_4 \end{bmatrix} = \begin{bmatrix} -100 & 0 & -10 & 0 \\ 0 & -2.5 & 2.5 & 0 \\ 50 & 2.5 & -2.5 & -50 \\ 0 & 0 & 5 & -350 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ V_3 \\ I_4 \end{bmatrix} + \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix} V_{in}$$

$$Y = \begin{bmatrix} 0 & 0 & 1 & -30 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \\ V_3 \\ I_4 \end{bmatrix}$$

Using Matlab to find the transfer function

```
>> A = [-100,0,-10,0 ; 0,-2.5,2.5,0 ; 50,2.5,-2.5,-50 ; 0,0,5,-350]
```

```

-100.0000      0 -10.0000      0
      0 -2.5000  2.5000      0
  50.0000  2.5000 -2.5000 -50.0000
      0      0  5.0000 -350.0000

```

```
>> B = [10;0;0;0]
```

```

10
 0
 0
 0

```

```
>> C = [0,0,1,-30]
```

```

 0      0      1  -30

```

```
>> D = 0;
```

```
>> G = ss(A,B,C,D);
```

```
>> zpk(G)
```

500 (s+2.5) (s+200)

(s+349.3) (s+94.5) (s+9.643) (s+1.571)

2) For the transfer function from V_{in} to Y

- Determine a 1st or 2nd-order approximation for this transfer function
- Plot the step response of the actual 4th-order system and its approximation

```
>> DC = evalfr(G,0)
```

```
DC = 0.5000
```


```
>> G1 = zpk([],-1.571,1.571*0.5);  
>> t = [0:0.01:5]';  
>> y4 = step(G,t);  
>> y1 = step(G1,t);  
>> plot(t,y4,t,y1);  
>> G1 = zpk(-2.5,-1.571,0.5*1.571/2.5)
```

```
0.3142 (s+2.5)
```

```
-----  
(s+1.571)
```

```
>> y4 = step(G,t);  
>> y1 = step(G1,t);  
>> plot(t,y4,'b',t,y1,'r');
```

```
>>
```

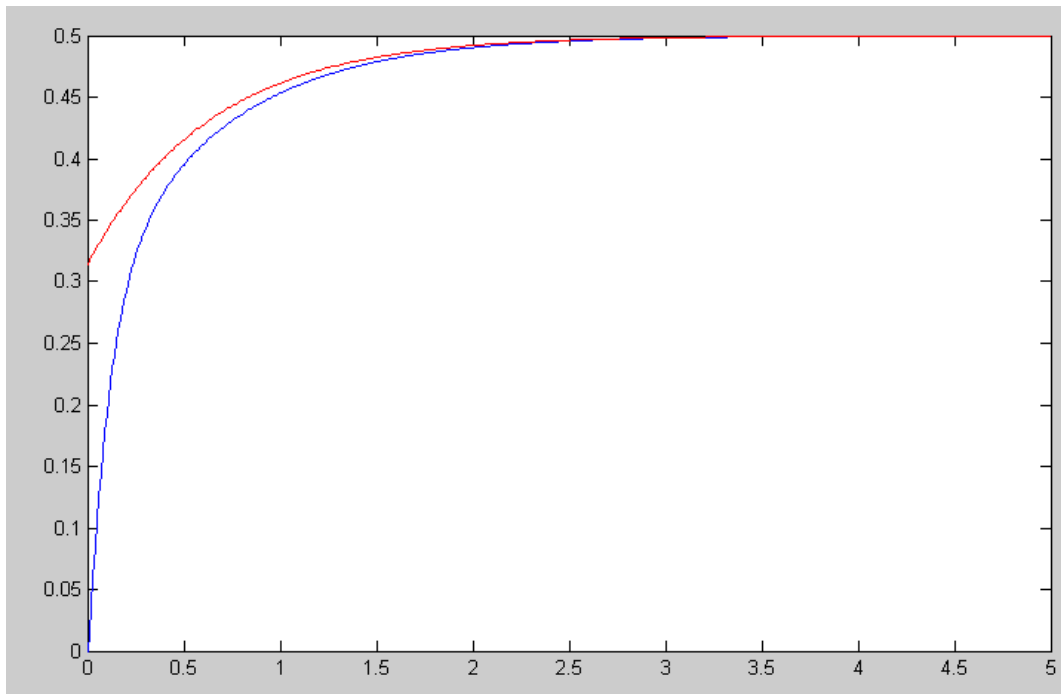

4th-order system (red) and its 1st-order approximation (blue)

3) For this circuit...

- What initial condition will the energy in the system decay as slowly as possible?
- What initial condition will the energy in the system decay as fast as possible?

This is an eigenvector problem

```
>> [M,V] = eig(A)
```

M =

I1	-0.0057	-0.8762	-0.1039	0.0354
V2	0.0010	-0.0131	-0.3285	-0.9368
V3	-0.1419	0.4817	0.9387	-0.3482
I4	-0.9899	0.0094	0.0138	-0.0050

V =

-349.2832	0	0	0
0	-94.5029	0	0
0	0	-9.6431	0
0	0	0	-1.5708

```
>>
```

Fast Mode: Make the initial condition the 1st eigenvector (red). That results in the initial conditions decaying as $\exp(-349t)$


Slow Mode: Make the initial condition the 4th eigenvector (blue). That results in the initial conditions decaying as $\exp(-1.57t)$

Problem 4-7: 10-Stage RC Filter.

note: You can turn in the Matlab code along with screen shots of the plots if you like.

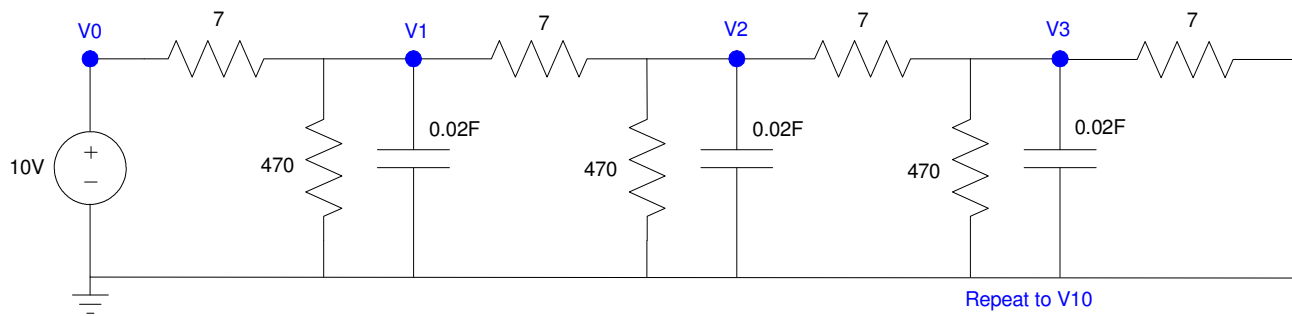4) For the following 10-stage RC circuit

- Specify the dynamics for the system (write N coupled differential equations)
 - note: Nodes 1..9 have the same form. Just write the node equation for node 1 and node 10.
- Express these dynamics in state-space form
- Determine the transfer function from V_{in} to V_{10}



At node V1:

$$0.02sV_1 = \left(\frac{V_0 - V_1}{7}\right) + \left(\frac{V_2 - V_1}{7}\right) - \left(\frac{V_1}{470}\right)$$

Simplifying (the same pattern holds for nodes 1..9)

$$sV_1 = 7.143V_0 - 14.288V_1 + 7.143V_2$$

$$sV_2 = 7.143V_1 - 14.288V_2 + 7.143V_3$$

⋮

$$sV_9 = 7.143V_8 - 14.288V_9 + 7.143V_{10}$$

Node #10 is slightly different since it's missing a 7-ohm resistor to the right

$$sV_{10} = 7.143V_9 - 7.145V_{10}$$

Put this into matrix form and then into Matlab

5) For the transfer function for problem #4

- Determine a 2nd-order approximation for this transfer function
- Plot the step response of the actual 10th-order system and its 2nd-order approximation

The 10th-order system is


$$\frac{345785279.7854}{(s+27.94)(s+26.09)(s+23.2)(s+19.51)(s+15.36)(s+11.11)(s+7.145)(s+3.816)(s+1.417)(s+0.1616)}$$

Keep the two dominant poles and match the DC gain

```
>> G2 = zpk([], [-0.1616, -1.417], 1);  
>> G10 = G;  
>> k = evalfr(G10, 0) / evalfr(G2, 0)  
  
k = 0.2255  
  
>> G2 = zpk([], [-0.1616, -1.417], 0.225)
```

$$\frac{0.225}{(s+0.1616)(s+1.417)}$$
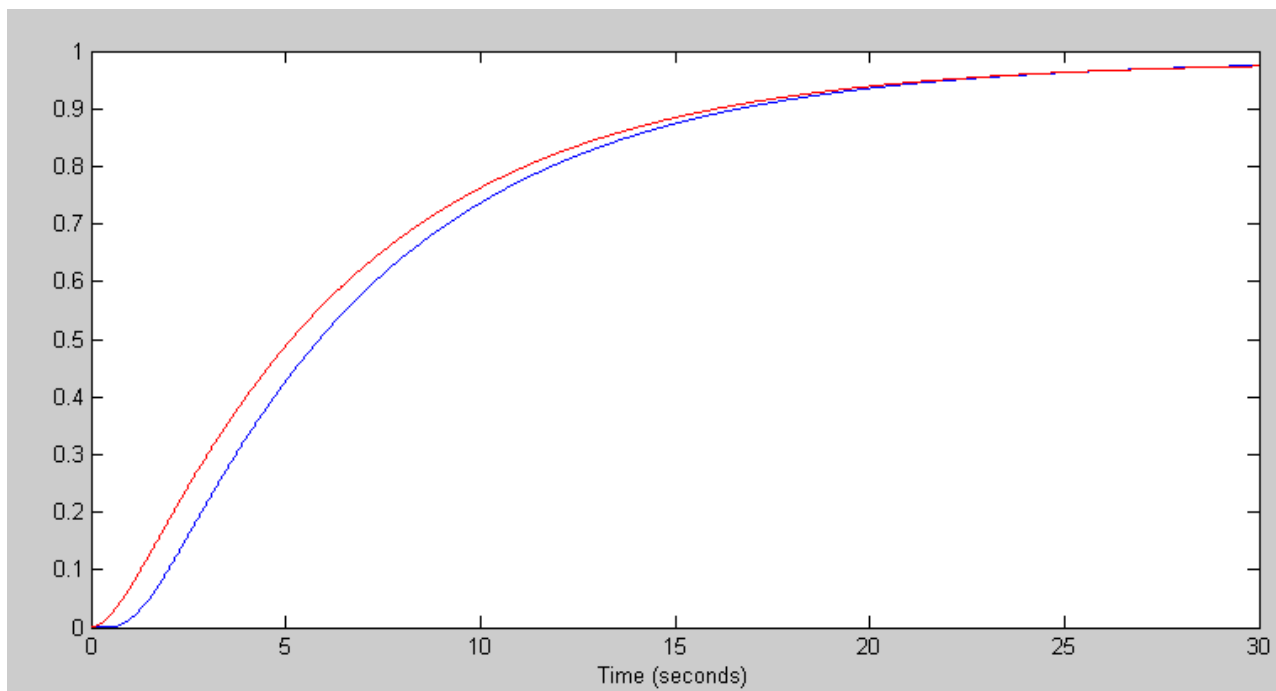
```
>>  
>> t = [0:0.01:30]';  
>> y10 = step(G10, t);  
>> y2 = step(G2, t);  
>> plot(t, y10, 'b', t, y2, 'r');  
>> xlabel('Time (seconds)')
```



Step response of the 10th-order system (blue) and its 2nd-order approximation (red)

6) For the circuit for problem #4

- What initial condition will decay as slowly as possible?
- What initial condition will decay as fast as possible?

This is an eigenvector problem

```
>> [M,V] = eig(A)
```

M =

-0.1286	-0.2459	0.3412	0.4063	0.4352	0.4255	0.3780	0.2969	-0.1894	0.0650
0.2459	0.4063	-0.4255	-0.2969	-0.0650	0.1894	0.3780	0.4352	-0.3412	0.1286
-0.3412	-0.4255	0.1894	-0.1894	-0.4255	-0.3412	0.0000	0.3412	-0.4255	0.1894
0.4063	0.2969	0.1894	0.4352	0.1286	-0.3412	-0.3780	0.0650	-0.4255	0.2459
-0.4352	-0.0650	-0.4255	-0.1286	0.4063	0.1894	-0.3780	-0.2459	-0.3412	0.2969
0.4255	-0.1894	0.3412	-0.3412	-0.1894	0.4255	-0.0000	-0.4255	-0.1894	0.3412
-0.3780	0.3780	0.0000	0.3780	-0.3780	0.0000	0.3780	-0.3780	0.0000	0.3780
0.2969	-0.4352	-0.3412	0.0650	0.2459	-0.4255	0.3780	-0.1286	0.1894	0.4063
-0.1894	0.3412	0.4255	-0.4255	0.3412	-0.1894	0.0000	0.1894	0.3412	0.4255
0.0650	-0.1286	-0.1894	0.2459	-0.2969	0.3412	-0.3780	0.4063	0.4255	0.4352

-27.9393	-26.0916	-23.1952	-19.5073	-15.3556	-11.1091	-7.1450	-3.8156	-1.4168	-0.1616
-----------------	----------	----------	----------	----------	----------	---------	---------	---------	----------------

```
>>
```

Fast Mode: If the initial condition is the 1st eigenvector (red), the transients will decay as $\exp(-27.93t)$

Slow Mode: If the initial condition is the 10th eigenvector (blue), the transients will decay as $\exp(-0.16t)$

7) Modify the program *heat.m* to match the dynamics you calculated for this problem.

- Give the program listing
- Give the response for $V_{in} = 0$ and the initial conditions being
 - The slowest eigenvector
 - The fastest eigenvector
 - A random set of voltages

Code:

```
% 10-stage RC Filter

V = rand(10,1);
dV = 0*V;

dt = 0.01;
t = 0;
V0 = 0;

REF = 1;
Z = 0;

DATA = [];


while(t < 2)

    dV(1) = 7.143*V0 - 14.288*V(1) + 7.143*V(2);
    dV(2) = 7.143*V(1) - 14.288*V(2) + 7.143*V(3);
    dV(3) = 7.143*V(2) - 14.288*V(3) + 7.143*V(4);
    dV(4) = 7.143*V(3) - 14.288*V(4) + 7.143*V(5);
    dV(5) = 7.143*V(4) - 14.288*V(5) + 7.143*V(6);
    dV(6) = 7.143*V(5) - 14.288*V(6) + 7.143*V(7);
    dV(7) = 7.143*V(6) - 14.288*V(7) + 7.143*V(8);
    dV(8) = 7.143*V(7) - 14.288*V(8) + 7.143*V(9);
    dV(9) = 7.143*V(8) - 14.288*V(9) + 7.143*V(10);
    dV(10) = 7.143*V(9) - 7.145*V(10);


    V = V + dV * dt;
    t = t + dt;

    plot([0:10], [V0;V], 'b.-');
    ylim([0,1.2]);
    xlim([0,10]);
    pause(0.01);
    DATA = [DATA ; V'];
end


%pause(2);
%plot(DATA)
```

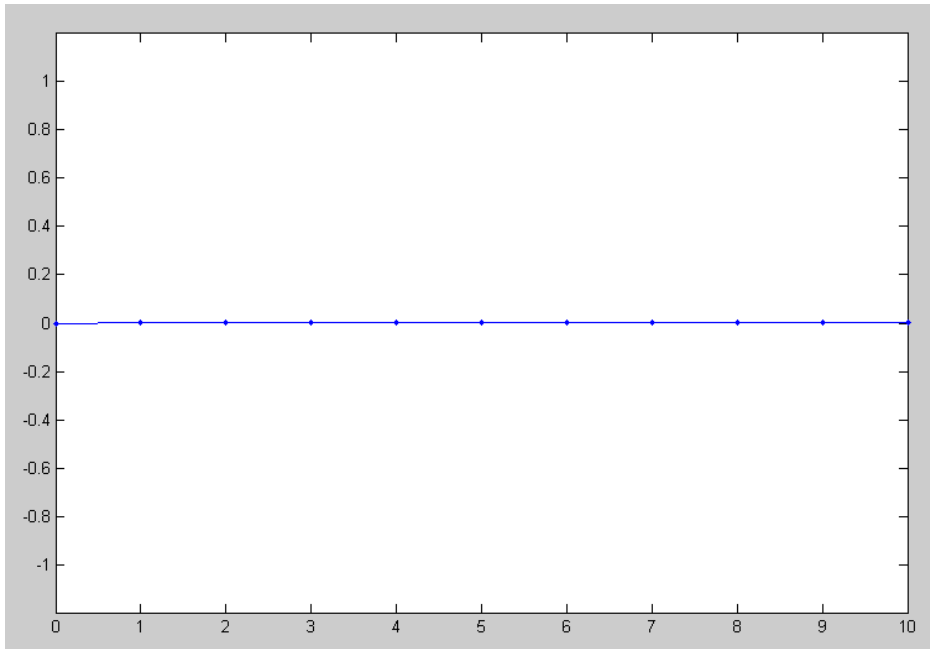

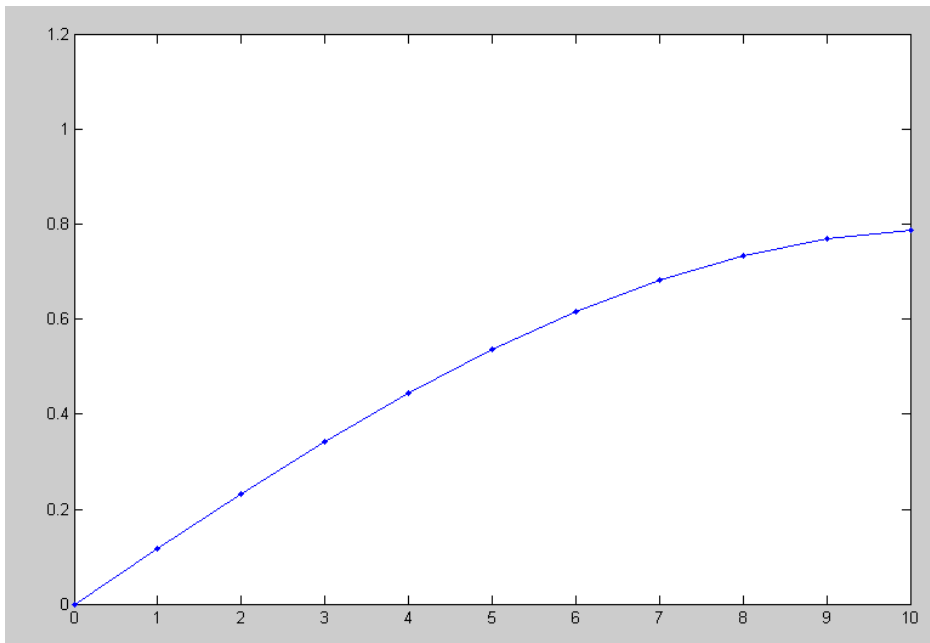Fast Eigenvector: Voltages at t = 2 seconds



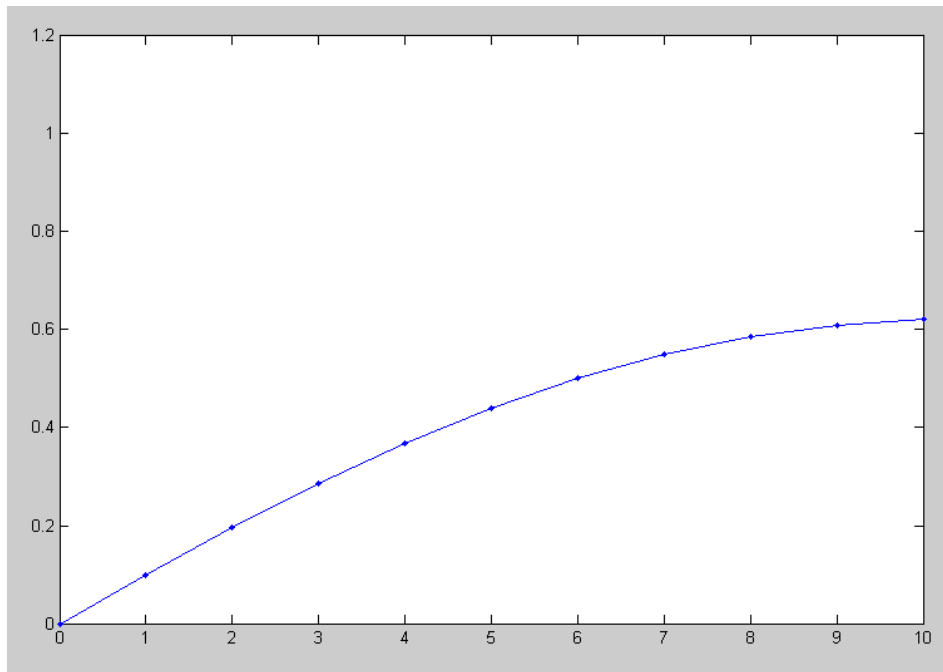Slow Eigenvector: Voltages at t = 2 seconds



Random Initial Condition: Voltages at $t = 2$ seconds