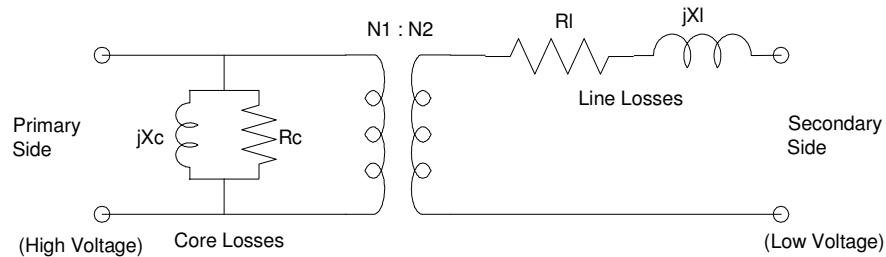


ECE 111: Homework 16

ECE 331 Energy Conversion

1) Determine the circuit model for a 13.2kV : 240V transformer is tested with the following test results:



Transformer Model

	V	Power	pf
Open-Circuit Test	$V_1 = 9.6\text{kV}$	15 W	0.015
Short-Circuit Test	$V_2 = 20\text{V}$	10 W	0.99

For the utility grid on the back of the page....

- 2) Convert the voltages and impedances to the 120V node (right side)
- 3) Write the voltage node equations for this circuit (with transformers removed)
- 4) Determine the voltages at each node
- 5) Determine the efficiency of this system
 - Ignoring the core losses
 - Assumes a large number of customers share these losses
 - Including the core losses
 - Assumes a single customer

