

EE 206: Homework #7

Op Amp Amplifiers. Due Monday, March 4th

1) Design an op-amp circuit to implement

$$Y = 2X$$

Simulate this circuit in PartSim with

- $x(t) = 1V_p$, 1kHz sine wave

Is Y double X and 180 degrees out of phase?

2) Design an op-amp circuit to implement

$$Y = -2X$$

Simulate this circuit in PartSim with

- $x(t) = 1V_p$, 1kHz sine wave

Is Y double X and 180 degrees out of phase?

3) Design an op-amp circuit to implement

$$Y = 2X - 10$$

4) Design an op-amp circuit which outputs

- -10V when $R = 1000$ Ohms
- +10V when $R = 2000$ Ohms

5) Simulate the circuit for problem #4. Plot the output voltage for $1000 < R < 2000$ Ohms

	Vout		
R	Calculated prob 4 - ignoring loading	Calculated including loading	Simulated prob 5
1000			
1200			
1400			
1600			
1800			
2000			