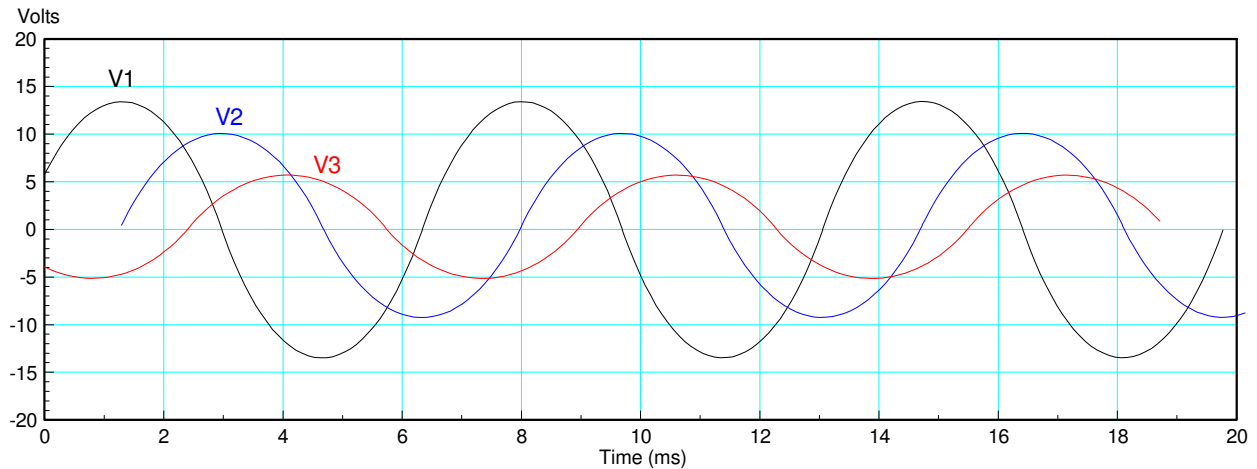


EE 206: Homework #9

Phasors, Passive Circuit Elements, Series and Parallel with Phasors, Voltage Nodes


Due Monday, April 1st

1) Find the frequency and phasor representation for the following voltages



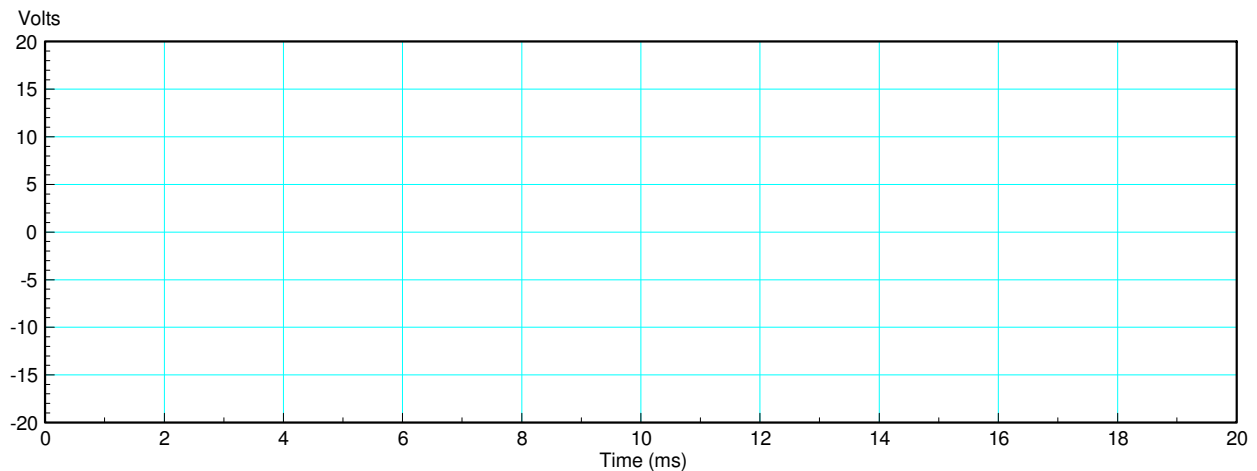2) Sketch $V(t)$. Assume 100Hz sine waves.

- $V(t) = 15\angle -70^\circ$
- $V(t) = 5 - j15$



3) Determine the impedance of a resistor, inductor, and capacitor at 10, 1000, and 10k rad/sec

	$R = 100 \text{ Ohms}$	$L = 10\text{mH}$	$C = 10\mu\text{F}$
10 rad/sec			
1000 rad/sec			
100k rad/sec			


Problem 4: Assume

$$V_{in} = 10 \cos(20t)$$

4a) Write the voltage node equations for the following circuit.

4b) Solve for V1, V2, and V3

4c) Simulate this circuit in PartSim and check your answers

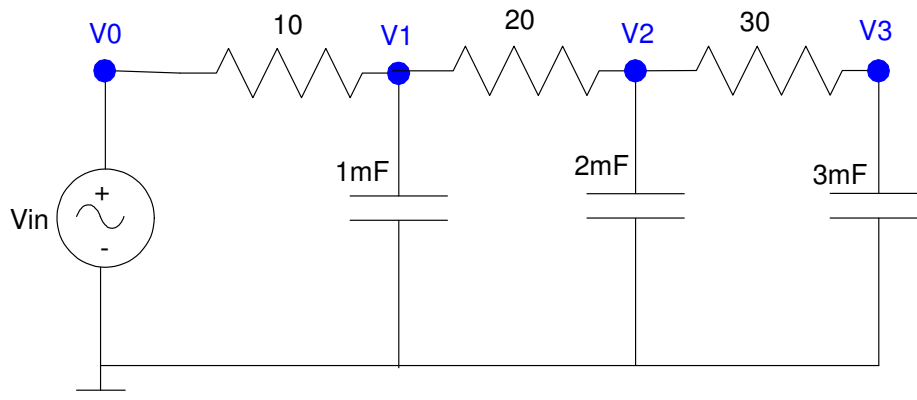

Problem 4


Problem 5) Assume

$$V_{in} = 5 \sin(10t)$$

5a) Write the voltage node equations for the following circuit

5b) Solve for V1, V2, and V3

5c) Simulate this circuit in PartSim and check your answers

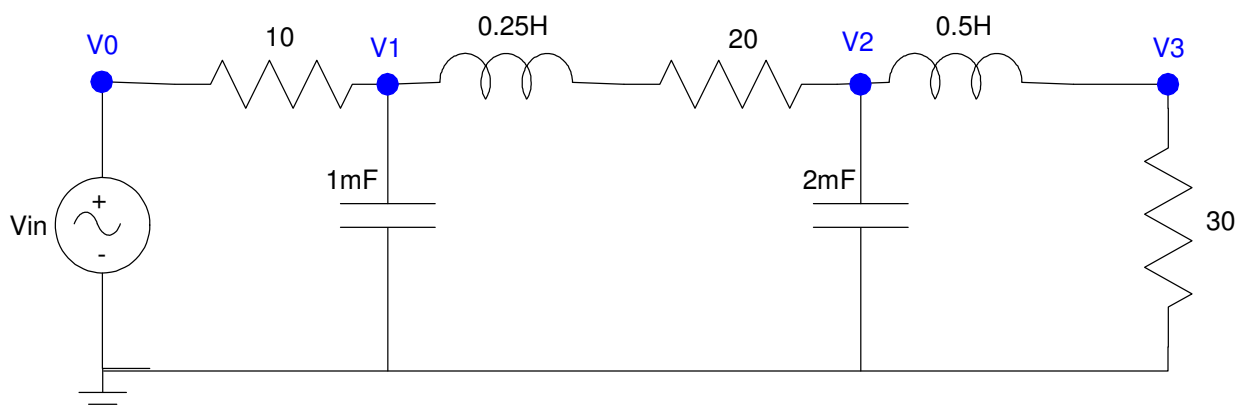

Problem 5