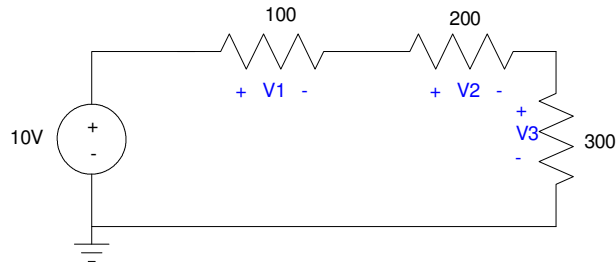


EE 206: Solution #3

Voltage and Current Division. Voltage Nodes. Due Mon, Jan 28th

Voltage Division:

- 1) Use voltage division to determine the voltages V_1 , V_2 , and V_3



$$V = \left(\frac{\text{what you measuring}}{\text{total resistance}} \right) V_{in}$$

$$V_1 = \left(\frac{100}{100+200+300} \right) 10V = 1.6667V$$


$$V_2 = \left(\frac{200}{100+200+300} \right) 10V = 3.3333V$$

$$V_3 = \left(\frac{300}{100+200+300} \right) 10V = 5.0000V$$

Note that

$$V_1 + V_2 + V_3 = 10V$$

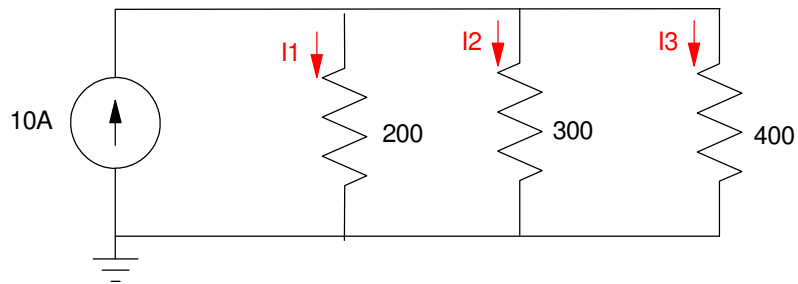2) Use current division to determine the current I_1 , I_2 , and I_3



$$I_x = \left(\frac{\text{Resistance of everything else}}{R_x + \text{Resistance of Everything Else}} \right) I_{in}$$

$$I_1 = \left(\frac{300 \parallel 400}{200 + 300 \parallel 400} \right) 10A$$

$$I_1 = \left(\frac{171.42}{200 + 171.42} \right) 10A = 4.6154A$$

$$I_2 = \left(\frac{200 \parallel 400}{300 + 200 \parallel 400} \right) 10A$$

$$I_2 = \left(\frac{133.33}{300 + 133.33} \right) 10A = 3.0769A$$


$$I_3 = \left(\frac{200 \parallel 300}{400 + 200 \parallel 300} \right) 10A$$

$$I_3 = \left(\frac{120}{400 + 120} \right) 10A = 2.3077A$$

Note that $I_1 + I_2 + I_3 = 10A$

Voltage Nodes:

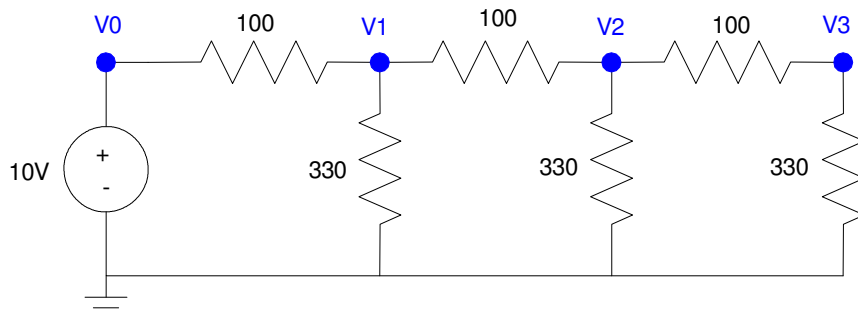3) Write the voltage node equations for the following circuit.



You need to write 4 equations for 4 unknowns. The sum of the currents from the nodes must be zero.

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{100}\right) + \left(\frac{V_1}{330}\right) + \left(\frac{V_1 - V_2}{100}\right) = 0$$

$$\left(\frac{V_2 - V_1}{100}\right) + \left(\frac{V_2}{330}\right) + \left(\frac{V_2 - V_3}{100}\right) = 0$$

$$\left(\frac{V_3 - V_2}{100}\right) + \left(\frac{V_3}{330}\right) = 0$$

Group terms.

$$V_0 = 10$$

$$-\left(\frac{1}{100}\right)V_0 + \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100}\right)V_1 - \left(\frac{1}{100}\right)V_2 = 0$$

$$-\left(\frac{1}{100}\right)V_1 + \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100}\right)V_2 - \left(\frac{1}{100}\right)V_3 = 0$$

$$-\left(\frac{1}{100}\right)V_2 + \left(\frac{1}{100} + \frac{1}{330}\right)V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ -\left(\frac{1}{100}\right) & \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100}\right) & -\left(\frac{1}{100}\right) & 0 \\ 0 & -\left(\frac{1}{100}\right) & \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100}\right) & -\left(\frac{1}{100}\right) \\ 0 & 0 & -\left(\frac{1}{100}\right) & \left(\frac{1}{100} + \frac{1}{330}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
a1 = [1,0,0,0];  
a2 = [-1/100, 1/100+1/330+1/100, -1/100, 0];  
a3 = [0, -1/100, 1/100+1/330+1/100, -1/100];  
a4 = [0, 0, -1/100, 1/100+1/330];
```

```
A = [a1;a2;a3;a4]
```

```
1.0000    0    0    0  
-0.0100    0.0230   -0.0100    0  
    0   -0.0100    0.0230   -0.0100  
    0    0   -0.0100    0.0130
```


```
B = [10;0;0;0]
```

```
10  
0  
0  
0
```


```
V = inv(A)*B
```

```
V0  10.0000  
V1   6.0539  
V2   3.9424  
V3   3.0256
```

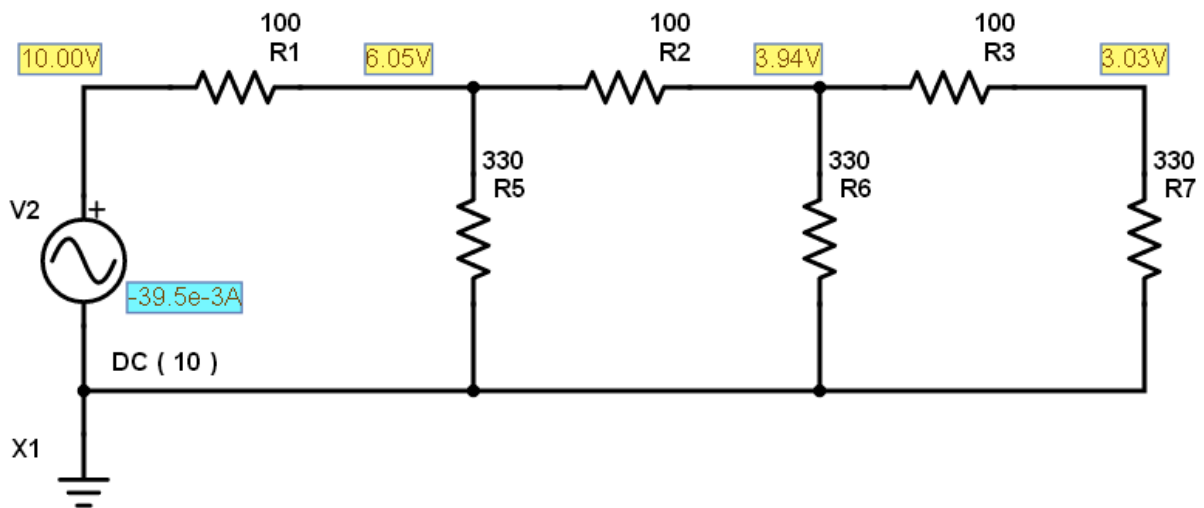4) Check your answers in PartSim (or similar program)



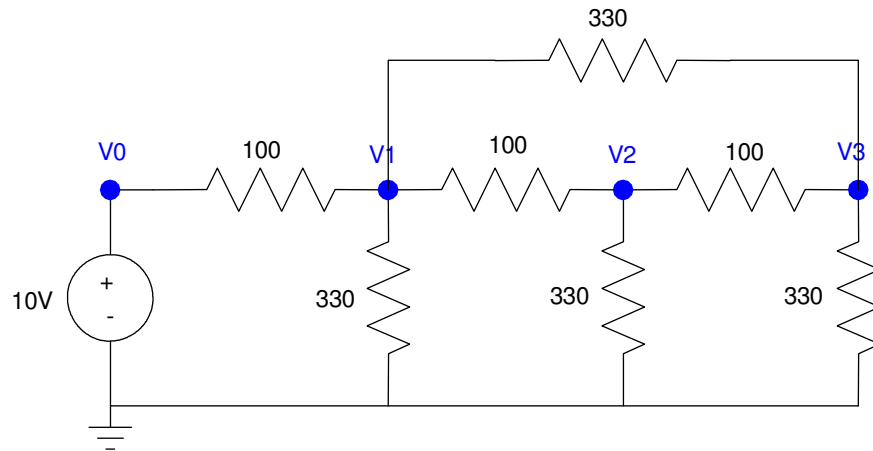5) Write the voltage node equations for the following circuit. Solve for V_1 .. V_3 using Matlab (or similar program)



With 4 voltage nodes, you need to write 4 equations for 4 unknowns (3 also works if you set $V_0 = 10$)

$$V_0 = 10$$

$$\left(\frac{V_1 - V_0}{100} \right) + \left(\frac{V_1}{330} \right) + \left(\frac{V_1 - V_2}{100} \right) + \left(\frac{V_1 - V_3}{330} \right) = 0$$

$$\left(\frac{V_2 - V_1}{100} \right) + \left(\frac{V_2}{330} \right) + \left(\frac{V_2 - V_3}{100} \right) = 0$$

$$\left(\frac{V_3 - V_2}{100} \right) + \left(\frac{V_3}{330} \right) + \left(\frac{V_3 - V_1}{330} \right) = 0$$

Group terms

$$V_0 = 10$$

$$-\left(\frac{1}{100} \right) V_0 + \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100} + \frac{1}{330} \right) V_1 - \left(\frac{1}{100} \right) V_2 - \left(\frac{1}{330} \right) V_3 = 0$$

$$-\left(\frac{1}{100} \right) V_1 + \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100} \right) V_2 - \left(\frac{1}{100} \right) V_3 = 0$$

$$-\left(\frac{1}{330} \right) V_1 - \left(\frac{1}{100} \right) V_2 + \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{330} \right) V_3 = 0$$

Place in matrix form

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ -\left(\frac{1}{100}\right) & \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100} + \frac{1}{330}\right) & -\left(\frac{1}{100}\right) & -\left(\frac{1}{330}\right) \\ 0 & -\left(\frac{1}{100}\right) & \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{100}\right) & -\left(\frac{1}{100}\right) \\ 0 & -\left(\frac{1}{330}\right) & -\left(\frac{1}{100}\right) & \left(\frac{1}{100} + \frac{1}{330} + \frac{1}{330}\right) \end{bmatrix} \begin{bmatrix} V_0 \\ V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Solve in Matlab

```
a1 = [1,0,0,0];
a2 = [-1/100, 1/100+1/330+1/100+1/330, -1/100, -1/330];
a3 = [0, -1/100, 1/100+1/330+1/100, -1/100];
a4 = [0, -1/330, -1/100, 1/100+1/330+1/330];
```

```
A = [a1;a2;a3;a4]
```

```
B = [10;0;0;0]
```

```
V = inv(A)*B
```

A =

```
1.0000    0    0    0
-0.0100    0.0261 -0.0100 -0.0030
0    -0.0100    0.0230 -0.0100
0    -0.0030 -0.0100    0.0161
```

B =


```
10
0
0
0
```

V =

```
v0    10.0000
v1     5.8547
v2     4.1415
v3     3.6833
```

```
>>
```

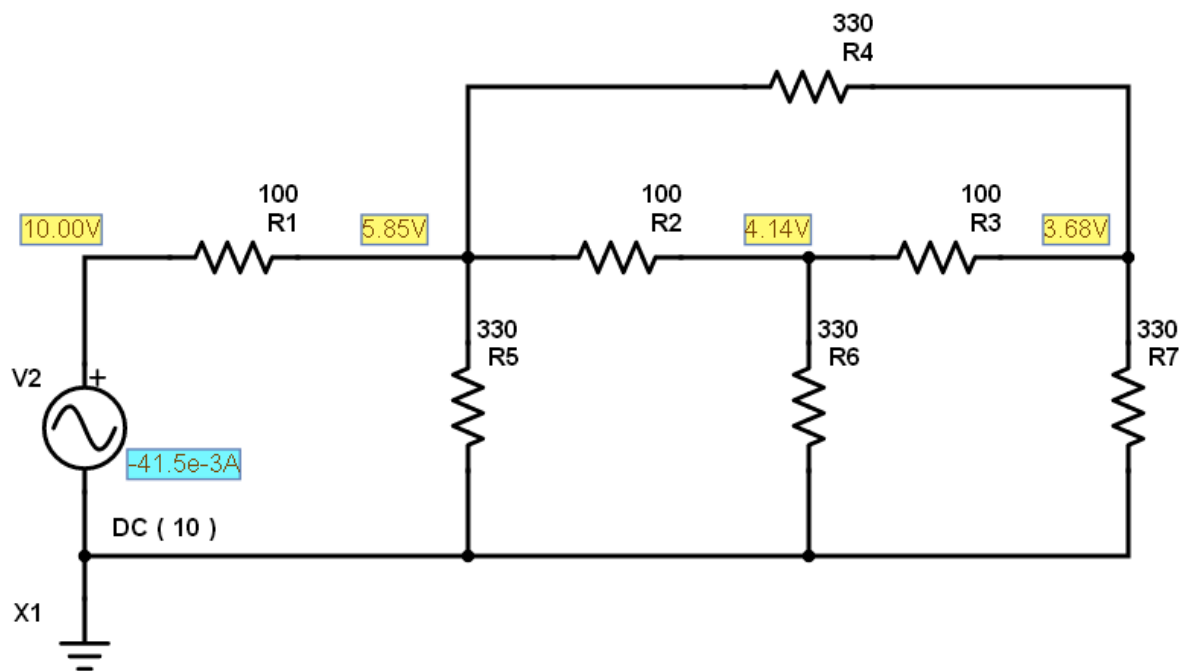6) Check your answers in PartSim (or similar program)



	Calculated prob 5	Simulated prob 6
V1	5.8547V	5.85 V
V2	4.1415V	4.14 V
V3	3.6833V	3.68 V