

## Superposition (take 3)

Previously, we looked at how to analyze an AC to DC converter and a Buck converter. To solve these circuits, we changed the problem so that the input contained


- A DC signal, and
- An AC signal

The resulting output that we calculated was close but slightly off from the actual output voltage.

A more accurate way to analyze these circuits is to express the input in terms of its Fourier Series. Then, superposition can be used to determine the output at each frequency.
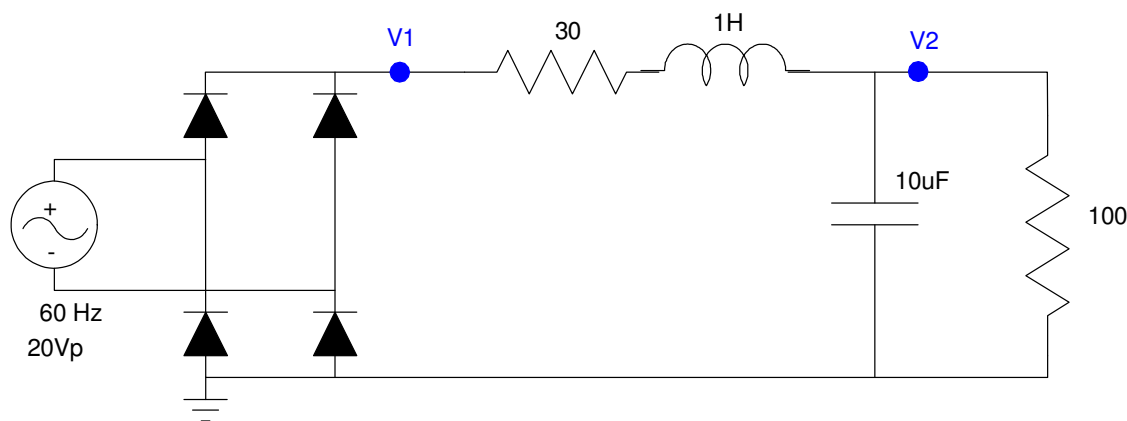
### Example 1: AC to DC Converter

The following circuit is an AC to DC converter that we'll cover in ECE 320 Electronics I. Determine the voltage at V2:



AC to DC Converter covered in ECE 320 Electronics I

From PartSim, the signal at V1 is

$$v_1(t) = |20 \sin(377t)| - 1.4$$

Previously, we approximated this as

- A DC term which matched the DC term of  $v_1$ , and
- An AC term which was the same frequency as  $v_1(t)$  (120Hz) and same peak-to-peak voltage

$$v_1(t) \approx 11.33 + 10 \cos(754t)$$

A more accurate approximation would be the Fourier Series approximation.

**Step 1: Find the Fourier Series Approximation for  $x(t)$ :**

```

T = pi;
t = [0:0.0001:1]' * T;
Wo = 2*pi/T;

x = 20*sin(t) - 1.4;

a0 = mean(x)

a1 = 2*mean(x .* cos(Wo*t))
a2 = 2*mean(x .* cos(2*Wo*t))
a3 = 2*mean(x .* cos(3*Wo*t))
a4 = 2*mean(x .* cos(4*Wo*t))
a5 = 2*mean(x .* cos(5*Wo*t))

b1 = 2*mean(x .* sin(Wo*t))
b2 = 2*mean(x .* sin(2*Wo*t))
b3 = 2*mean(x .* sin(3*Wo*t))
b4 = 2*mean(x .* sin(4*Wo*t))
b5 = 2*mean(x .* sin(5*Wo*t))

```

resulting in

n	0	1	2	3	4	5
w (rad/sec)	0	754	1,508	2,262	3,016	3,770
$a_n$	11.331	-8.488	-1.698	-0.728	-0.404	-0.257
$b_n$	0	0	0	0	0	0

meaning

$$v_1(t) = 11.331 - 8.488 \cos(754t) - 1.698 \cos(1508t) - 0.728 \cos(2262t) \\ - 0.404 \cos(3016t) - 0.257 \cos(3770t)$$

Not that this is a little different from what we previously approximated the waveform at V1 as:

$$v_1(t) \approx 11.33 + 10 \cos(754t)$$

The Fourier series approximation is

- More accurate, but
- Much harder to determine.


Proceeding with the Fourier Series approximation, the actual waveform at V1 and it's approximation taken out to the 5th harmonic are:

```

y = a0 + a1*cos(Wo*t) + a2*cos(2*Wo*t) + a3*cos(3*Wo*t) + a4*cos(4*Wo*t) + a5*cos(5*Wo*t);
y = y + b1*sin(Wo*t) + b2*sin(2*Wo*t) + b3*sin(3*Wo*t) + b4*sin(4*Wo*t) + b5*sin(5*Wo*t);


```

```
plot(t,x,'b',t,y,'r');
```

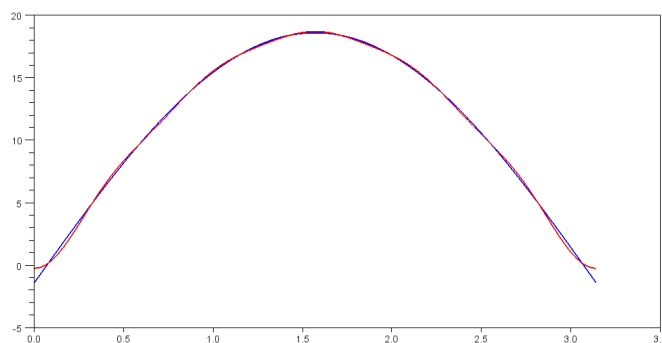

Signal at V1 (blue) and Fourier Series Approximation (red)
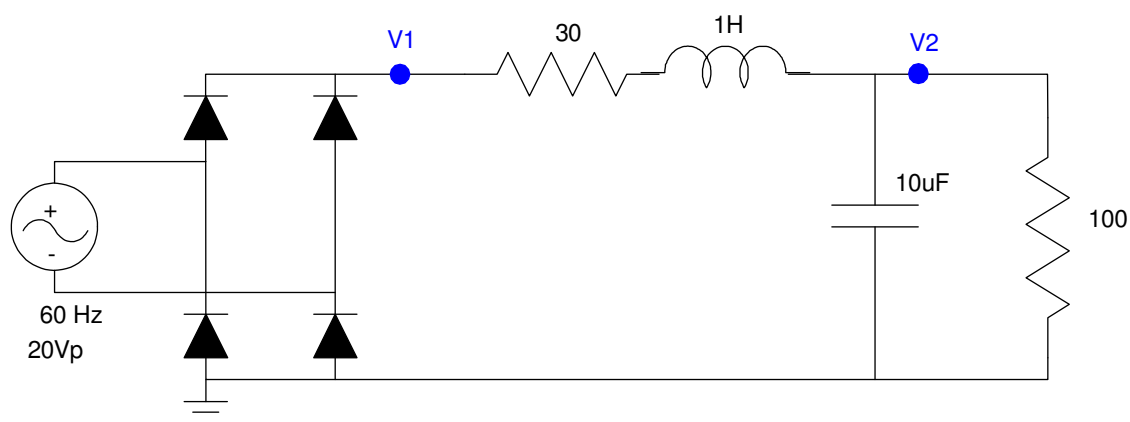
### Step 2: Use Superposition at Each Frequency



$$v_1(t) = 11.331 - 8.488 \cos(754t) - 1.698 \cos(1508t) - 0.728 \cos(2262t) \\ - 0.404 \cos(3016t) - 0.257 \cos(3770t)$$

DC:

$$V_1 = 11.331$$

$$V_2 = \left( \frac{100}{100+30} \right) \cdot 11.331$$

$$V_2 = 8.716$$

754 rad/sec (120Hz: fundamental)

$$v_1(t) = -8.488 \cos(754t)$$

$$V_1 = -8.488 + j0$$

$$C \rightarrow \frac{1}{j\omega C} = -j132.6\Omega$$

$$L \rightarrow j\omega L = j754\Omega$$

$$-j132.6 \parallel 100 = 63.76 - j48.07$$

$$V_2 = \left( \frac{(63.76 - j48.07)}{(63.76 - j48.07) + (30 + j754)} \right) \cdot (8.488 + j0)$$

$$V_2 = -0.468 - j0.829$$

$$v_2(t) = -0.468 \cos(754t) + 0.829 \sin(754t)$$

At 1508 rad/sec (240Hz: 2nd harmonic)

$$v_1 = -1.698 \cos(1508t)$$

$$V_1 = -1.698 + j0$$

$$\omega = 1508$$

$$C \rightarrow \frac{1}{j\omega C} = -j66.31\Omega$$

$$L \rightarrow j\omega L = j1508\Omega$$

$$100 \parallel -j66.31 = 30.54 - j46.05$$

$$V_2 = \left( \frac{30.54 - j46.05}{(30.54 - j46.05) + (30 + j1508)} \right) \cdot (-1.698 + j0)$$

$$V_2 = 0.052 + j0.038$$

$$v_2(t) = 0.052 \cos(1508t) - 0.038 \sin(1508t)$$

---

At 2262 rad/sec: (360Hz: 3rd harmonic)

$$v_1(t) = -0.728 \cos(2262t)$$

$$\omega = 2262$$

$$V_1 = -0.728 + j0$$

$$C \rightarrow \frac{1}{j\omega C} = -j44.21\Omega$$

$$L \rightarrow j\omega L = j2262\Omega$$

$$100 \parallel -j44.21 = 16.35 - j36.98$$

$$V_2 = \left( \frac{(16.35 - j36.98)}{(16.35 - j36.98) + (30 + j2262)} \right) \cdot (-0.728 + j0)$$

$$V_2 = 0.012 + j0.006$$

$$v_2(t) = 0.012 \cos(2262t) - 0.006 \sin(2262t)$$

At 3016 rad/sec (480Hz: 4th harmonic)

$$v_1(t) = -0.404 \cos(3016t)$$

$$V_1 = -0.404 + j0$$

$$C \rightarrow \frac{1}{j\omega C} = -j33.15\Omega$$

$$L \rightarrow j\omega L = j3016\Omega$$

$$100 \parallel -j33.15\Omega = 9.90 - j29.87$$

$$V_2 = \left( \frac{(9.90 - j29.87)}{(9.90 - j29.87) + (30 + j3016)} \right) \cdot (-0.404 + j0)$$

$$V_2 = 0.004 + j0.001$$

$$v_2(t) = 0.004 \cos(3016t) - 0.001 \sin(3016t)$$

At 3770 rad/sec (5th harmonic)

$$v_1(t) = -0.257 \cos(3770t)$$

$$V_1 = -0.257 + j0$$

$$C \rightarrow \frac{1}{j\omega C} = -j26.53\Omega$$

$$L \rightarrow j\omega L = j3770\Omega$$

$$100 \parallel -j26.53\Omega = 6.58 - j24.79$$

$$V_2 = \left( \frac{(6.58 - j24.79)}{(6.58 - j24.79) + (30 + j3770)} \right) \cdot (-0.257 + j0)$$

$$V_2 = 0.0017 + j0.0005$$


$$v_2(t) = 0.0017 \cos(3370t) - 0.0005 \sin(3370t)$$

The total answer will be the sum of all the terms


$$v_2(t) = 8.716$$

$$\begin{aligned} & -0.468 \cos(754t) + 0.829 \sin(754t) \\ & +0.052 \cos(1508t) - 0.038 \sin(1508t) \\ & +0.012 \cos(2262t) - 0.006 \sin(2262t) \\ & +0.004 \cos(3016t) - 0.001 \sin(3016t) \\ & +0.0017 \cos(3370t) - 0.0005 \sin(3370t) \\ & +\dots \end{aligned}$$

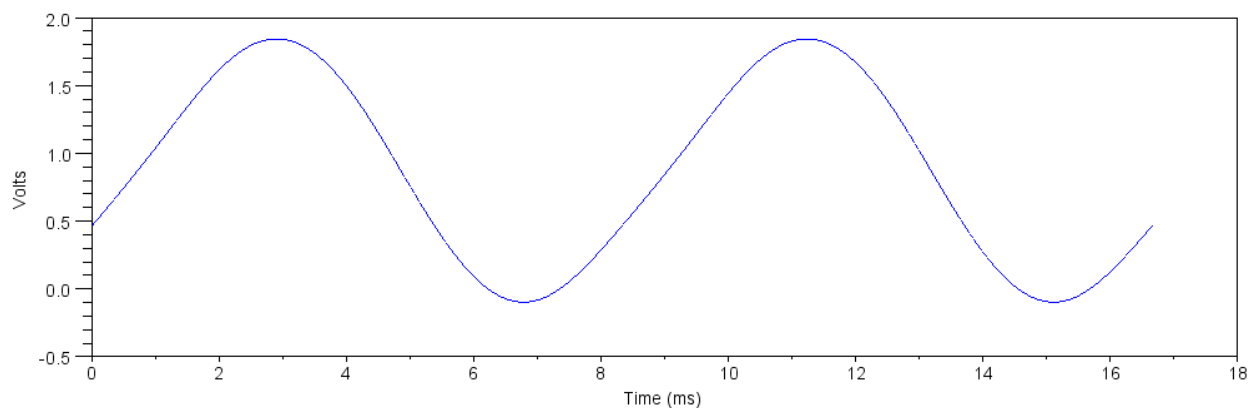Comparing the calculated and PartSim signal at V2:



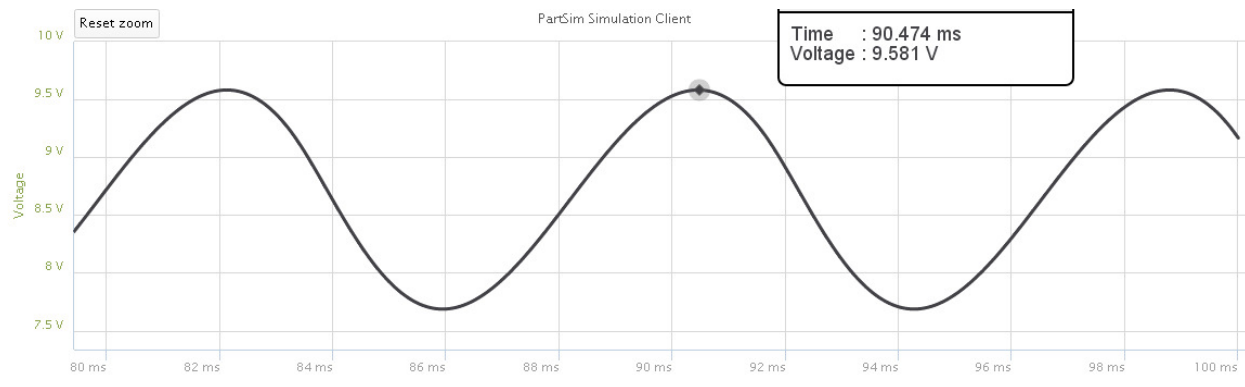Calculate Signal At V2: Fourier Series Taken Out to the 5th Harmonic



Signal at V2 as computed by PartSim

	Calculated V2 (lecture #30)	PartSim V2	Calculated V2 (Fourier Series)
DC Value	8.70 V	8.644 V	8.716 V
AC Value	2.242 Vpp	1.895 Vpp	1.903Vpp

---

Note the following:

- By taking the Fourier Series approximation for the signal at V1, our computed answer (column #4) matches up with the simulation results very well.
- The reason our previous answer from lecture #30 (column #2) was off is we overestimated the 1st harmonic. Since V1 is 20Vpp, we assumed that the 1st harmonic was also 20Vpp. Actually, it's 16.98Vpp (2 x 8.488V)
- In theory, you have to take the Fourier Series out to infinity. Actually, you can get a pretty good approximation just using the DC term and the 1st harmonic. The signal at V2 was

$$\begin{aligned}
 v_2(t) = & 8.716 \\
 & -0.468 \cos(754t) + 0.829 \sin(754t) \\
 & +0.052 \cos(1508t) - 0.038 \sin(1508t) \\
 & +0.012 \cos(2262t) - 0.006 \sin(2262t) \\
 & +0.004 \cos(3016t) - 0.001 \sin(3016t) \\
 & +0.0017 \cos(3370t) - 0.0005 \sin(3370t) \\
 & +\dots
 \end{aligned}$$

It isn't that bad of an approximation to only include the first two terms of V2:

$$v_2(t) \approx 8.716 - 0.468 \cos(754t) + 0.829 \sin(754t)$$

meaning it isn't that bad of an approximation to take V1:

$$\begin{aligned}
 v_1(t) = & 11.331 - 8.488 \cos(754t) - 1.698 \cos(1508t) - 0.728 \cos(2262t) \\
 & -0.404 \cos(3016t) - 0.257 \cos(3370t)
 \end{aligned}$$

and only consider the first two terms:

$$v_1(t) \approx 11.331 - 8.488 \cos(754t)$$

This is what we did back in lecture #30, only with a slightly less accurate way of determining the amplitude of the 1st harmonic. A better (and harder) way to do this is to use a Fourier Series approximation taken out to two terms (DC and AC fundamental).