

---

# **Resistors in Series and Parallel**

## **ECE 211 Circuits I Lecture #3**

Please visit [Bison Academy](#) for corresponding  
lecture notes, homework sets, and solutions

---

# Objective

- Simplify a resistor network
- Find the equivalent resistance between two terminals

## Approach

- Combine resistors that are in series
- Combine resistors that are in parallel
- Keep going until you are left with a single resistance

## Note:

- Not always possible
-

## Resistors in Series:

- Series: All the current through R1 also goes through R2
- $I(R1) = I(R2) = I(R3)$

Problem: Find the net resistance of this circuit:


Using Kirchoff's voltage law:

$$V_{in} = V1 + V2 + V3$$

$$V_{in} = I \cdot R_1 + I \cdot R_2 + I \cdot R_3$$

$$V_{in} = I \cdot (R_1 + R_2 + R_3)$$

$$V_{in} = I \cdot R$$

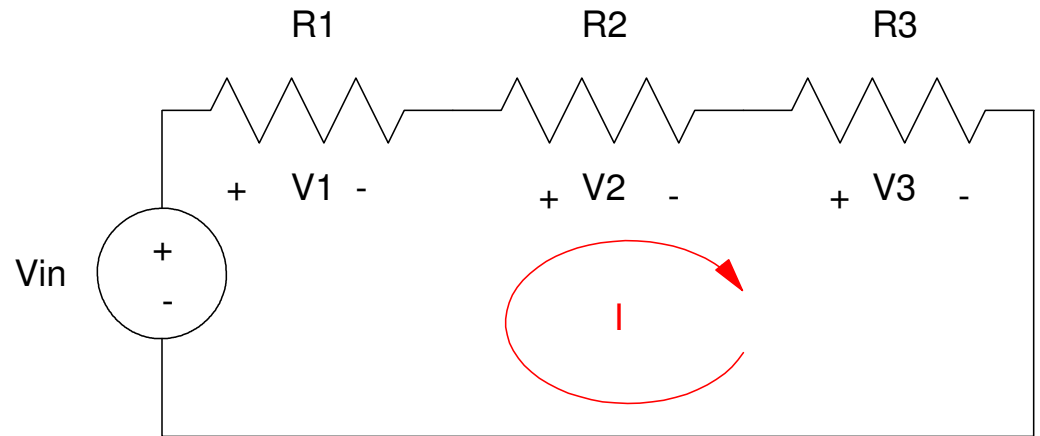

Resistors in series add

## Examples:

Let  $R_1 = 100\ \Omega$ ,  $R_2 = 200\ \Omega$ ,  $R_3 = 300\ \Omega$ . Find the total resistance.

$$R_{net} = R_1 + R_2 + R_3$$

$$R_{net} = 100\ \Omega + 200\ \Omega + 300\ \Omega$$

$$R_{net} = 600\ \Omega$$


Let  $R_1 = 100\ \Omega$ ,  $R_2 = 200\ \Omega$ ,  
 $R_{net} = 1000\ \Omega$ . Find  $R_3$ .

Answer: Resistors in series add:

$$R_{net} = R_1 + R_2 + R_3$$

$$1000\ \Omega = 100\ \Omega + 200\ \Omega + R_3$$

$$R_3 = 700\ \Omega$$

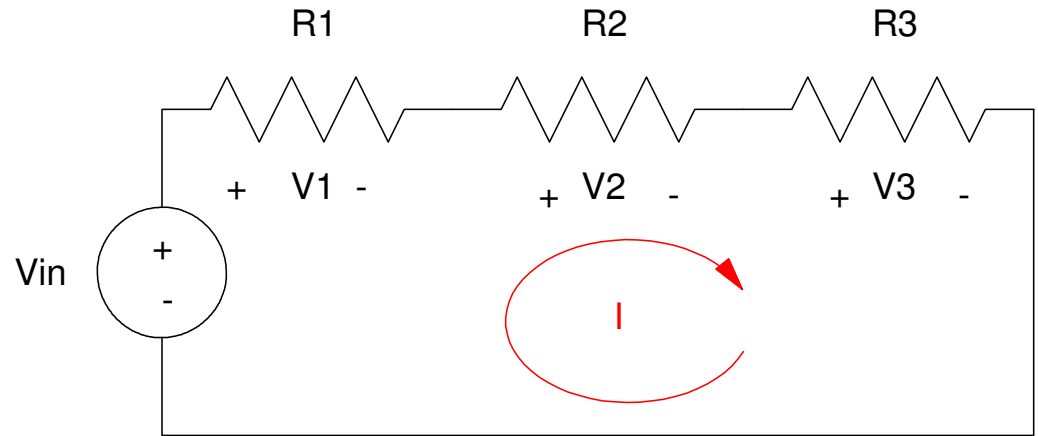

## Resistors in Parallel:

- Parallel: The voltages are the same on both sides of each resistor
- $V_{a1} = V_{b1} = V_{c1}$
- $V_{a2} = V_{b2} = V_{c2}$

Find the net resistance:

$$I_{in} = I_1 + I_2 + I_3$$

$$I_{in} = \left(\frac{V_{in}}{R_1}\right) + \left(\frac{V_{in}}{R_2}\right) + \left(\frac{V_{in}}{R_3}\right)$$


$$I_{in} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) V_{in}$$

$$V_{in} = I_{in} \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)^{-1}$$

$$V_{in} = I_{in} \cdot R$$

In general:
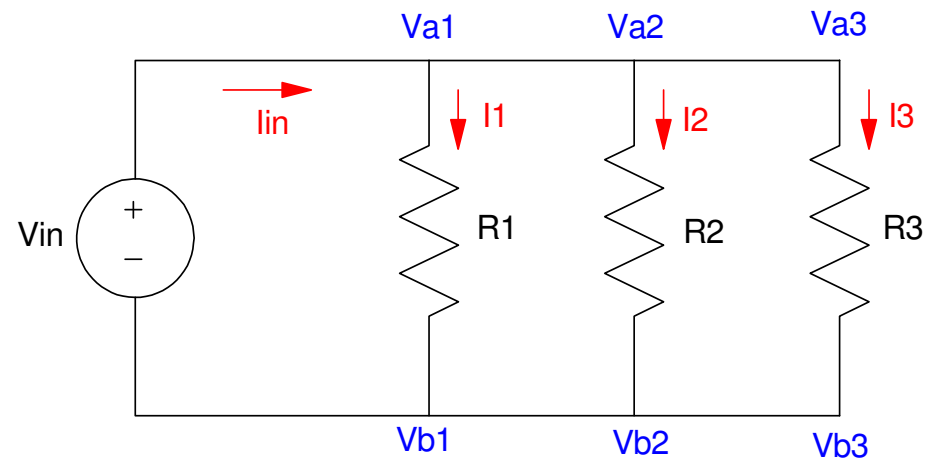
$$R_{net} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots\right)^{-1}$$



## Examples:

Let  $R_1 = 100 \text{ Ohms}$ ,  $R_2 = 200 \text{ Ohms}$ ,  $R_3 = 300 \text{ Ohms}$ . Find the total resistance.

$$R_{net} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$


$$R_{net} = \left( \frac{1}{100} + \frac{1}{200} + \frac{1}{300} \right)^{-1}$$

$$R_{net} = 54.54 \Omega$$

Let  $R_2 = 200 \text{ Ohms}$ ,  $R_3 = 300 \text{ Ohms}$ ,  $R_{net} = 100 \text{ Ohms}$ . Find  $R_1$ .

$$R_{net} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$
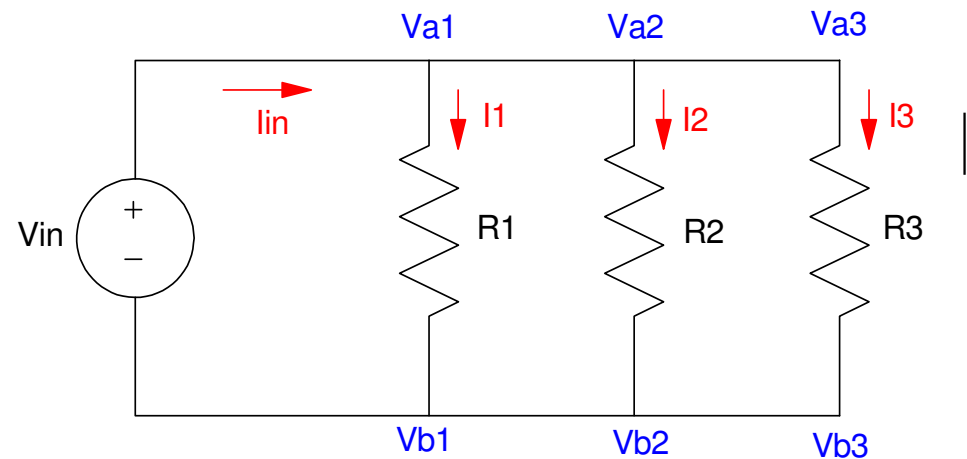
$$100 \Omega = \left( \frac{1}{R_1} + \frac{1}{200} + \frac{1}{300} \right)^{-1}$$



---

## Find the resistance from a to b


Combine resistors that are in series and parallel

Series:

- All current through R1 also goes through R2

Parallel

- Voltages on the same on both sides

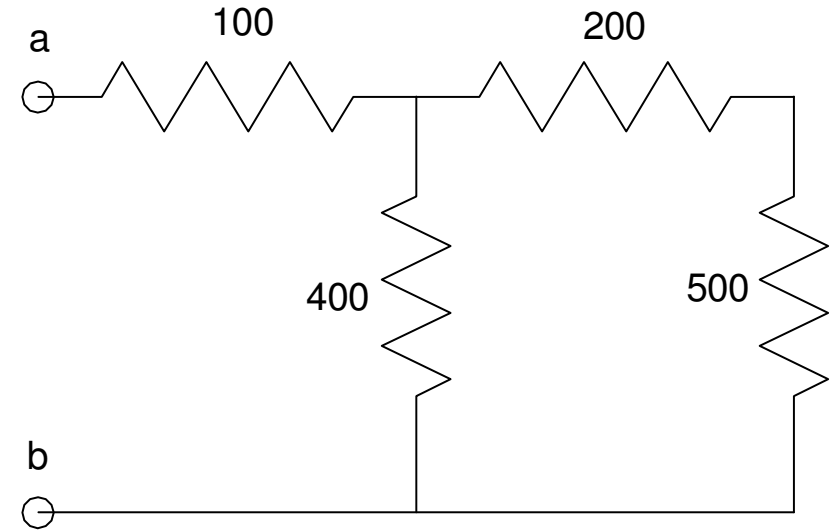

---

## Solution:

The 200 and 500 Ohm resistor are in series

$$200 + 500 = 700$$


This is in parallel with 400 Ohms

$$700 \parallel 400 = \left( \frac{1}{700} + \frac{1}{400} \right)^{-1} = 254.54$$

This is in series with 100 Ohms

$$254.54 + 100 = 354.54$$

The net resistance is 354.54 Ohms.

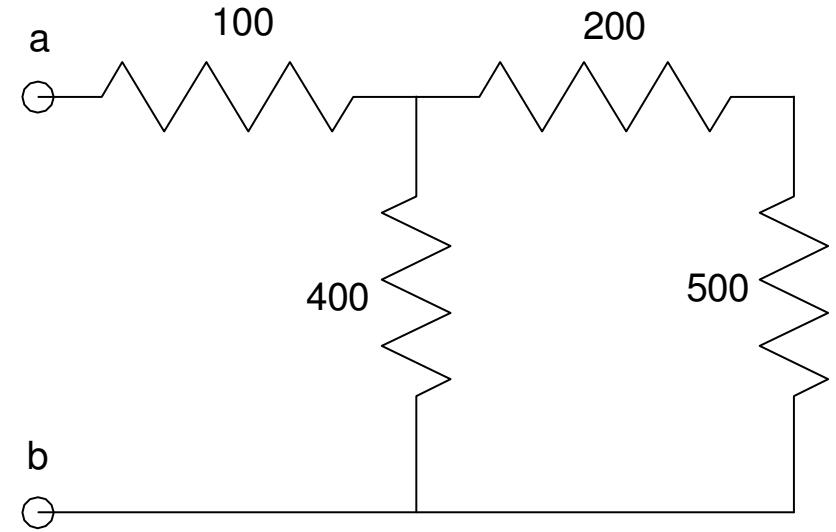

# Matlab Calculations

```
>> R1 = 200 + 500
```


```
R1 = 700
```

```
>> R2 = 1 / (1/R1 + 1/400)
```

```
R2 = 254.5455
```

```
>> R3 = R2 + 100
```

```
R3 = 354.5455
```

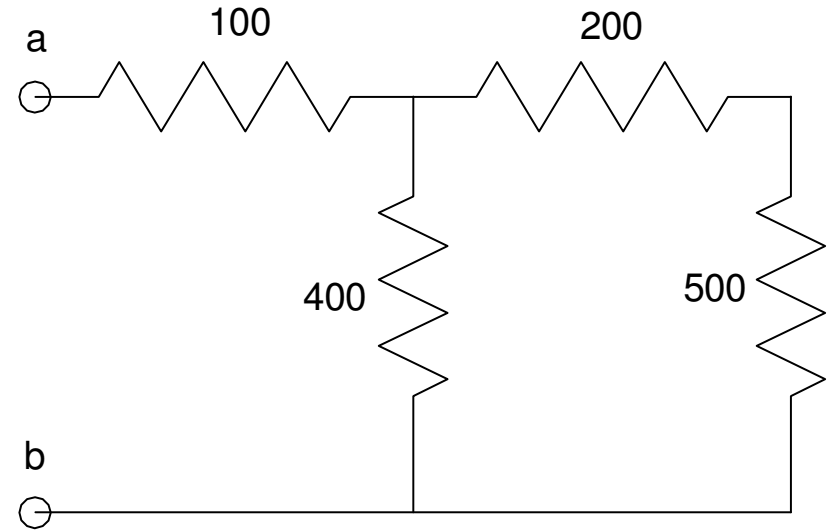

# HP42 Calculations (Free42 app)

RPN Calculators are really efficient at these types of calculations

- HP is essentially a company of electrical and computer engineers
- They likewise build really good calculators for ECE majors
- Free app on your cell phone



Note: These use Reverse Polish Notation (RPN)

- No equals sign
- Operation operate on the stack
  - +  $Y + X \rightarrow X$
  - -  $Y - X \rightarrow X$
  - \*  $Y * X \rightarrow X$
  - /  $Y / X \rightarrow X$


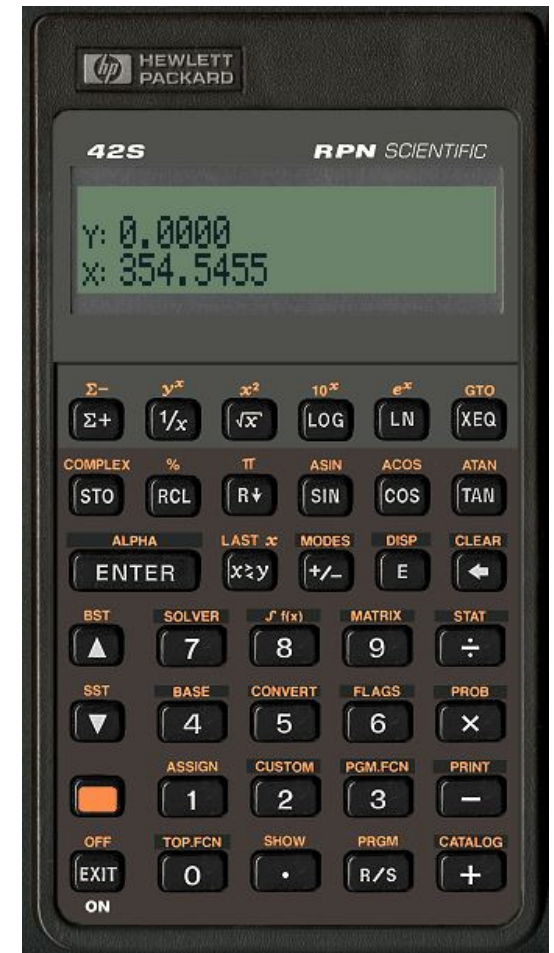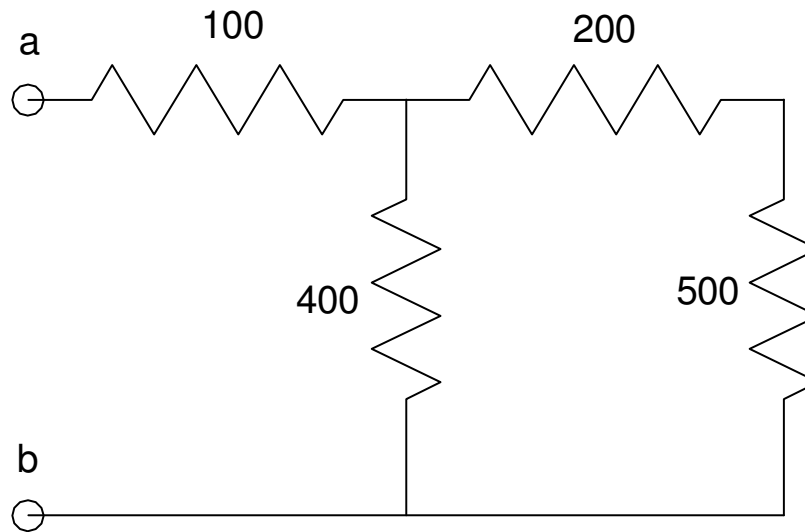
# RPN Calculations

200  
enter  
500  
+  
  
1/x  
400  
1/x  
+  
1/x  
  
100  
+



# Checking in CircuitLab



Build the circuit in CircuitLab

- Apply a test voltage (10V)
- Measure the net current draw
  - $I = 28.21\text{mA}$
- Compute the net resistance

$$R = \frac{V}{I}$$

$$R = \frac{10\text{V}}{28.21\text{mA}}$$

$$R = 354.48\Omega$$

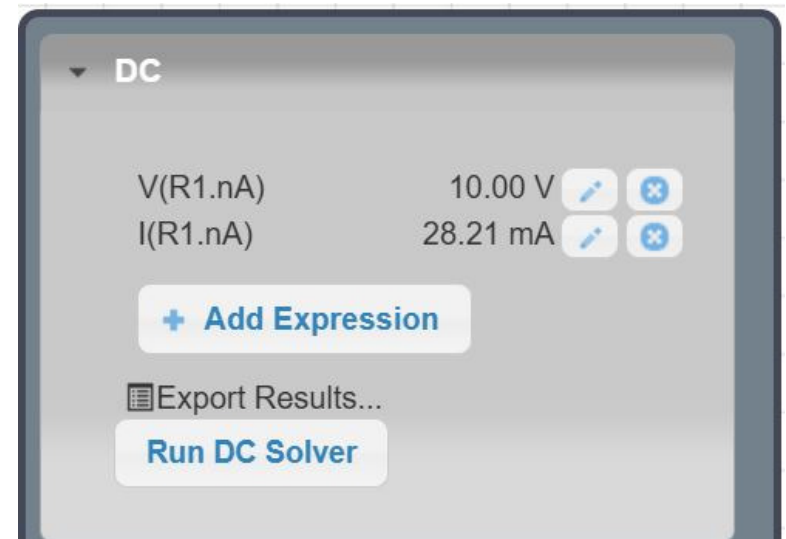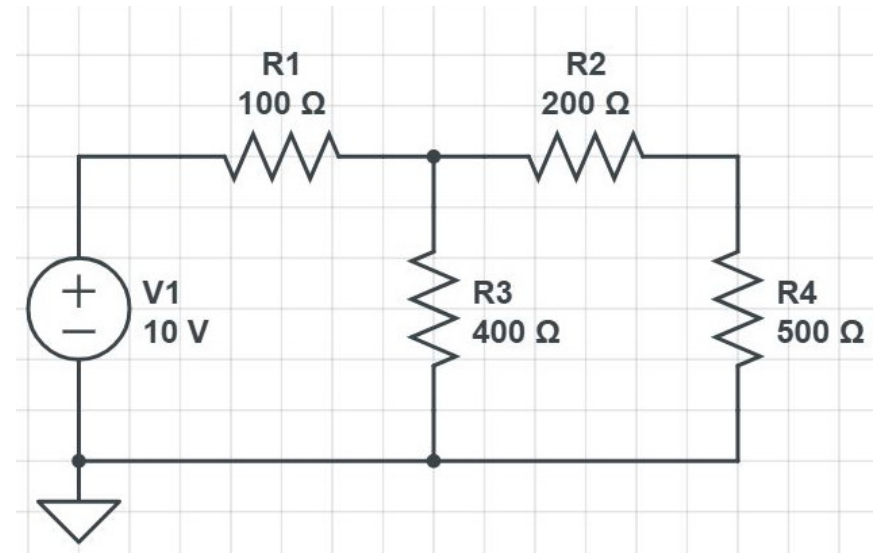

# Check in Lab

Build the circuit on a breadboard


Apply a test voltage

- Whatever is convenient
- 5.0V is usually available

Measure the current draw

- Measure the voltage across the 100 Ohm resistor
- Compute the current

$$I = \frac{V_1}{R_1}$$

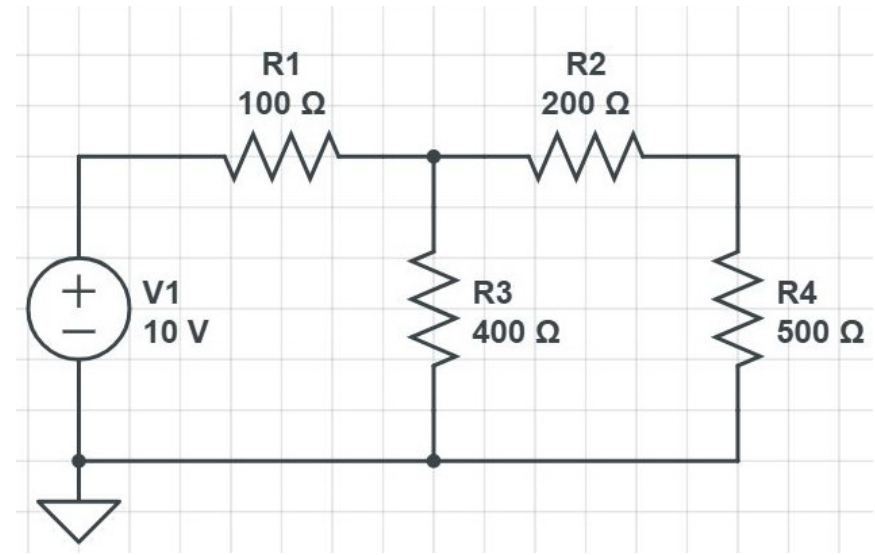

---

# CircuitLab vs Chegg vs ChatGPT

CircuitLab is really useful


- You can check your calculations using CircuitLab
- Your results should match
- Chegg isn't needed
- ChatGPT isn't needed

If you want to know if your calculations are correct

- Check using CircuitLab, or
- Build the circuit and take measurements in lab
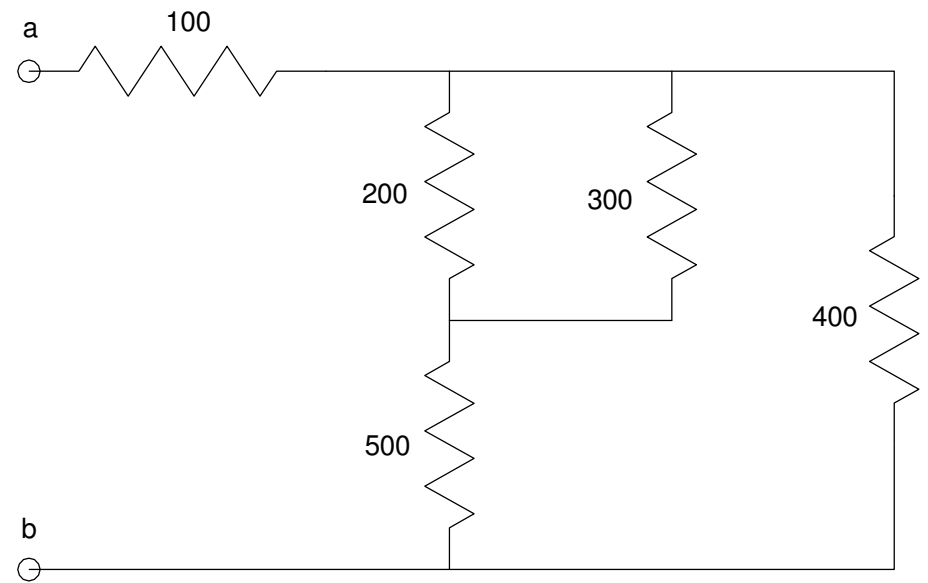
## Example 2: Find $R_{ab}$

- Combine resistors that are in series
- Combine resistors that are in parallel



## Calculations

The 200 and 300 are in parallel

$$200 \parallel 300 = 120 \text{ Ohms}$$

This is in series with 500


$$120 + 500 = 620$$

This is in parallel with 400

$$620 \parallel 400 = 243.137$$

This is in series with 100

$$243.137 + 100 = \mathbf{343.137}$$

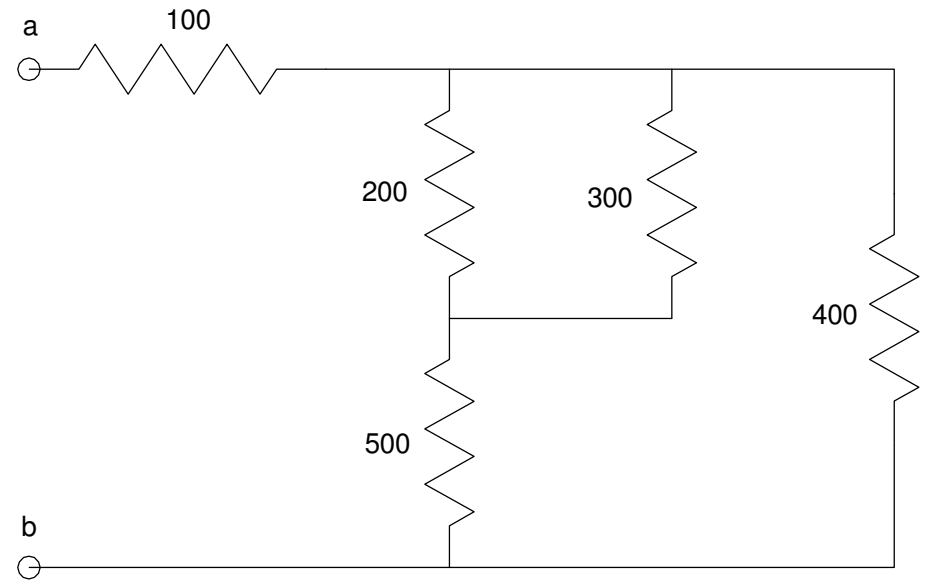

# Calculations in Matlab

```
>> R1 = 1 / (1/200 + 1/300)
```

```
R1 = 120
```

```
>> R2 = R1 + 500
```


```
R2 = 620
```

```
>> R3 = 1 / ( 1/R2 + 1/400)
```

```
R3 = 243.1373
```



```
>> Rab = R3 + 100
```

```
Rab = 343.1373
```

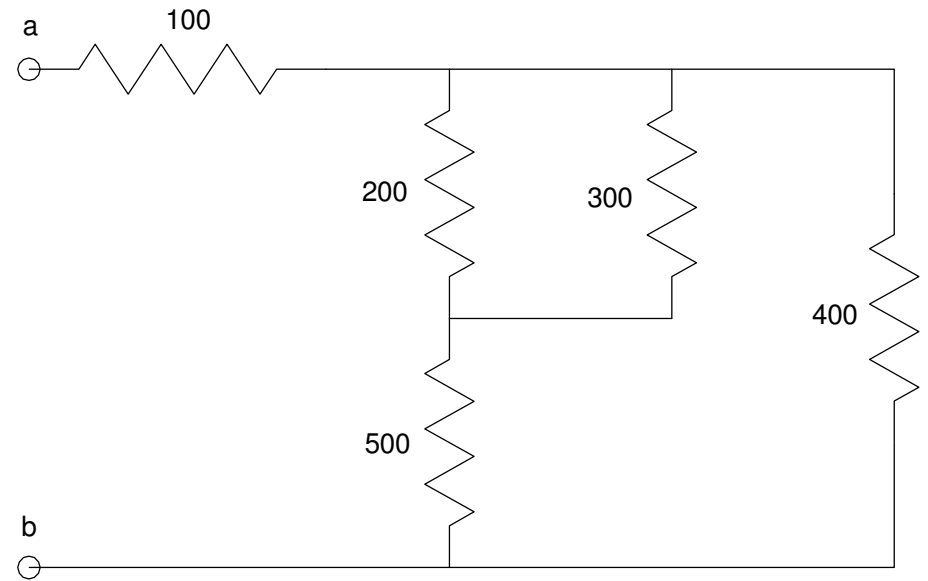
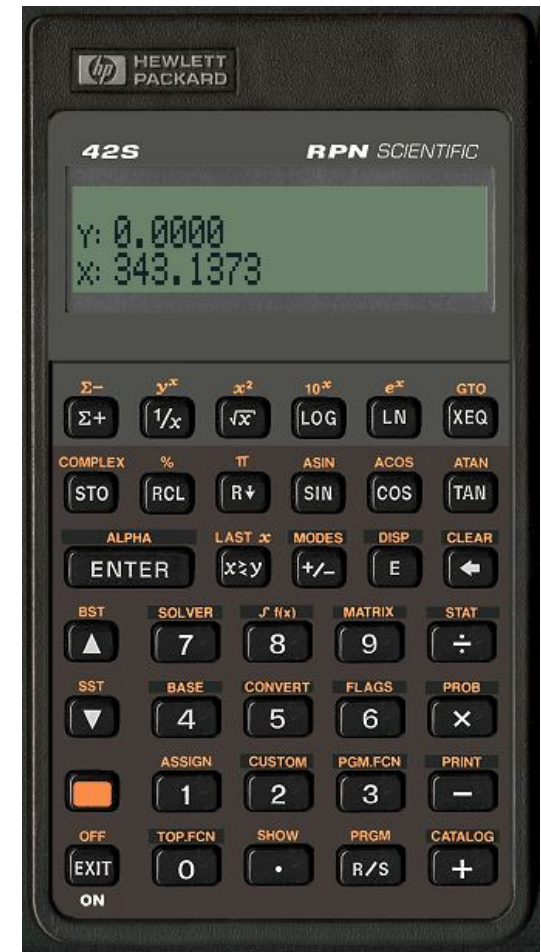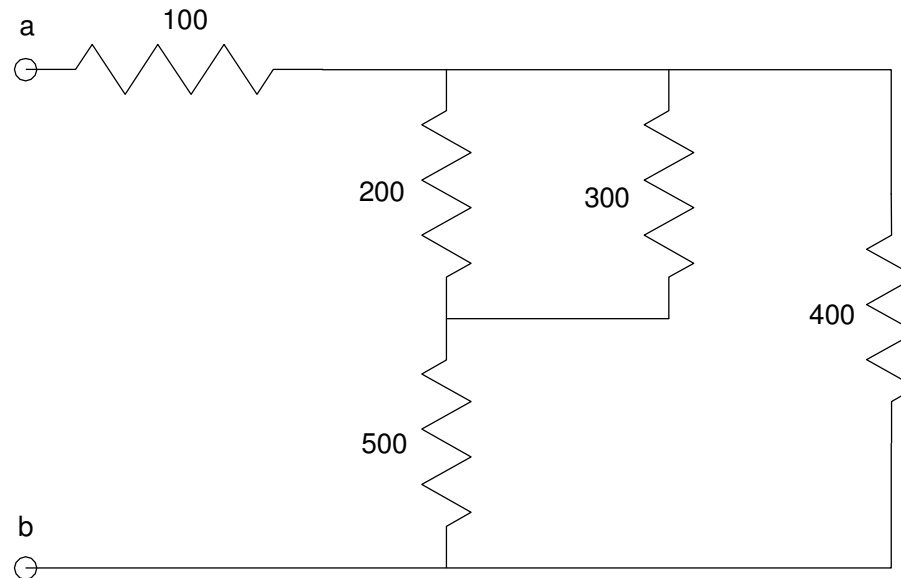
# Calculations with an HP42

200  
1/x  
300  
1/x  
+  
1/x  
  
500  
+  
  
1/x  
400  
1/x  
+  
1/x  
  
100  
+





# CircuitLab Calculations

- Build the circuit
- Apply a test voltage (10V)
- Measure the net current draw
- Compute R


$$R = \frac{V}{I}$$

$$R = \frac{10V}{29.14mA}$$

$$R = 343.17\Omega$$

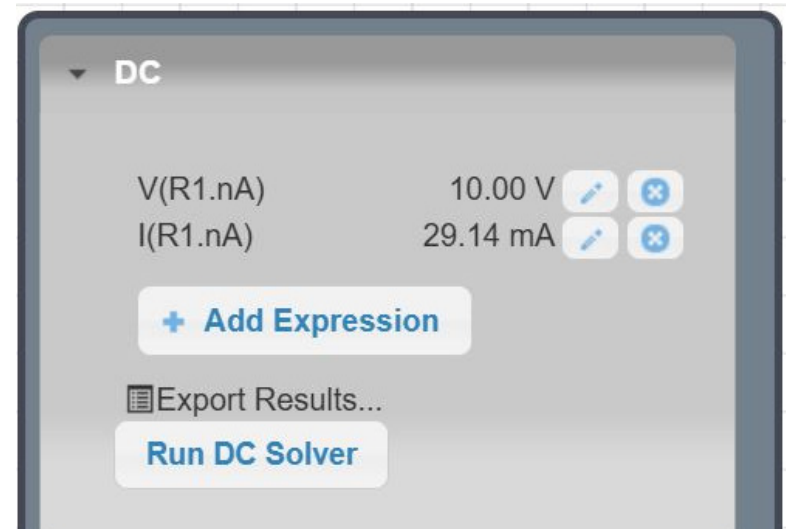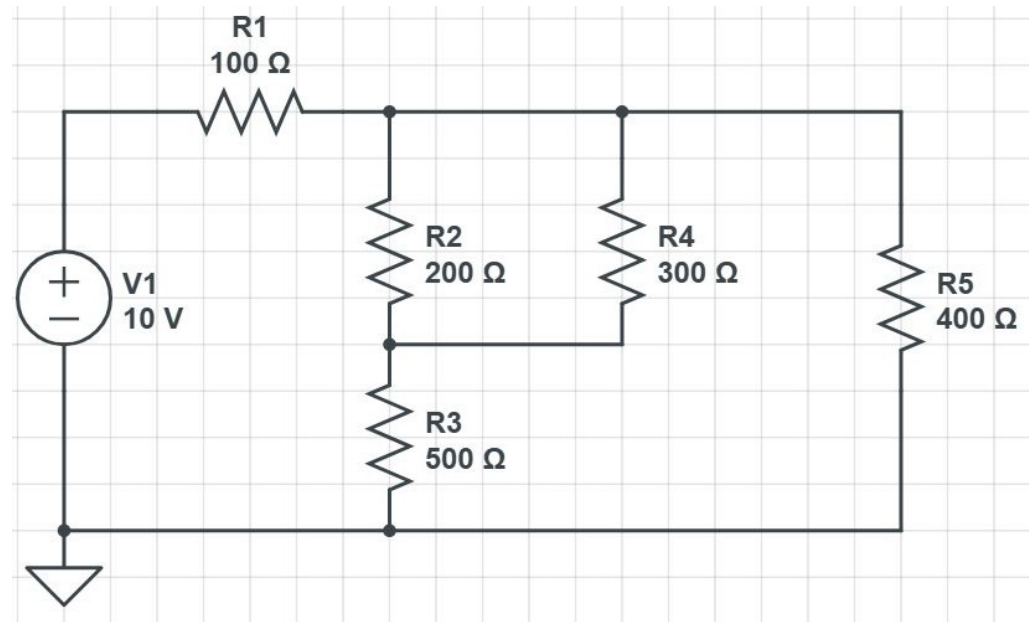

## Handout: Find $R_{ab}$

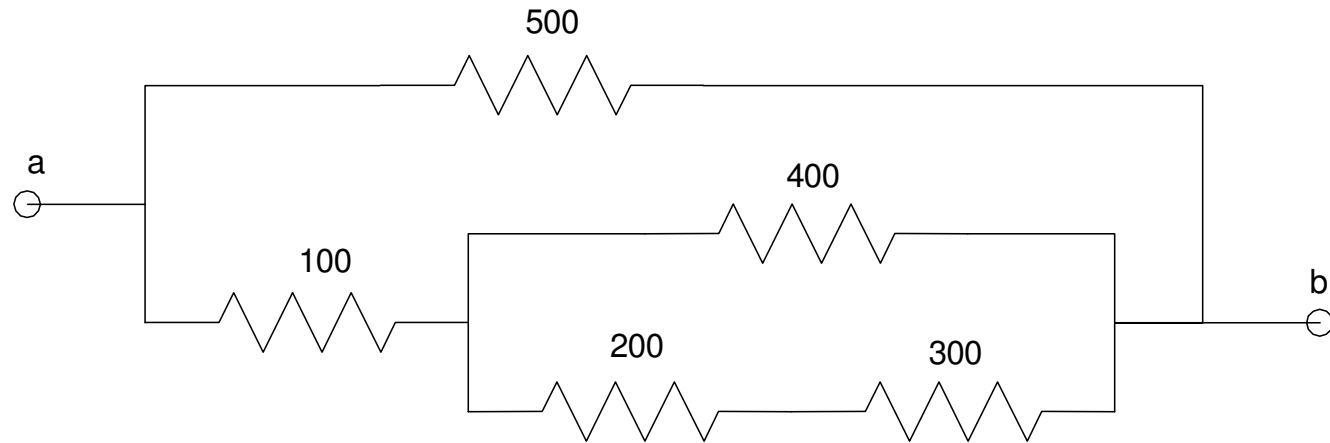


---

## Comment

Series & parallel simplification doesn't always work

- CircuitLab always works though

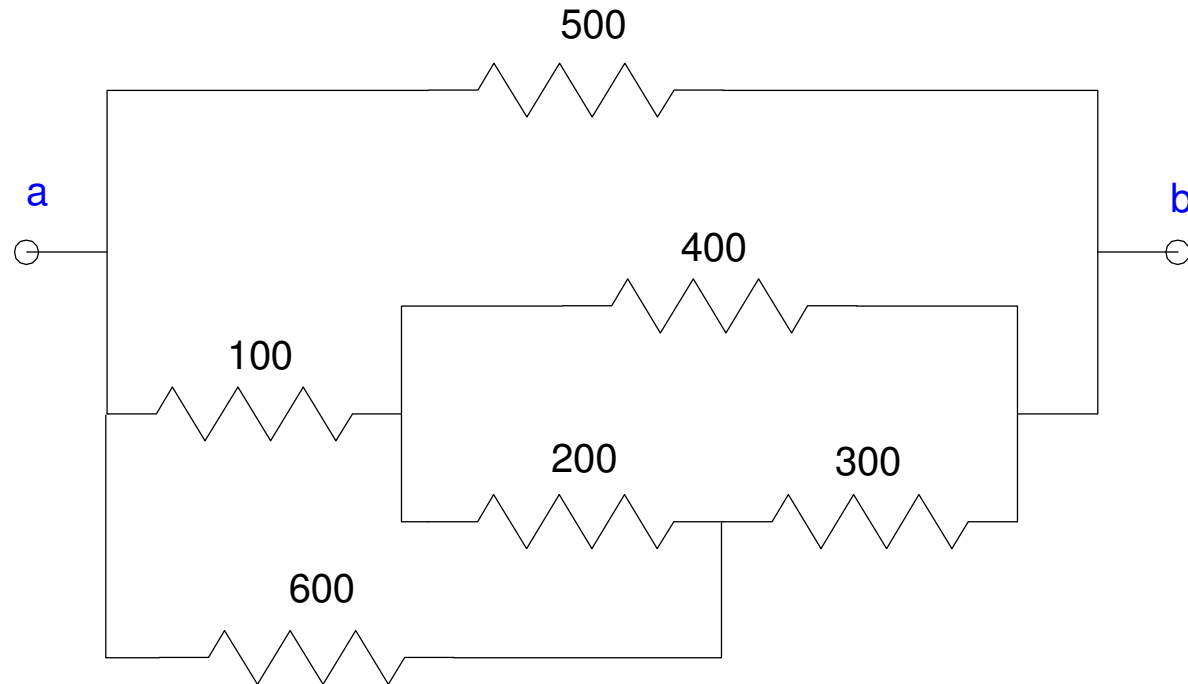Methods to compute the net resistance in these cases will be covered later in this course



---

## Summary

Resistors in series add

$$R_{net} = R_1 + R_2 + R_3$$

Resistors in parallel add as

$$\frac{1}{R_{net}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

CircuitLab can be used to check your answers

You can also build the circuit in lab to check your answers

---