
Super-Nodes

ECE 211 Circuits I

Lecture #6

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions

Background: Voltage Nodes

The previous lecture looked at finding the voltage in a circuit using Voltage Nodes

- Write N equations for N unknowns
- The sum of the currents from a given node must be zero

Voltage source to ground isn't a problem

- Defines the voltage at a given node

$$V_1 = 5$$


Resistors aren't a problem

- Sum the currents to zero from that node

$$\left(\frac{V_2 - V_1}{4}\right) + \left(\frac{V_2}{6}\right) + \left(\frac{V_2 - V_3}{8}\right) = 0$$

$$\left(\frac{V_3 - V_1}{2}\right) + \left(\frac{V_3 - V_2}{8}\right) + \left(\frac{V_3}{10}\right) = 0$$

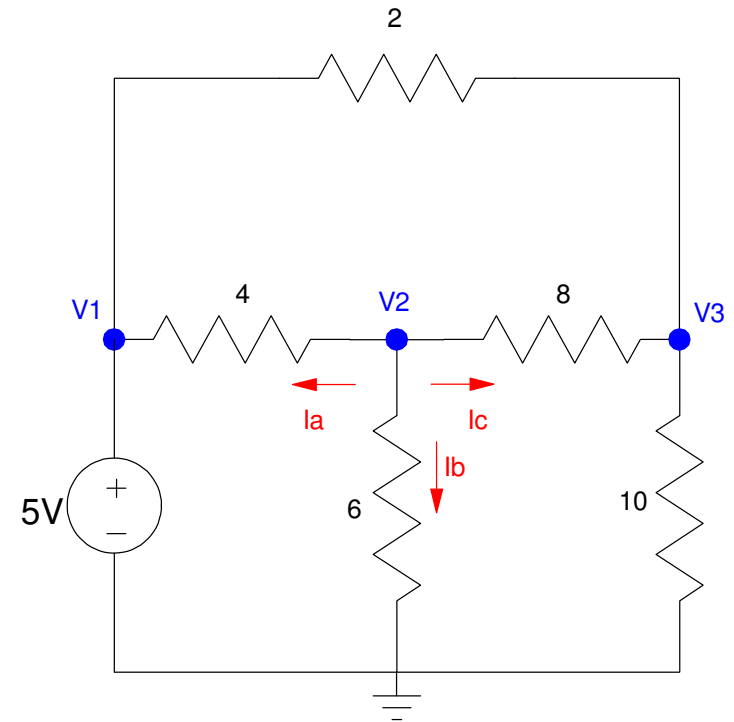This results in 3 equations for 3 unknowns.



Problem with Voltage Nodes

What do you do with voltage sources between nodes?

- The current in and out are unknown
- All you know is the voltage across the source

Equation #1


$$V_1 - V_3 = 5$$

Equation #2 (node V2)

$$\left(\frac{V_2 - V_1}{4}\right) + \left(\frac{V_2}{6}\right) + \left(\frac{V_2 - V_3}{8}\right) = 0$$

Equation #3

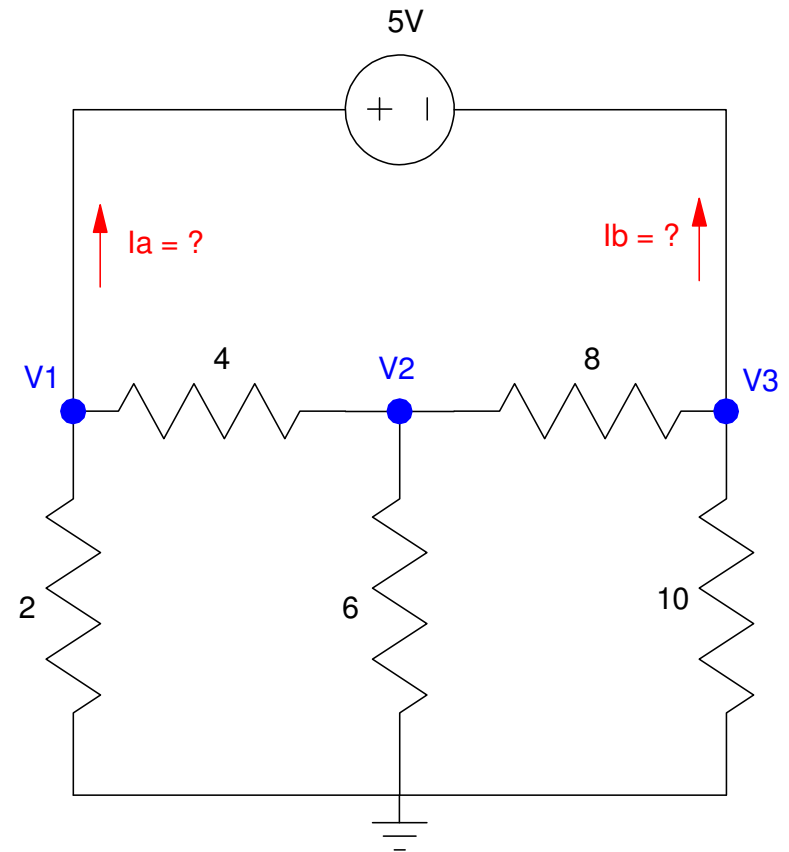- Problem
- I_a is unknown
 - node V1 doesn't work
- I_b is unknown
 - node V3 doesn't work



Solution: Super-Nodes


Super-Nodes:

- A closed path that encloses 2+ nodes
- The current coming out of any closed path must sum to zero
 - Conservation of current

Equation #3 (super-node)

$$I_1 + I_2 + I_3 = 0$$
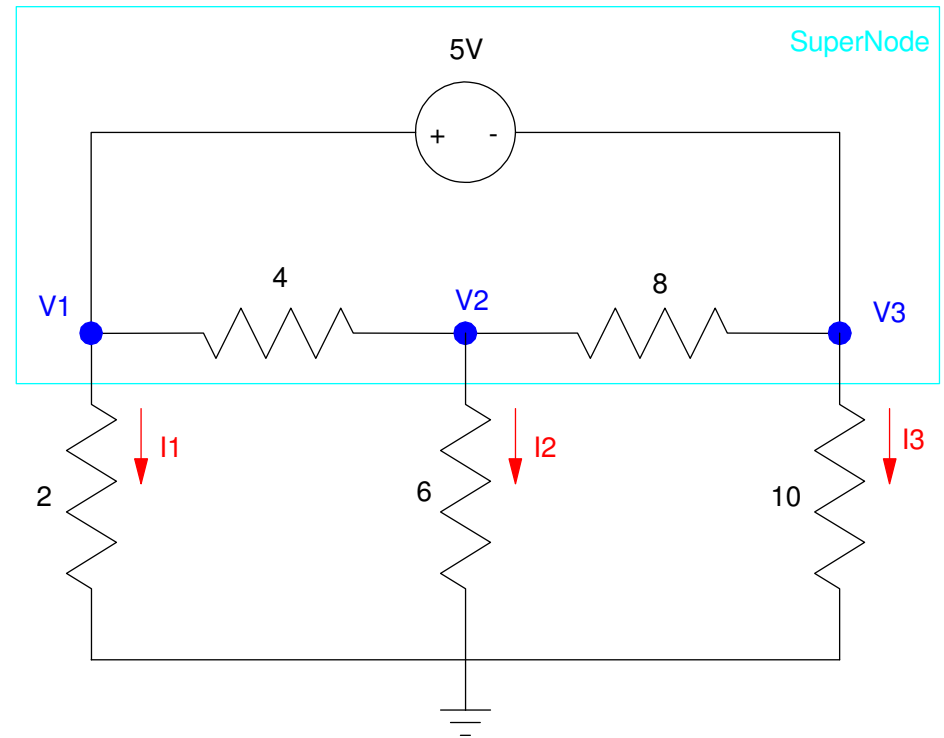
$$\left(\frac{V_1}{2}\right) + \left(\frac{V_2}{6}\right) + \left(\frac{V_3}{10}\right) = 10$$



Super-Node (take 2):

Super-nodes are not unique

- Any closed surface works
- As long as you know the currents in each path


Equation #3

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$\left(\frac{V_1}{2}\right) + \left(\frac{V_1 - V_2}{4}\right) + \left(\frac{V_3 - V_2}{8}\right) + \left(\frac{V_3}{10}\right) = 0$$

note: With super-nodes,

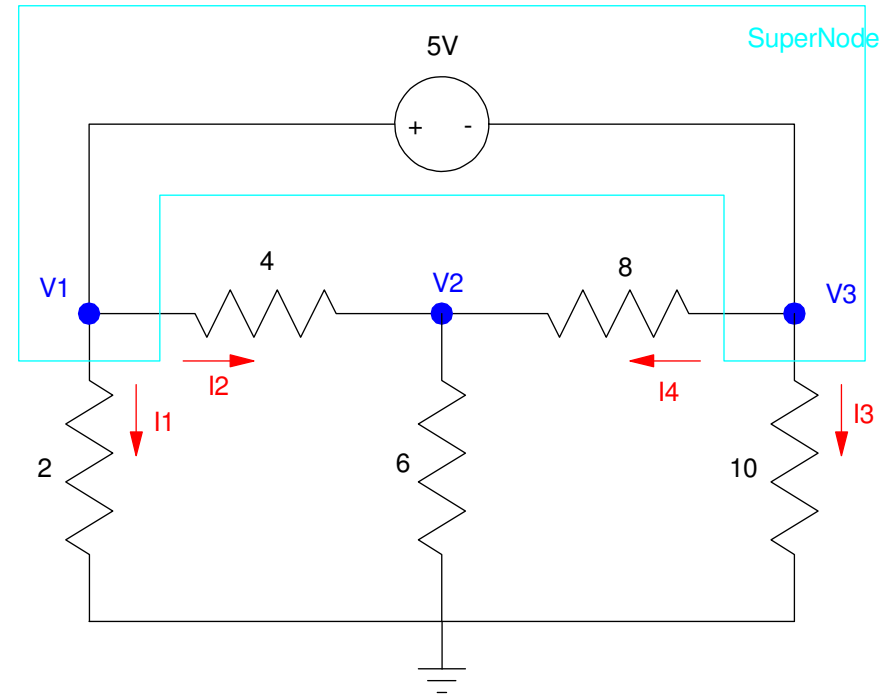- The signs for the voltages for the nodes enclosed are positive
- The signs for other nodes are negative



Solve:

Group terms:


$$V_1 - V_3 = 5$$

$$\left(\frac{-1}{4}\right)V_1 + \left(\frac{1}{4} + \frac{1}{6} + \frac{1}{8}\right)V_2 + \left(\frac{-1}{8}\right)V_3 = 0$$

$$\left(\frac{V_1}{2}\right) + \left(\frac{V_2}{6}\right) + \left(\frac{V_3}{10}\right) = 0$$

Place in matrix form
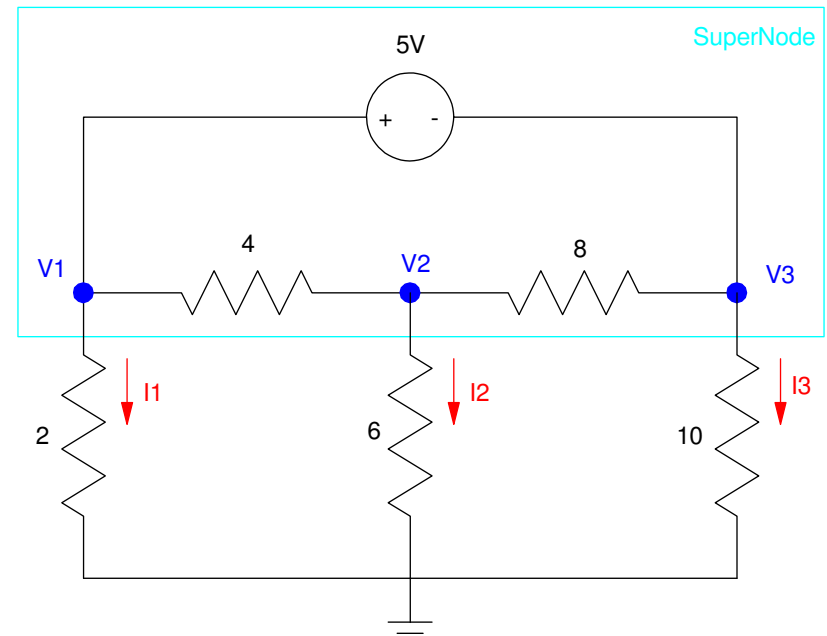
$$\begin{bmatrix} 1 & 0 & -1 \\ \left(\frac{-1}{4}\right) & \left(\frac{1}{4} + \frac{1}{6} + \frac{1}{8}\right) & \left(\frac{-1}{8}\right) \\ \left(\frac{1}{2}\right) & \left(\frac{1}{6}\right) & \left(\frac{1}{10}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$



Solve in Matlab

```
A = [1, 0, -1 ; -1/4, 1/4+1/6+1/8, -1/8 ; 1/2, 1/6, 1/10]
```


```
    1.0000         0    -1.0000  
   -0.2500    0.5417   -0.1250  
    0.5000    0.1667    0.1000
```

```
B = [5; 0; 0]
```


```
    5  
    0  
    0
```

```
V = inv(A) * B
```
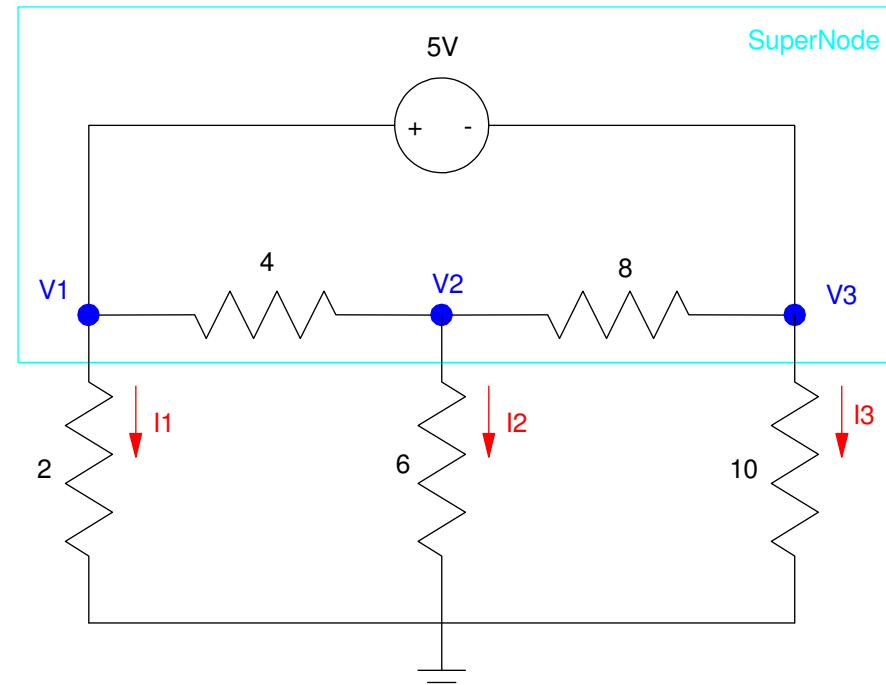
```
V1    0.9677  
V2   -0.4838  
V3   -4.0323
```



Same as CircuitLab

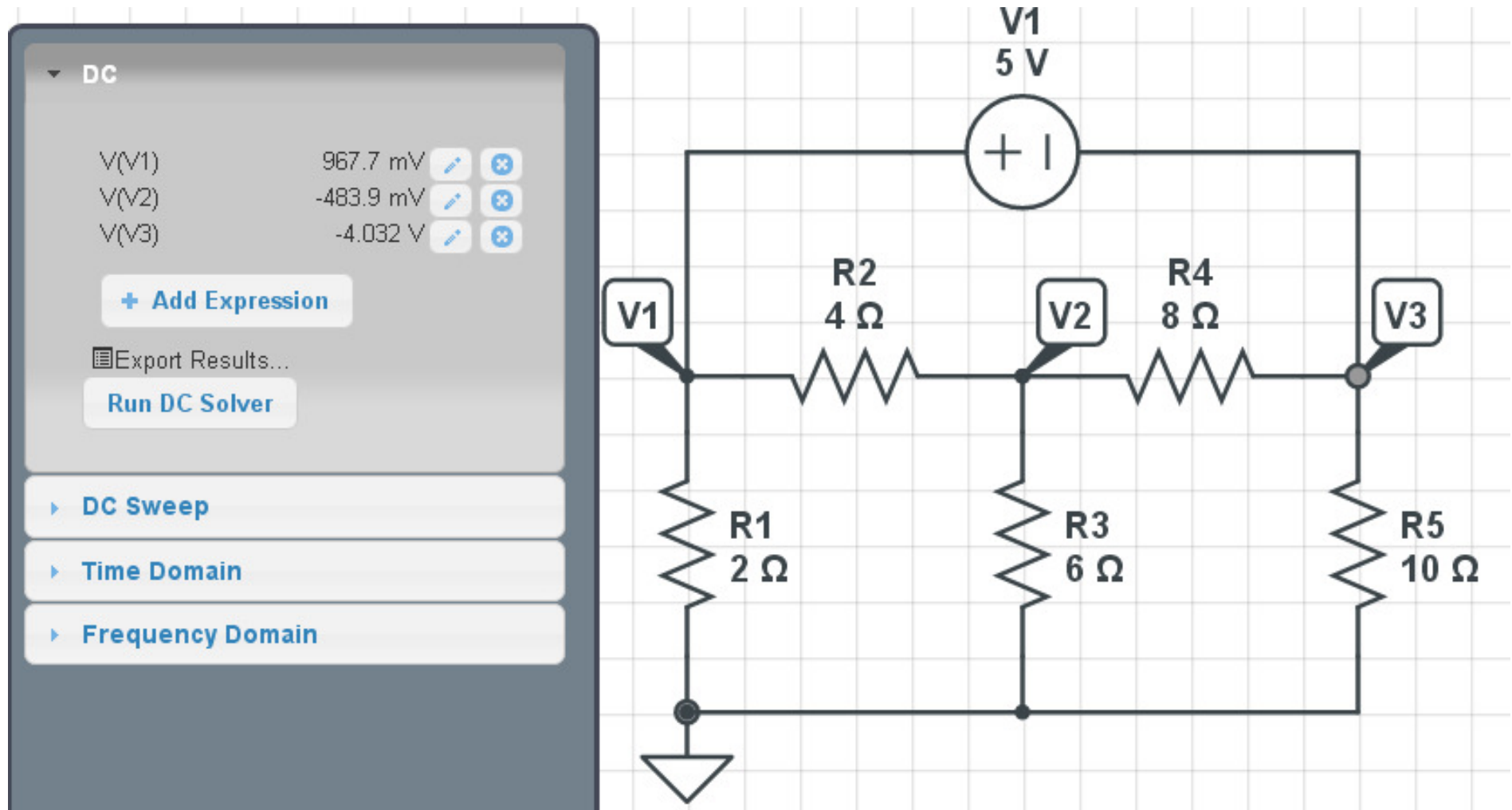

Practice Problem


Write a 4th equation to find $\{V_1, V_2, V_3, \text{ and } V_4\}$

(1) $V_1 - V_3 = 10$

(2) $-2 + \left(\frac{V_2 - V_1}{10}\right) + \left(\frac{V_2 - V_3}{3}\right) = 0$

(3) $\left(\frac{V_4 - V_1}{15}\right) + \left(\frac{V_4 - V_3}{4}\right) + \left(\frac{V_4}{30}\right) = 0$

(4) ?

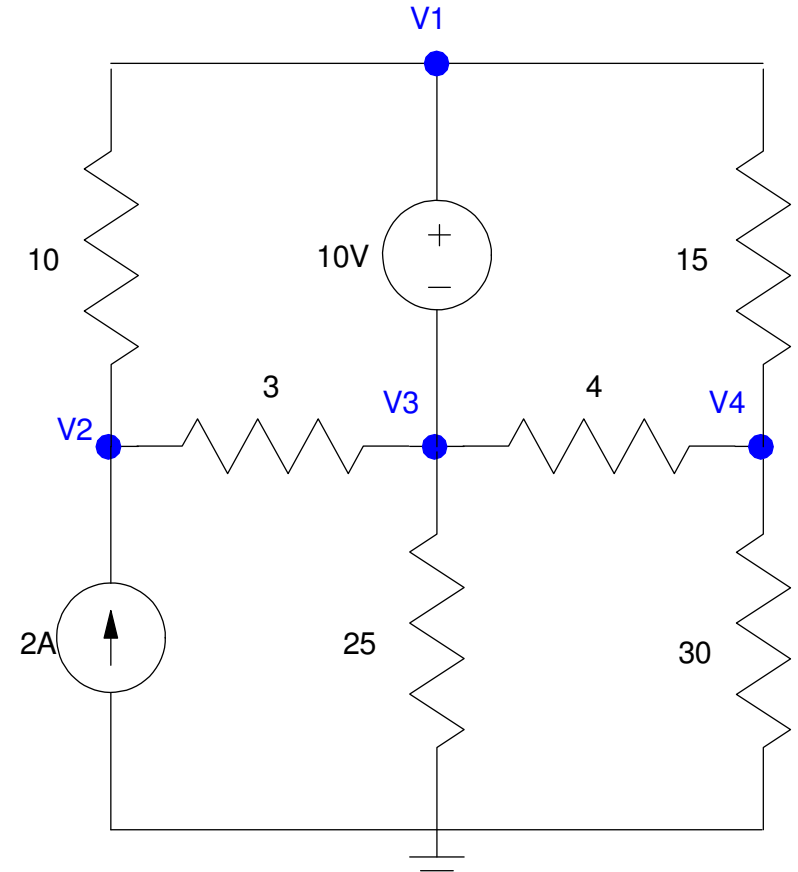

When is a Super-Node Equation Valid?

- Some super-node equations are valid
- Some are not
- How do you tell if your equation is valid?

Method #1: All circuit elements are included


$$(1) \quad V_1 - V_3 = 10$$

$$(2) \quad -2 + \left(\frac{V_2 - V_1}{10} \right) + \left(\frac{V_2 - V_3}{3} \right) = 0$$

$$(3) \quad \left(\frac{V_4 - V_1}{15} \right) + \left(\frac{V_4 - V_3}{4} \right) + \left(\frac{V_4}{30} \right) = 0$$

Note that the 25 Ohm resistor doesn't show up in any equation

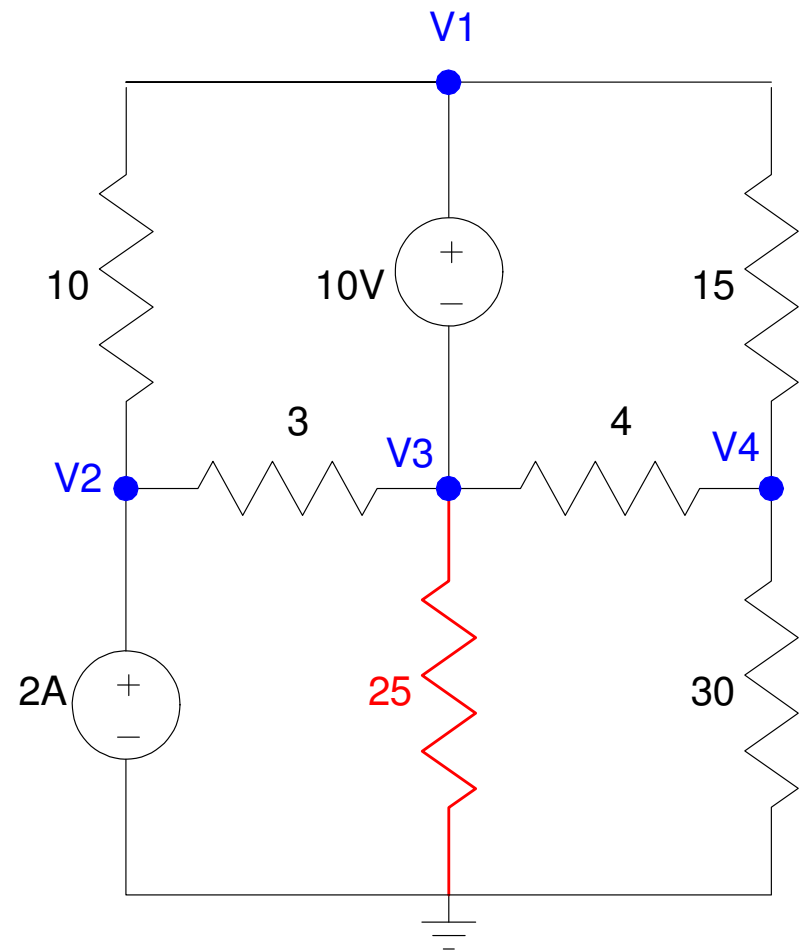- The super-node needs to include this resistor



Method #2: Matlab

If the super-node equation is valid, you will be able to invert the matrix

$$AV = B$$

$$V = A^{-1}B$$

If the super-node equation is invalid, you will get an error

```
>> V = inv(A)*B
```

Warning: Matrix is singular to working precision.


```
V =
```

```
NaN
```

```
NaN
```


```
NaN
```

```
NaN
```

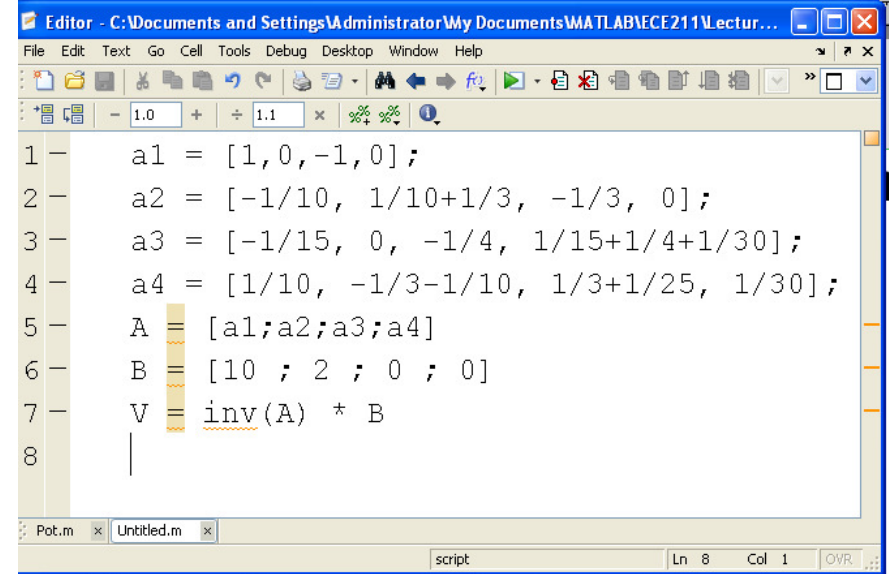

The image shows a MATLAB Editor window with the following code:
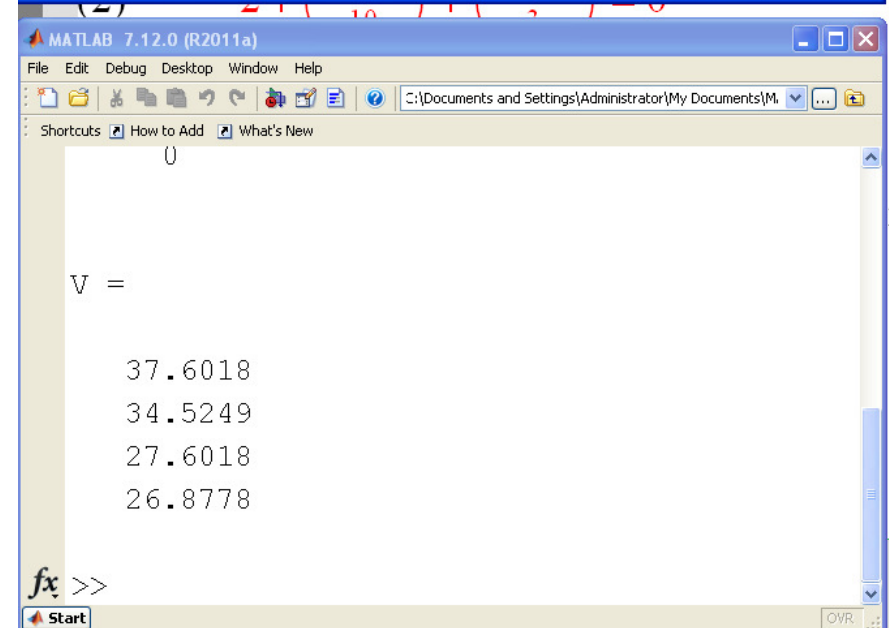
```
1 - a1 = [1,0,-1,0];  
2 - a2 = [-1/10, 1/10+1/3, -1/3, 0];  
3 - a3 = [-1/15, 0, -1/4, 1/15+1/4+1/30];  
4 - a4 = [1/10, -1/3-1/10, 1/3+1/25, 1/30];  
5 - A = [a1;a2;a3;a4]  
6 - B = [10 ; 2 ; 0 ; 0]  
7 - V = inv(A) * B  
8 -
```



The image shows the MATLAB Command Window with the following output:




```
0  
  
V =  
  
    37.6018  
    34.5249  
    27.6018  
    26.8778
```

What's Happening?

To solve for 4 unknown voltages, you need 4 linearly independent equations

If the 4th equation is redundant (linear combination for the first three),

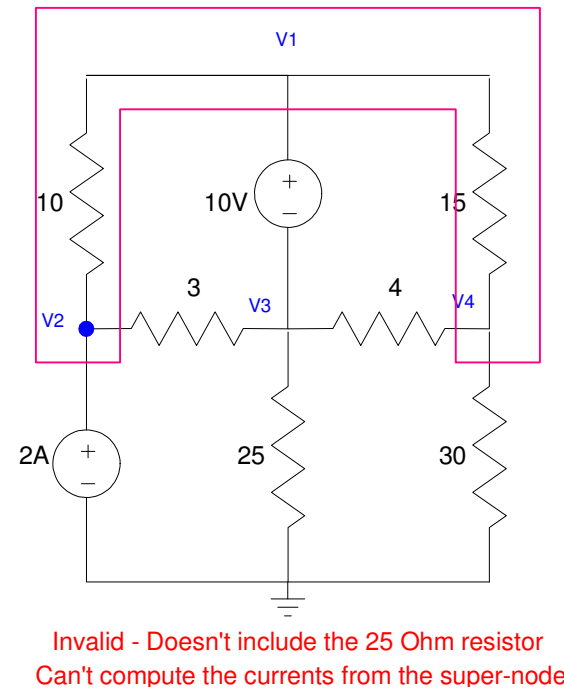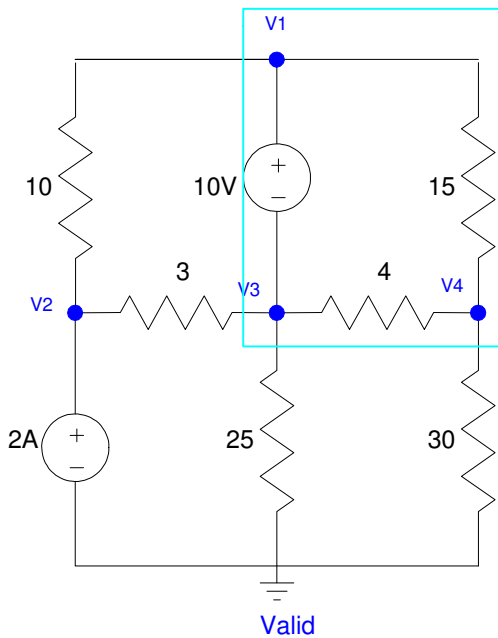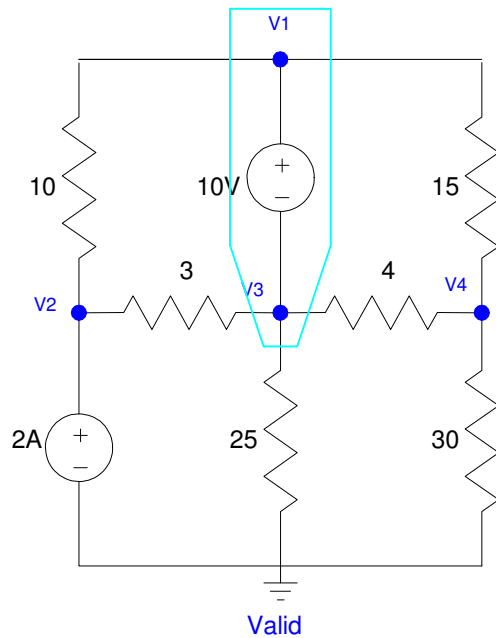- There's no new information
- There's not enough information to solve
- The A matrix is not invertible



Voltage Nodes with Dependent Sources

- Same as voltage nodes
- Plus one equation for each dependent source

Example: Find V_1 , V_2 , V_3 , V_x

- 4 equations for 4 unknowns

Easy ones:


$$V_x = V_3 - V_2$$

$$V_1 = 12$$

$$V_3 = 4V_x$$

Node equation at V_2
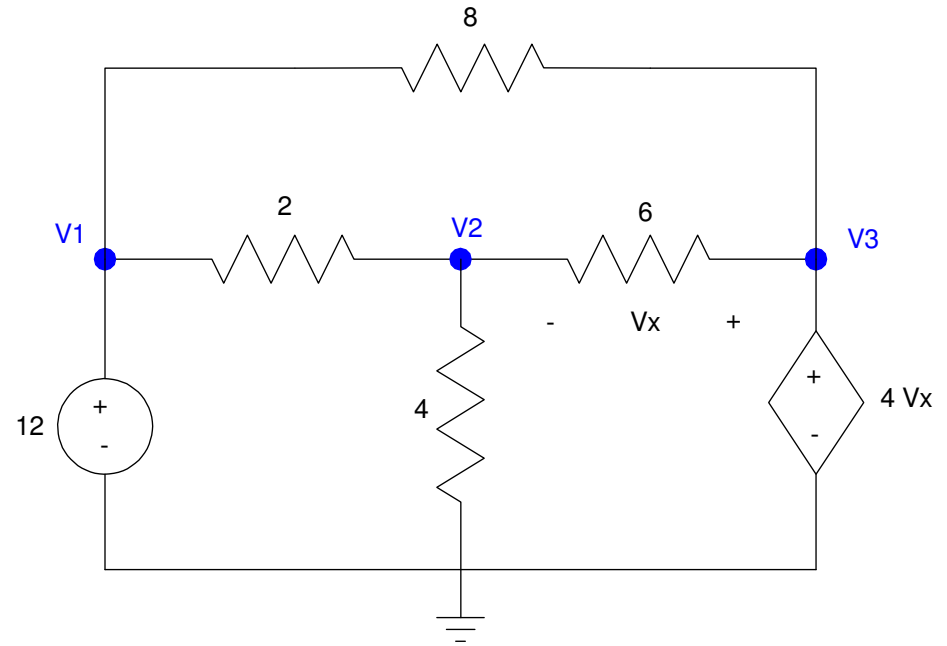
$$\left(\frac{V_2 - V_1}{2}\right) + \left(\frac{V_2}{4}\right) + \left(\frac{V_2 - V_3}{6}\right) = 0$$



Solve: Group terms

$$V_x - V_3 + V_2 = 0$$


$$V_1 = 12$$

$$V_3 - 4V_x = 0$$

$$\left(\frac{-1}{2}\right)V_1 + \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{6}\right)V_2 + \left(\frac{-1}{6}\right)V_3 = 0$$

Placing in matrix form
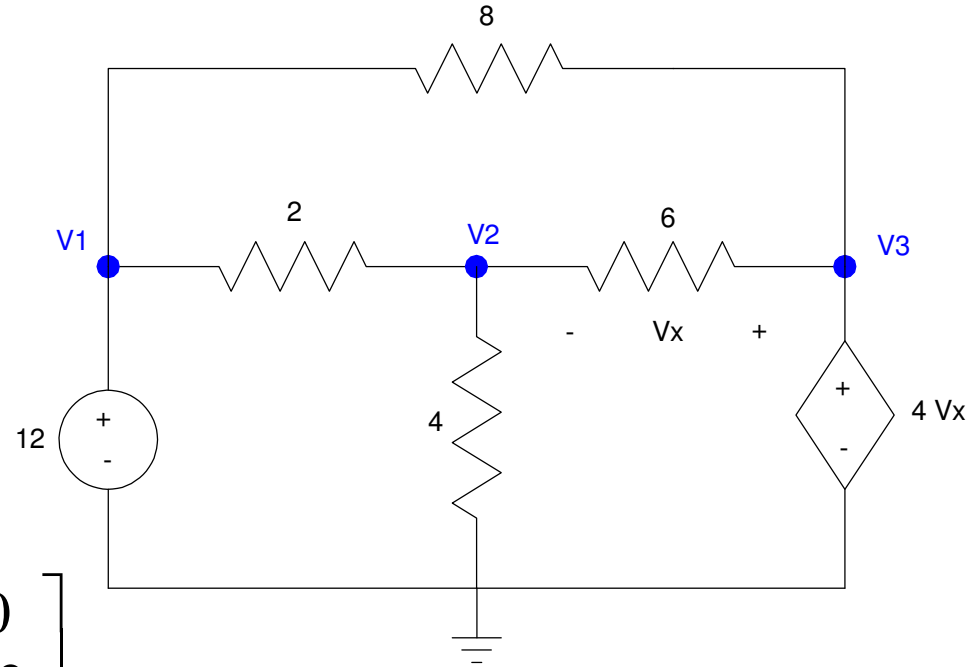
$$\begin{bmatrix} 0 & 1 & -1 & 1 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -4 \\ \left(\frac{-1}{2}\right) & \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{6}\right) & \left(\frac{-1}{6}\right) & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_x \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \\ 0 \end{bmatrix}$$



Solve in Matlab

```
A = [0,1,-1,1 ; 1,0,0,0 ; 0,0,1,-4 ; -1/2,1/2+1/4+1/6,-1/6,0]
```


```
      0      1.0000     -1.0000      1.0000
1.0000         0         0         0
      0         0      1.0000     -4.0000
-0.5000     0.9167     -0.1666         0
```

```
B = [0;12;0;0]
```

```
0
12
0
0
```





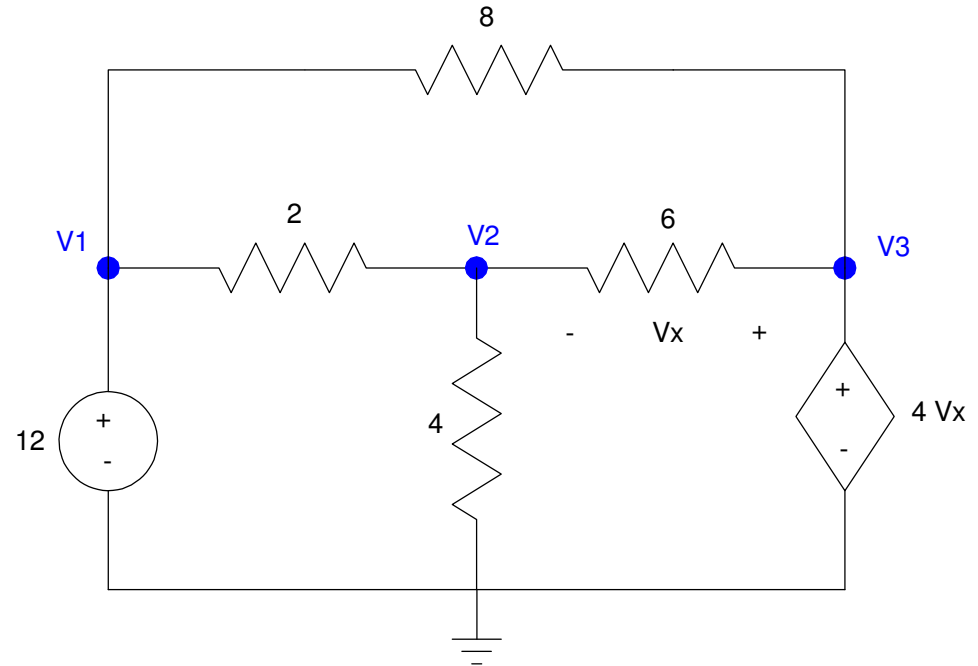

```
V = inv(A)*B
```

```
V1    12.0000
V2     8.6385
V3    11.5180
Vx     2.8795
```




Checking in Circuitlab - the voltages match

▼ DC

V(V0)	12.00 V		
V(V1)	8.640 V		
V(V2)	11.52 V		

[+ Add Expression](#)


 Export Results...

[Run DC Solver](#)

► DC Sweep

► Time Domain

► Frequency Domain

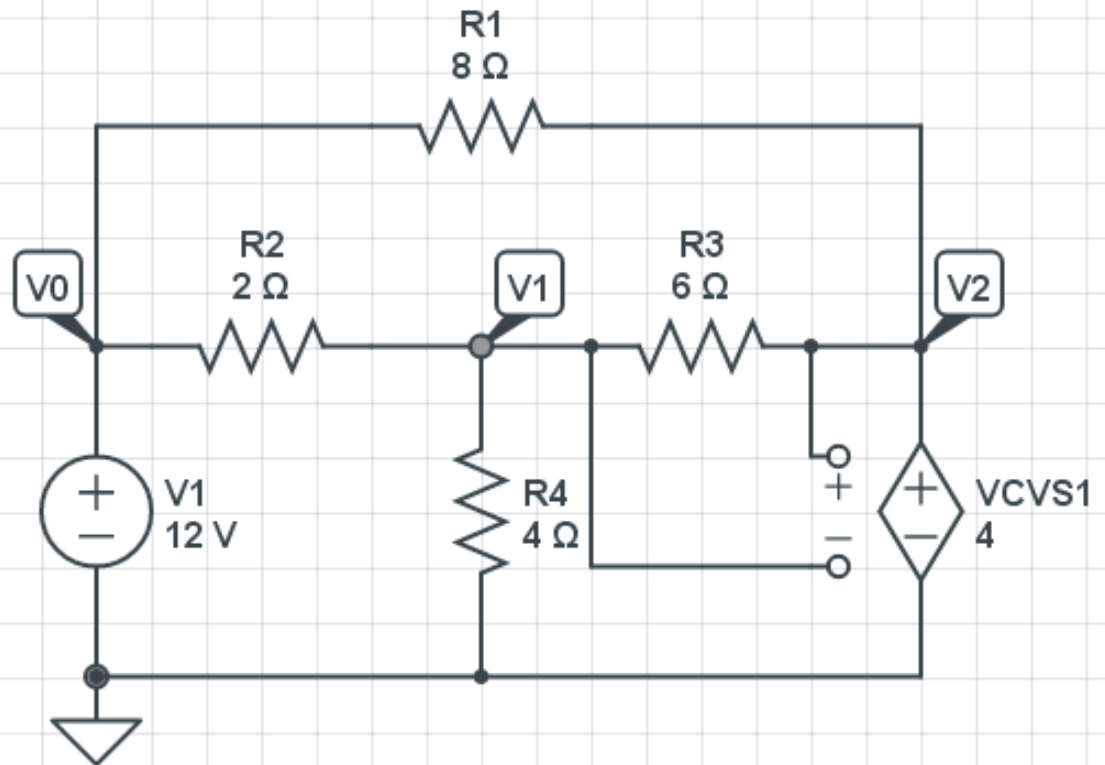

Super-Nodes and Dependent Sources

- If needed, define a closed-path (i.e. a Super-node) to give the rest of the N equations needed

Example: Find { V_1 , V_2 , V_3 , I_x }

Easy Equations:

$$I_x = \left(\frac{V_1 - V_2}{2} \right)$$


$$V_1 = 12$$

$$V_2 - V_3 = 5I_x$$

Define a Super-Node

- Current out of the Super-Node = 0
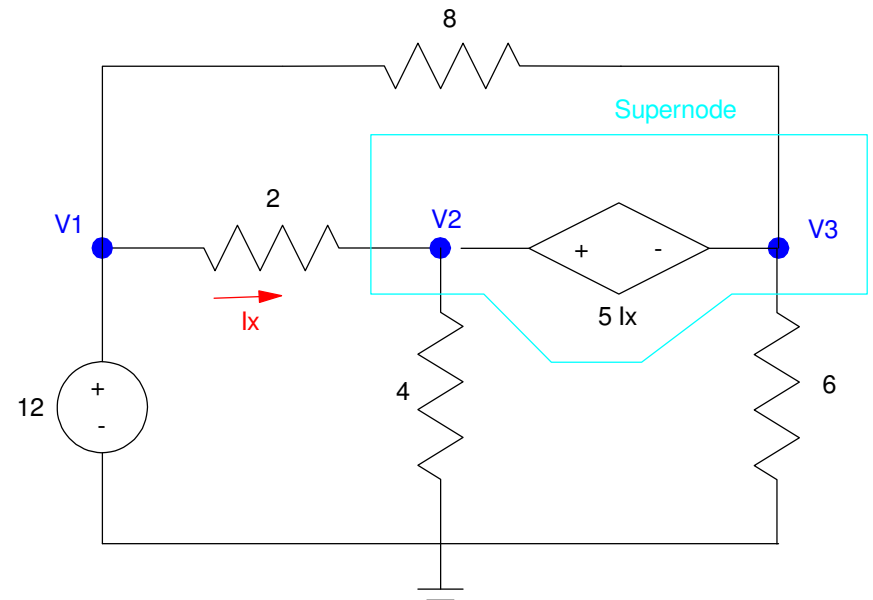
$$\left(\frac{V_2 - V_1}{2} \right) + \left(\frac{V_2}{4} \right) + \left(\frac{V_3}{6} \right) + \left(\frac{V_3 - V_1}{8} \right) = 0$$



Group Terms

$$V_1 - V_2 - 2I_x = 0$$


$$V_1 = 12$$

$$V_2 - V_3 - 5I_x = 0$$

$$\left(\frac{-1}{2} + \frac{-1}{8}\right)V_1 + \left(\frac{1}{2} + \frac{1}{4}\right)V_2 + \left(\frac{1}{6} + \frac{1}{8}\right)V_3 = 0$$

Place in matrix form
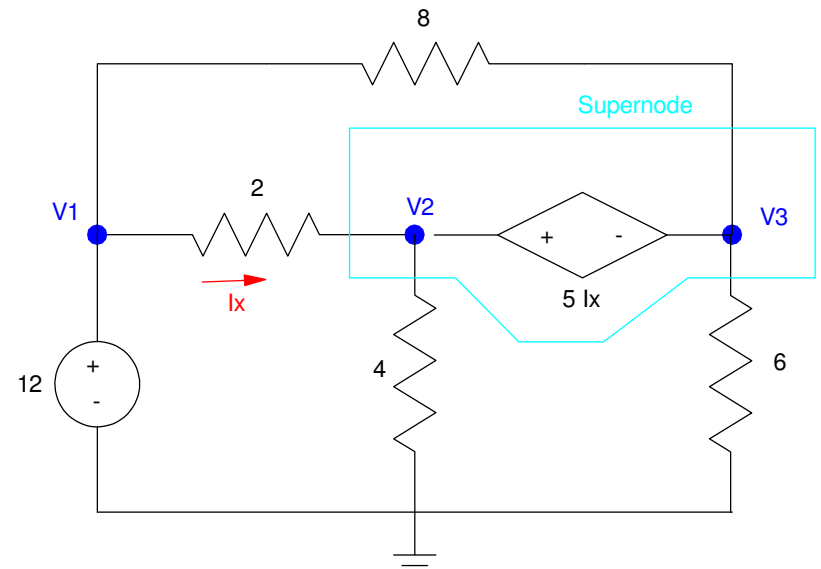
$$\begin{bmatrix} 1 & -1 & 0 & -2 \\ 1 & 0 & 0 & 0 \\ 0 & 1 & -1 & -5 \\ -0.625 & 0.75 & 0.2917 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ I_x \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \\ 0 \end{bmatrix}$$



Solve in Matlab

```
A = [1,-1,0,-2 ; 1,0,0,0 ; 0,1,-1,-5 ; -0.625,0.75,0.2917,0]
```


```
1.0000    -1.0000         0    -2.0000
1.0000         0         0         0
         0    1.0000   -1.0000   -5.0000
-0.6250    0.7500    0.2917         0
```

```
B = [0;12;0;0]
```


```
0
12
0
0
```

```
V = inv(A)*B
```
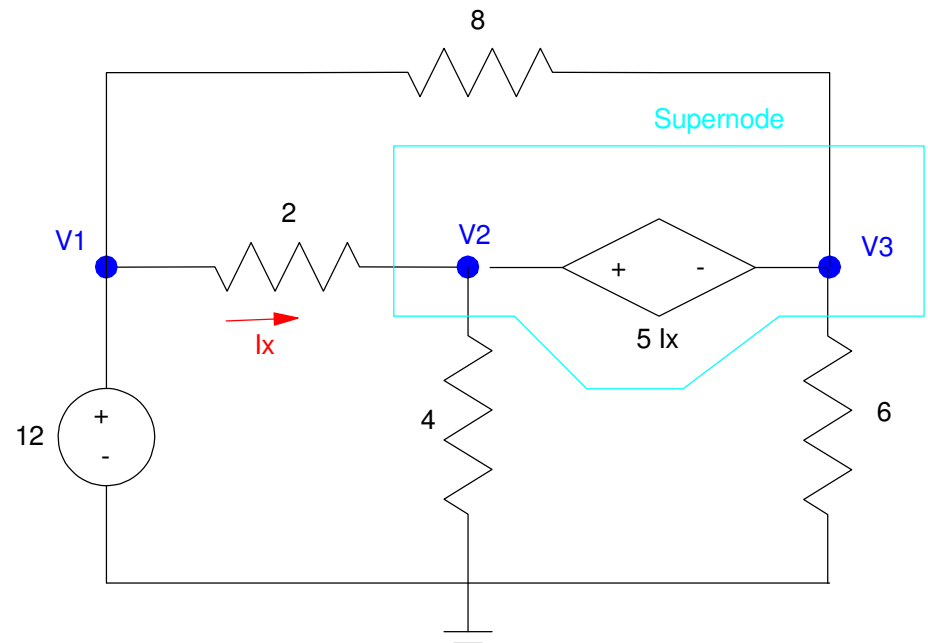
```
V1    12.0000
V2    9.1764
V3    2.1175
Ix    1.4118
```




Verify using Circuitlab

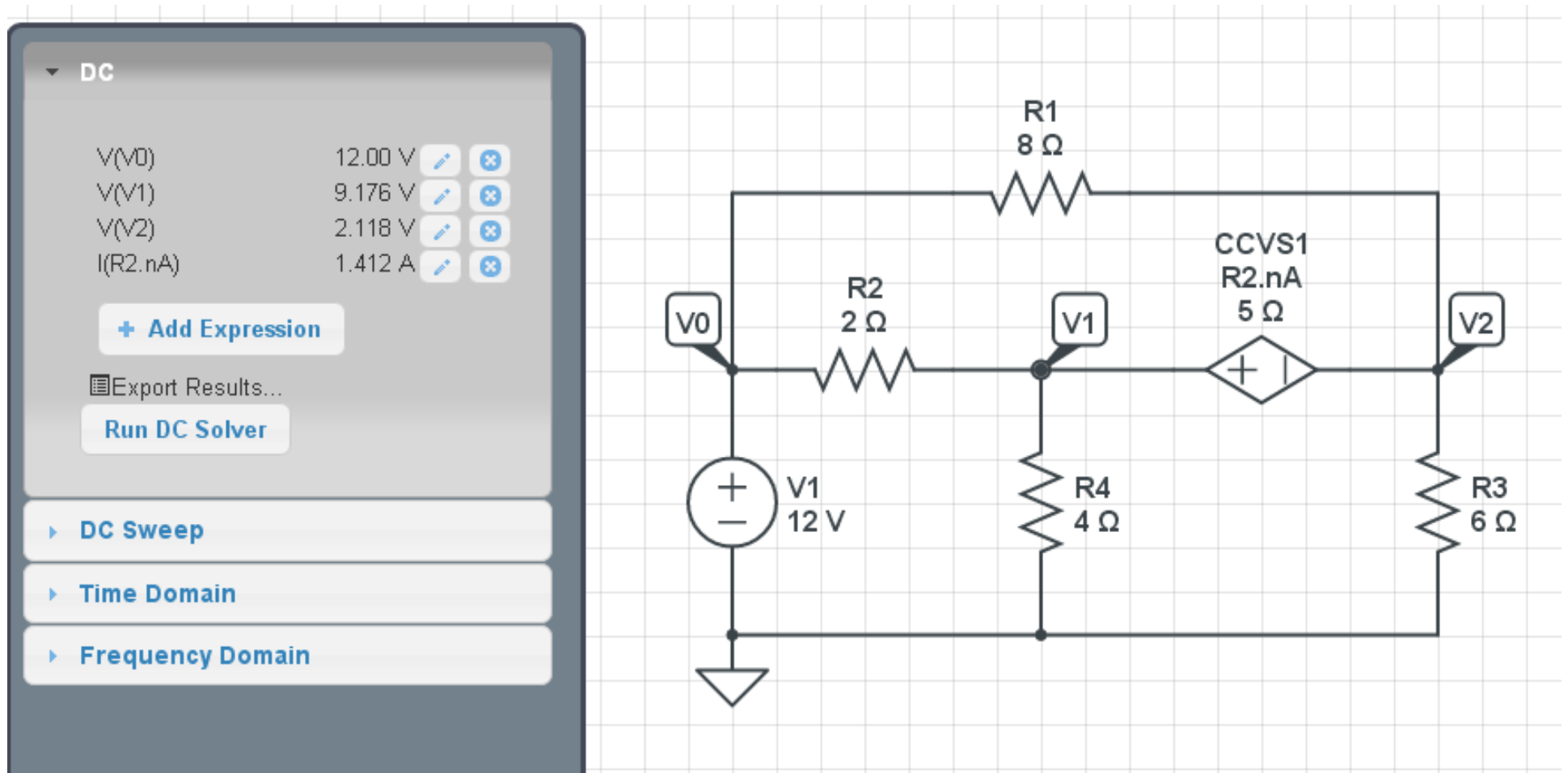

Practice Problem

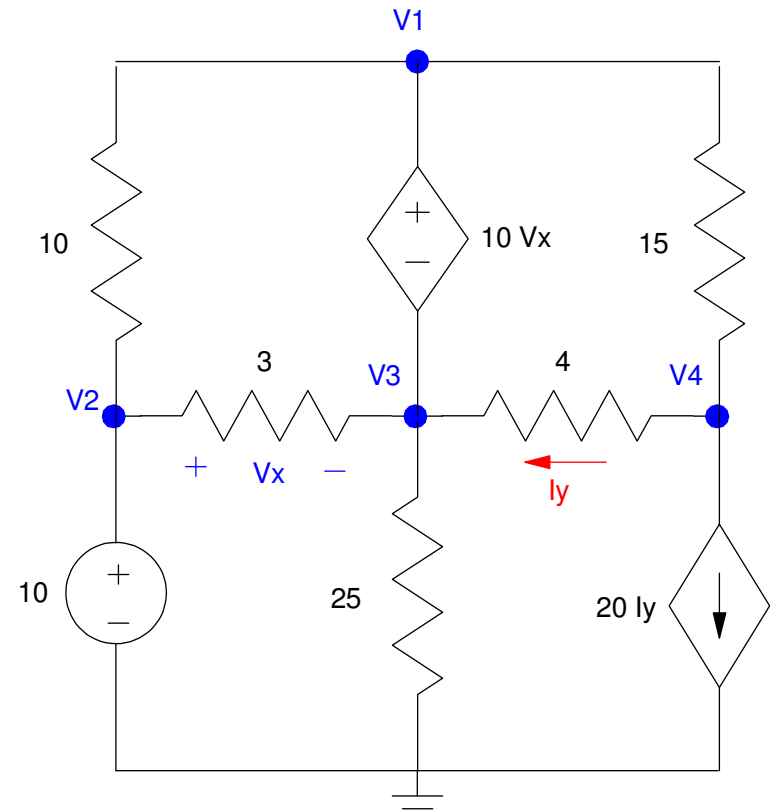Write the voltage node equations for the following circuit



Summary

Conservation of current applies to any closed path

- The sum of all currents from a closed region is zero

If you are having problems coming up with N equations for N unknowns, add a super-node

- Define a closed-path
- Such that all currents from the super-node are known

Super-nodes are not unique

- Several closed paths could be used
- Each should give the same result
- It helps the grader if you show what super-node you're using in homework sets and exams

