
Superposition

ECE 211 Circuits I

Lecture #12

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions

Superposition

- A circuit composed of resistors, inductors, capacitors, voltage sources, current sources, and dependent sources is a linear system.
- Linear systems have the property

$$f(a + b) = f(a) + f(b)$$

Meaning....

- If a circuit has two or more inputs,
- You treat this as two separate circuits, each with just one of the inputs.
- The net voltages (and currents) will be the sum of the separate problems

This is called *superposition*

Example 1:

$$V_0 = 10$$


$$\left(\frac{V_1 - V_0}{10}\right) + \left(\frac{V_1}{100}\right) + \left(\frac{V_1 - V_2}{20}\right) = 0$$

$$\left(\frac{V_2 - V_1}{20}\right) + \left(\frac{V_2}{200}\right) + \left(\frac{V_2 - V_3}{30}\right) = 0$$

$$\left(\frac{V_3 - V_2}{30}\right) + \left(\frac{V_3}{300}\right) + \left(\frac{V_3 - V_4}{40}\right) = 0$$

$$\left(\frac{V_4 - V_3}{40}\right) + \left(\frac{V_4}{400}\right) = 0$$

$$V_4 = 5$$

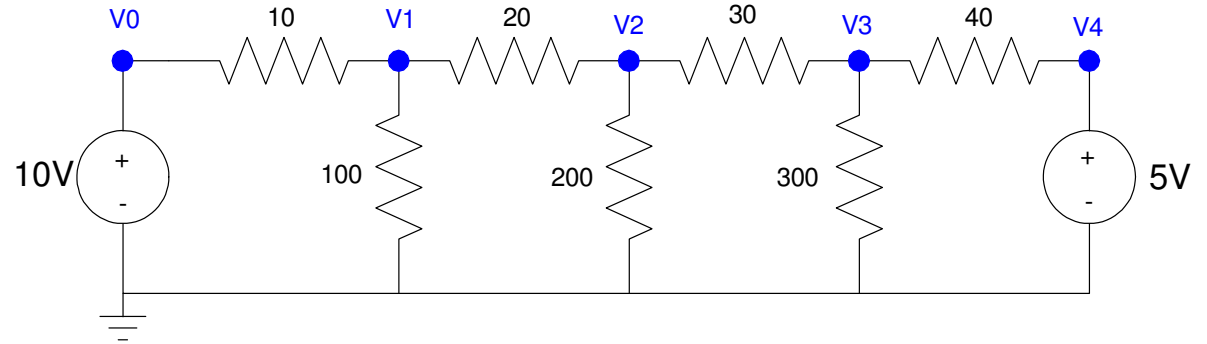


Result

	V0	V1	V2	V3	V4
V0 = 10V V4 = 5V	10.00 V	8.42 V	6.95 V	5.78 V	5.00 V

Superposition (take 1):

- $V_0 = \text{on}$
- $V_4 = \text{off}$


	V_0	V_1	V_2	V_3	V_4
$V_0 = 10\text{V}$ $V_4 = 0\text{V}$	10.00V	8.04 V	5.71 V	3.09 V	0.00 V

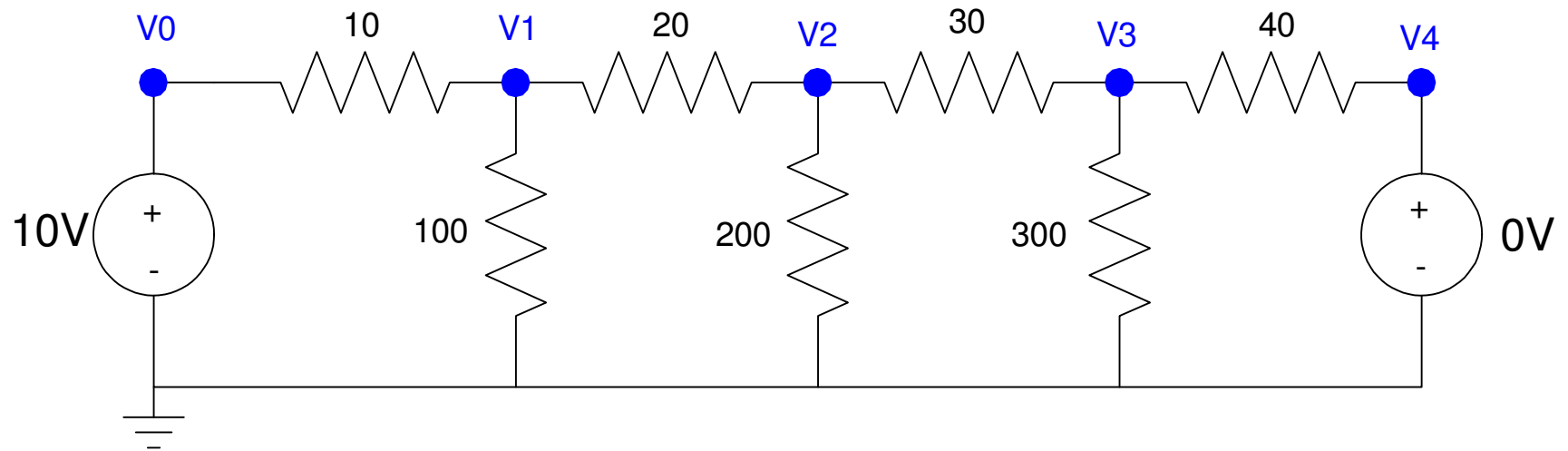

Superpositon (take 2)

- $V0 = \text{off}$
- $V4 = \text{on}$

	V0	V1	V2	V3	V4
$V0 = 0V$ $V4 = 5V$	0.00 V	0.386 V	1.24 V	2.69 V	5.00 V

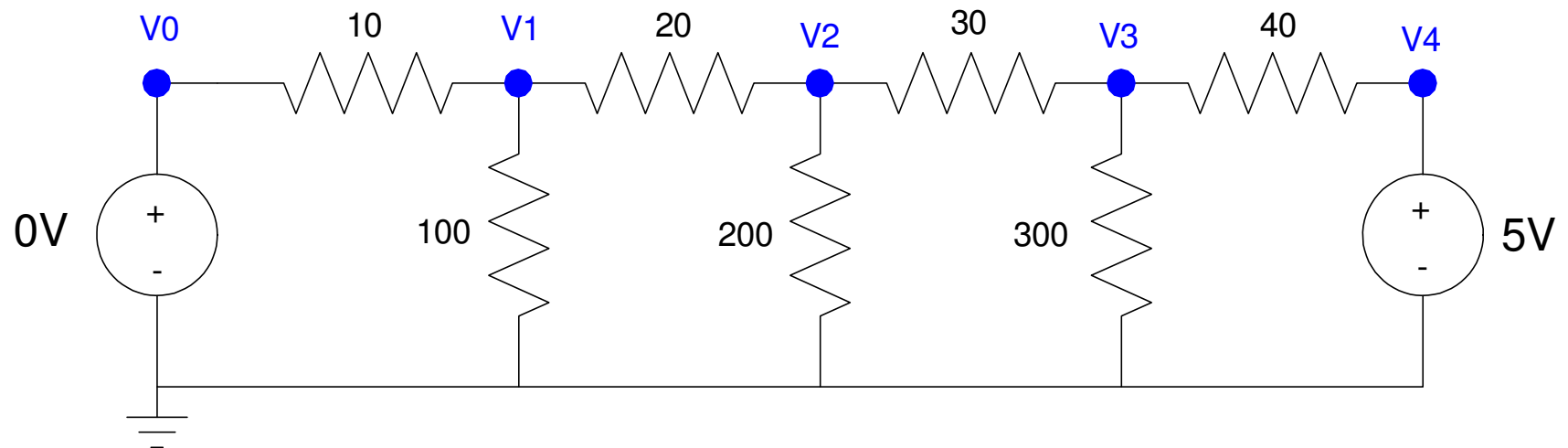

Superposition (take 3)

Note that the voltages add up


	V0	V1	V2	V3	V4
V0 = 10V, V4 = 0V	10.00V	8.04 V	5.71 V	3.09 V	0.00 V
V0 = 0V V4 = 5V	0.00 V	0.386 V	1.24 V	2.69 V	5.00 V
V0 = 10V V4 = 5V	10.00 V	8.42 V	6.95 V	5.78 V	5.00 V

Example 2: R-2R Ladder.

Determine Y as a function of A , B , C , and D

By superposition, we know that


$$Y = aA + bB + cC + dD$$

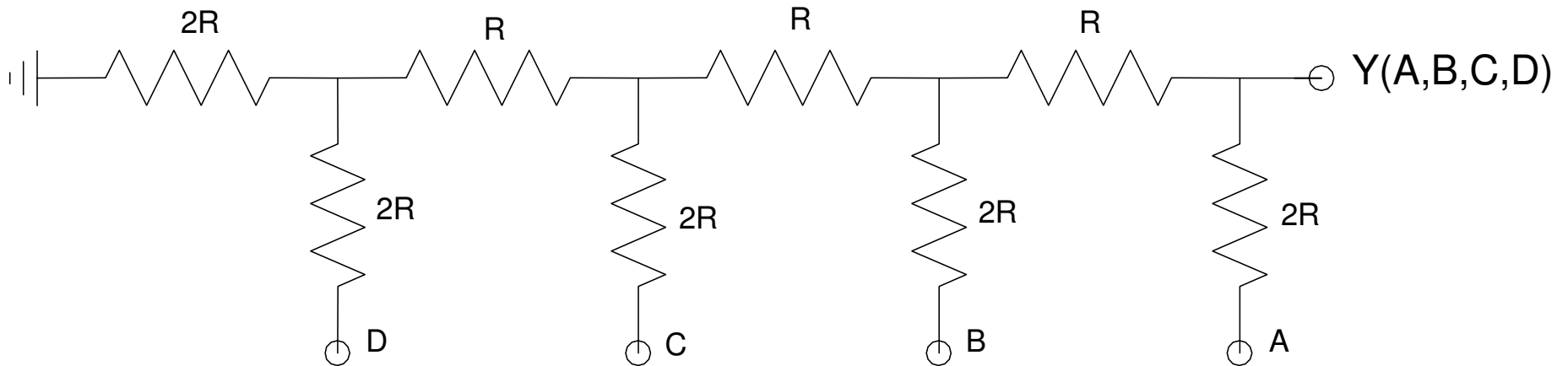

Case 1: $A = 1, B = C = D = 0.$

- Take the Thevenin equivalent of the circuit looking left at x. All you see is $2R \parallel 2R = R$ to ground.
- Repeat at y. All you see is $2R \parallel 2R = R$ to ground.
- Repeat at z. All you see is $2R \parallel 2R = R$ to ground.
- By voltage division, $Y = 1/2$ volt.


$$a = 1/2$$

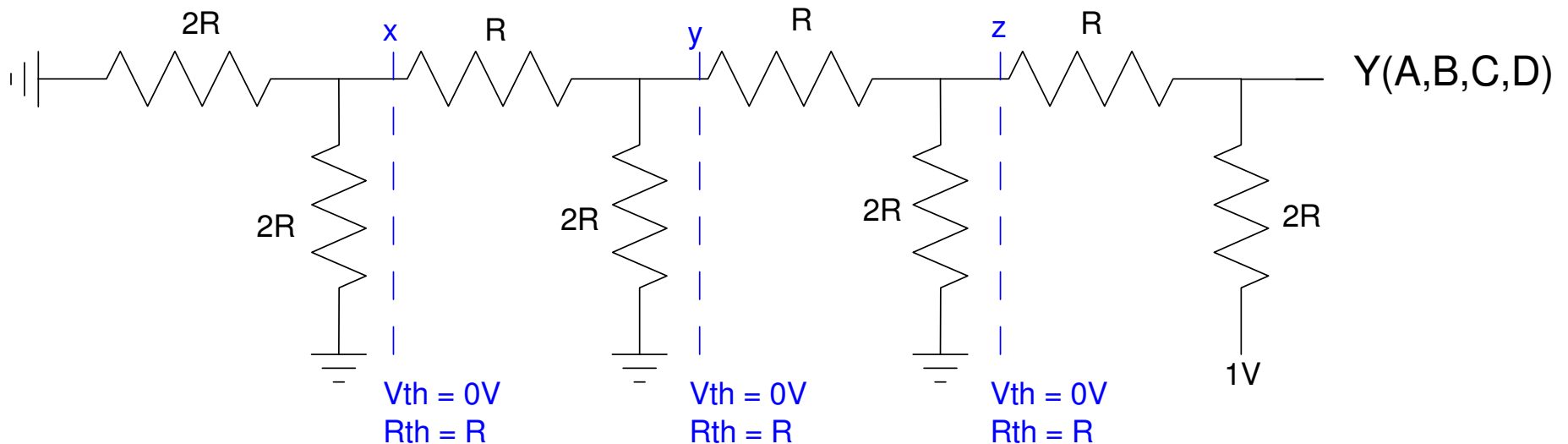

Case 2: $A = 0, B = 1, C = D = 0.$


- At w looking left, all you see is $2R \parallel 2R = R$
- At x looking left, all you see is $2R \parallel 2R = R$
- At y looking left, all you get
 - $R_{th} = 2R \parallel 2R = R$ $V_{th} = 1/2 V$
- At z looking left, you get
 - $R_{th} = 2R \parallel 2R = R$ $V_{th} = 1/2 * 1/2 = 1/4$

$$b = 1/4$$

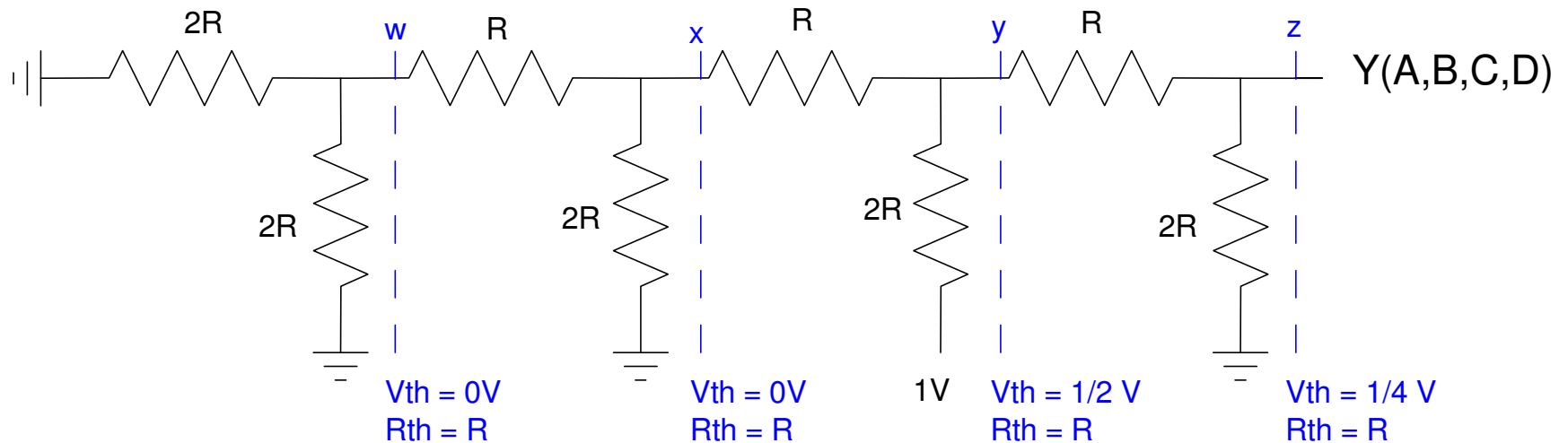

Case 3: $A = B = D = 0$. $C = 1$.

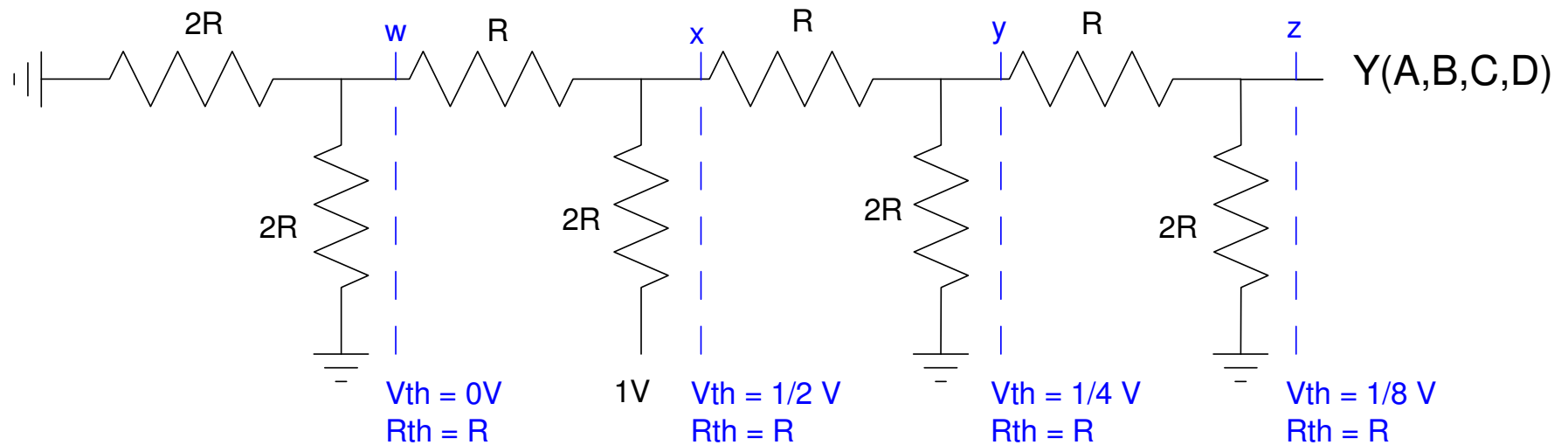
- Taking the Thevenin equivalents looking left, you wind up with
- $Y = 1/8 \text{ V}$ ($c = 1/8$)



Net Result

$$Y = \left(\frac{1}{2}\right)A + \left(\frac{1}{4}\right)B + \left(\frac{1}{8}\right)C + \left(\frac{1}{16}\right)D$$

- This circuit converts a binary number into an analog voltage

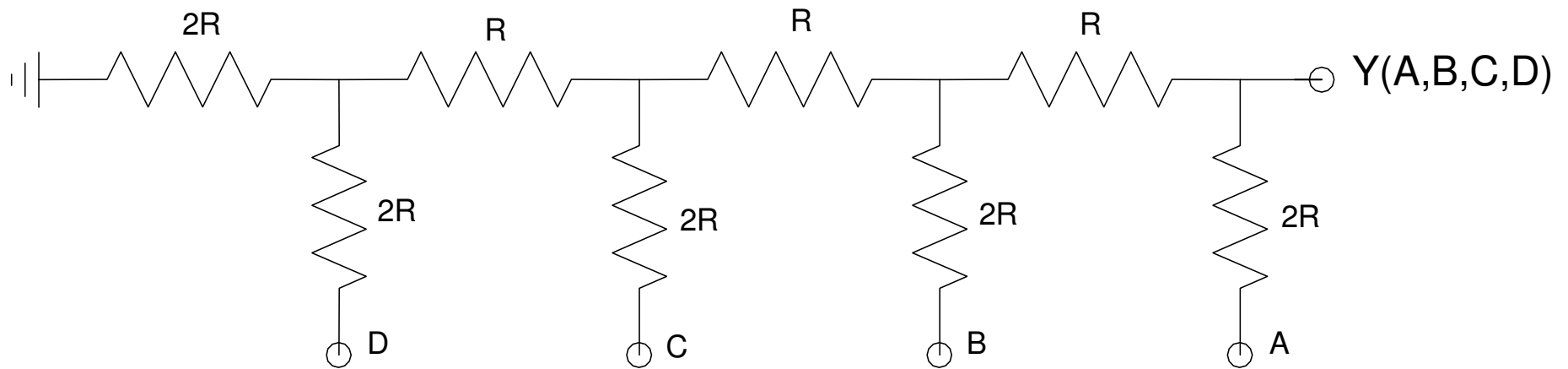

Example 3: Weighted Average

Case 1: Design a circuit so that Y is the average of $\{ A, B, C \}$


$$Y = \left(\frac{A+B+C}{3} \right)$$

By symmetry, use three resistors:

$$\left(\frac{Y-A}{R} \right) + \left(\frac{Y-B}{R} \right) + \left(\frac{Y-C}{R} \right) = 0$$

$$3Y = A + B + C$$


$$Y = \left(\frac{A+B+C}{3} \right)$$

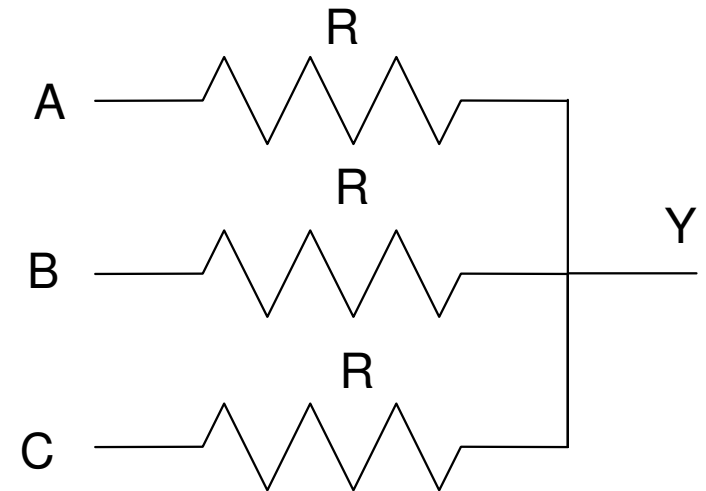

Case 2: Design a circuit so that Y is the weighted average:

$$Y = \left(\frac{2A+B+C}{4} \right)$$


Solution: Add A twice. This is equivalent to reducing R by 2:

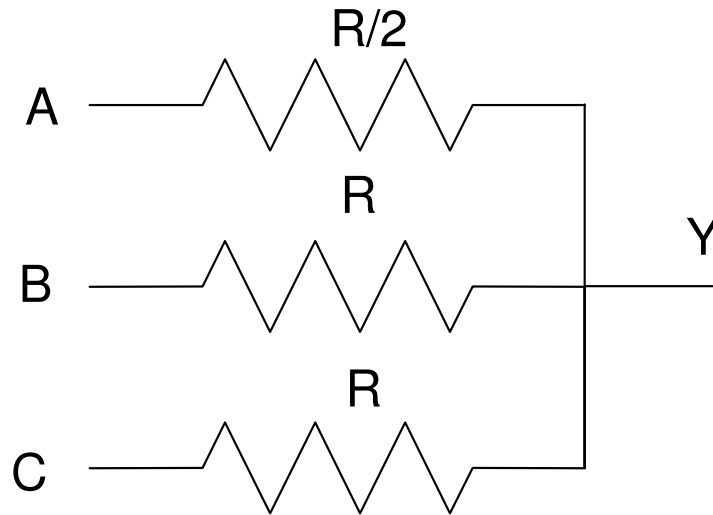

Case 3: Design a circuit to implement

$$Y = \left(\frac{aA + bB + cC}{a + b + c} \right)$$

Solution:

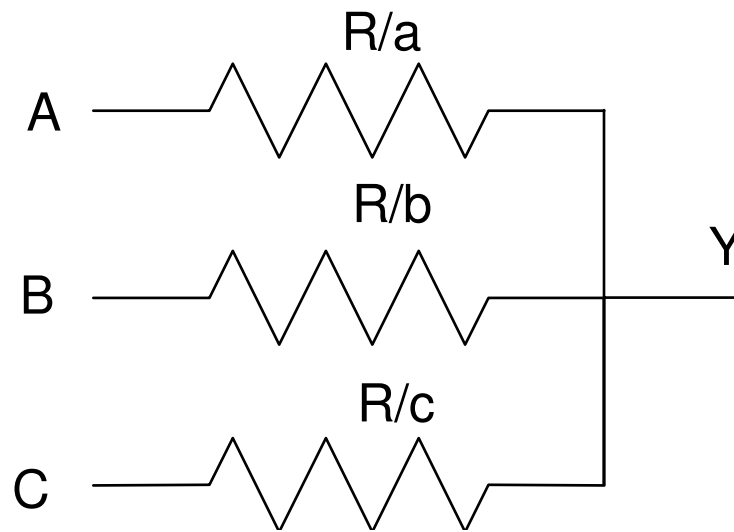

Y is the weighted average of A, B, C

Example: Level Shifting

- Let A be an analog signal in the range of (-10V, +10V)

Design a circuit to shift this voltage to the range of 0..5V.

Solution: Y is related to A as

$$Y = \frac{1}{4}A + 2.5$$

Rewrite as

$$Y = \frac{1}{4}A + \frac{1}{2}(5V) + \frac{1}{4}(0V)$$

$$Y = \left(\frac{1 \cdot (A) + 2 \cdot (5V) + 1 \cdot (0V)}{4} \right)$$

