
Ideal Op-Amp

ECE 211 Circuits I

Lecture #14

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions

Op-Amp Models


Last lecture looked at circuit models for an op-amp

- Replace it with it's circuit model
- Write the voltage node equations
- Solve

This resulted in somewhat painful analysis for simple circuits

- It gets worse with multiple op-amps

We need a better tool

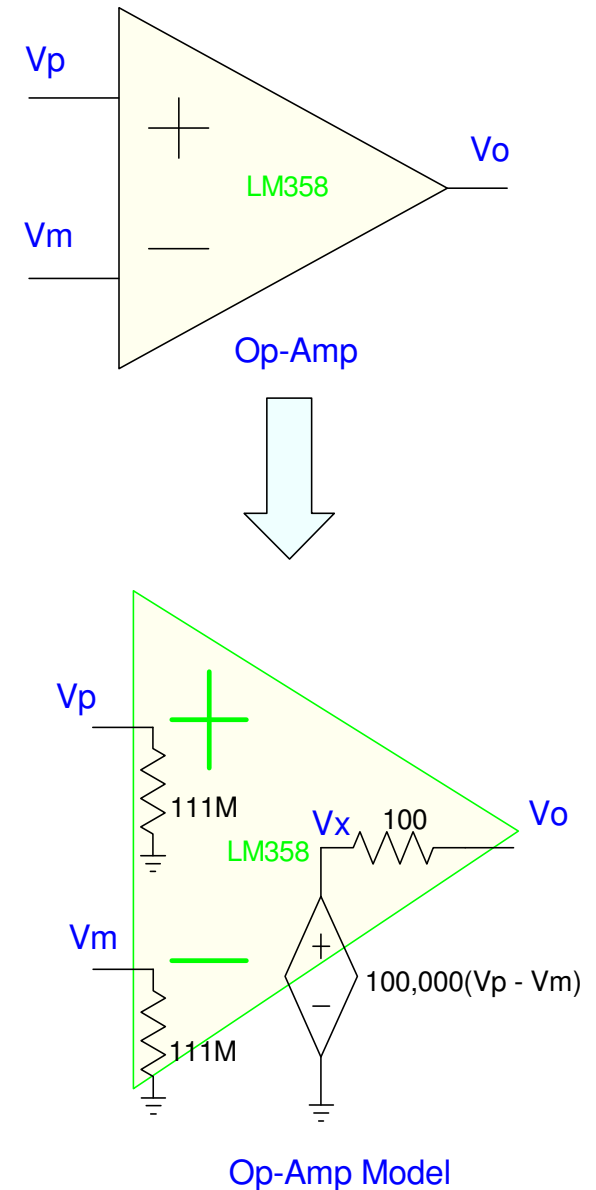

Ideal Op-Amp

Engineering solution:

- If you have a difficult problem, change the problem
- Make it simpler while
- Keeping the flavor of the original problem

Assume

- The differential gain is infinity
 - *vs. 100,000*
- The input current is zero
 - *Input impedance = infinity*
 - *vs. 111M Ohms*

It may not seem like it, but this greatly simplifies op-amp circuit analysis

Term	LM358	Ideal
Input Bias Current	45nA	0nA
(Input Impedance @ 5V)	111M	infinity
Open-Loop Gain	100,000	infinity
Gain Bandwidth Product	1MHz	infinity
Slew Rate	250,000 V/s	infinity
Voltage swing from rail	1.5V	0V
Output Current	20mA	infinity
Output Resistance	100 Ohms	0 Ohms

Circuit Analysis with Ideal Op-Amps

- Two methods commonly used

Method #1

Voltage Nodes

- Assume circuit has N voltage nodes
- Write N nodal equations
- $V_p = V_m$ is usually one equation
 - *This is the equation at V_o*
 - *Usually true with negative feedback*

Solve N equations for N unknowns

Method #2


What voltages make the circuit work?

Subject to...

- $V_p = V_m$
 - *Usually true with negative feedback*
- Currents must balance


Example #1: Find the voltages

Find $\{V1, V2, V3, V4\}$

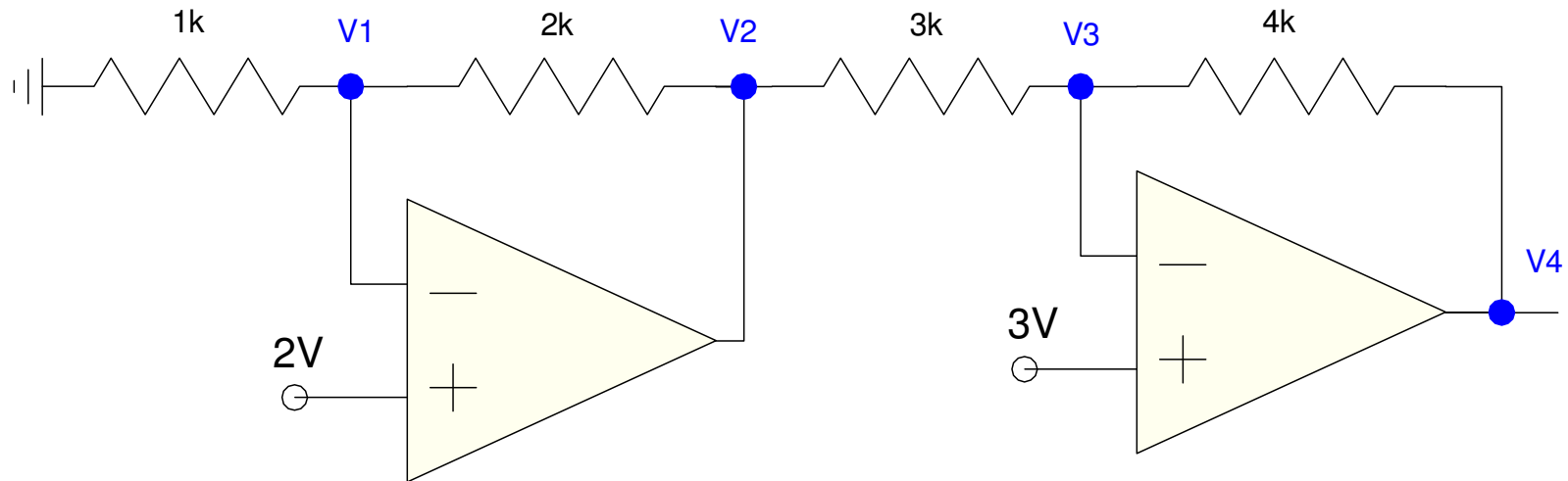

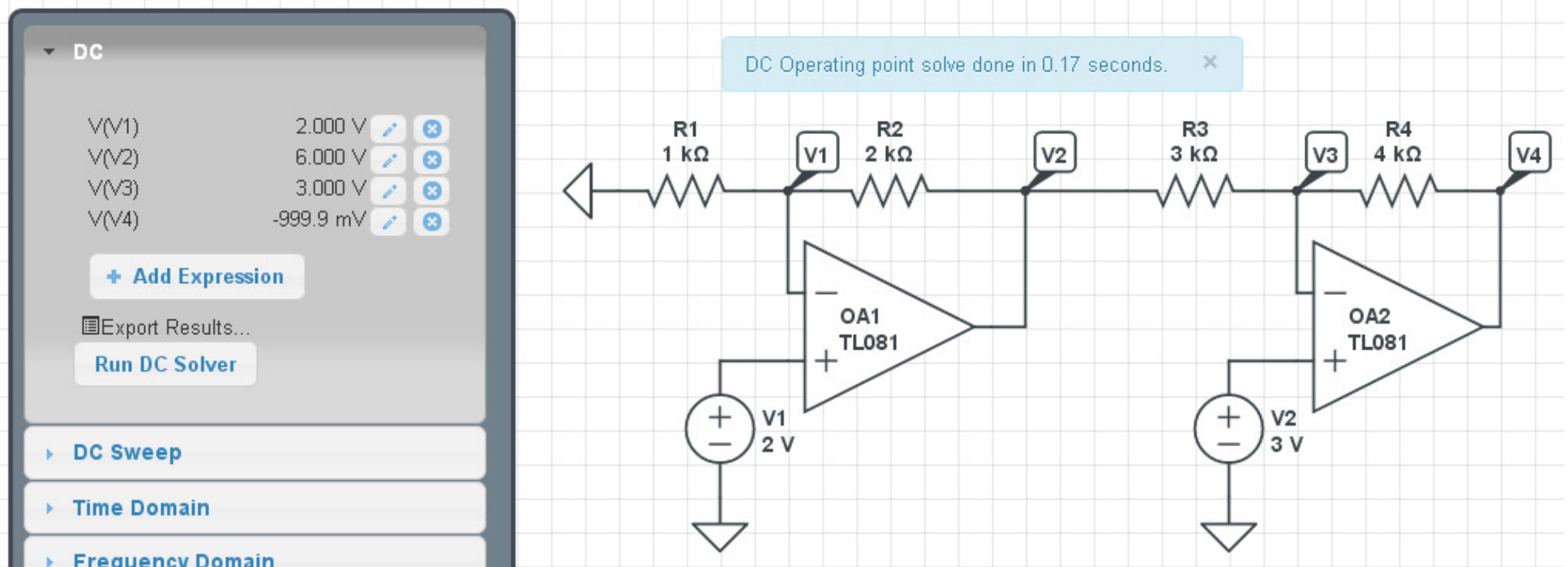
Example #1: CircuitLab

- note: All op-amps give about the same result
- All are differential amplifiers with high gain and high input impedance



Example #1: Voltage Nodes

Write 4 equations for 4 unknowns

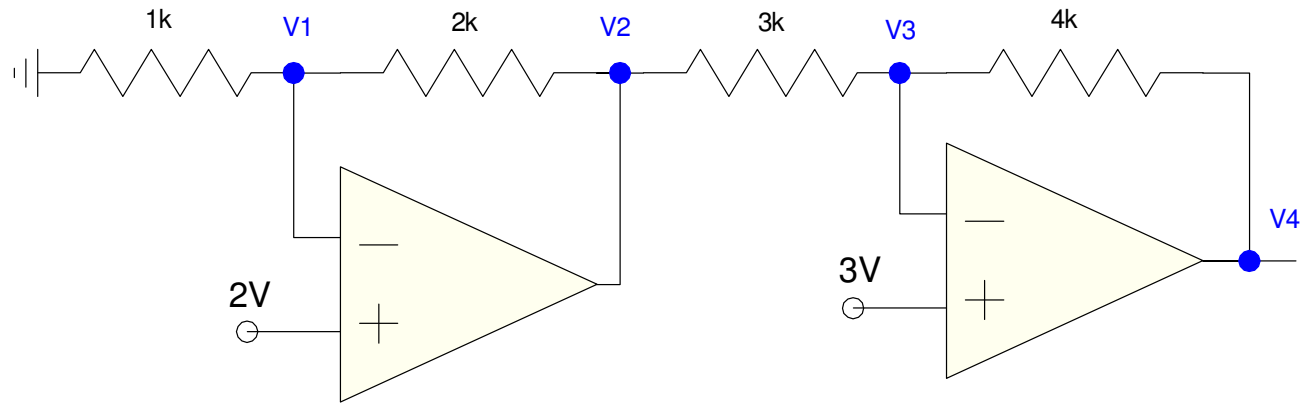

Example #1: Voltage Nodes

Easy ones: $V_p = V_m$

$$V_1 = 2$$


$$V_3 = 3$$

Two node equations

$$\left(\frac{V_1}{1k}\right) + \left(\frac{V_1 - V_2}{2k}\right) = 0$$


$$\left(\frac{V_3 - V_2}{3k}\right) + \left(\frac{V_3 - V_4}{4k}\right) = 0$$

Solve

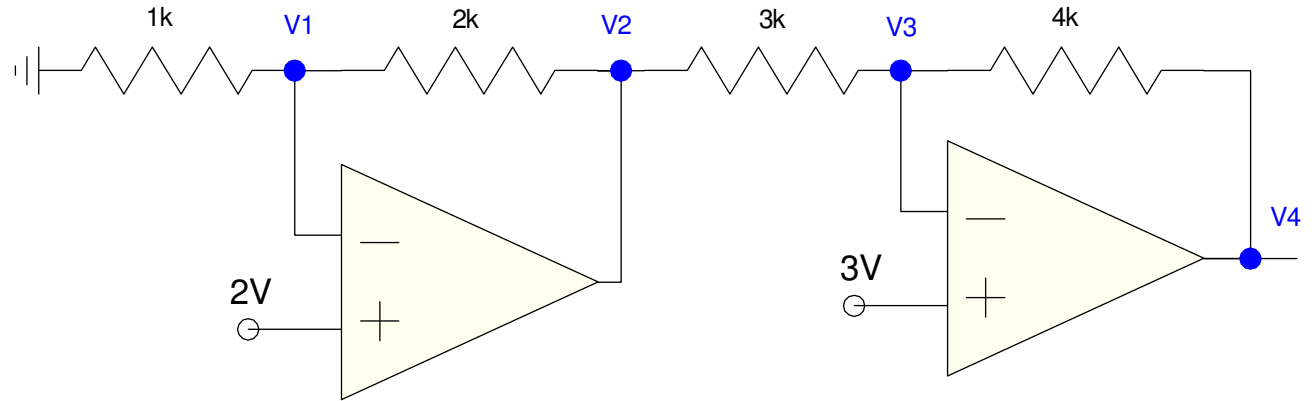

Example #1: Figure out voltages

- $V_p = V_m$
- Currents balance

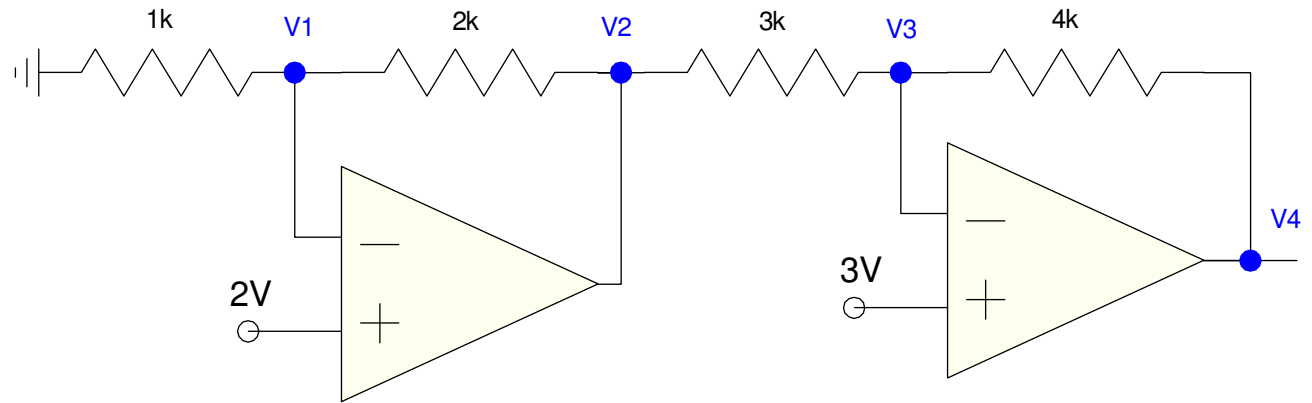

Example #1: Figure out voltages

Start with


- $V1 = 2V$
- $V3 = 3V$

First op-amp


- $I(1k) = 2mA$ ($2V$ @ $1k$)
- $I(2k) = 2mA$ (current in = current out)
- $V2 = 6V$ ($V1 + 2k * 2mA$)

Second op-amp

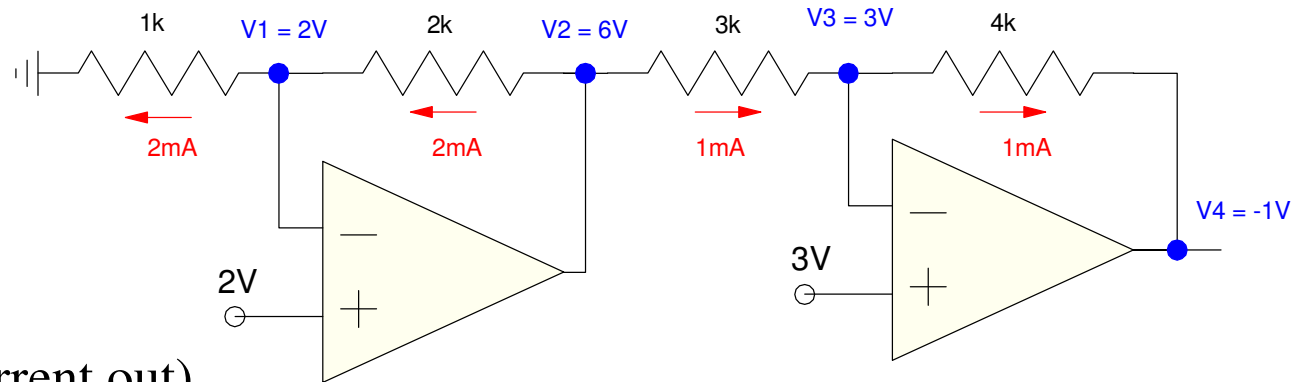- $I(3k) = 1mA$ ($3V$ @ $3k$)
- $I(4k) = 1mA$ (current in = current out)
- $V4 = -1V$ ($V3 - 4k * 1mA$)



Example #2: Determine the voltages

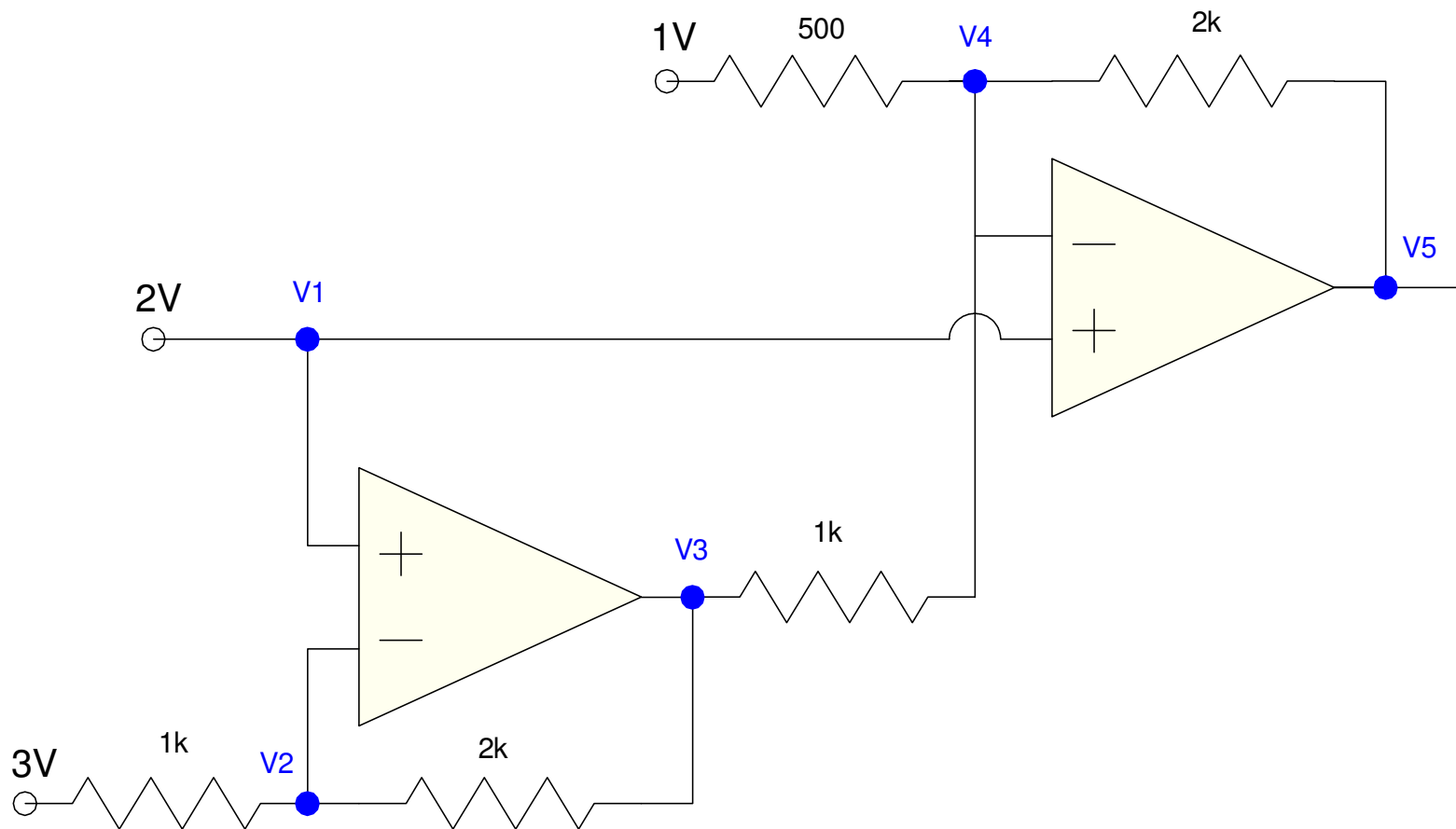

Example #2: CircuitLab

▼ DC

V(V1)	2.000 V		
V(V2)	2.000 V		
V(V3)	99.00 μ V		
V(V4)	2.000 V		
V(V5)	9.999 V		

+ Add Expression


Export Results...

Run DC Solver

► DC Sweep


► Time Domain

► Frequency Domain

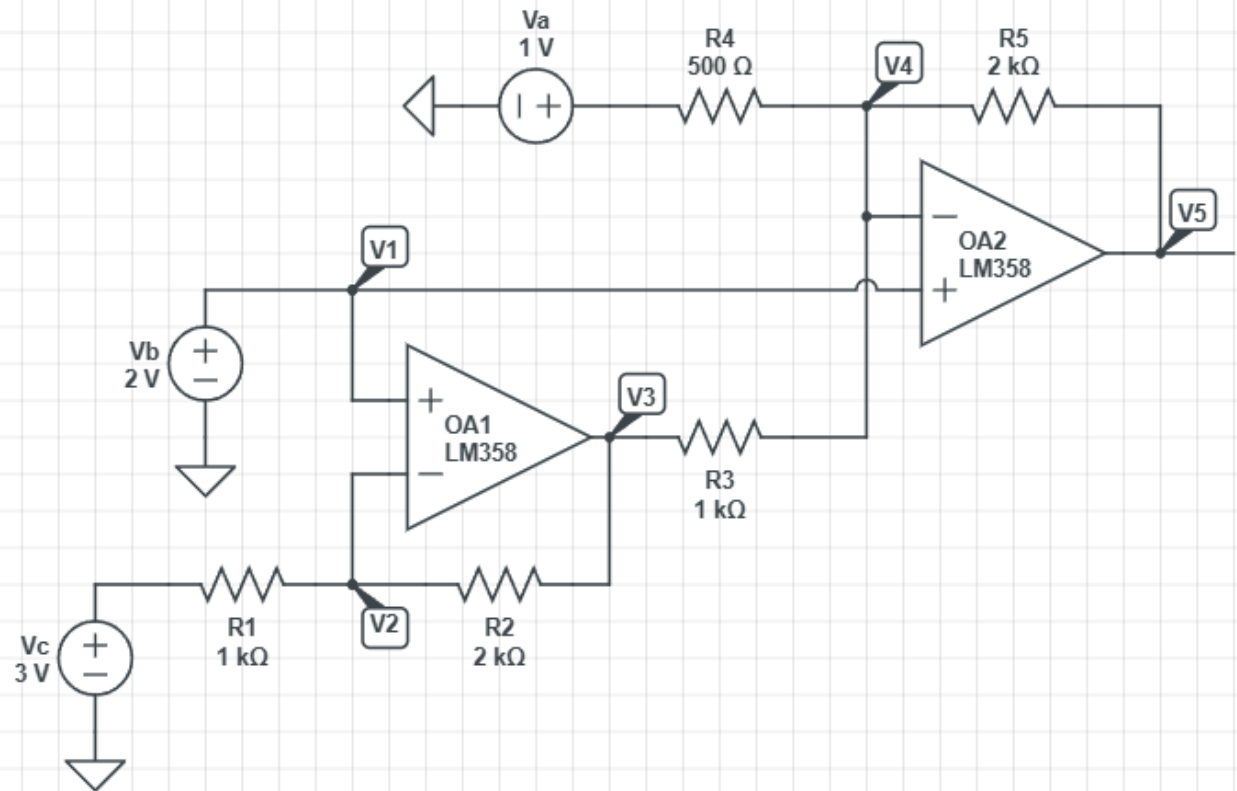

Example #2: Nodal Equations

Write 5 equations for 5 unknowns

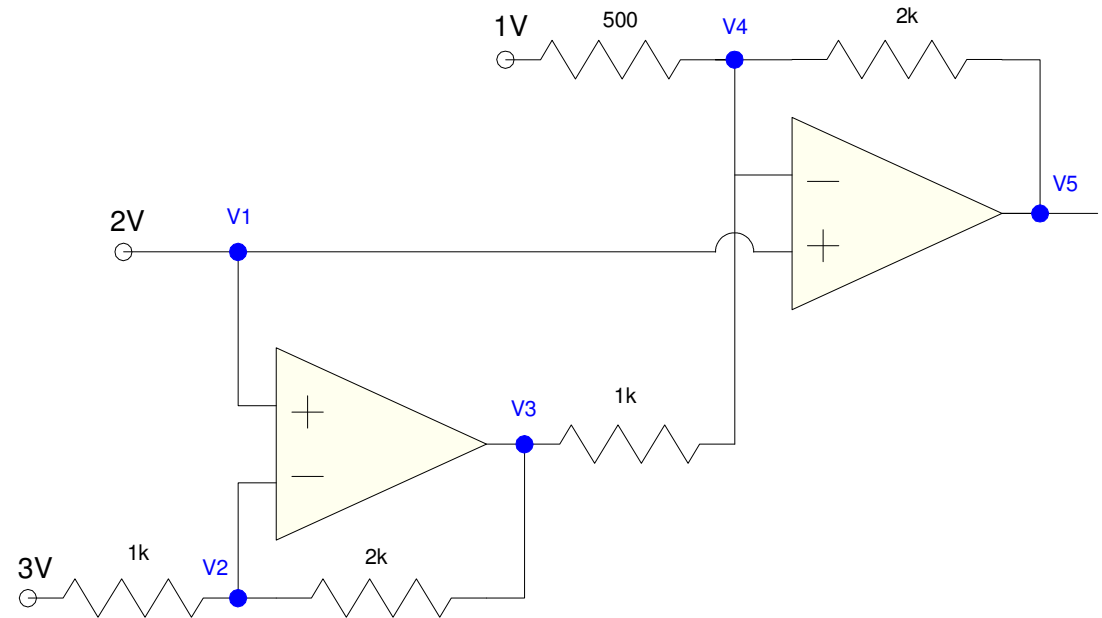

Example #2: Nodal Equations

Easy ones ($V_p = V_m$)

$$V_1 = 2$$

$$V_2 = V_1$$


$$V_4 = V_1$$

Write two more node equations:


$$\left(\frac{V_2 - 3}{1k} \right) + \left(\frac{V_2 - V_3}{2k} \right) = 0$$

$$\left(\frac{V_4 - 1}{500} \right) + \left(\frac{V_4 - V_5}{2k} \right) + \left(\frac{V_4 - V_3}{1k} \right) = 0$$

Solve

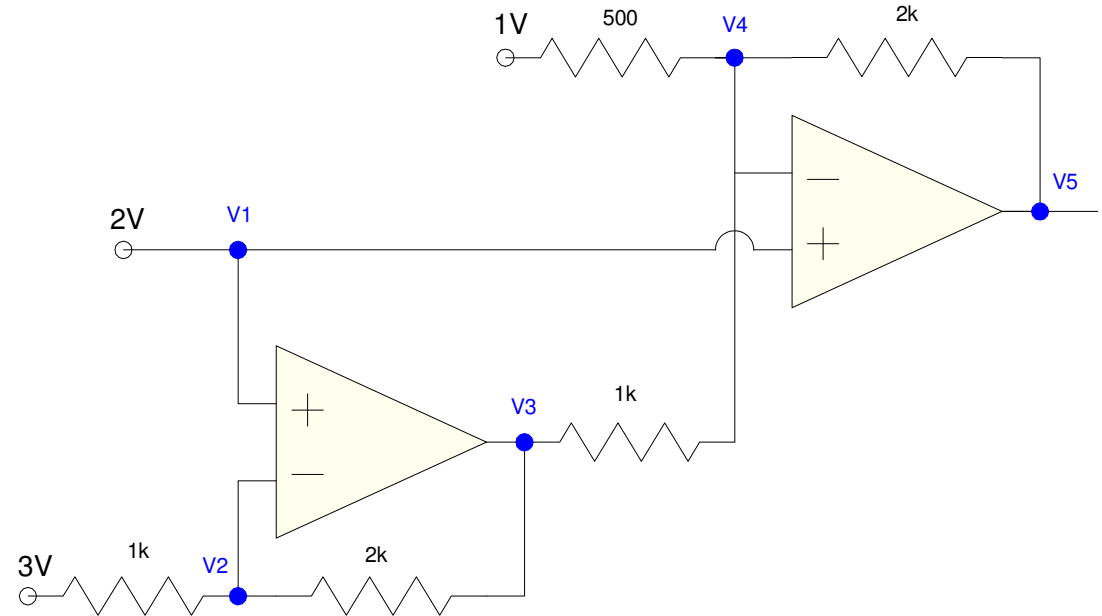

Example #2: Figure it out

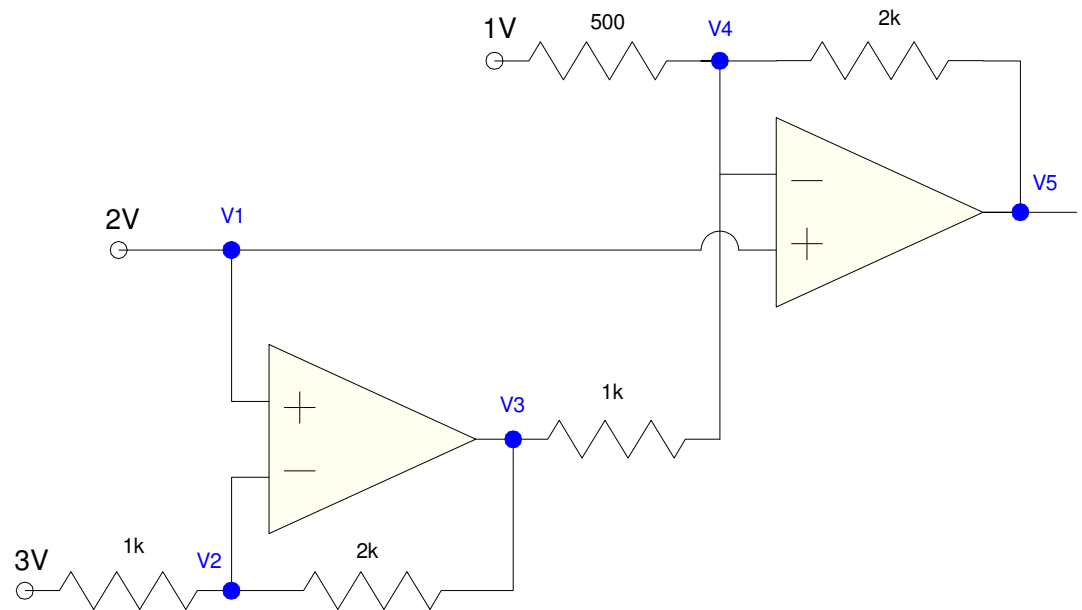


Example #2: Figure it Out

Easy Ones

- $V_1 = 2V$
- $V_2 = V_1 = 2V$
- $V_4 = V_1 = 2V$


Make the currents balance

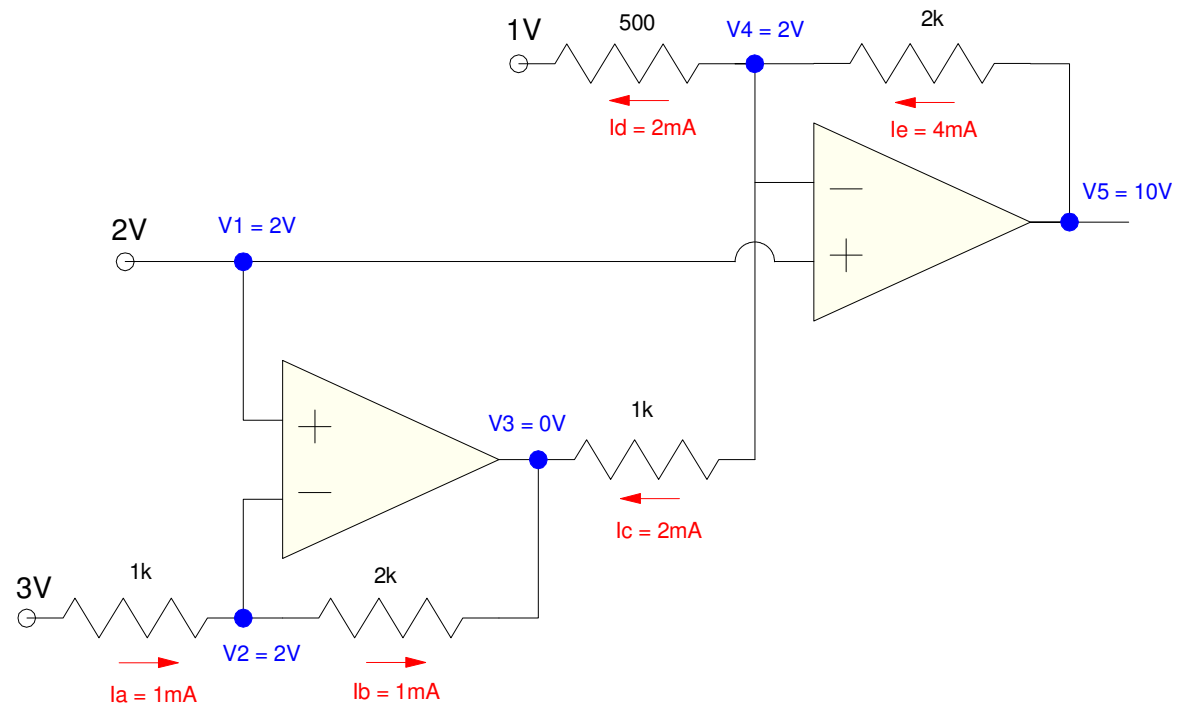- $I_a = 1mA$
- $I_b = I_a = 1mA$
- $V_3 = V_2 - I_b * 2k = 0V$
- $I_c = 2mA$
- $I_d = 2mA$
- $I_e = I_c + I_d = 4mA$
- $V_5 = V_4 + 2k * I_e = 10V$



Example #3: Determine the Voltages

- Write 5 equations for 5 unknowns

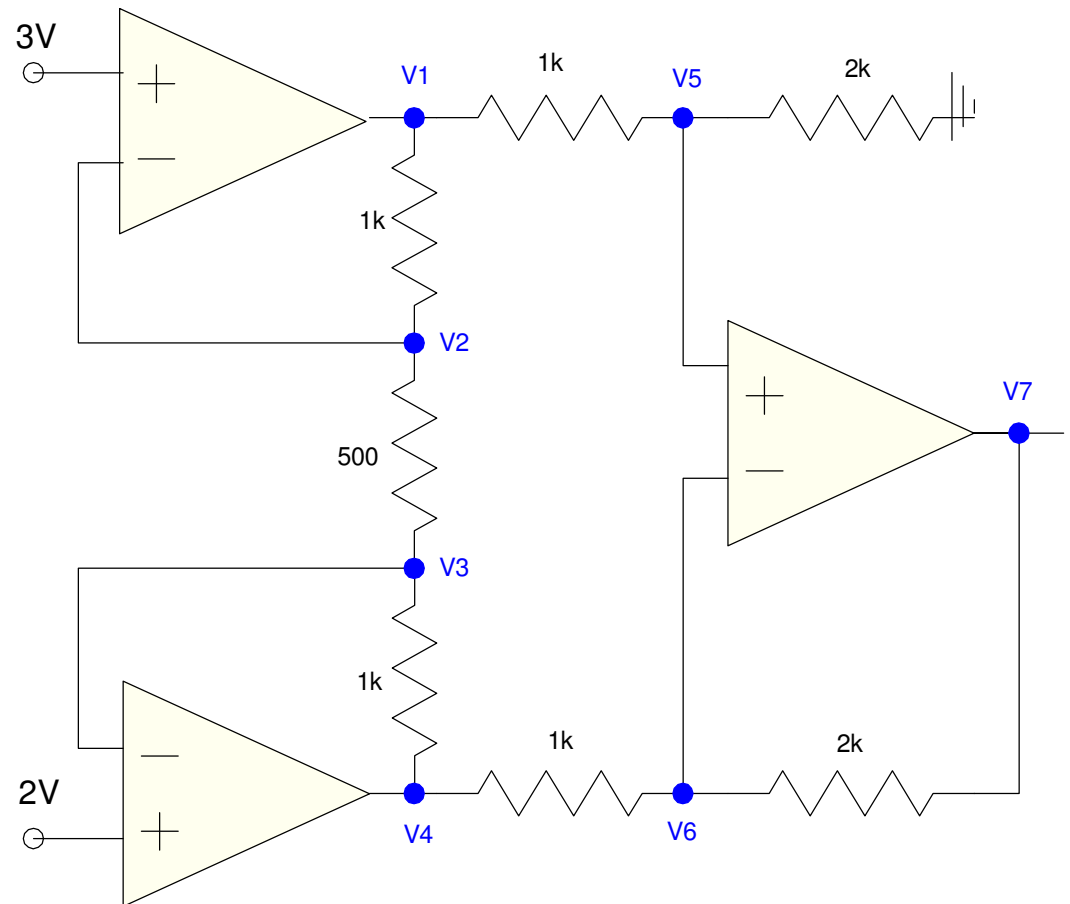

Example #3: Nodal Equations

Easy Ones ($V_p = V_n$)

$$V_2 = 3V$$

$$V_3 = 2V$$

$$V_5 = V_6$$


Node equations

$$\left(\frac{V_2 - V_1}{1k} \right) + \left(\frac{V_2 - V_3}{500} \right) = 0$$


$$\left(\frac{V_3 - V_2}{500} \right) + \left(\frac{V_3 - V_4}{1k} \right) = 0$$

$$\left(\frac{V_5 - V_1}{1k} \right) + \left(\frac{V_5}{2k} \right) = 0$$
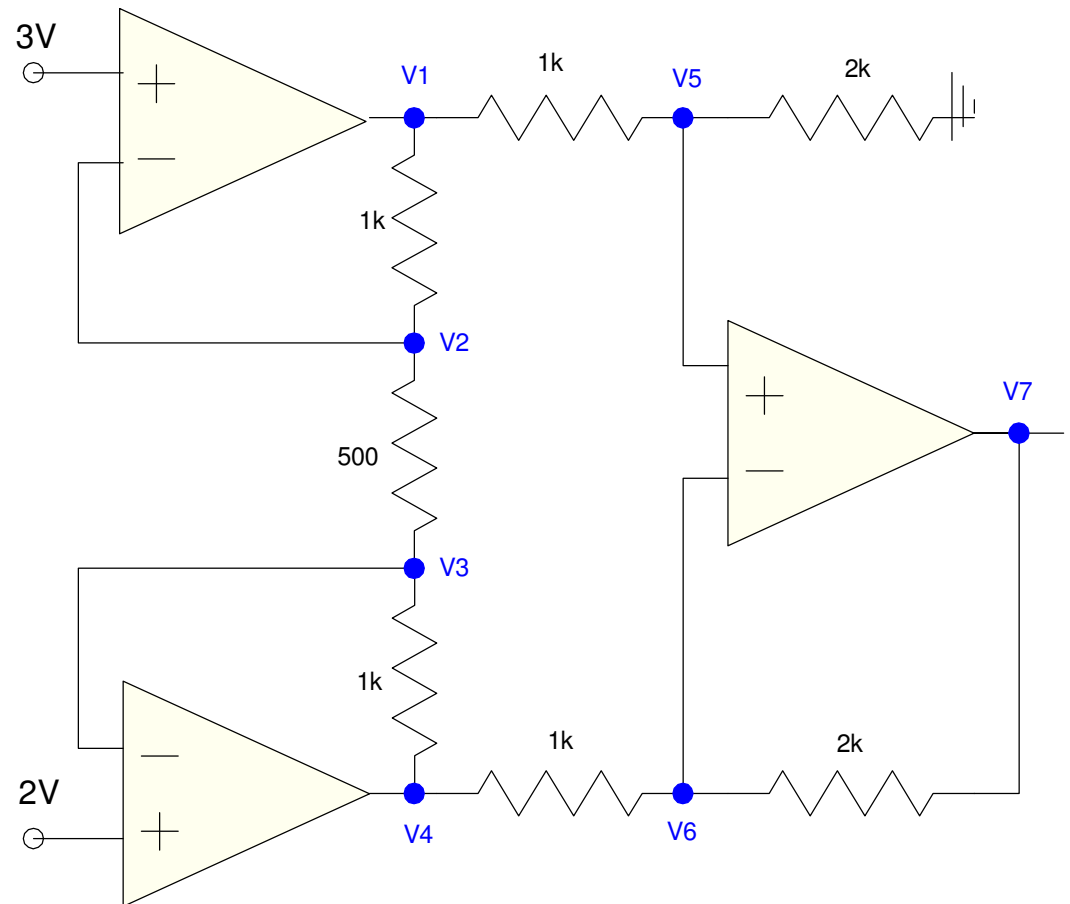
$$\left(\frac{V_6 - V_4}{1k} \right) + \left(\frac{V_6 - V_7}{2k} \right) = 0$$



Example #3: Figure out the voltages

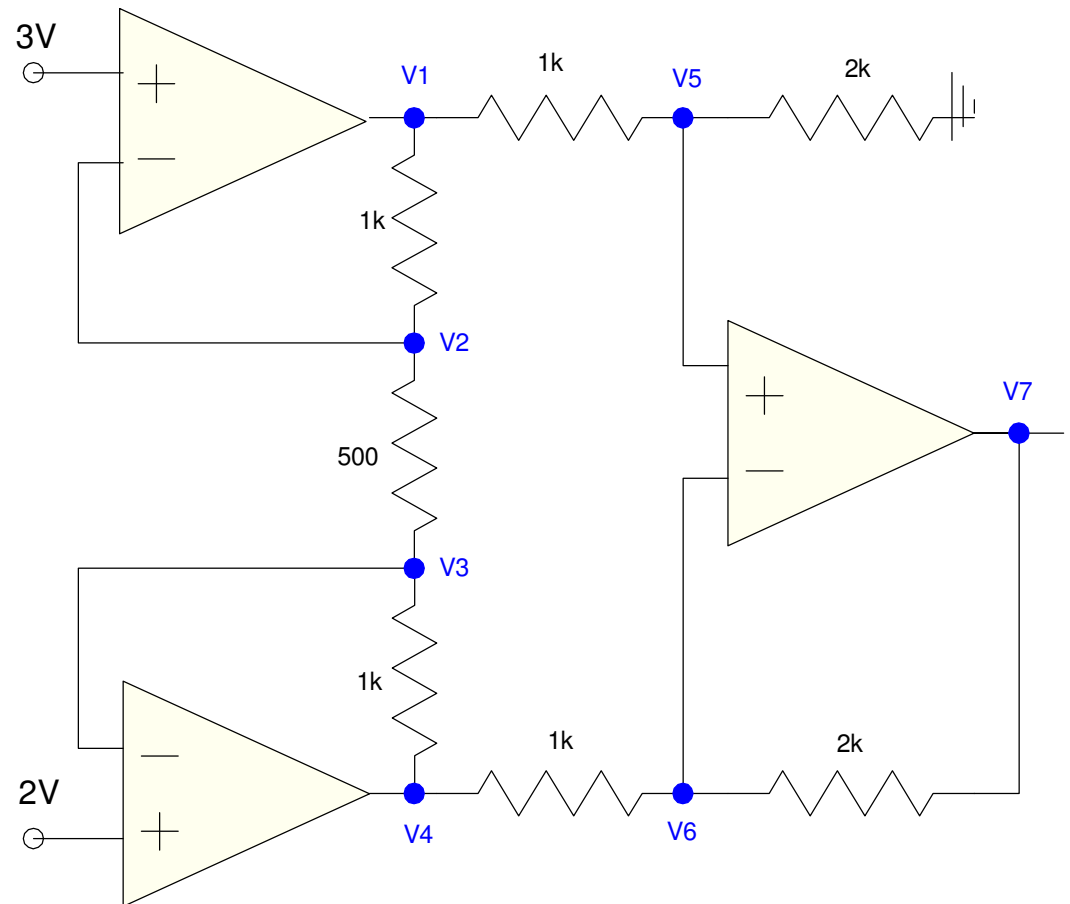

Example #3: Figure out the voltages

Start with

$$V2 = 3V$$

$$V3 = 2V$$

$$I_a = (V2 - V3) / 500 = 2\text{mA}$$

$$I_b = I_c = I_a = 2\text{mA}$$

$$V1 = V2 + I_b * 1k$$

$$V4 = V3 - I_c * 1k$$

$$I_d = V1 / 3k = 1.67\text{mA}$$


$$V5 = 2k * I_d = 3.33V$$

$$V6 = V5 = 3.33V$$

$$I_e = (V6 - V4) / 1k = 3.33\text{mA}$$

$$I_f = I_e = 3.33\text{mA}$$

$$V7 = V6 + 2k * I_f$$

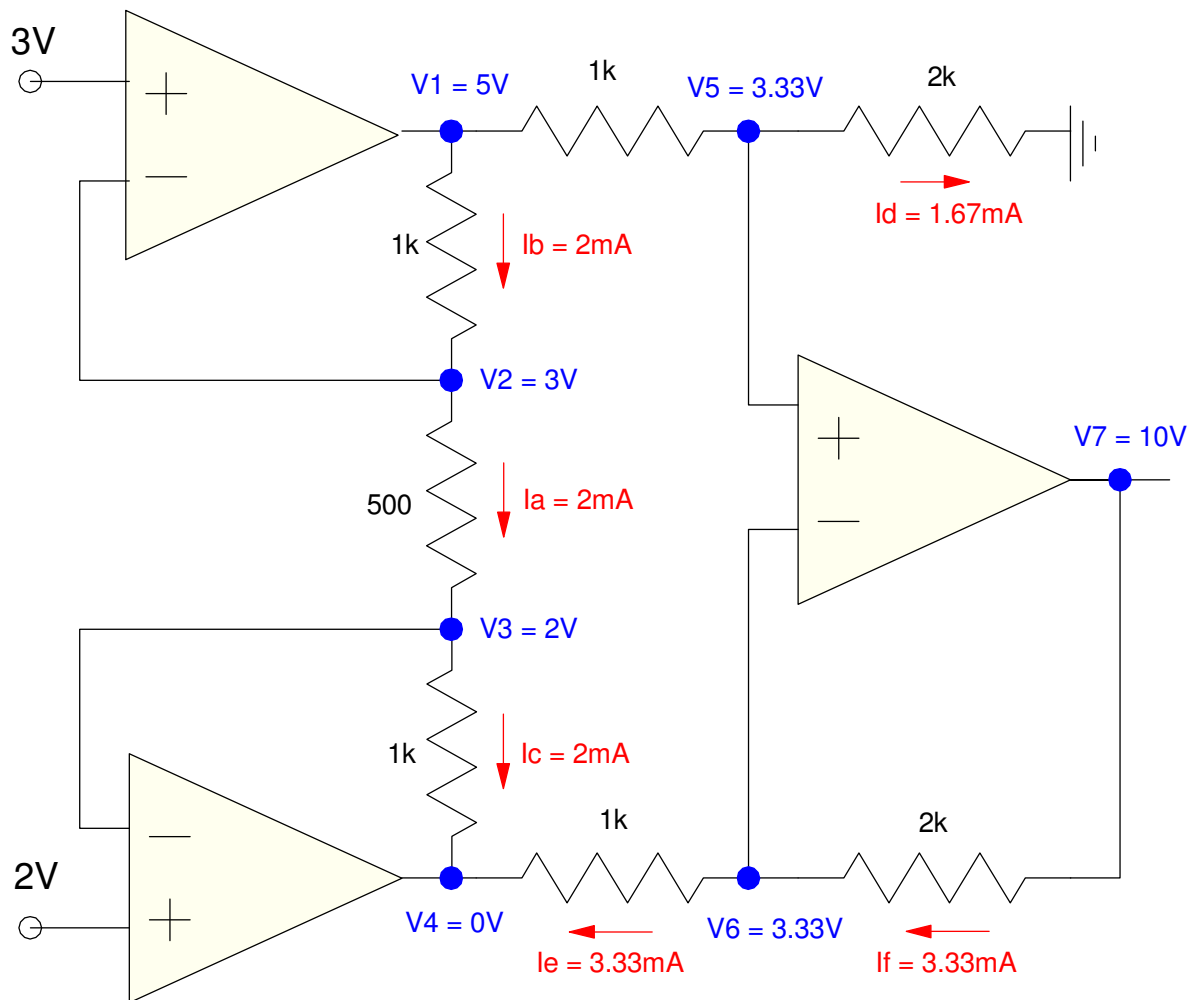

Summary

There are two main methods for analyzing op-amp circuits

- Assume ideal op-amps
- Assume $V_p = V_m$
 - *Usually the case when there's negative feedback*

a) Voltage nodes

- Start with $V_p = V_m$
- Write remaining N equations for N unknowns

b) Figure it out

- Currents have to balance
 - $V_p = V_m$ *usually* holds
-