
Capacitors & The Heat Equation

ECE 211 Circuits I

Lecture #17

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions


Capacitors

A capacitor is a set of parallel plates¹ with the capacitance equal to

$$C = \epsilon \frac{A}{d} \text{ (Farads)}$$

where

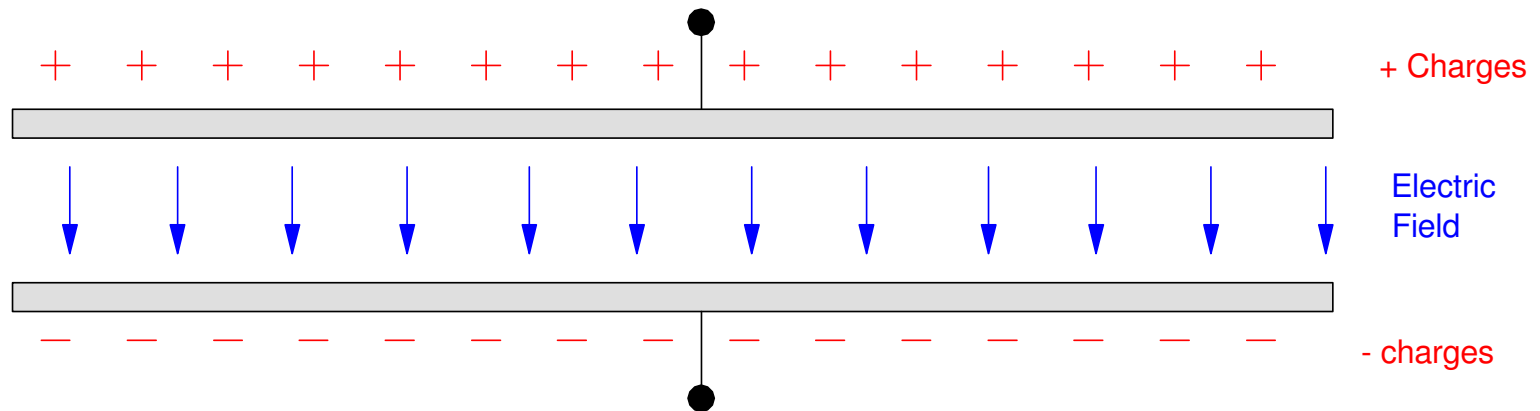- ϵ is the dielectric constant of the material between plates (air = $8.84 \cdot 10^{-12}$)
- A is the area of the capacitor, and
- d is the distance between plates.



¹ <http://www.electronics-tutorials.ws/>

The area you need for 1 Farad with plates 1mm apart is

$$1 = (8.84 \cdot 10^{-12}) \frac{A}{0.001m}$$

$$A = 113,122,171 m^2$$

Equal to 10.6km x 10.6km

- Most capacitors on the order of μF or nF

The charge stored is

$$Q = C \cdot V$$

Q = charge (Coulombs - one Coulomb is equal to $6.242 \cdot 10^{18}$ electrons).

Voltage - Current Relationship

$$Q = CV$$

$$I = \frac{dQ}{dt} = C \frac{dV}{dt} + V \frac{dC}{dt}$$

Assuming the capacitance is constant

$$I = C \frac{dV}{dt}$$

This means that capacitors are integrators:

$$V = \frac{1}{C} \int I \cdot dt$$

Capacitors and Energy Storage

The energy stored is

- $E = \frac{1}{2}CV^2$
- 12.5J = 12.5kW for 1ms
- Capacitors provide energy for short bursts

Item	Energy (Joules)	Cost	\$ / MJ
1 pound Wyoming Coal	3,600,000	\$0.028	\$0.0078
1 pound ND Lignite	1,565,217	\$0.017	\$0.0108
1 pint of gasoline	15,000,000	\$0.37	\$0.0247
Lithium battery (D cell)	246,240	\$22	\$89.43
1F Capacitor (5V)	12.5	\$2.87	\$229,600

Numerical Integration and Capacitors

Capacitors are inherently integrators:

$$I = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int I dt$$

Differential equations are required to described circuits with capacitors

- Each capacitor adds a 1st-order differential equation
- N capacitors means an Nth-order differential equation

Calculus: Solving differtial equations using calculus

Circuits I: Solving differetial equations using phasors (coming soon) and numerical methods

Circuits II, Signals & Systems: Solving differential equtions using LaPlace transforms

Numerical Integration

- Solve a differential equation using numerical methods (i.e. Matlab)
- Whole field of mathematics deals with numerical integration

Several types of numerical integration

- Euler Integration
- Trapezoid Rule
- Runge Kutta Integration
- more...

All are approximate


- Use Calculus or LaPlace transforms to get closed-form, exact solutions

Euler Integration

- $y(t) = y(t - T) + x(t) \cdot dt$
- Sample $x(t)$ every T seconds,
- Use rectangles to approximate the area every T seconds, and
- Sum up the area of each rectangle.


Result is the simplest and least accurate of the three forms.

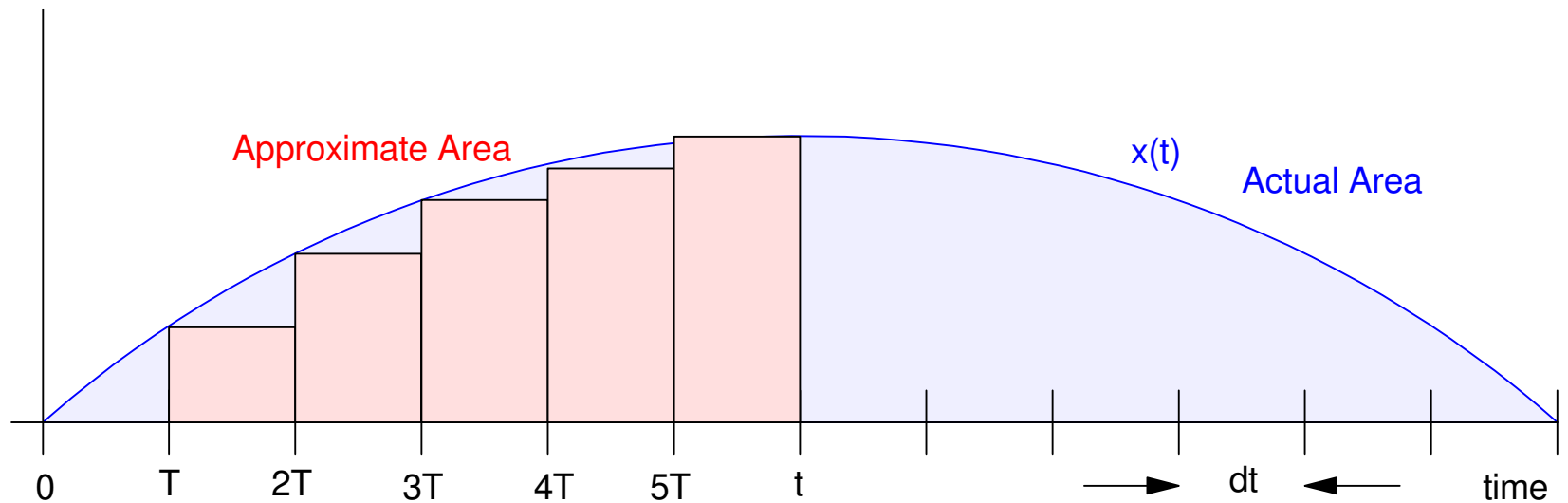- Not too bad if you keep the sampling time (dt) small.




Trapezoid (Bilinear) Integration:

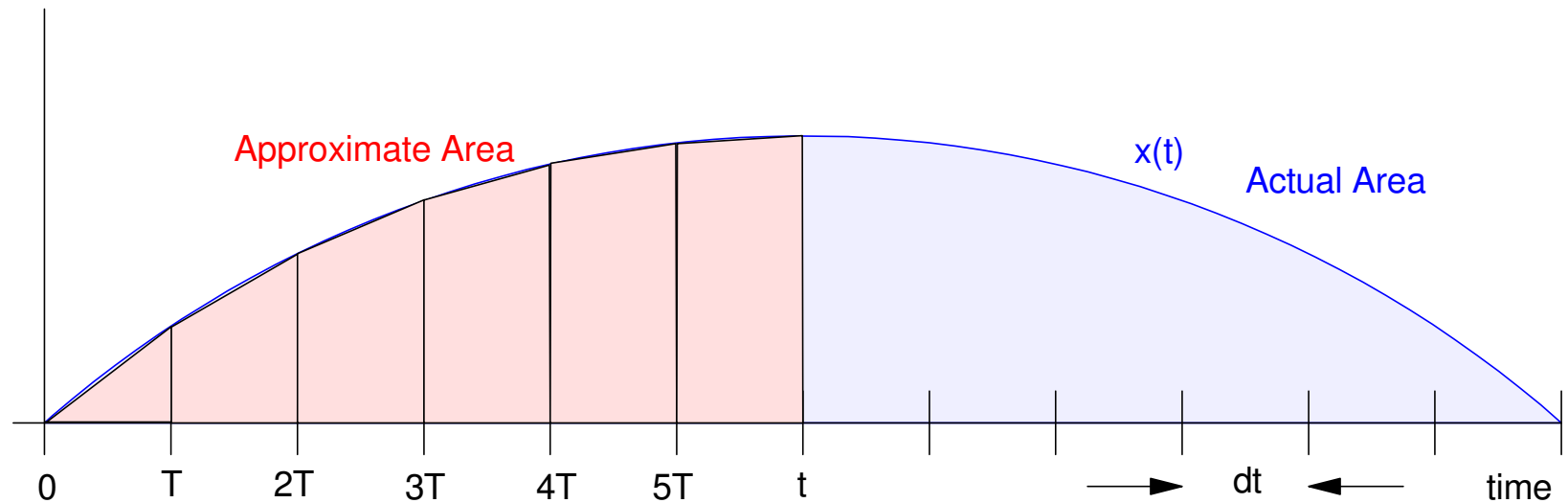- $y(t) = y(t - T) + \left(\frac{x(t) + x(t-T)}{2} \right) \cdot dt$
- Sample $x(t)$ every T seconds,
- Use trapezoids to approximate the area every T seconds
- *Much* better than Euler
- Required memory (need to recall previous input)



Runge Kutta Integration:

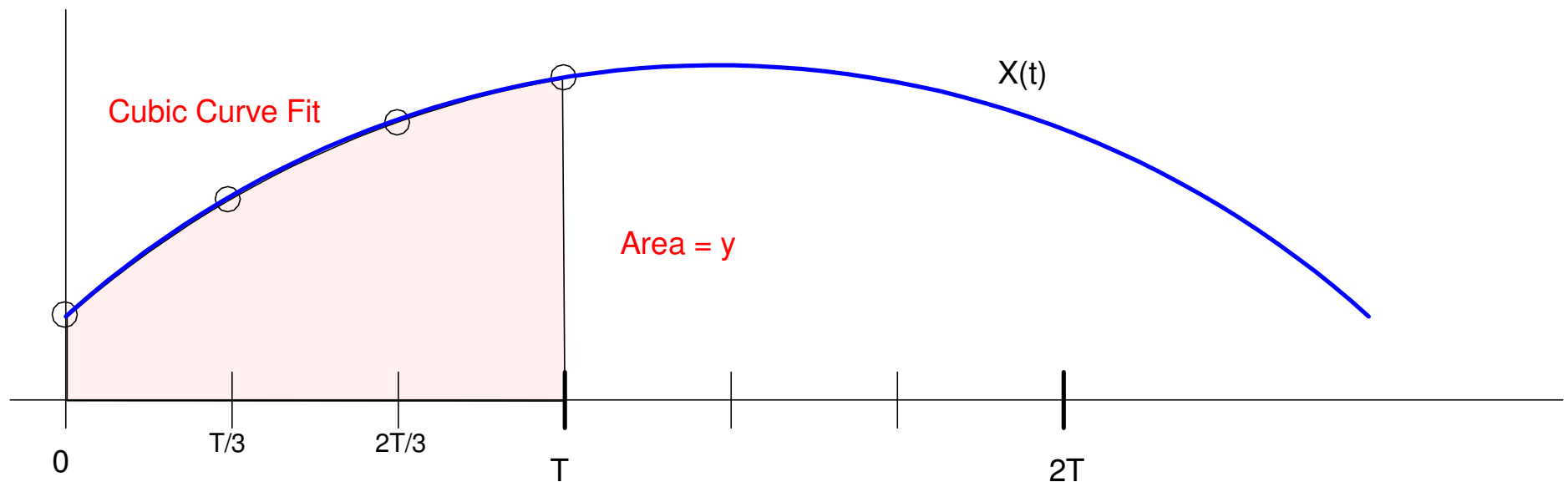- Sample $x(t)$ every T seconds,
- Use parabola, cubics, etc. to approximate the area
- Required memory and data inbetween samples




Stick with Euler integration

To find the voltage across a capacitor

- Compute the current to the capacitor, and
- Integrate using Euler integration:

$$dV = I / C$$

$$V = V + dV * dt$$

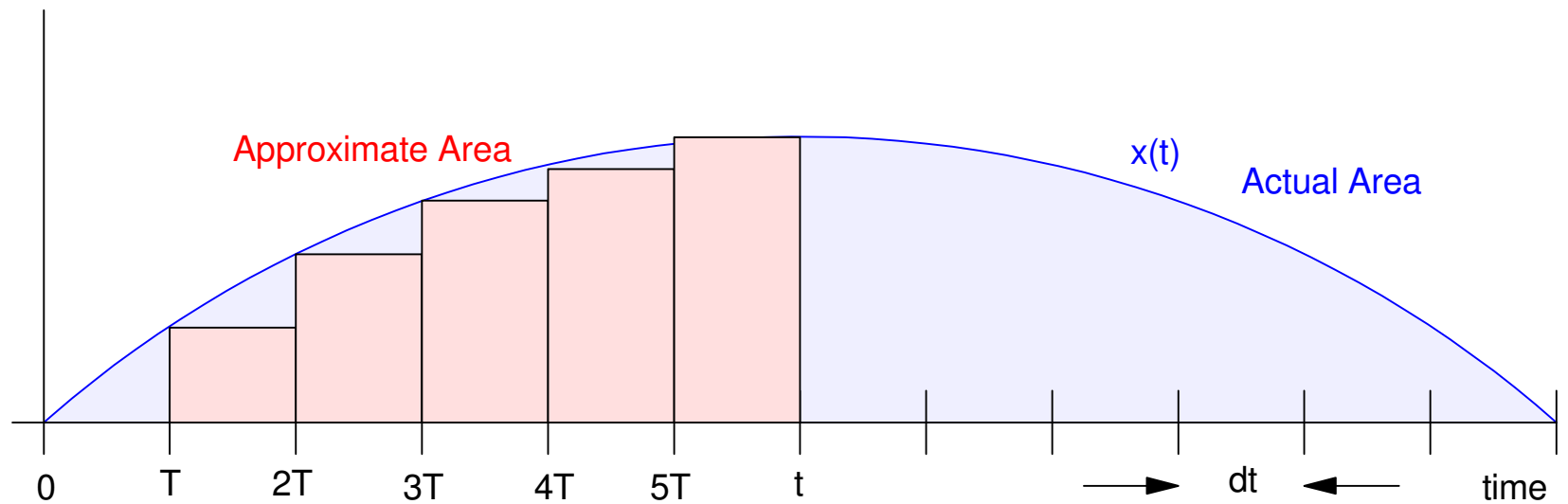

Example 1: 1-Stage RC Circuit

Find $V_1(t)$ with


$$V_0(t) = 10u(t) = \begin{cases} 0V & t < 0 \\ 10V & t > 0 \end{cases}$$

Solution

$$I_c = I_a + I_b$$

$$C \frac{dV_1}{dt} = I_c = \left(\frac{V_0 - V_1}{2} \right) + \left(\frac{0 - V_1}{100} \right)$$

$$\frac{dV_1}{dt} = -5.1 V_1 + 5 V_0$$

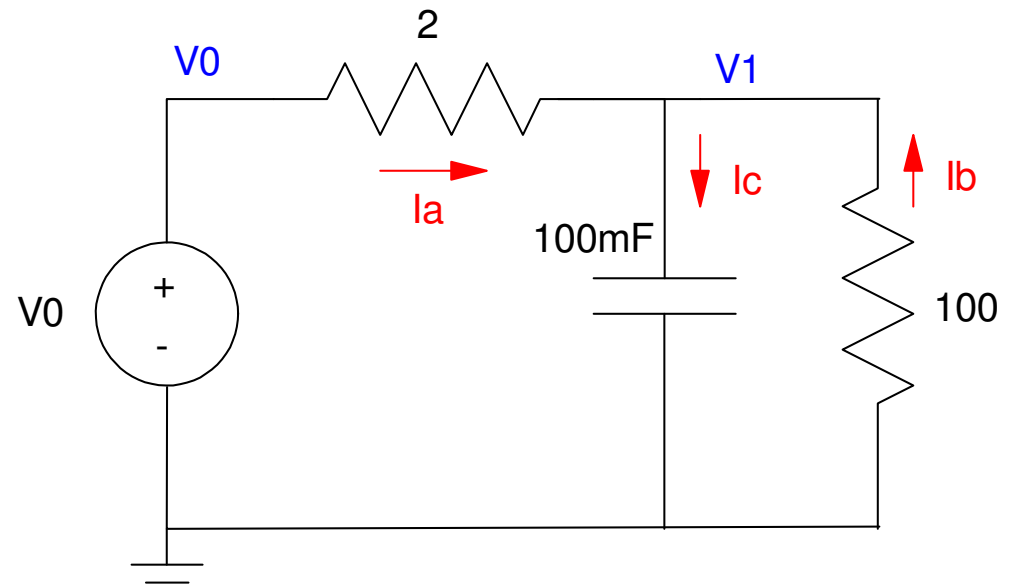

Solve in Matlab


```
% 1-stage RC Filter

V = 0;
V0 = 10;
dt = 0.01;
t = 0;
Y = [];

while(t < 1)
    dV = -5.1*V + 5*V0;
    V = V + dV*dt;
    t = t + dt;
    Y = [Y ; V];
end


t = [1:length(Y)]' * dt;

plot(t, Y);
```

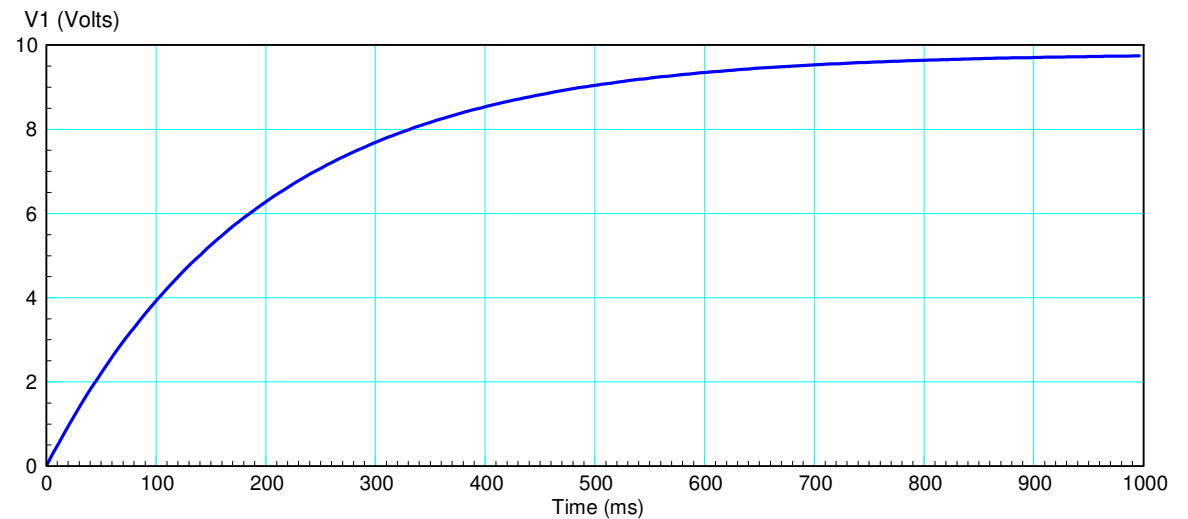

Solve in CircuitLab

- V1 = 10V square wave, 0.1Hz, 0.1 degree phase shift
- Run a time-domain simulation for 1 second
- Gives the same answer
- CircuitLab also solves using numerical integration

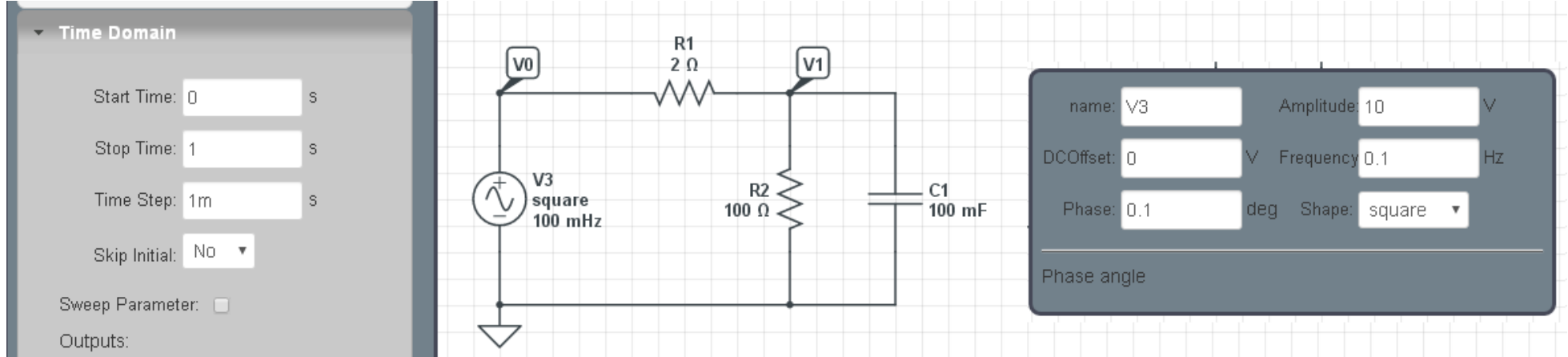


Example 2: 3-Stage RC Filter

$$V_0(t) = 10u(t)$$

$$C_1 \frac{dV_1}{dt} = I_1 = \left(\frac{V_0 - V_1}{2} \right) + \left(\frac{0 - V_1}{100} \right) + \left(\frac{V_2 - V_1}{2} \right)$$

$$C_2 \frac{dV_2}{dt} = I_2 = \left(\frac{V_1 - V_2}{2} \right) + \left(\frac{0 - V_2}{100} \right) + \left(\frac{V_3 - V_2}{2} \right)$$
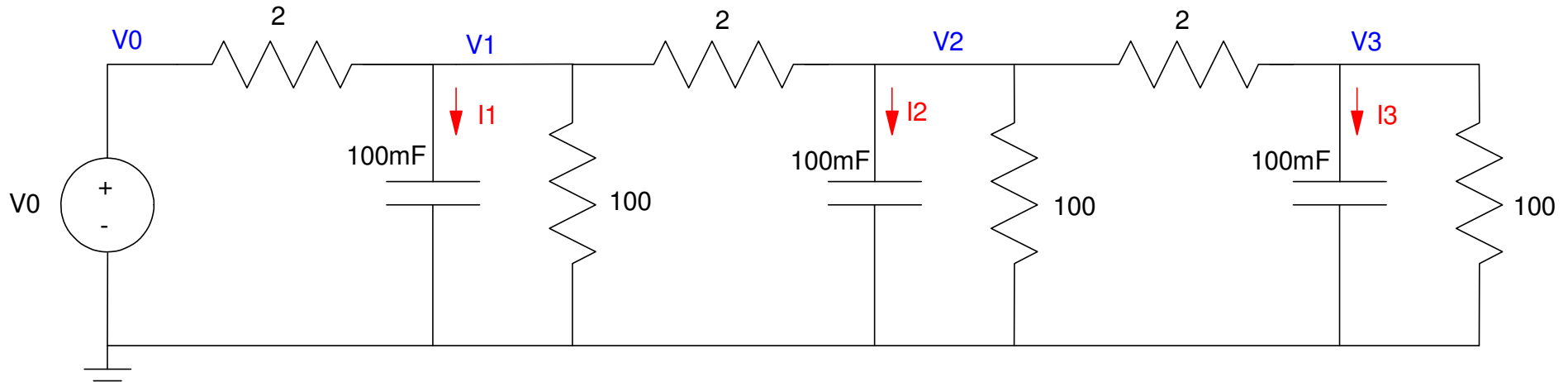
$$C_3 \frac{dV_3}{dt} = I_3 = \left(\frac{V_2 - V_3}{2} \right) + \left(\frac{0 - V_3}{100} \right)$$




Determine dV/dt

$$\frac{dV_1}{dt} = 5V_0 - 10.1V_1 + 5V_2$$


$$\frac{dV_2}{dt} = 5V_1 - 10.1V_2 + 5V_3$$

$$\frac{dV_3}{dt} = 5V_2 - 5.1V_3$$

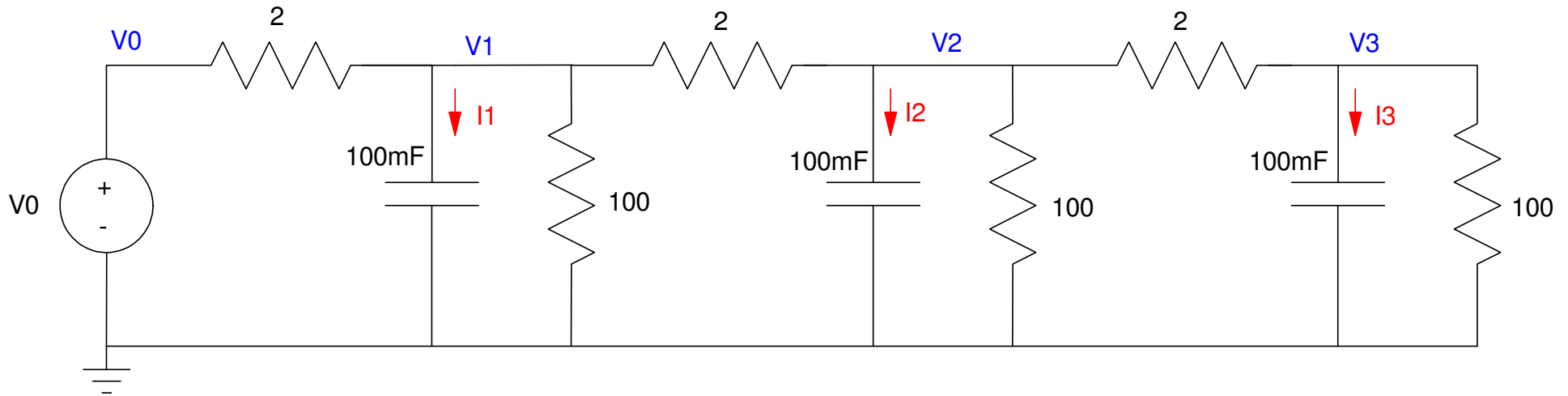

Solve in Matlab:


```
V0 = 10;  
V1 = 0; V2 = 0; V3 = 0;  
dt = 0.01;  
t = 0;  
Y = [];  
  
while(t < 4)  
    dV1 = 5*V0 - 10.1*V1 + 5*V2;  
    dV2 = 5*V1 - 10.1*V2 + 5*V3;  
    dV3 = 5*V2 - 5.1*V3;  
  
    V1 = V1 + dV1 * dt;  
    V2 = V2 + dV2 * dt;  
    V3 = V3 + dV3 * dt;  
  
    t = t + dt;  
  
    Y = [Y ; [V1, V2, V3] ];  
end  
  
t = [1:length(Y)]' * dt;  
plot(t, Y);
```

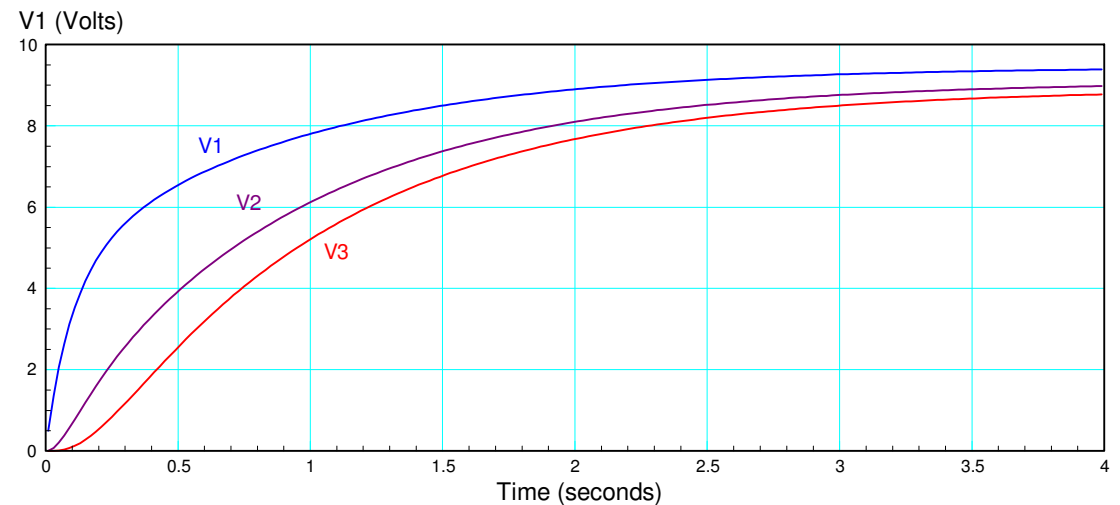

Case 3: 10-Stage RC Filter: Heat Equation

$$\frac{dV_n}{dt} = 5V_{n-1} - 10.1V_n + 5V_{n+1} \quad 1 < n < 9$$
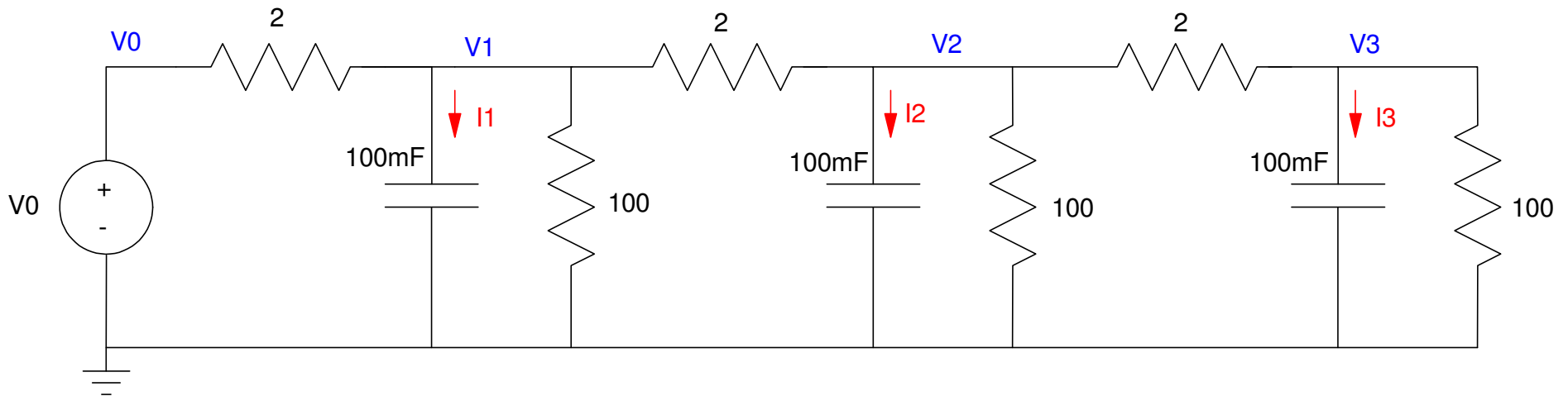
$$\frac{dV_{10}}{dt} = 5V_9 - 5.1V_{10}$$



In Matlab, use a for-loop:

```
% 10-stage RC Filter


V0 = 10;
V = zeros(10,1);
dV = 0*V;
dt = 0.01;
t = 0;
Y = [];

while(t < 10)
    dV(1) = 5*V0 - 10.1*V(1) + 5*V(2);
    for i=2:9
        dV(i) = 5*V(i-1) - 10.1*V(i) + 5*V(i+1);
    end
    dV(10) = 5*V(9) - 5.1*V(10);


    V = V + dV * dt;
    t = t + dt;

    N = [0:10];
    plot(N, [V0; V], 'b.-');
    ylim([0,10]);
    pause(0.01);
```

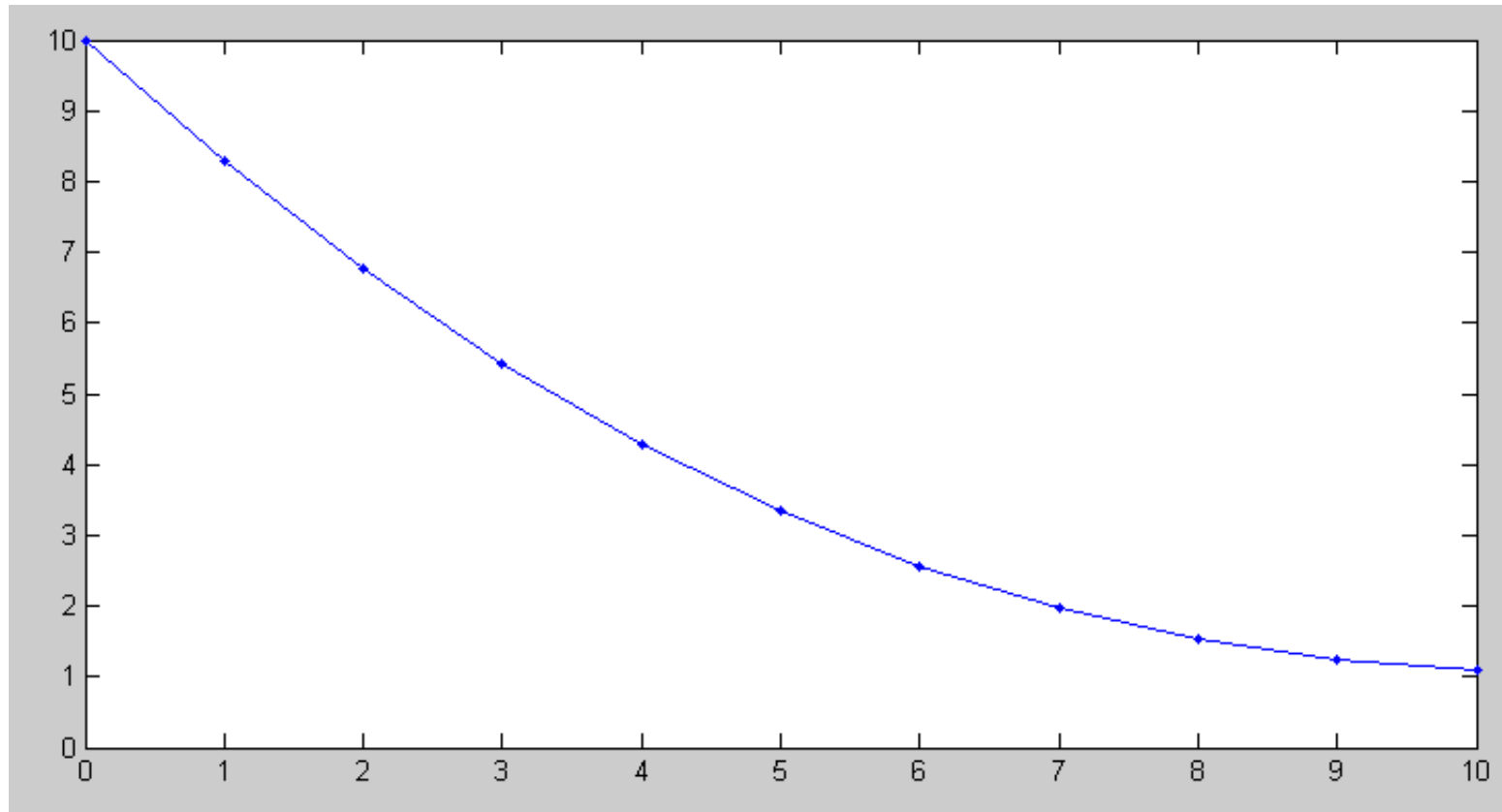For the first 10 seconds, this program shows the voltages along the circuit



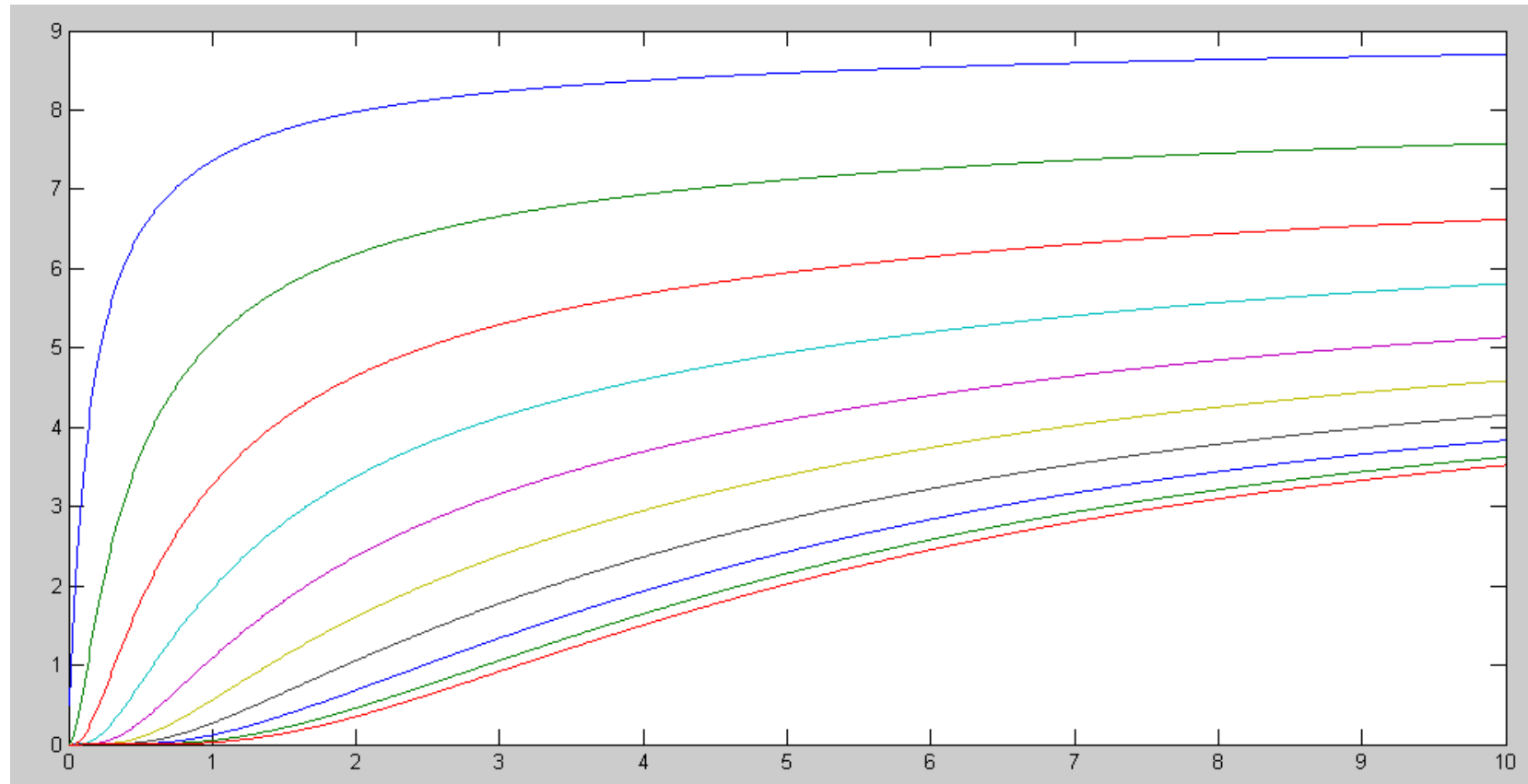Then, the final voltages vs. time are displayed



Note: This program

- Solves a 10-order coupled differential equation
- V1..V10 represent the voltages on each capacitor as they charge
- V1..V10 also are the temperatures along a metal bar as they heat up

Coupled 1st-order differential equations

- Describe RC circuits
 - Describe heat flow
 - Are called *the heat equation*
-

Eigenvalues and Eigenvectors

The dynamics for the 10-stage RC filter are:

$$\frac{dV_1}{dt} = \dot{V}_1 = 5V_0 - 10.1V_1 + 5V_2$$

$$\frac{dV_2}{dt} = \dot{V}_2 = 5V_1 - 10.1V_2 + 5V_3$$

$\vdots$

$$\frac{dV_9}{dt} = \dot{V}_9 = 5V_8 - 10.1V_9 + 5V_{10}$$

$$\frac{dV_{10}}{dt} = \dot{V}_{10} = 5V_9 - 5.1V_{10}$$

In matrix form, this can be written as

$$\dot{V} = AV + BV_0$$

or

$$\begin{bmatrix} \dot{V}_1 \\ \dot{V}_2 \\ \dot{V}_3 \\ \dot{V}_4 \\ \dot{V}_5 \\ \dot{V}_6 \\ \dot{V}_7 \\ \dot{V}_8 \\ \dot{V}_9 \\ \dot{V}_{10} \end{bmatrix} = \begin{bmatrix} -10.1 & 5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 5 & -10.1 & 5 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 5 & -10.1 & 5 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 5 & -10.1 & 5 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 5 & -10.1 & 5 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 5 & -10.1 & 5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 5 & -10.1 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 5 & -10.1 & 5 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 5 & -10.1 & 5 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 5 & -5.1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ V_6 \\ V_7 \\ V_8 \\ V_9 \\ V_{10} \end{bmatrix} + \begin{bmatrix} 5 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} V_0$$

A has 10 eigenvalues and 10 eigenvectors:

```
[M,V] = eig(A)
```

```
M = Eigenvectors:
```

-0.1286	-0.2459	0.3412	0.4063	0.4352	0.4255	0.3780	0.2969	-0.1894	0.0650
0.2459	0.4063	-0.4255	-0.2969	-0.0650	0.1894	0.3780	0.4352	-0.3412	0.1286
-0.3412	-0.4255	0.1894	-0.1894	-0.4255	-0.3412	-0.0000	0.3412	-0.4255	0.1894
0.4063	0.2969	0.1894	0.4352	0.1286	-0.3412	-0.3780	0.0650	-0.4255	0.2459
-0.4352	-0.0650	-0.4255	-0.1286	0.4063	0.1894	-0.3780	-0.2459	-0.3412	0.2969
0.4255	-0.1894	0.3412	-0.3412	-0.1894	0.4255	0.0000	-0.4255	-0.1894	0.3412
-0.3780	0.3780	-0.0000	0.3780	-0.3780	0.0000	0.3780	-0.3780	-0.0000	0.3780
0.2969	-0.4352	-0.3412	0.0650	0.2459	-0.4255	0.3780	-0.1286	0.1894	0.4063
-0.1894	0.3412	0.4255	-0.4255	0.3412	-0.1894	0.0000	0.1894	0.3412	0.4255
0.0650	-0.1286	-0.1894	0.2459	-0.2969	0.3412	-0.3780	0.4063	0.4255	0.4352

```
V = Eigenvalues:
```


-19.6557	-18.3624	-16.3349	-13.7534	-10.8473	-7.8748	-5.1000	-2.7695	-1.0903	-0.2117
----------	----------	----------	----------	----------	---------	---------	---------	---------	---------

The eigenvalues tell you *how* the mode behaves

The eigenvector tells you *what* behaves that way.


Slow Eigenvector

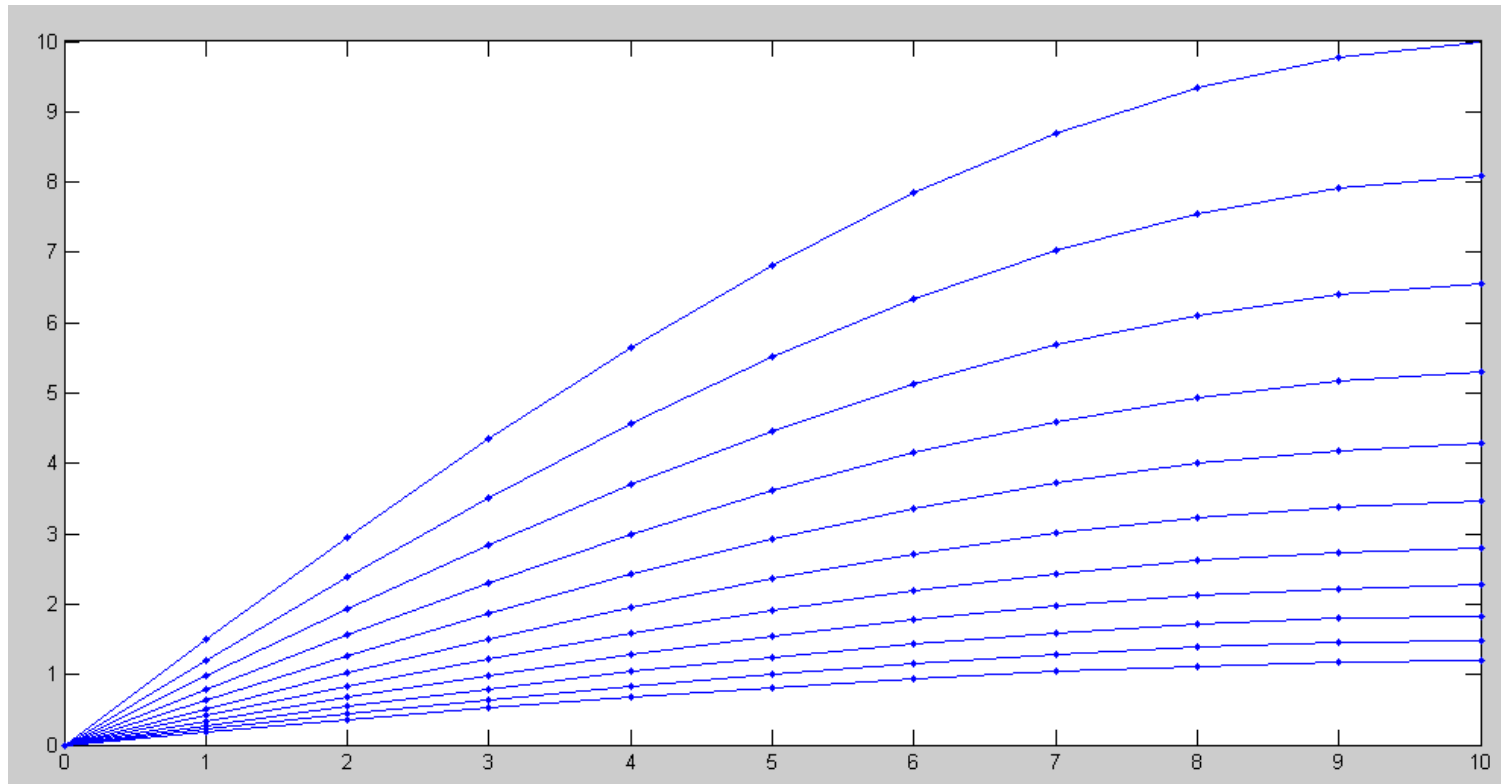- $V_0 = 0$
- $V(0) = \text{slow eigenvector}$
- $V(t) = V_0 e^{-0.2117t}$



Fast Eigenvector

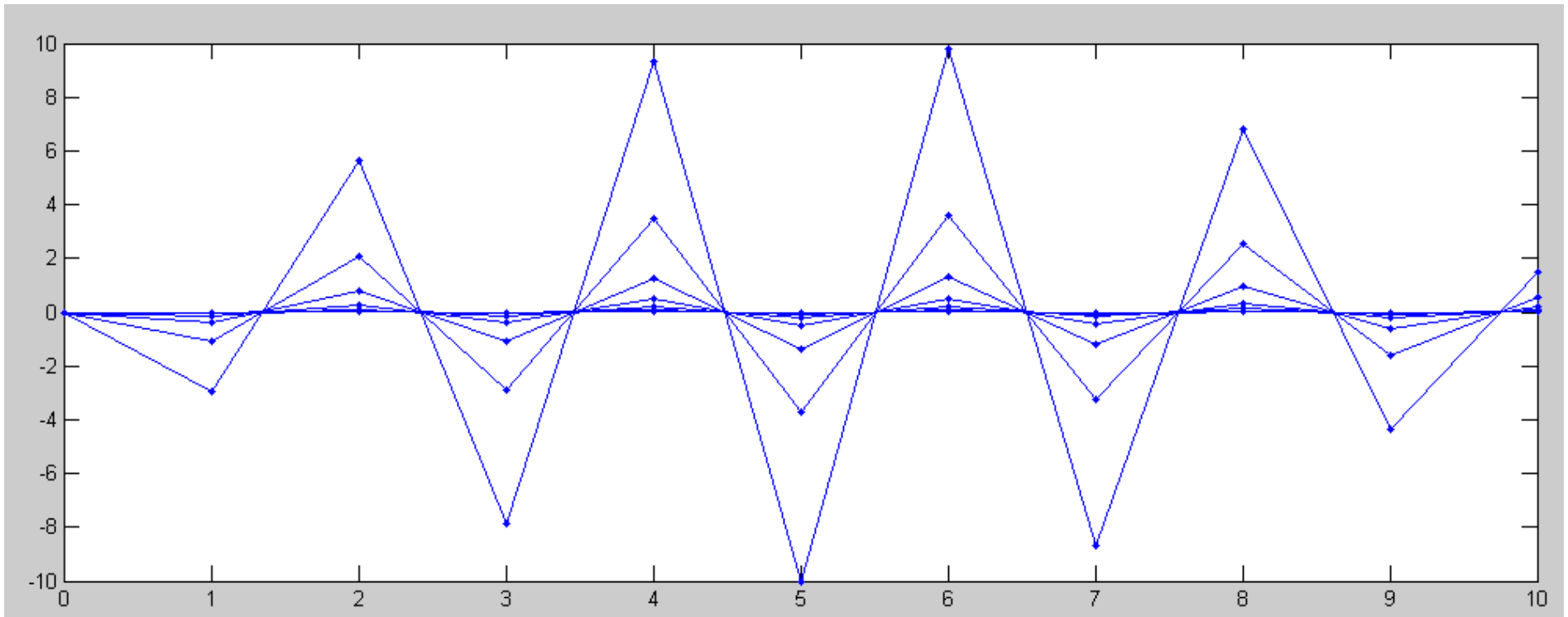- $V_0 = 0$
- $V(0) = \text{fast eigenvector}$
- $V(t) = V_0 e^{-19.65t}$



Voltages plotted every 0.05 seconds when the initial condition is the fast eigenvector

Random Initial Condition

- All eigenvectors will be excited
- The fast ones quickly decay,
- Leaving the slow eigenvector

