
Current Loops with Phasors

ECE 211 Circuits I

Lecture #26

Please visit [Bison Academy](#) for corresponding
lecture notes, homework sets, and solutions


Current Loops with Phasors

Current loops also works with phasors

	VI relationship	Phasor Notation
Voltage	$v(t) = a \cos(\omega t) + b \sin(\omega t)$	$V = a - jb$
Resistor	$v = iR$	$Z_R = R$
Inductor	$v = L \frac{di}{dt}$	$Z_L = j\omega L$
Capacitor	$i = C \frac{dv}{dt}$	$Z_C = \frac{1}{j\omega C}$

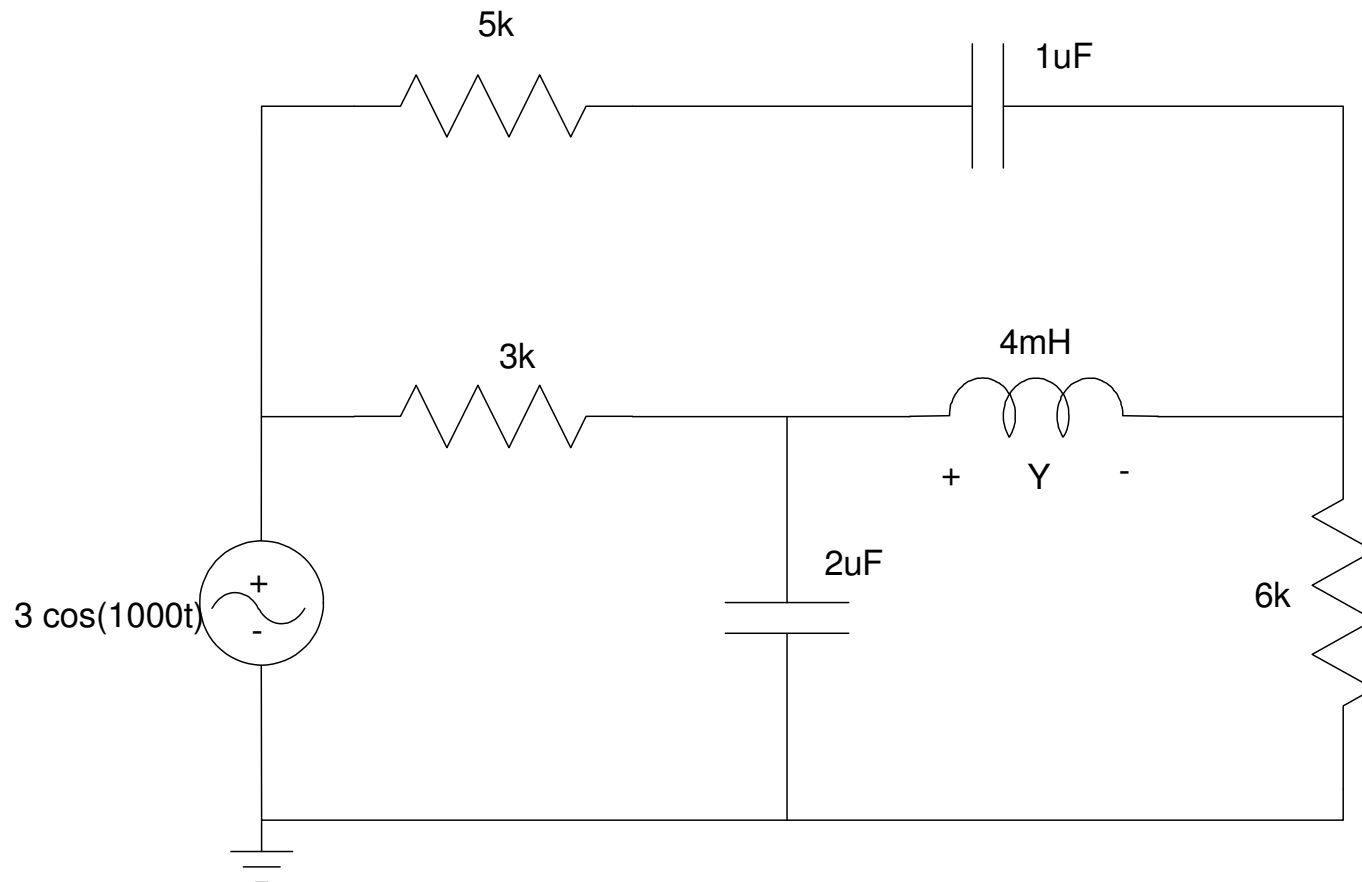
Example 1:

Determine the currents in the following circuit



Step 1:

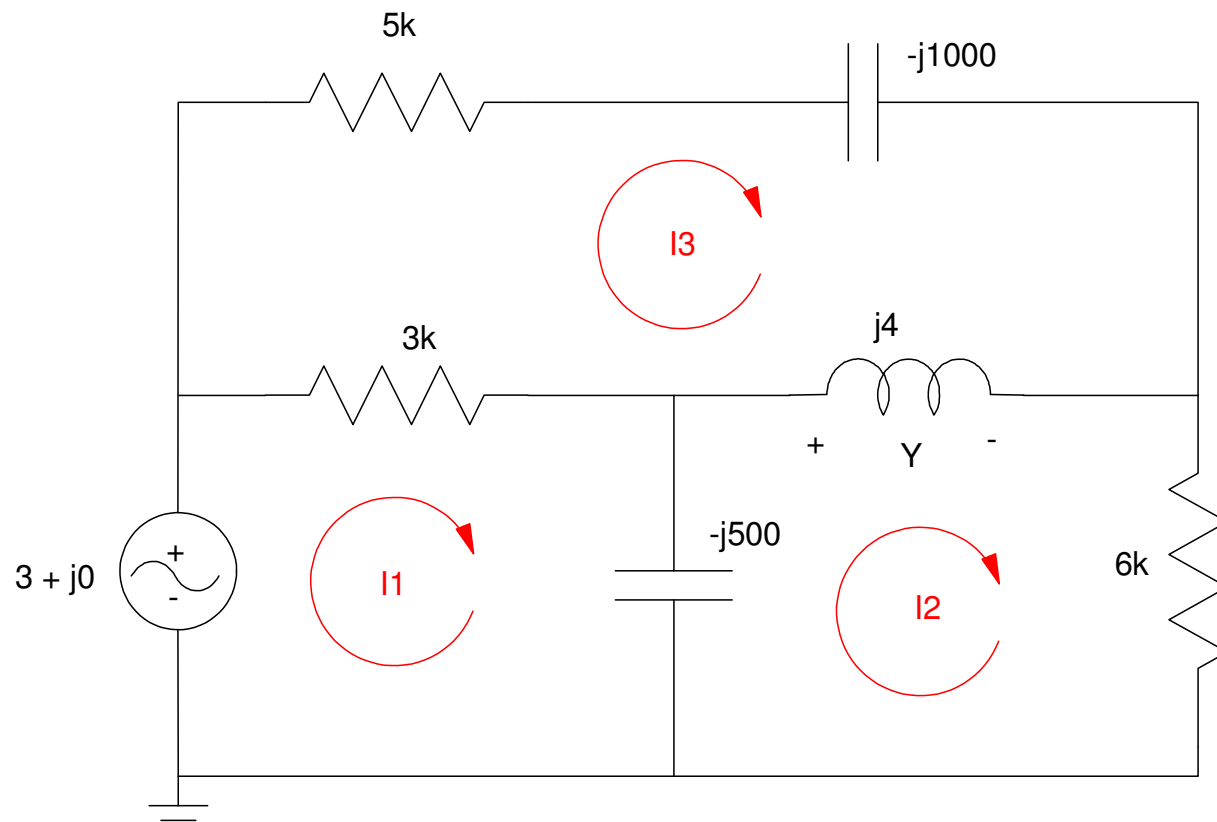- Define the currents
- Convert to Phasors




Step 2: Write the current loop equations

3 equations for 3 unknowns

$$-3 + 3000(I_1 - I_3) - j500(I_1 - I_2) = 0$$

$$-j500(I_2 - I_1) + j4(I_2 - I_3) + 6000I_2 = 0$$
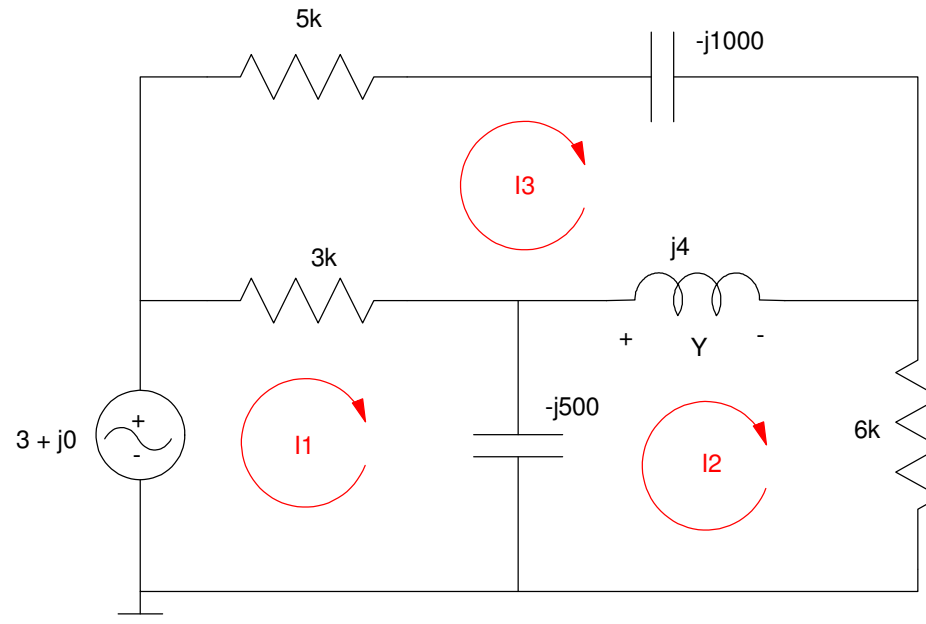
$$-j1000(I_3) + 5000(I_3) + j4(I_3 - I_2) + 3000(I_3 - I_1) = 0$$



Step 3: Solve

Group terms:

$$(3000 - j500)I_1 + (j500)I_2 + (-3000)I_3 = 3$$

$$(j500)I_1 + (6000 - j496)I_2 + (-j4)I_3 = 0$$

$$(-3000)I_1 + (-j4)I_2 + (8000 - j996)I_3 = 0$$

$$A = \begin{bmatrix} 3000 - j*500 & j*500 & -3000 \\ j*500 & 6000 - j*496 & -j*4 \\ -3000 & -j*4 & 8000 - j*996 \end{bmatrix}$$

$$\begin{array}{rrr} 3000. & - & 500.i & 500.i & & - & 3000. \\ 500.i & & & 6000. & - & 496.i & - & 4.i \\ - & 3000. & & - & 4.i & & 8000. & - & 996.i \end{array}$$

$$I = \text{inv}(A) * [3; 0; 0]$$

$$I1: \quad 0.0014008 + 0.0004598i$$

$$I2: \quad 0.0000475 - 0.0001125i$$

$$I3: \quad 0.0004962 + 0.0002342i$$

Step 4: Convert back to time

In phasor form:

$$I_1: \quad 0.0014008 + 0.0004598i$$

$$I_2: \quad 0.0000475 - 0.0001125i$$

$$I_3: \quad 0.0004962 + 0.0002342i$$

In the time-domain

$$i_1(t) = 1.4008 \cos(1000t) - 0.4598 \sin(1000t) \text{ mA}$$


$$i_2(t) = 0.0475 \cos(1000t) + 0.1125 \sin(1000t) \text{ mA}$$

$$i_3(t) = 0.4962 \cos(1000t) - 0.2342 \sin(1000t) \text{ mA}$$

Current Loops with Dependent Sources

Not surprisingly, it also works with dependent sources

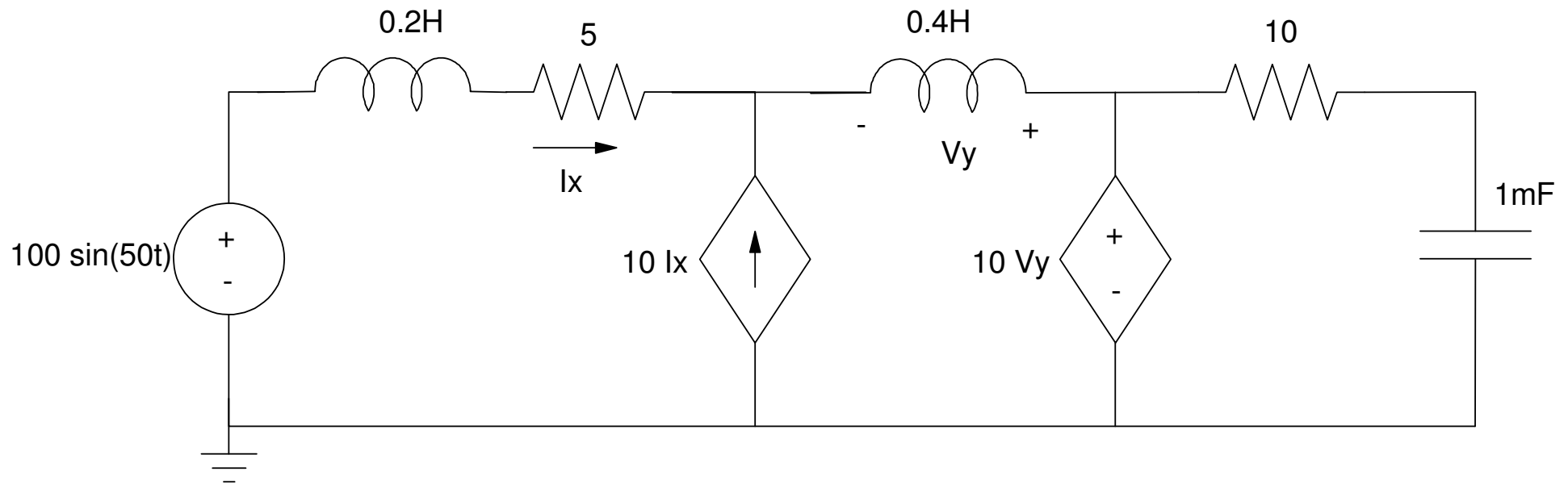Example: Determine the currents in the following circuit



Step 1:


Define the loop currents

Convert to the phasor domain: (shown in blue)

$$a \cos(\omega t) + b \sin(\omega t) \rightarrow a - jb$$

$$L \rightarrow j\omega L$$

$$C \rightarrow \frac{1}{j\omega C}$$

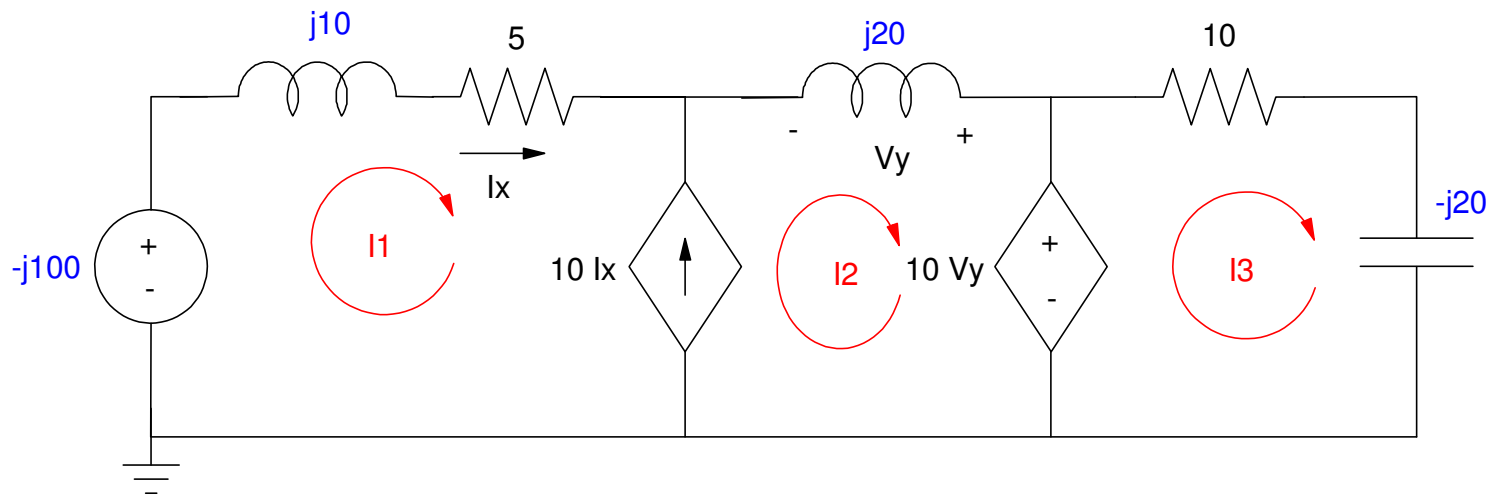

Step 2: Write N equations for N unknowns


$$I_x = I_1$$

$$V_y = j20 \cdot I_2$$

$$10I_x = I_1 - I_2$$

$$-10V_y + 10I_3 - j20I_3 = 0$$
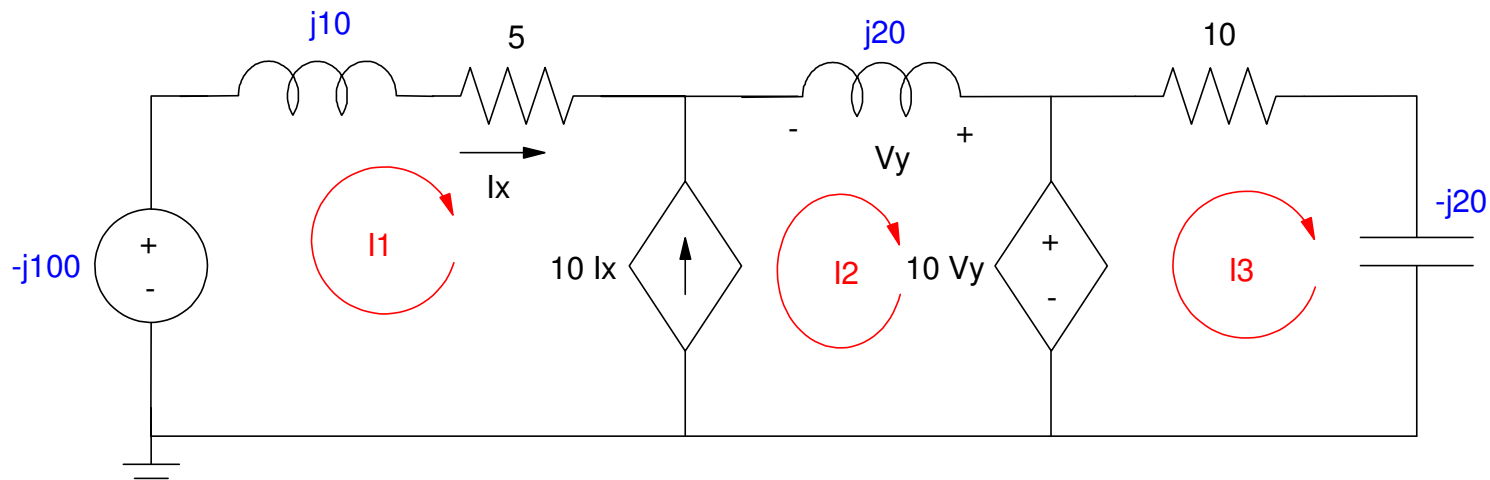
$$-(0 - j100) + (5 + j10)I_1 + j20 \cdot I_2 + (10 - j20)I_3 = 0 \quad \text{super loop}$$



Step 3: Solve

Group terms

$$I_x - I_1 = 0$$

$$V_y - j20 \cdot I_2 = 0$$

$$10I_x - I_1 + I_2 = 0$$

$$-10V_y + 10I_3 - j20I_3 = 0$$

$$(5 + j10)I_1 + j20 \cdot I_2 + (10 - j20)I_3 = -j100$$

Place in matrix form

$$\begin{bmatrix} -1 & 0 & 0 & 1 & 0 \\ 0 & -j20 & 0 & 0 & 1 \\ -1 & 1 & 0 & 10 & 0 \\ 0 & 0 & 10 - j20 & 0 & -10 \\ (5 + j10) & (j20) & (10 - j20) & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_x \\ V_y \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -j100 \end{bmatrix}$$

Solve in Matlab

```
A = [-1,0,0,1,0 ; 0,-j*20,0,0,1];  
A = [A; -1,1,0,10,0 ; 0,0,10-j*20,0,-10];  
A = [A ; 5+j*10,j*20,10-j*20,0,0]  
B = [0;0;0;0;-j*100]  
I = inv(A)*B
```

```
I1      0.0507611   -0.0001288i  
I2     -0.4568498   +0.0011595i  
I3      3.6501607   -1.8366755i  
Ix      0.0507611   -0.0001288i  
Vy     -0.0231903   -9.136997i
```

Step 4: Convert back to the time domain

Phasor domain

I1	0.0507611	-0.0001288i
I2	-0.4568498	+0.0011595i
I3	3.6501607	-1.8366755i
I_x	0.0507611	-0.0001288i
V_y	-0.0231903	-9.136997i

Time Domain

$$i_1(t) = 0.0507 \cos(50t) + 0.0001288 \sin(50t)$$

$$i_2(t) = -0.4568 \cos(50t) - 0.0011 \sin(50t)$$

$$i_3(t) = -0.0232 \cos(50t) + 1.8367 \sin(50t)$$
