

---

# **Superposition with Phasors (take 2)**

## **ECE 211 Circuits I**

### **Lecture #30**

Please visit [Bison Academy](#) for corresponding  
lecture notes, homework sets, and solutions

---

---

## Superposition (take 2)

Superposition allows you to analyze circuits with multiple sinusoidal inputs.  
If this is the case

- Treat the problem as  $N$  separate problems, each with a single sinusoidal input.
  - Solve each of the  $N$  problems separately using phasor analysis
  - Add up all of the answers to get the total output.
-

---


## Problem:

Suppose your circuit has an input that *isn't* a sum of sinusoids. A typical engineering solution is to change the problem so that the inputs *are* sinusoids. The trick is you want to change the problem so that

- It is solvable (a big plus), and
- It keeps the flavor of the original problem.
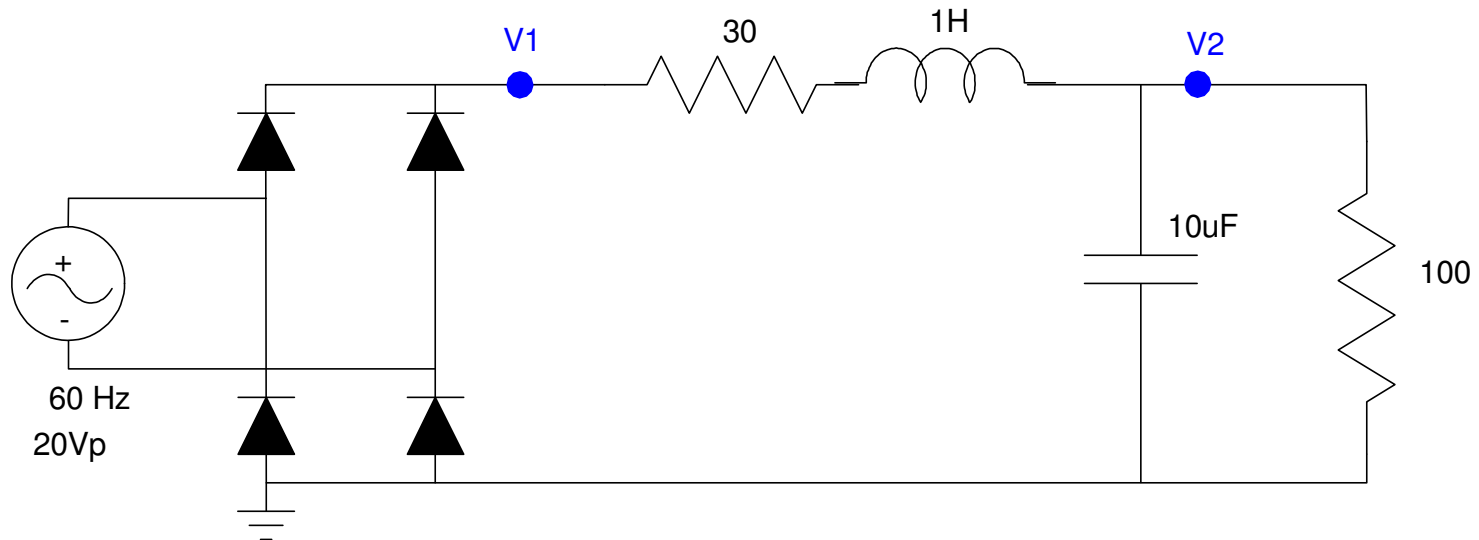
## Example 1: AC to DC Converter

The following circuit is an AC to DC converter that we'll cover in ECE 320 Electronics I. Determine the voltage at V2:




AC to DC Converter covered in ECE 320 Electronics I

---

Problem: V1 isn't a sine wave


$$V_1 \approx |19.3 \sin(754t)| - 0.7$$

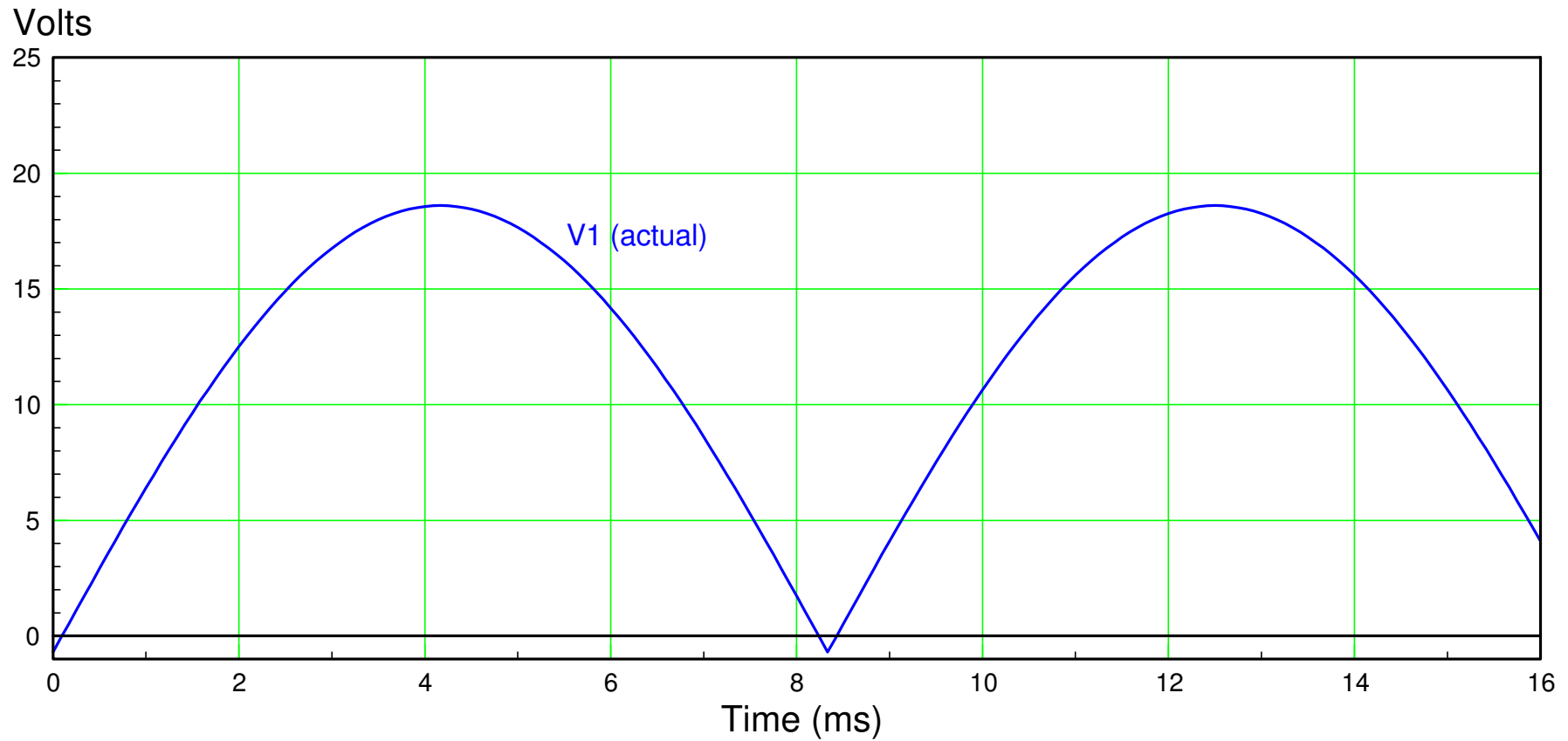

---

Change the problem:

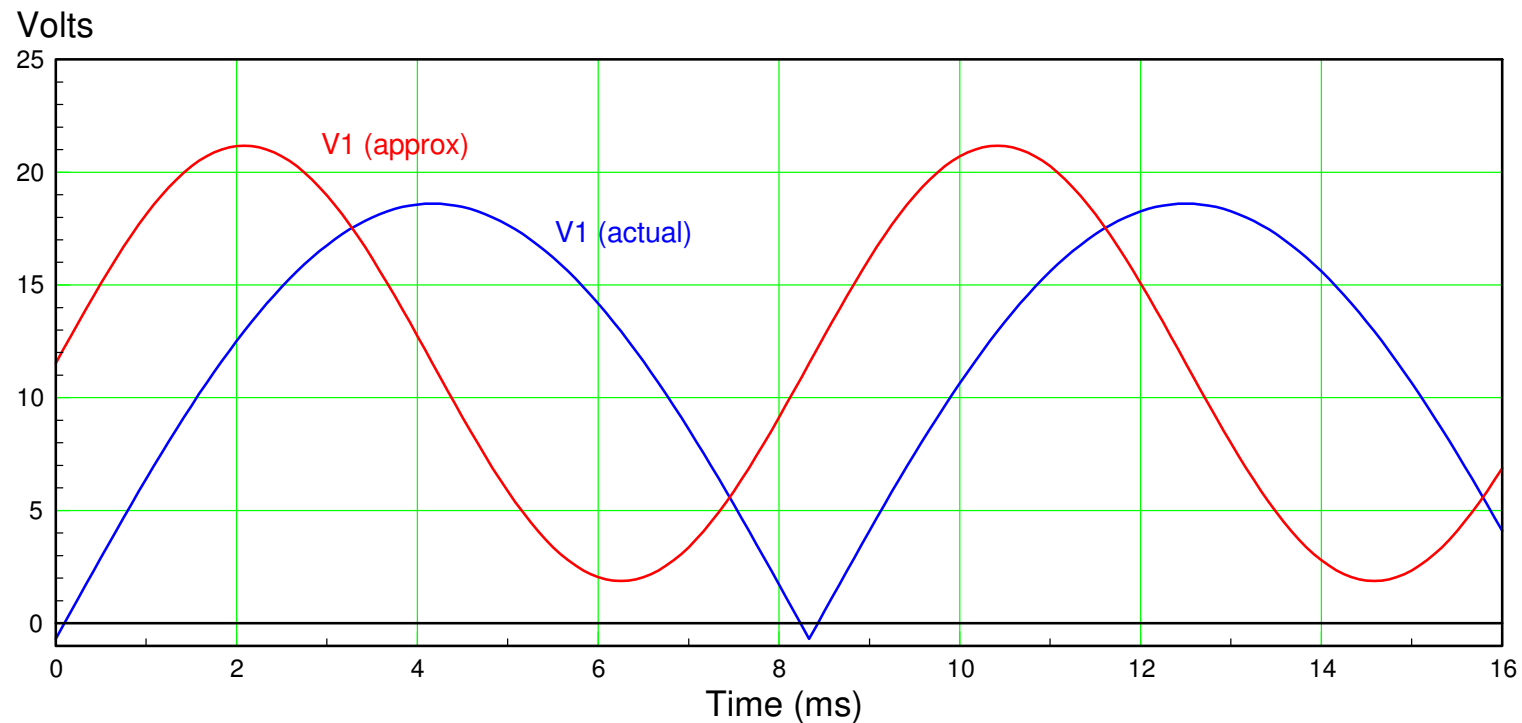- The DC level of V1 is 11.31V
- The frequency of V1 is 120Hz (754 rad/sec)
- $V1 = 19.3V_{pp}$



---

## Solve using Superposition

$$V_1(t) = 11.31 + 9.65 \cos(754t)$$

DC Analysis: The capacitor is open and the inductor is a short. By voltage division

$$X = 11.31 + j0$$

$$\omega = 0$$

$$V_2 = \left( \frac{100}{100+30} \right) 11.31V$$

$$V_2 = 8.70V$$


---

## AC Analysis:

- Convert to Phasors & Solve


$$V_2 = \left( \frac{(63.75 - j48.07)}{(63.75 - j48.07) + (30 + j754)} \right) \cdot (19.3V_{pp})$$

$$V_2 = 2.164V_{pp}$$

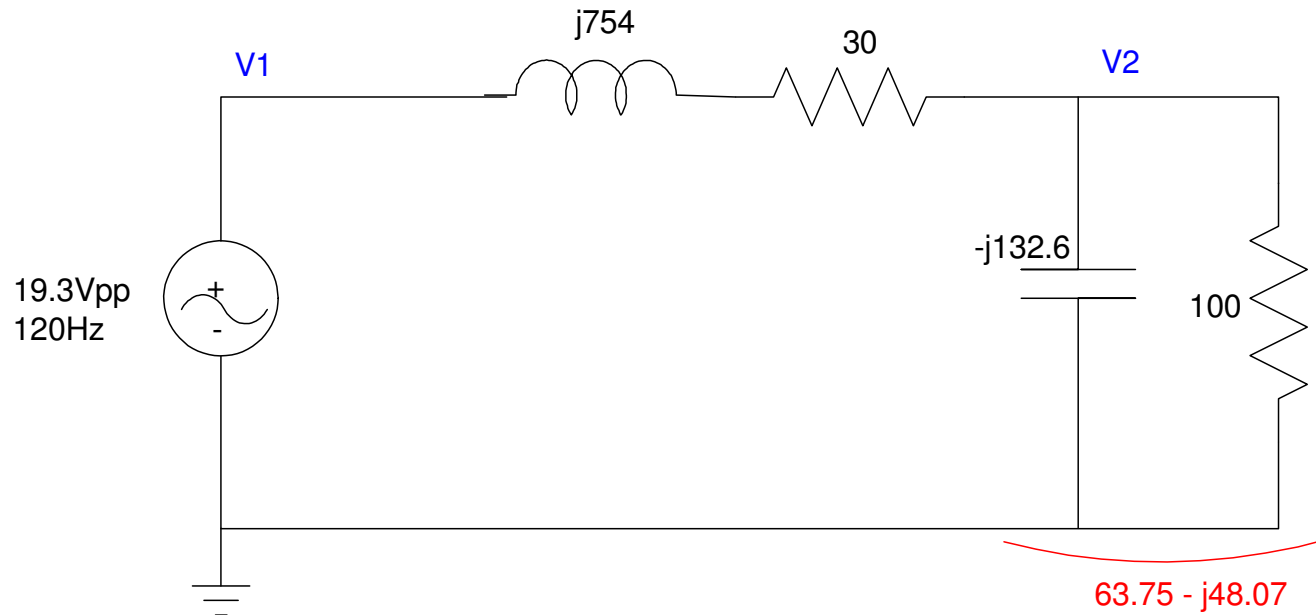



# Simulation Results:

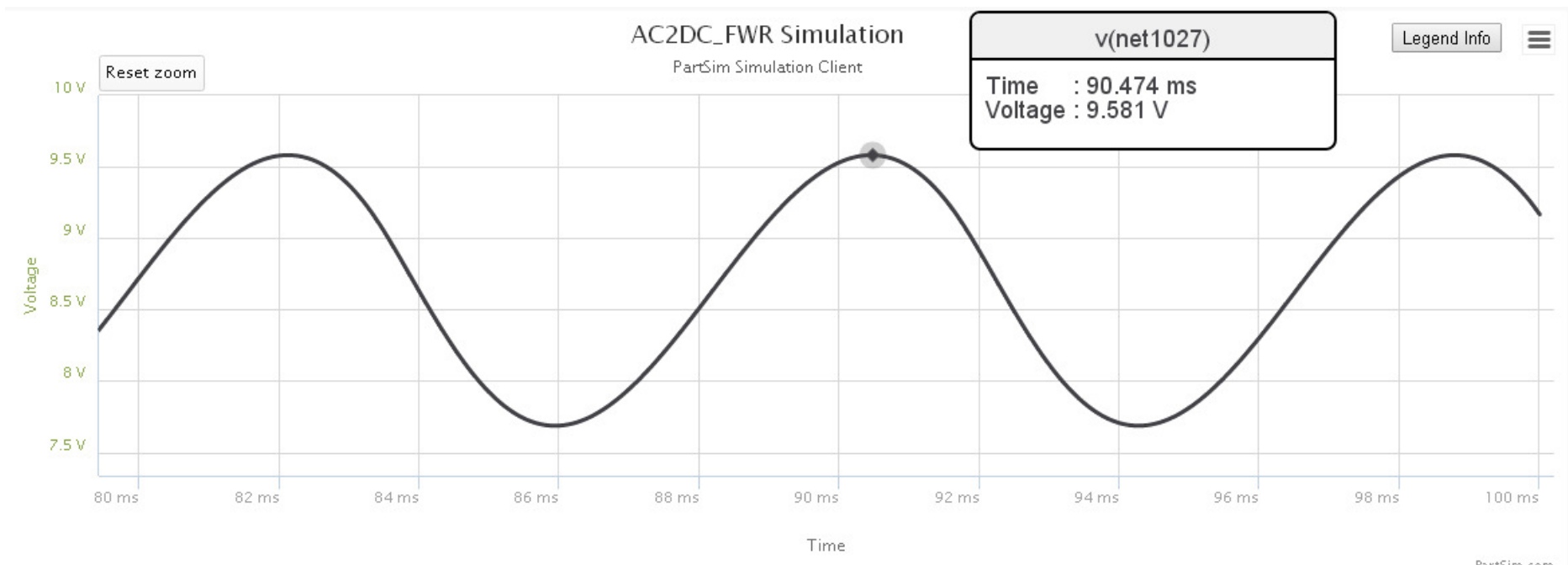

	Calculated V2	PartSim V2
DC Value	8.70 V	8.634 V
AC Value	2.164 Vpp	1.895 Vpp

---

## Note:

- The answers are fairly close. We kept the flavor of the problem
- The answers are a little off. This isn't surprising since the input isn't a pure sine wave like assumed.

Even though the input is *very* different from a sine wave, the output is almost a pure sine wave with a DC offset. This means that treating this as a superposition problem with two terms


- A DC term, and
- A 120Hz term

was a pretty good assumption.

---

## Example 2: Buck Converter


- Convert 12VDC from a car battery to 5VDC for your cell phone
- Convert 20VDC to 15.8VDC

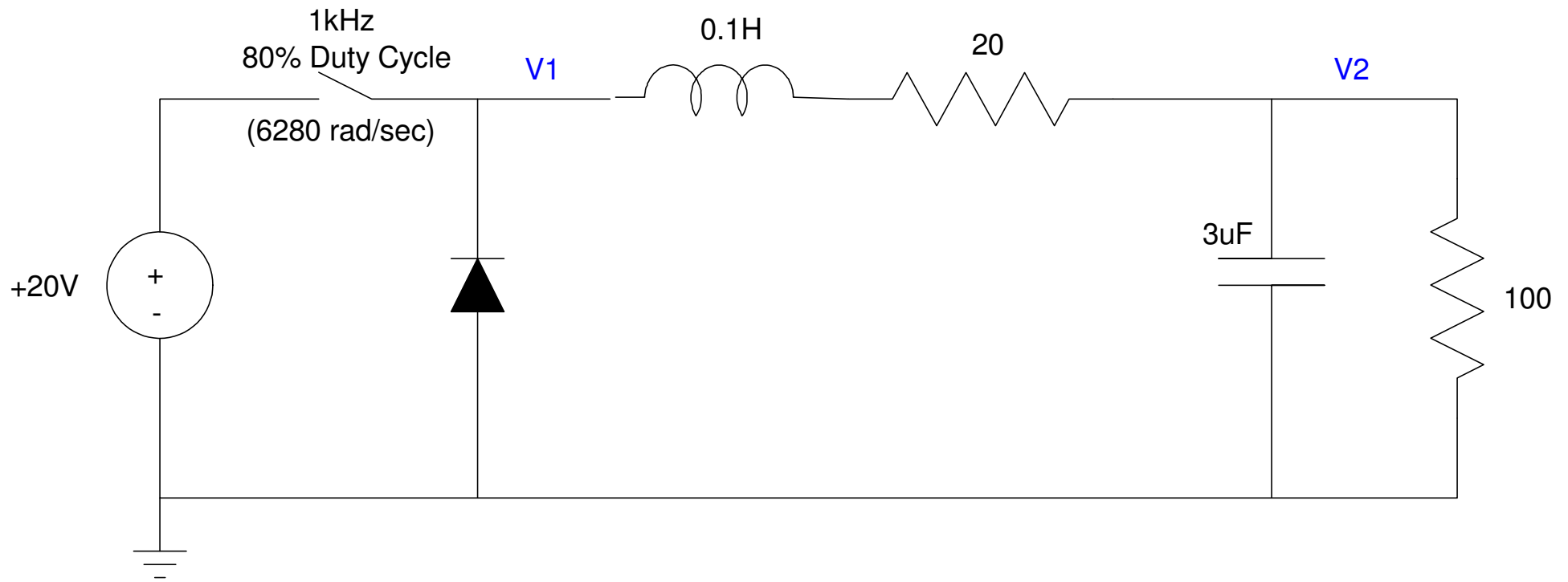

Example 2: A Buck Converter (covered in ECE 320 Electronics I)

---

Problem: V1 isn't a sine wave

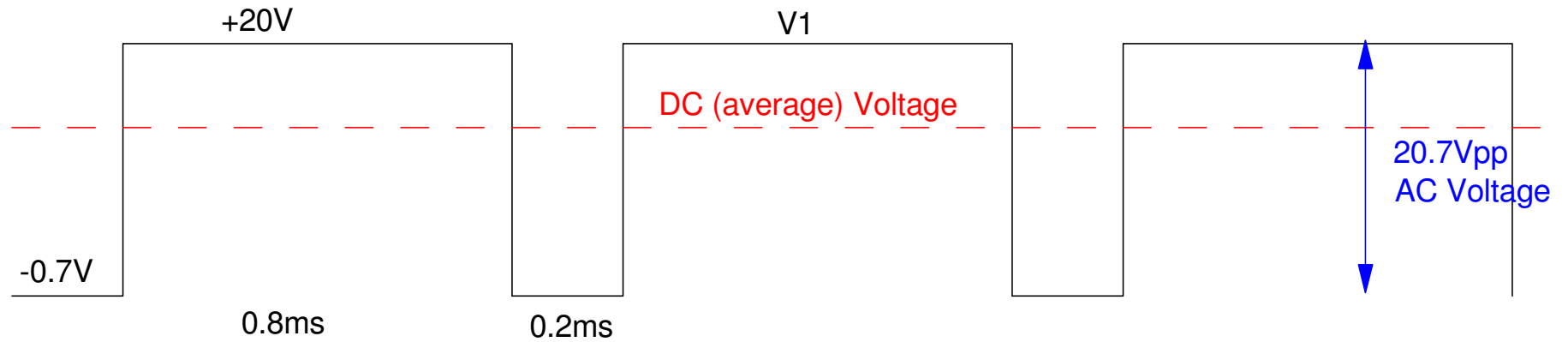

Voltage at V1 with a Buck Converter

---

---

Solution: Change the problem so that  $V_1$  is a sine wave

- Keep the DC value (15.86V)
- Keep the frequency (1kHz)
- Keep  $V_{pp}$  unchanged (20.7V<sub>pp</sub>)

$$V_1 \approx 15.86 + 10.35 \cos(6280t)$$

---

## DC Analysis:

$$V_1 = 15.86$$

$$V_2 = \left( \frac{100}{100+20} \right) V_1 = 13.21V$$

---


## AC Analysis (1kHz)

$$V_1 = 20.7V_{pp}$$

$$V_2 = \left( \frac{(21.98 - j41.41)}{(21.98 - j41.41) + (20 + j628)} \right) (20.7V_{pp})$$

$$V_2 = 1.65V_{pp} \quad \text{only care about magnitude}$$


# Simulation Results

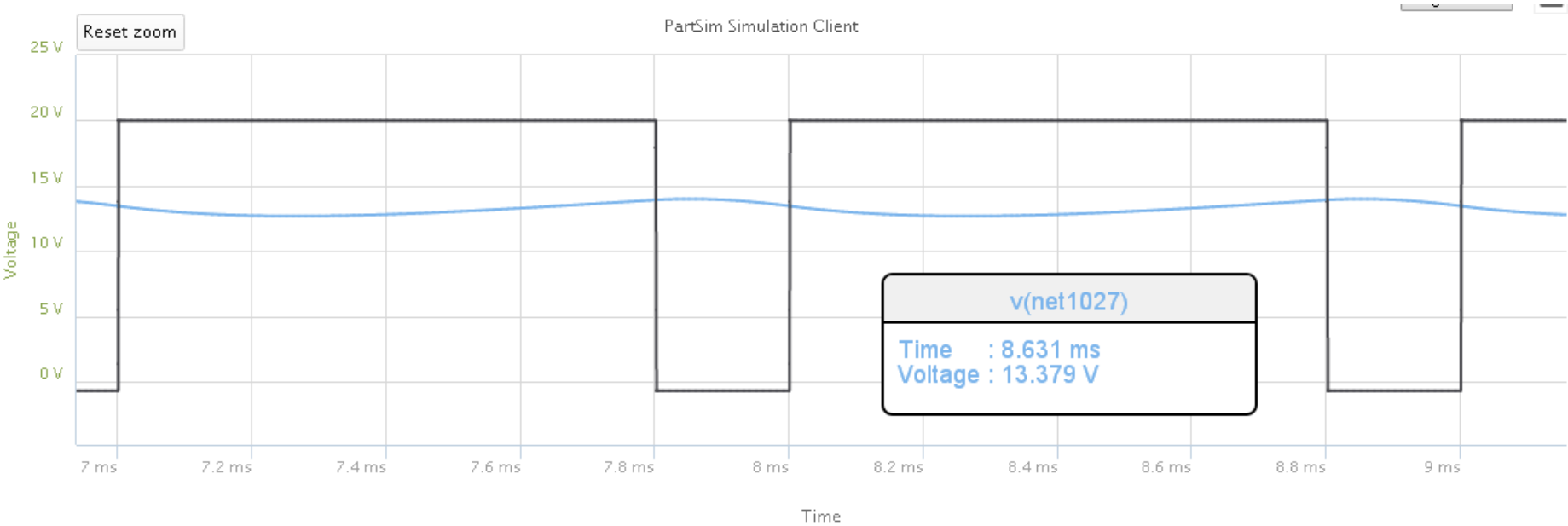

V1 (black) and V2 (blue)



# Simulation Results for V2 (expanded)

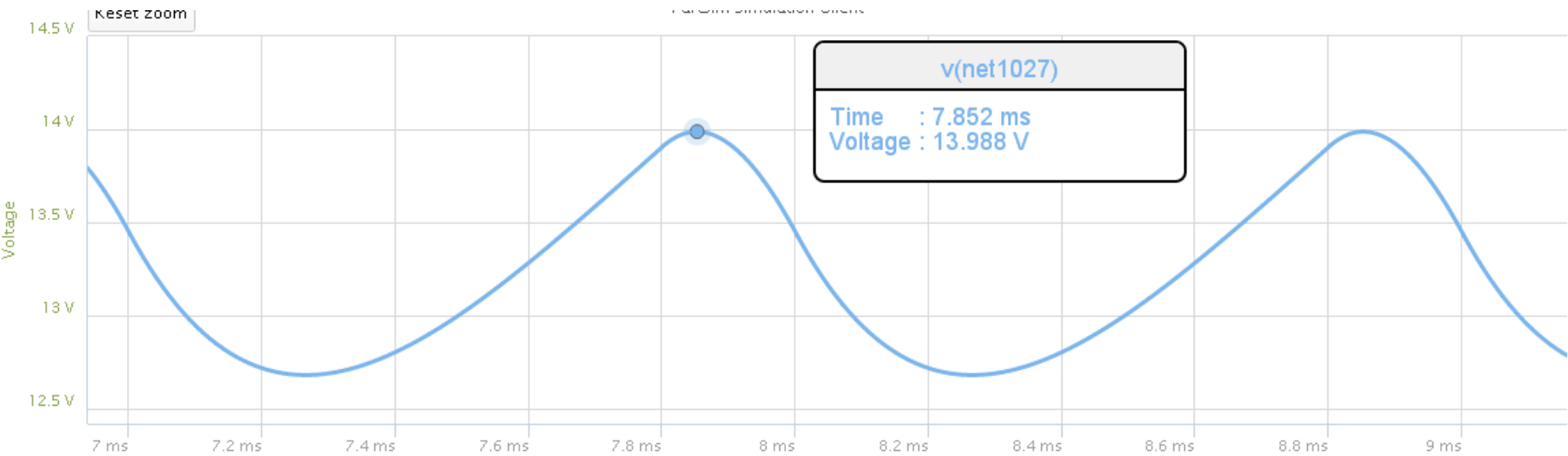

	Calculated V2	CircuitLab V2
DC Value	13.21 V	13.32 V
AC Value	1.65 Vpp	1.285 Vpp

---

## Summary

Our results are close. By changing the problem to include

- A DC offset, and
- A sine wave

We were able to

- Solve for  $V_2$
  - Without significantly changing the results (keeping the flavor of the problem)
-