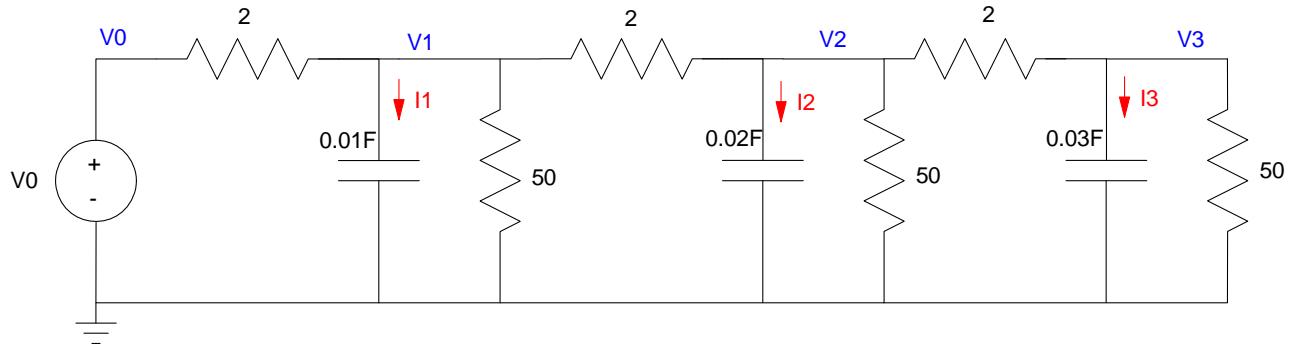


ECE 311 - Homework #19

Transfer Functions and State Variable Solution


Problem 1: Find the transfer function from V_o to V_3 using state-space methods.

Problem 2: Find the transfer function from V_0 to V_2



Problem 1 & 2

Problem 3: Find the transfer function from V_{in} to y using state-space methods

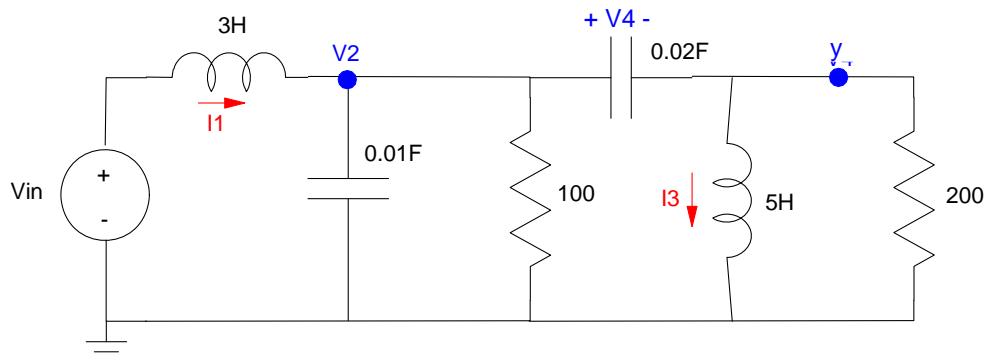

Problem 3