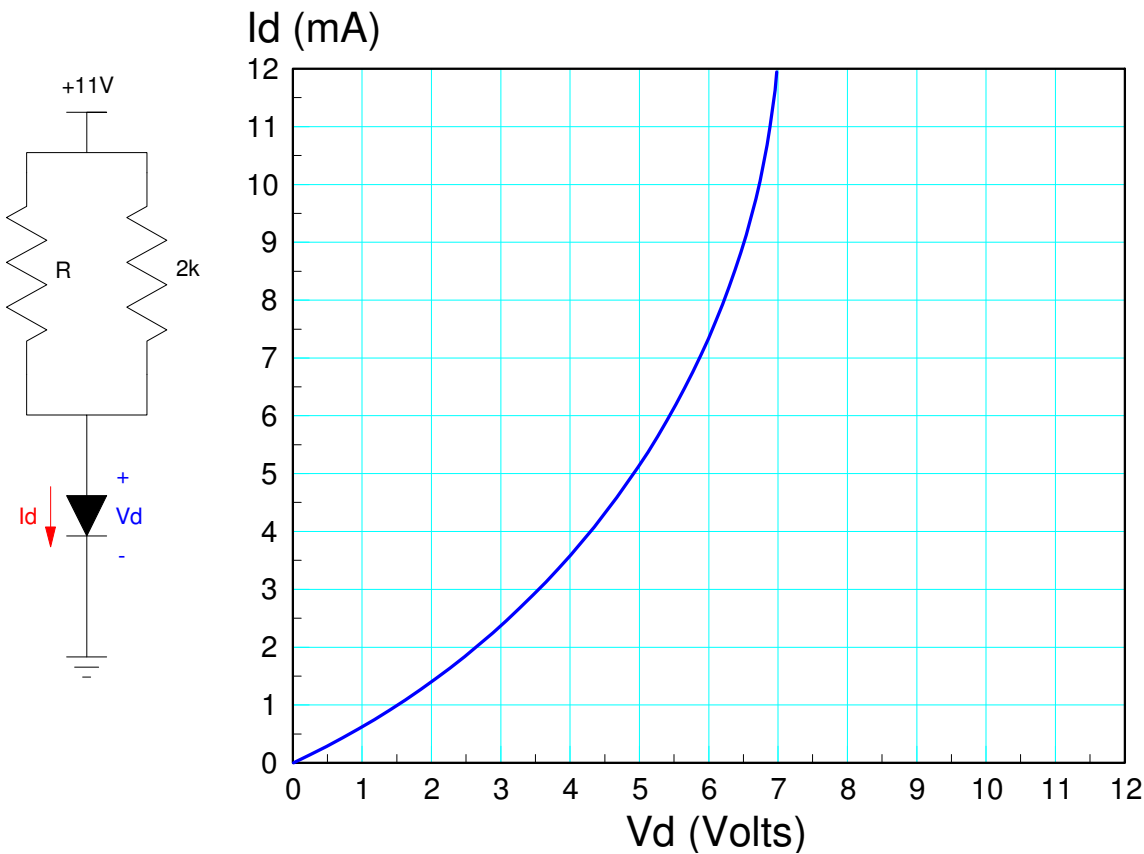


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes

1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_d and V_d . Assume $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.

R 1000 + 100*mo + day	Load Line x-intercept (volts)	Load Line y-intercept (mA)	Vd Volts	Id mA




2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.052 \ln(10^8 \cdot I_d + 1) \quad I_d = 10^{-8} \cdot \left(\exp\left(\frac{V_d}{0.052}\right) - 1 \right)$$

Write N equations to solve for N unknowns: $\{V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}\}$.

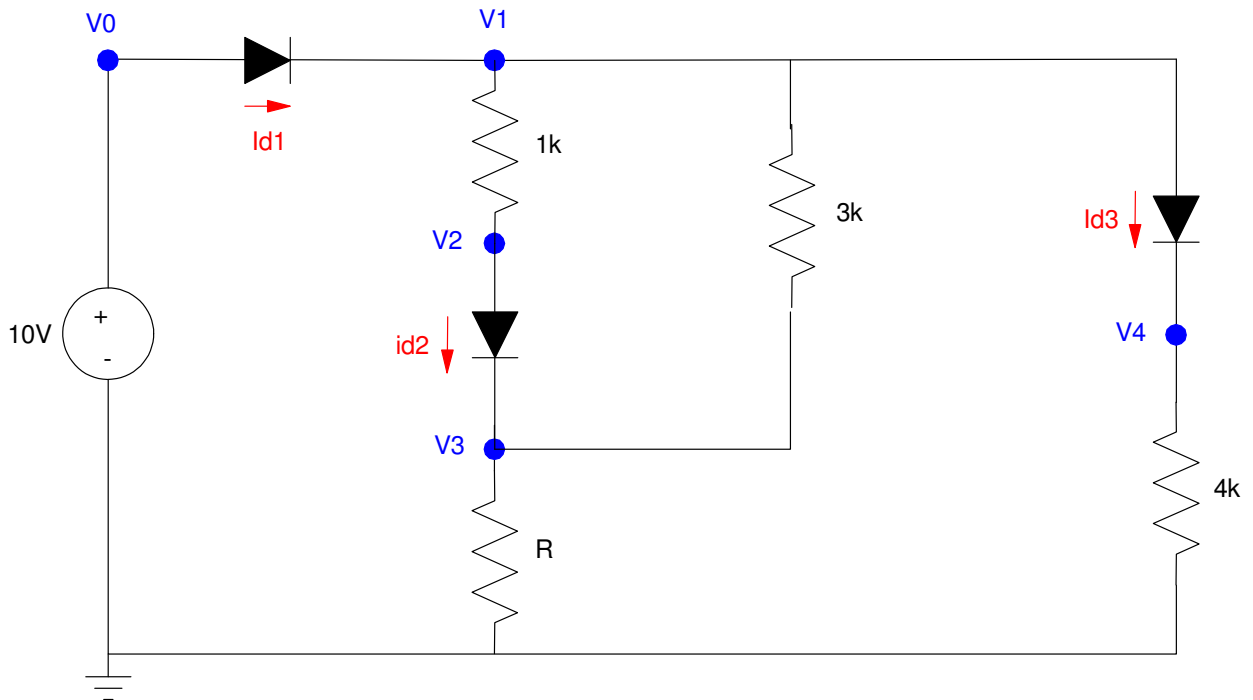
- Note: you do not need to solve.
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.



3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:


- $V_d = 0.7V$ $I_d > 0$
- $I_d = 0$ $V_d < 0.7V$
- $R = 1000 + 100 * (\text{your birth month}) + (\text{birth date})$. For example, May 14th gives 1514 Ohms.

R	I_{d1}	V1	V2	V3	V4

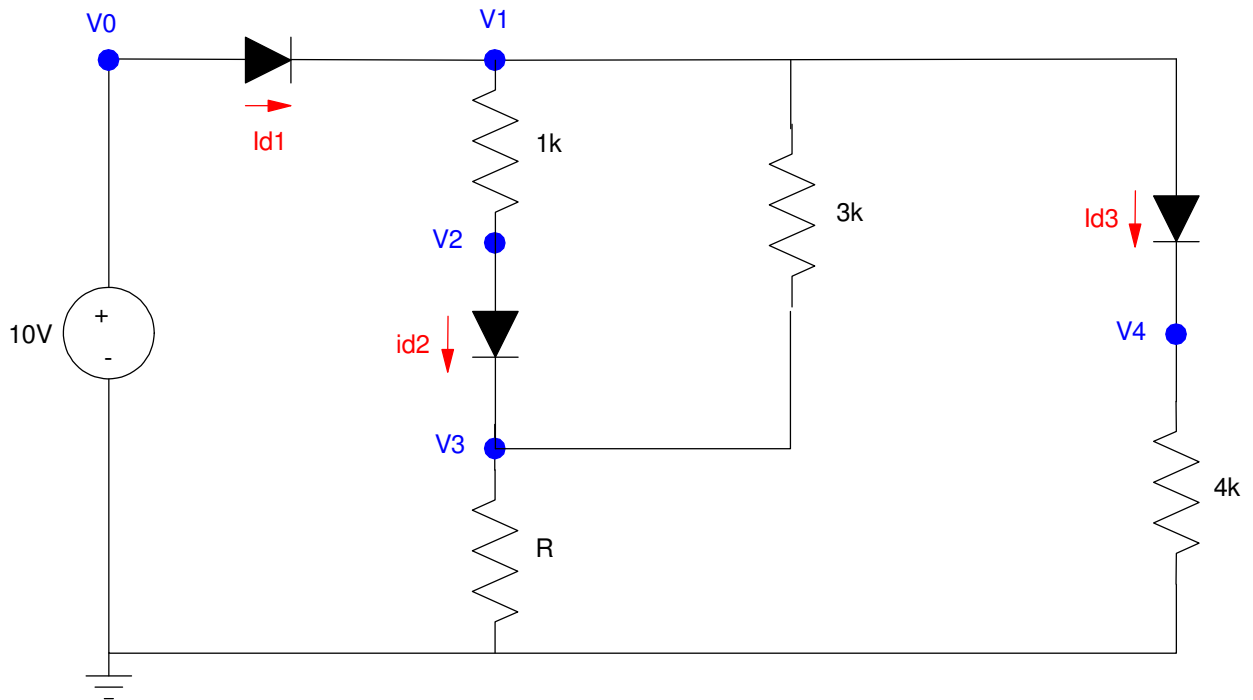

4) AC to DC: Analysis: Determine V1 and V2 (both DC and AC) for the following AC to DC converter



R	V1		V2	
	DC	AC	DC	AC

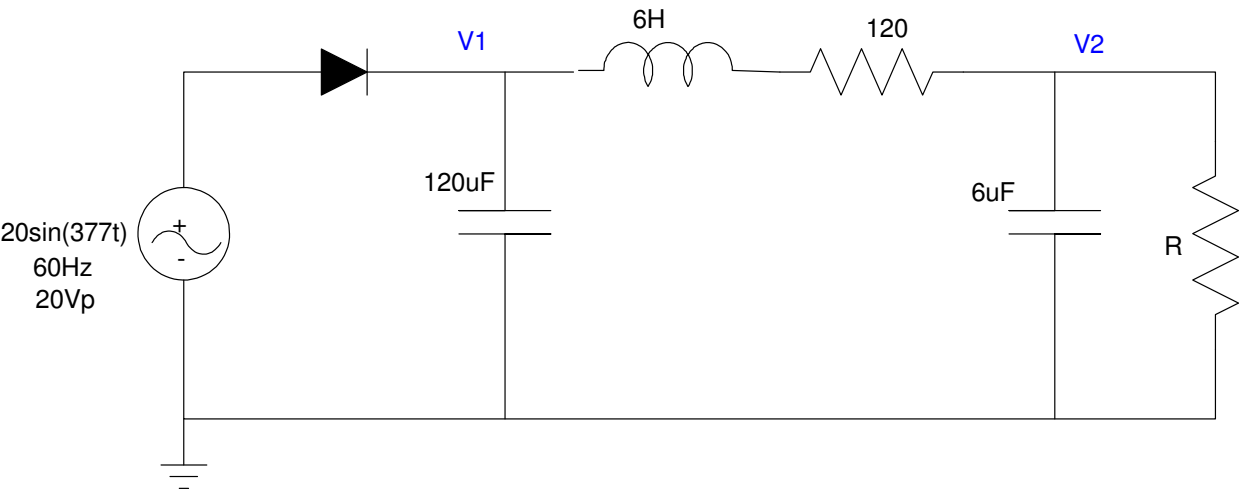

5) Clipper Circuit: Determine the resistors and zener voltages to implement the following function: $Y = f(X)$. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth date})$

R 1000 + 100*mo day	R0	R1	Vz1	R2	Vz2

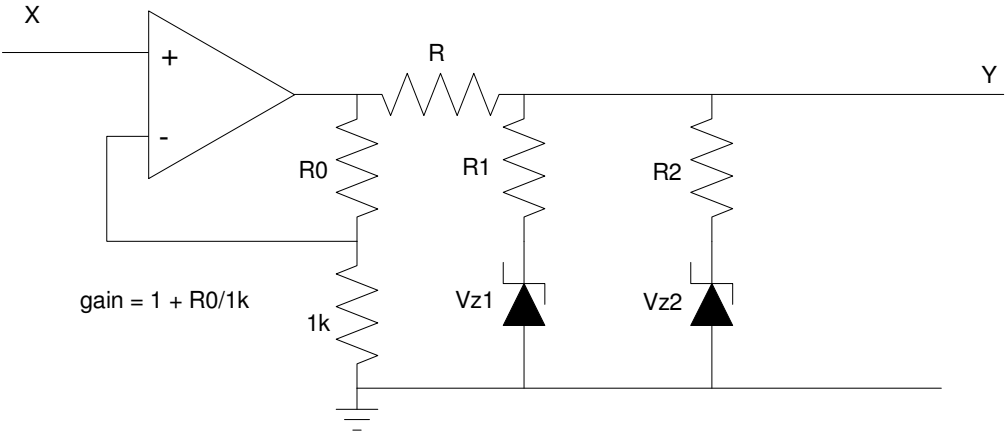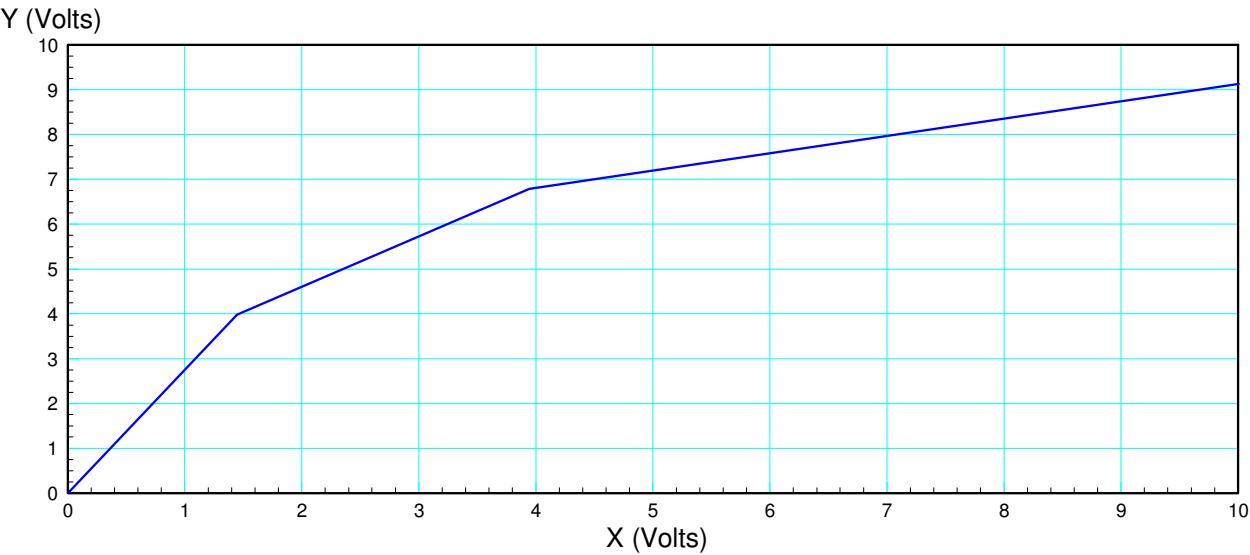


ECE 320 - Final (pt 2) - Name _____

Transistors and Mosfets

6) Determine the current gain, β . Also draw the load line and determine the operating point when $V_{in} = 5V$

R 1000 + 100*Mo + Day	Current Gain $h_{fe} = \beta$	Load Line x-intercept (Volts)	Load Line y-intercept (mA)	Vce $V_{in} = 5V$	Ic $V_{in} = 5V$

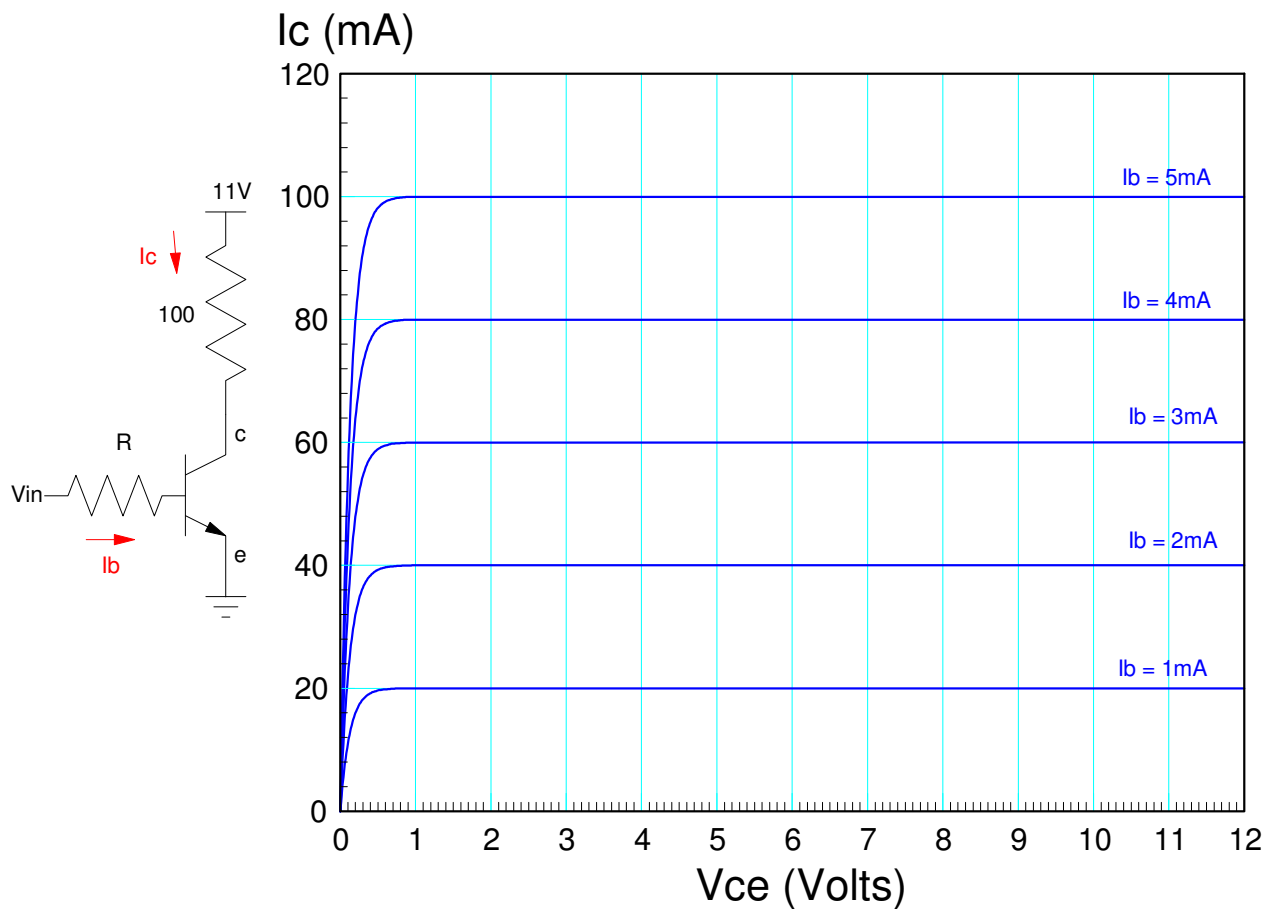


7) Design a Schmitt Trigger & transistor switch so that

- Turns on the LED at 200mA when $R_T > 1500$ Ohms
- Turns off the LED when $R_T < 1200$ Ohms

Assume

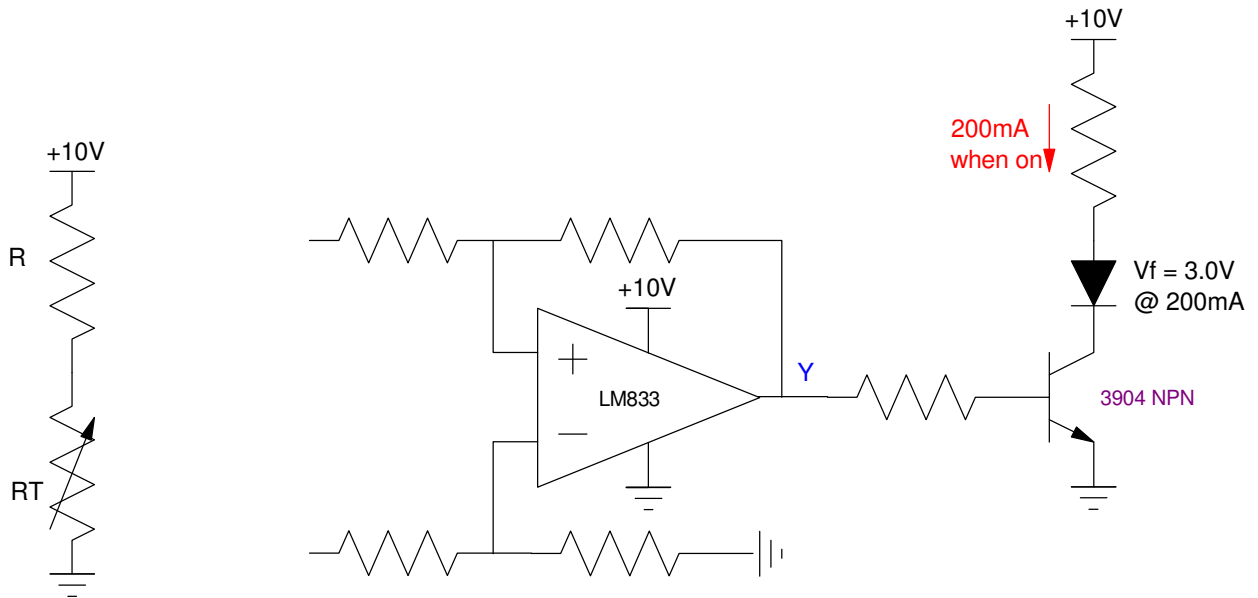- $R = 1000 + 100 * (\text{your birth month}) + (\text{your birth date})$
- $V_{ce(sat)} = 0.2V$
- Current gain (β) = 100




- $R = 1000 + 100 \cdot (\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 100$)

9) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line (x and y intercept), and
- Determine $\{V_{ds}, I_{ds}\}$ when $V_g = 7V$

R 1000 + 100*mo + day	kn transconductance gain	Load Line x=intercept	Load Line y intercept	Vds Vg = 7V	Ids Vg = 7V	Operating Region off / active / ohmic

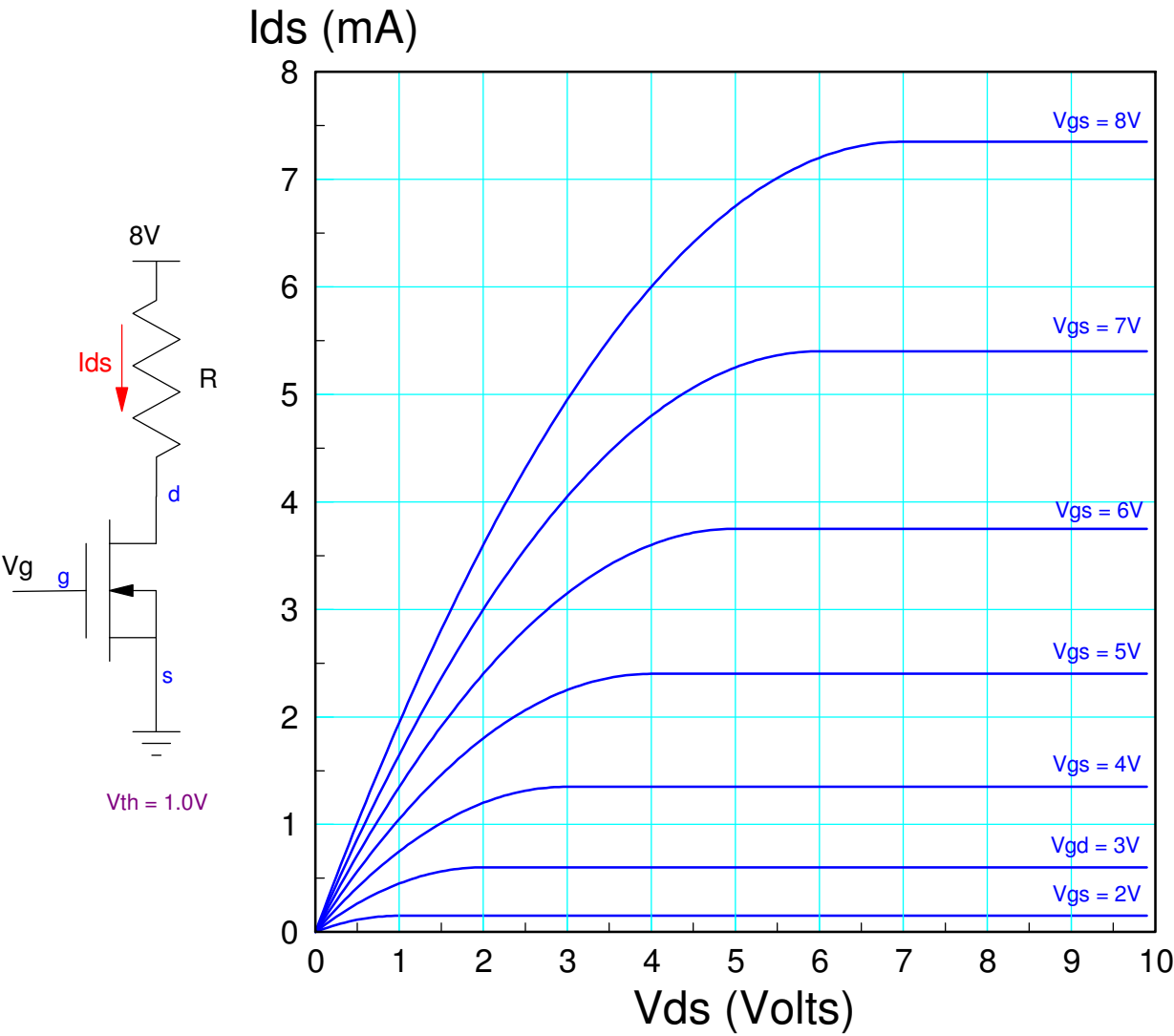

10) CMOS Logic

a) Design a CMOS logic gate to implement $Y=f(A,B,C,D)$

		CD			
		00	01	11	10
AB	00	1	1	0	0
	01	1	x	x	0
	11	0	x	x	1
	10	0	0	1	1