

ECE 320 - Quiz #7 - Name _____

Fourier Transforms, DC to AC, SCR


Fourier Transforms

1) Assume the Fourier transform for $X(t)$ is

$$x(t) = 10 + 11 \sin(t) + 12 \cos(2t)$$

Find $y(t)$. Let R be $1000 + 100 \cdot (\text{your birth month}) + (\text{your birth day})$. March 14th would give $R = 1514$ Ohms.

R 1000 + 100*Month + Day	$y(t)$
1514	$10 + 11 \sin(t) + 12 \cos(2t)$

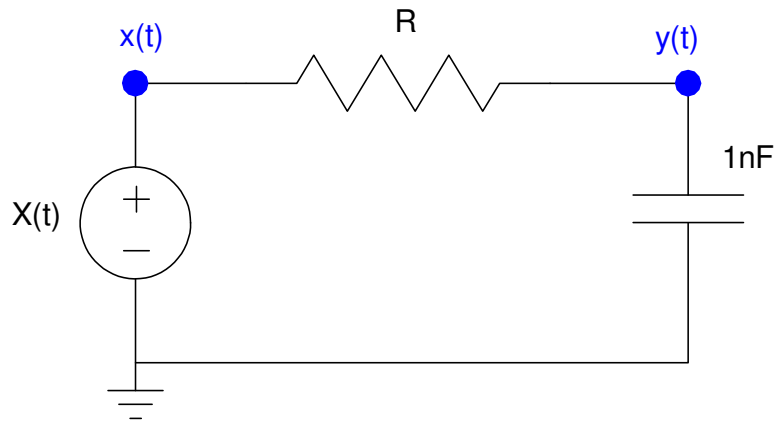

DC:

$$C \rightarrow \frac{1}{j\omega C} = \infty$$

$$Y = X = 10$$

1 rad/sec

$$X = 0 - j11$$

$$C \rightarrow \frac{1}{\omega C} = -j1G\Omega$$

$$Y = \left(\frac{-j1G\Omega}{1514 - j1G\Omega} \right) (0 - j11) = 0 - j11$$

2 rad/sec

$$X = 12 + j0$$

$$C \rightarrow \frac{1}{\omega C} = -j500M\Omega$$

$$Y = \left(\frac{-j500M\Omega}{1514 - j500M\Omega} \right) (12 + j0) = 12 + j0$$

Problem #1 (change C to 1000uF)

$$x(t) = 10 + 11 \sin(t) + 12 \cos(2t)$$

DC

$$Y = X = 10$$

1 rad/sec

$$C \rightarrow \frac{1}{j\omega C} = -j1000\Omega$$

$$X = 0 - j11$$

$$Y = \left(\frac{-j1000}{1514 - j1000} \right) (0 - j11) = -5.059 - j3.341$$

$$y(t) = -5.059 \cos(t) + 3.341 \sin(t)$$

2 rad/sec

$$C \rightarrow \frac{1}{j\omega C} = -j500\Omega$$

$$X = 12 + j0$$

$$Y = \left(\frac{-j500}{1514 - j500} \right) (12 + j0) = 1.180 - j3.573$$

$$y(t) = 1.180 \cos(2t) + 3.573 \sin(2t)$$

y(t)

$$y(t) = 10 - 5.059 \cos(t) + 3.341 \sin(t) + 1.180 \cos(2t) + 3.573 \sin(2t)$$

Fourier Transforms

2) Assume a 1 rad/sec parabolic sine wave (of Ninja Turtles fame).

$$\begin{aligned} x(t) &= t(\pi - t) & 0 < t < \pi \\ &t(\pi + t) & -\pi < t < 0 \end{aligned} \quad x(t + \pi) = x(t)$$

Determine the magnitude of the 3rd harmonic of the Fourier Transform for $x(t)$:

$$a_3 = \frac{1}{\pi} \int_{-\pi}^{\pi} x(t) \cdot \cos(3t) \cdot dt = 0 \quad \text{it's an odd function}$$

$$b_3 = \frac{1}{\pi} \int_{-\pi}^{\pi} x(t) \cdot \sin(3t) \cdot dt \quad \text{solve for } b_3$$

note:

- Hand calculations, Matlab, calculators, etc. are allowed...

b3	Method / Resource used to solve for b3
0.0943	Matlab & numerical integration

In Matlab

```
>> t = [-1:0.001:1]' * pi;  
>> x = t.*(pi-t).*(t>0) + t.*(pi+t).*(t<0);  
>> a0 = mean(x)  
a0 = 1.2135e-017
```

```
>> a1 = 2*mean(x .* cos(t))  
a1 = -1.3804e-016
```

```
>> b1 = 2*mean(x .* sin(t))  
b1 = 2.5452
```

```
>> a2 = 2*mean(x .* cos(2*t))  
a2 = -8.9705e-017
```

```
>> b2 = 2*mean(x .* sin(2*t))  
b2 = -1.4294e-016
```

```
>> a3 = 2*mean(x .* cos(3*t))  
a3 = 1.7176e-017
```

```
>> b3 = 2*mean(x .* sin(3*t))  
b3 = 0.0943
```

```
>>
```

DC to AC Converter

3) Assume the Fourier transform for the output of a DC to AC converter driving a 1 Ohms resistor is as follows:

- note: units are Vp (peak voltage)

Harmonic	0 (DC)	1	2	3	4	5
an (cosine)	0	18.3	0	2.6	0	0.7
bn (sine)	0	2.7	0	0	1.4	0
Energy (W) $(a_n^2 + b_n^2)/2$	0	171.09	0	3.38	0.98	0.24

Determine the following:

Total Energy in the signal	Energy in the 1st harmonic	Efficiency % of energy in the 1st harmonic
175.69W	171.09W	97.4%


DC to AC Converter: Differential equations for a Circuit

4) Determine the differential equations which describe the following circuit. Note

- $V_L = L \frac{dI_L}{dt}$
- $I_C = C \frac{dV_1}{dt}$

Assume $R = 1000 + 100 * (\text{Birth Month}) + (\text{Birth day})$. For May 15th, for example, $R = 1514$ Ohms.

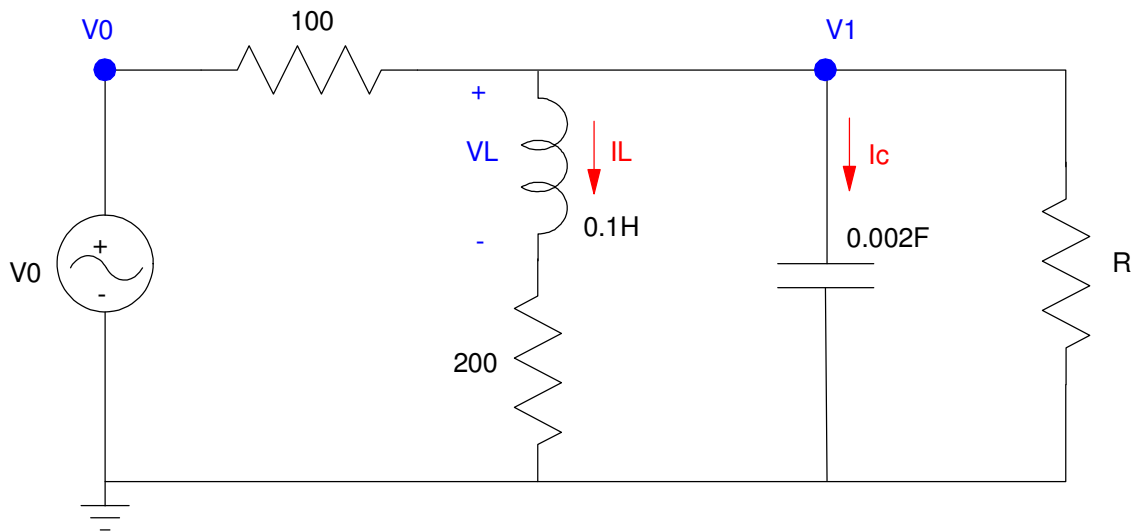$\frac{dI_L}{dt} = 10V_1 - 2000I_L$
$\frac{dV_1}{dt} = 5V_0 - 5.33V_1 - 500I_L$



$$V_L = 0.1 \frac{dI_L}{dt} = V_1 - 200I_L$$

$$\frac{dI_L}{dt} = 10V_1 - 2000I_L$$


$$0.002 \frac{dV_1}{dt} = \left(\frac{V_0 - V_1}{100} \right) - I_L - \frac{V_1}{1514}$$

$$\frac{dV_1}{dt} = 5V_0 - 5V_1 - 500I_L - 0.33V_1$$

SCR (5 diode version)

5) SCR: Analysis. Determine the voltages at V1 and V2 (both DC). Assume a firing angle of 35 degrees.

R 1000 + 100*Mo + Day	V1		V2	
	DC	AC (V1pp)	DC	AC (V2pp)
1514	10.48	19.3Vpp	9.83	4.39Vpp

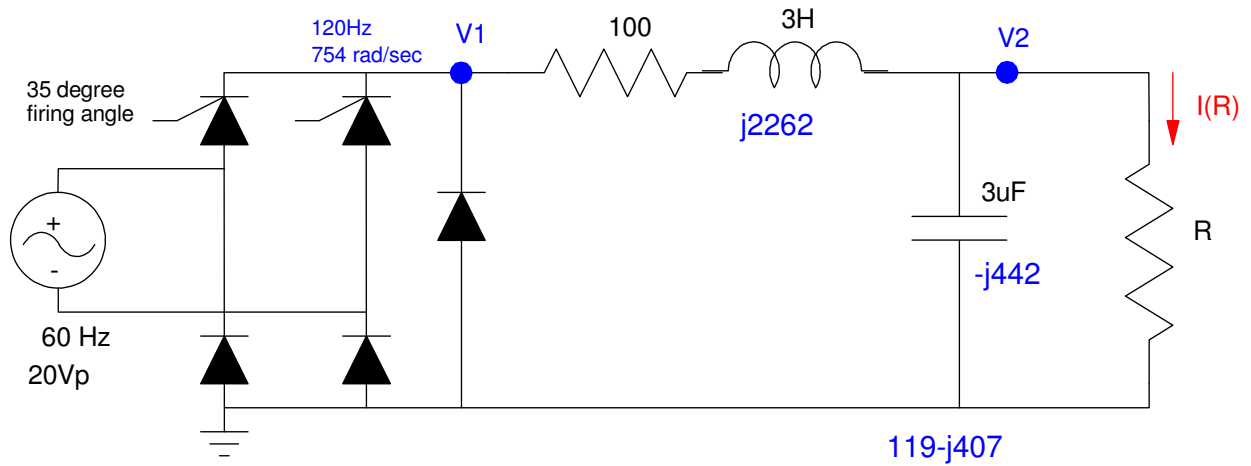

35 degrees

$$V_1(DC) = \left(\frac{18.6V + 0.7V}{\pi} \right) (1 + \cos(35^\circ)) - 0.7 = 10.476V$$

$$V_1(AC) = 19.3V_{pp}$$


$$V_2(DC) = \left(\frac{1514}{1514 + 100} \right) 10.476V = 9.827V$$

$$V_2(AC) = \left(\frac{119 - j407}{(119 - j407) + (100 + j2262)} \right) 19.3V_{pp} = 4.386V_{pp}$$

6) SCR Design. Determine the firing angle and C so that

- $V_2(\text{DC}) = 4.5\text{V}$
- $V_2(\text{AC}) = 500\text{mV}_{pp}$
- $R = 1000 + 100 * (\text{Birth Month}) + (\text{Birth Day})$. May 14th would give $R = 1514\text{ Ohms}$.

$V_1(\text{DC})$	Firing Angle	C	R 1000 + 100*Mo + Day
4.797V	96.03 deg	18.1uF	1514

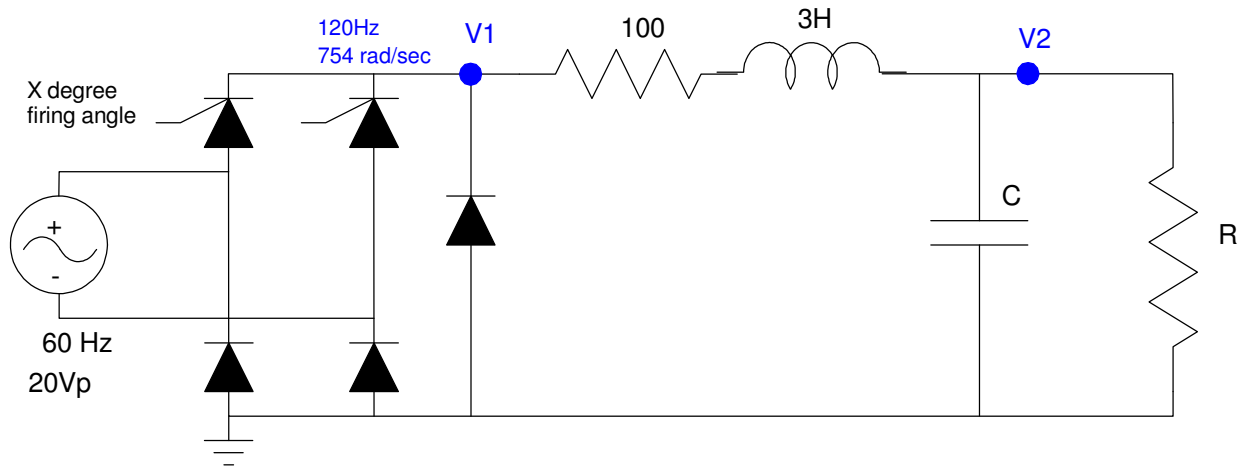

$$V_2 = \left(\frac{1514}{1514+11} \right) V_1 = 4.50\text{V}$$

$$V_1 = 4.797\text{V}$$

$$V_1 = 4.797\text{V} = \left(\frac{18.6\text{V}+0.7\text{V}}{\pi} \right) (1 + \cos(\theta)) - 0.7$$

$$\theta = 96.037^\circ$$

$$V_1(\text{AC}) = 18.489\text{V} - (-0.7\text{V}) = 19.189\text{V}_{pp}$$

If $C = 0$

$$V_2(\text{AC}) = \left(\frac{1514}{1514+(100+j2262)} \right) 19.189\text{V}_{pp} = 10.373\text{V}$$

to bring the ripple down to 0.5V_{pp}

$$\left| \frac{1}{j\omega C} \right| = \left(\frac{0.5\text{V}_{pp}}{10.373\text{V}_{pp}} \right) 1514\Omega = 72.98\Omega$$

$$C = 18.1\mu\text{F}$$