

# ECE 320 - Quiz #8 - Name \_\_\_\_\_

Boolean Logic, DTL, TTL Logic.


## Boolean Logic

1) Implement the following logic using NAND gates (circuit the ones).

- $Y = 1$  if ABCD is prime: {2, 3, 5, 7, 11, 13}

| Y | AB | CD |    |    |    |
|---|----|----|----|----|----|
|   |    | 00 | 01 | 11 | 10 |
|   | 00 | 0  | 0  | 1  | 1  |
|   | 01 | 0  | 1  | 1  | 0  |
|   | 11 | 0  | 1  | 0  | 0  |
|   | 10 | 0  | 0  | 1  | 0  |

$$Y = A'B'C + B'CD + A'BD + BC'D$$

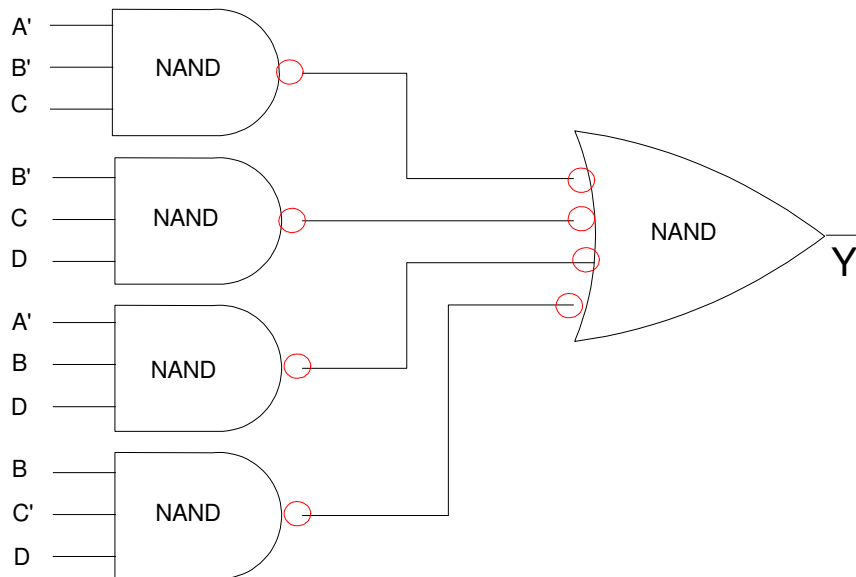

## Boolean Logic

2) Implement the following logic using NOR gates (circuit the zeros).


- $Y = 1$  if ABCD is prime: {2, 3, 5, 7, 11, 13}

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | CD |    |    |    |
|    |    | 00 | 01 | 11 | 10 |
| AB | 00 | 0  | 0  | 1  | 1  |
|    | 01 | 0  | 1  | 1  | 0  |
|    | 11 | 0  | 1  | 0  | 0  |
|    | 10 | 0  | 0  | 1  | 0  |

$$Y' = B'C' + C'D' + ABC + AD' + BD'$$

using DeMorgan's theorem
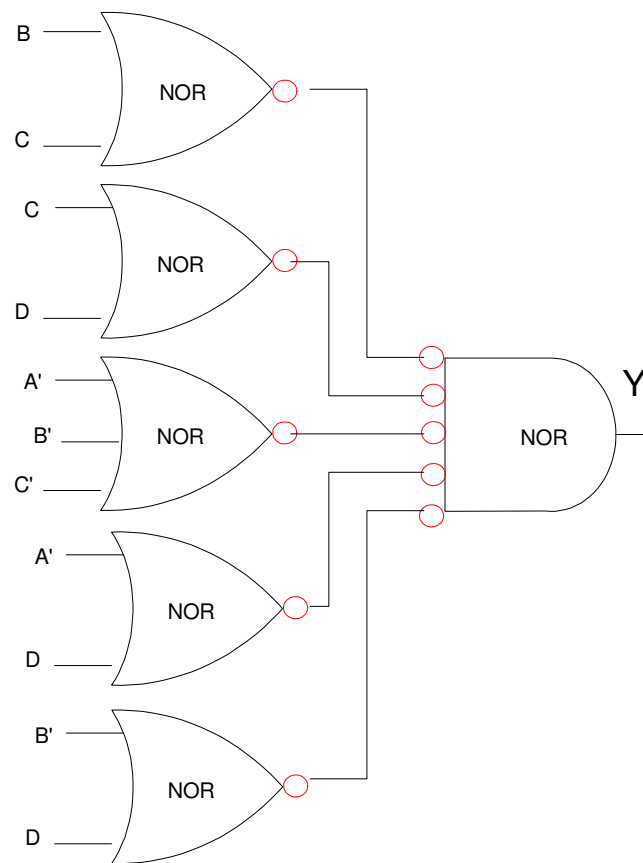
$$Y = (B + C)(C + D)(A' + B' + C')(A' + D)(B' + D)$$




**DTL Logic Gate:**

3) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ , gain = 100)
- Ideal silicon diodes ( $V_f = 0.7V$ )
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.


| R           | V1          | V2                          | V3          | V4                     |
|-------------|-------------|-----------------------------|-------------|------------------------|
| <b>1514</b> | <b>1.4V</b> | <b>0.2V</b><br>T1 saturated | <b>0.9V</b> | <b>4.76V</b><br>T2 off |

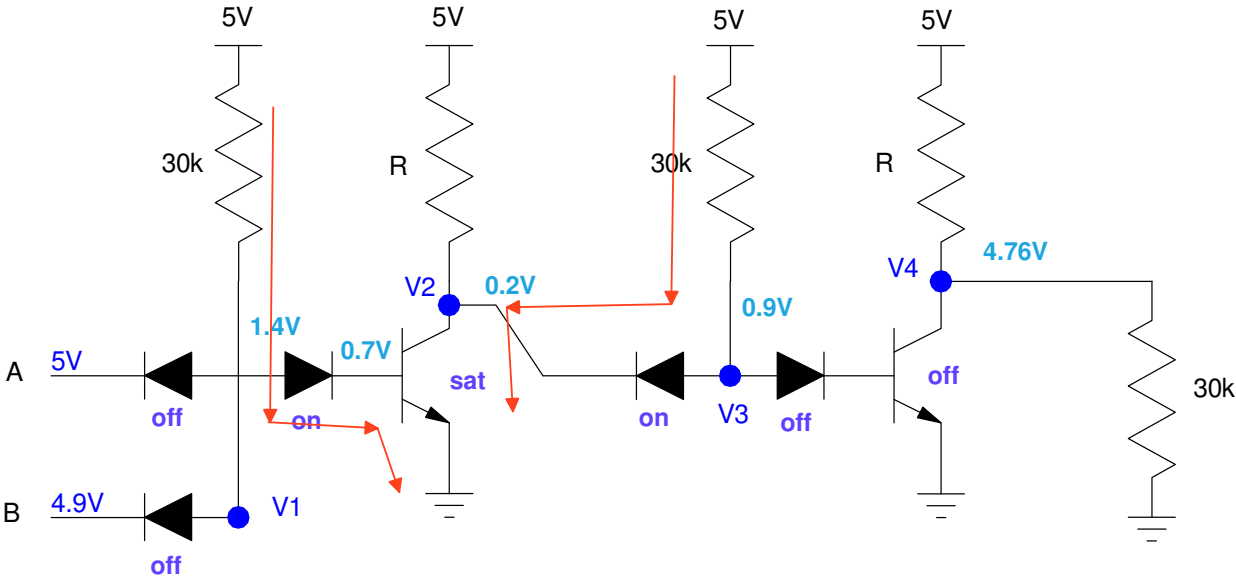

**DTL Logic Gate:**

- 4) Determine the voltages and currents for the following DTL gate. Assume
- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ , gain = 100)
  - Ideal silicon diodes ( $V_f = 0.7V$ )
  - $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

| R    | V1   | V2 | V3   | V4   |
|------|------|----|------|------|
| 1514 | 0.7V | 5V | 1.4V | 0.2V |

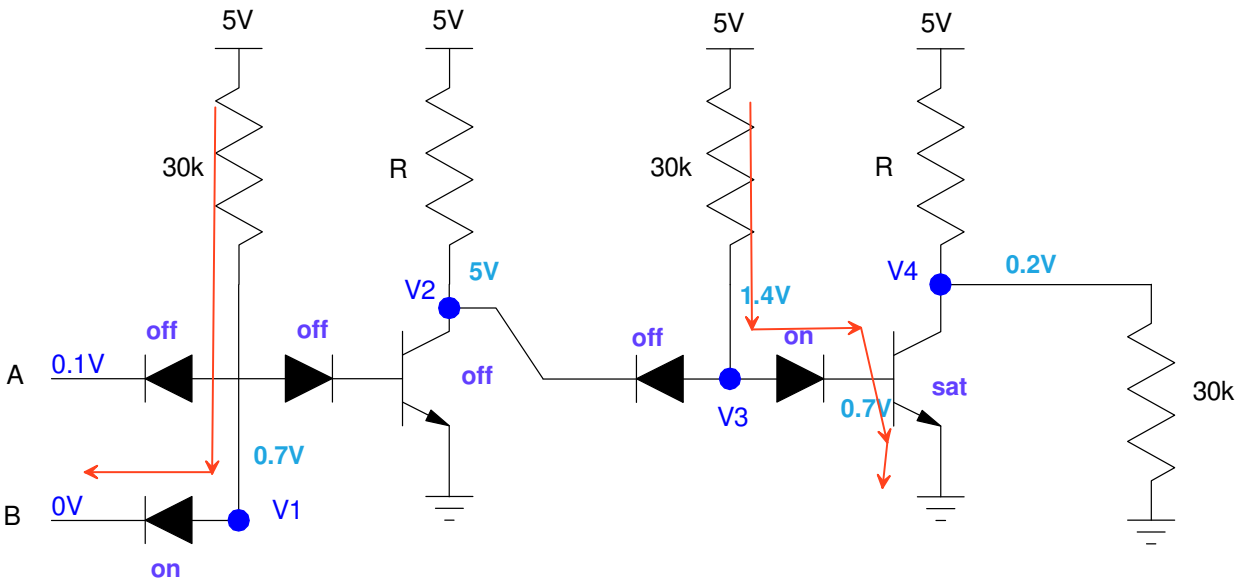


## Open Collector Logic

5) Determine the voltages and currents for the following circuit. Assume

- Ideal silicon diodes ( $V_f = 0.7V$ )
- $V_{be} = 0.7V$
- $\beta = 100$
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

| R           | I1           | I2           | I3       | V4                       |
|-------------|--------------|--------------|----------|--------------------------|
| <b>1514</b> | <b>120uA</b> | <b>120uA</b> | <b>0</b> | <b>0.2V</b><br>saturated |

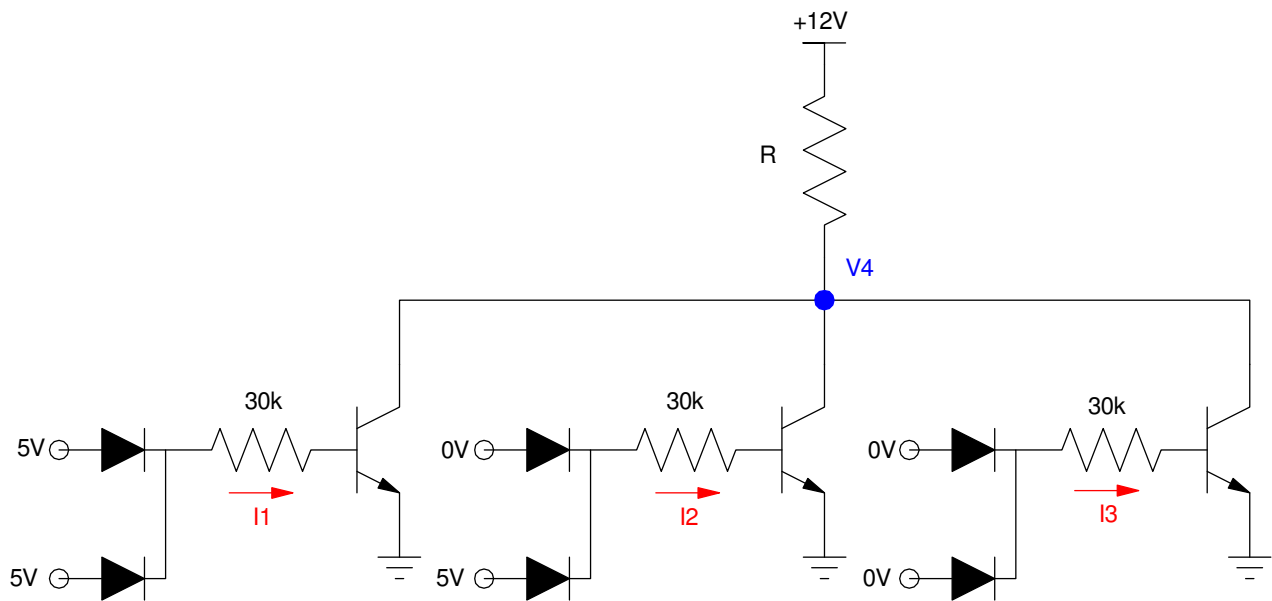

$$I_1 = \left( \frac{5V - 1.4V}{30k} \right) = 120\mu A$$

$$I_2 = \left( \frac{5V - 1.4V}{30k} \right) = 120\mu A$$

$$I_3 = 0$$

$$I_R = \left( \frac{12V - 0.2V}{1514} \right) = 7.794mA$$

Check that the transistors are saturated

$$\beta I_b = 100 \cdot 120\mu A = 12mA \quad (\times 2 \text{ meaning the transistors together allow } 24mA \text{ to flow})$$

$$24mA > 7.74mA \quad \text{saturated}$$

## TTL Logic

6) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ( $V_{be} = 0.7V$ ,  $V_{ce(sat)} = 0.2V$ ,  $\beta = 2$  (left) or 100 (right) transistor
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$ . For example, May 14th gives  $R = 1514$  Ohms.

| R           | V1            | V2          | V3          | V4          |
|-------------|---------------|-------------|-------------|-------------|
| <b>1514</b> | <b>4.273V</b> | <b>1.4V</b> | <b>0.7V</b> | <b>0.2V</b> |

