

ECE 320 - Quiz #8 - Name _____

Boolean Logic, DTL, TTL Logic.

Boolean Logic

1) Implement the following logic using NAND gates (circuit the ones).

- $Y = 1$ if ABCD is prime: {2, 3, 5, 7, 11, 13}

		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	0	1	1	0
	11	0	1	0	0
	10	0	0	1	0

Boolean Logic

2) Implement the following logic using NOR gates (circuit the zeros).

- $Y = 1$ if ABCD is prime: {2, 3, 5, 7, 11, 13}


		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	0	1	1	0
	11	0	1	0	0
	10	0	0	1	0

DTL Logic Gate:

3) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$. For example, May 14th gives $R = 1514$ Ohms.

R	V1	V2	V3	V4

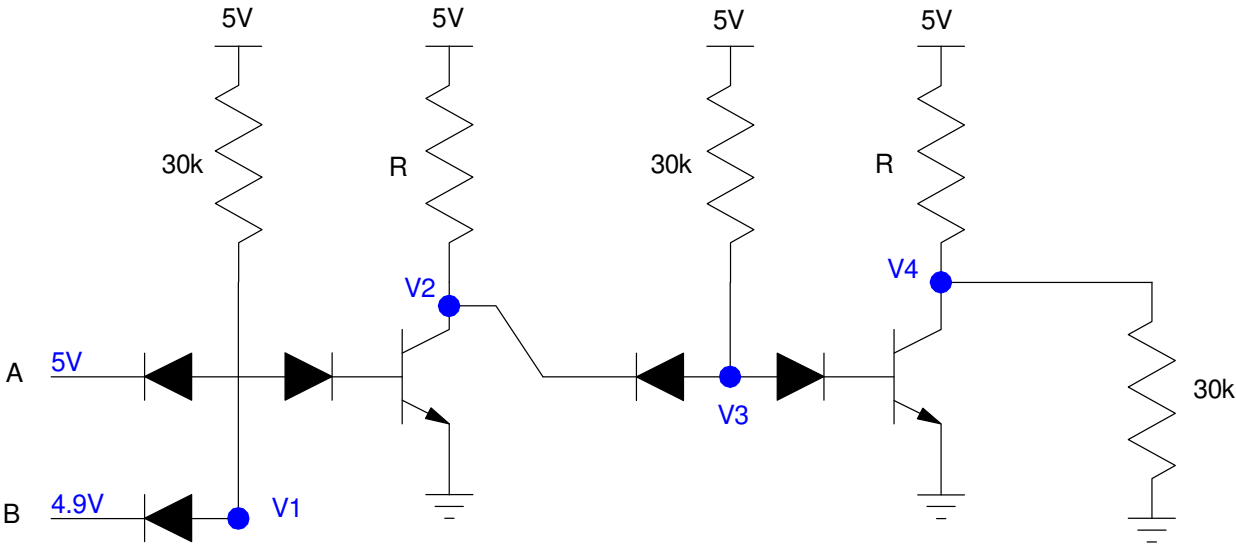


DTL Logic Gate:

4) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$. For example, May 14th gives $R = 1514$ Ohms.

R	V1	V2	V3	V4

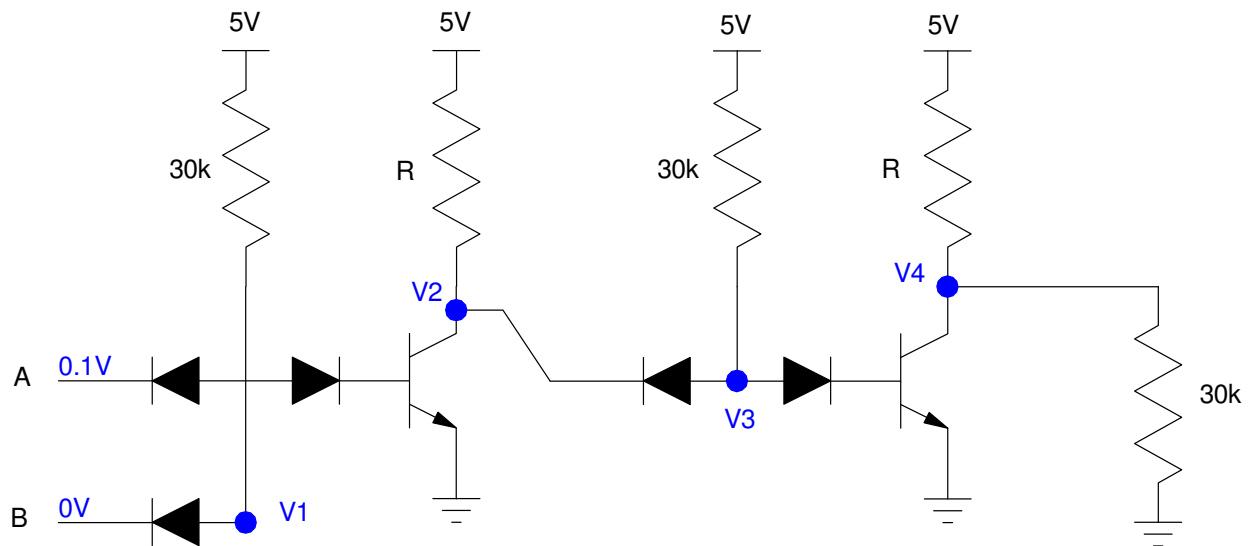


Open Collector Logic

5) Determine the voltages and currents for the following circuit. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $V_{be} = 0.7V$
- $\beta = 100$
- $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$. For example, May 14th gives $R = 1514$ Ohms.

R	I1	I2	I3	V4

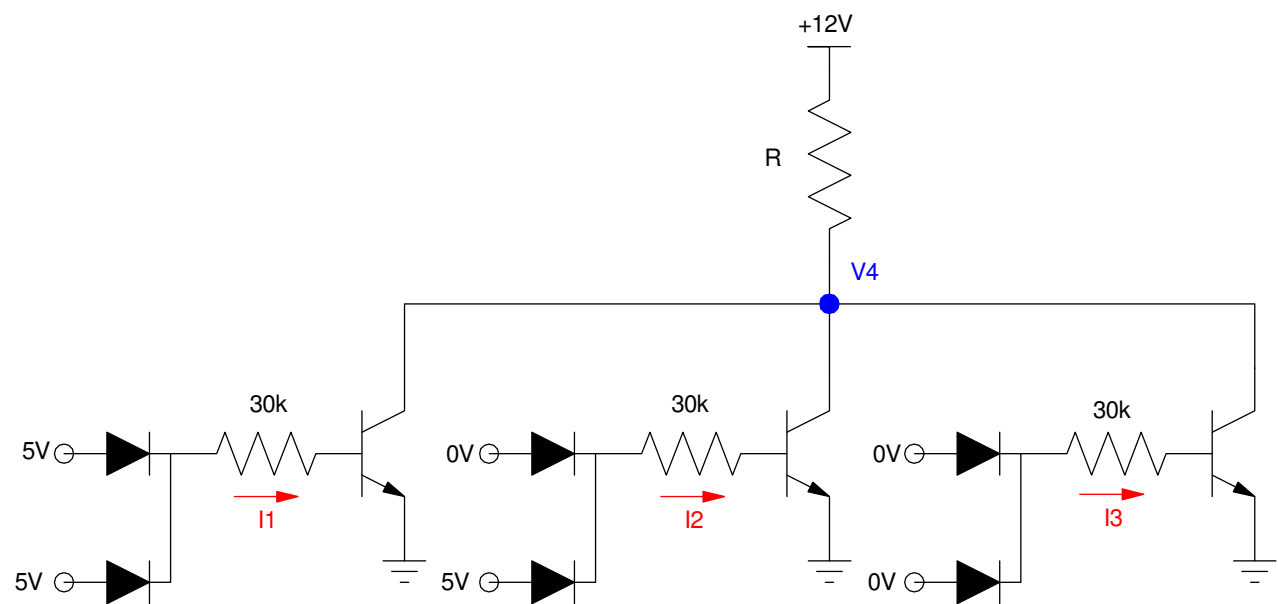

TTL Logic

- 6) Determine the voltges and currents for the following DTL gate. Assume
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 2$ (left) or 100 (right) transistor
 - $R = 1000 + 100(\text{Birth Month}) + (\text{Birth Day})$. For example, May 14th gives $R = 1514$ Ohms.

R	V1	V2	V3	V4

