
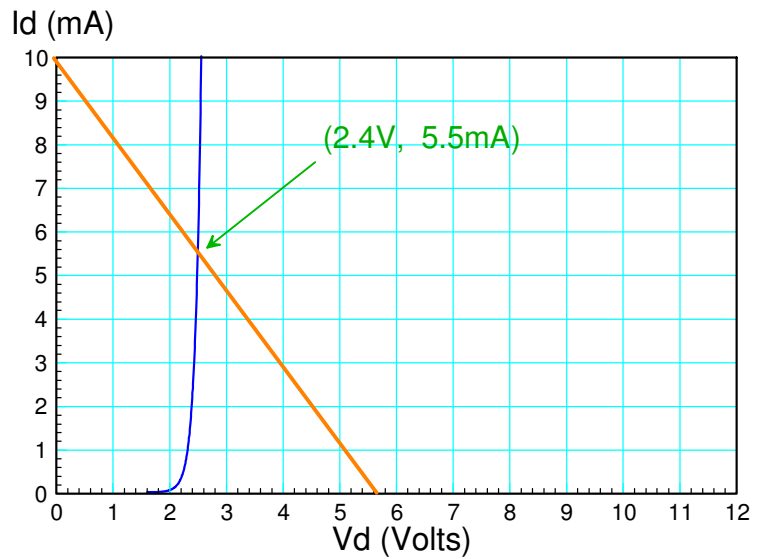


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes

1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_d and V_d . Assume $R = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.

R 900 + 100*mo + day	Load Line x-intercept (volts)	Load Line y-intercept (mA)	V _d Volts	I _d mA
1414	5.857V	10.0mA	2.4V	5.5mA

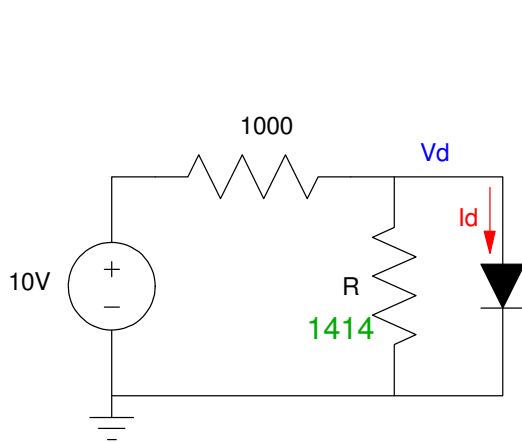

x-intercept ($I_d = 0$)

$$V_d = \left(\frac{1414}{1414 + 1000} \right) 10V = 5.857V$$

y-intercept ($V_d = 0$)

$$I_d = \left(\frac{10V}{1000\Omega} \right) = 10mA$$


2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.038 \ln(10^{11} \cdot I_d + 1) \quad I_d = 10^{-11} \cdot \left(\exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

Write N equations to solve for N unknowns: $\{V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}\}$.

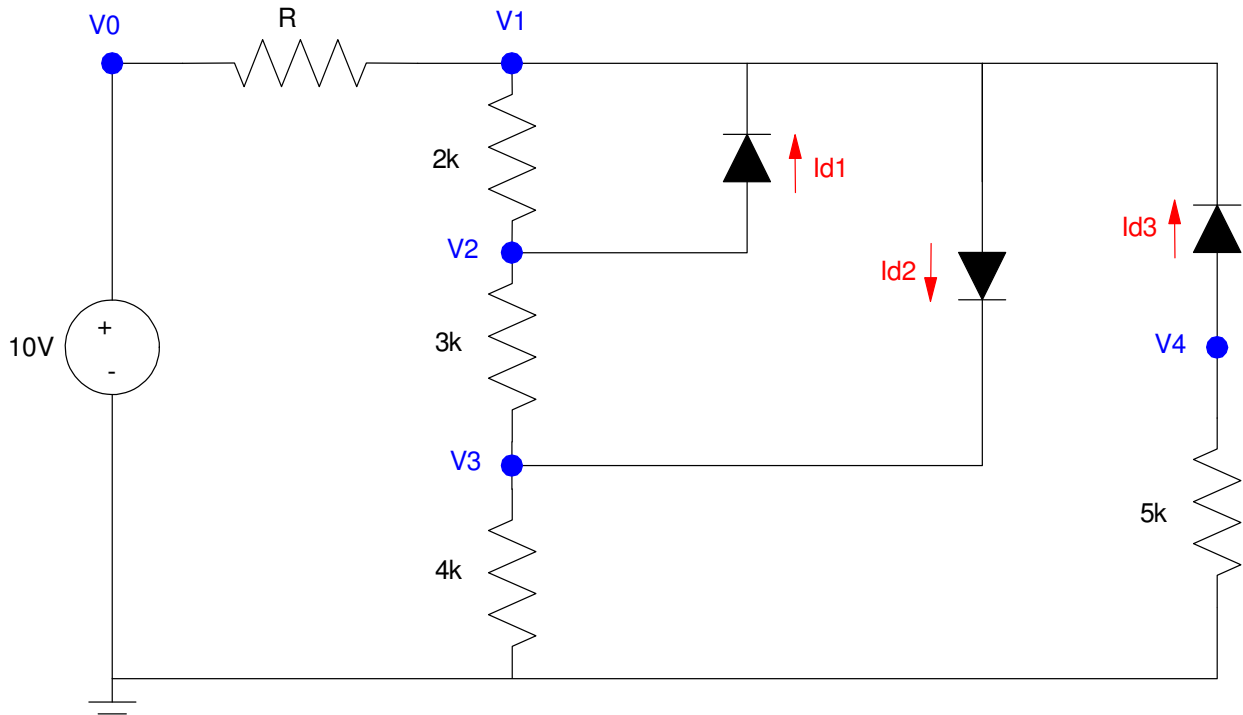- Note: you do not need to solve.
- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{birth date})$.



$$I_{d1} = 10^{-11} \cdot \left(\exp\left(\frac{V_2 - V_1}{0.038}\right) - 1 \right)$$

$$I_{d2} = 10^{-11} \cdot \left(\exp\left(\frac{V_1 - V_3}{0.038}\right) - 1 \right)$$

$$I_{d3} = 10^{-11} \cdot \left(\exp\left(\frac{V_4 - V_1}{0.038}\right) - 1 \right)$$

$$\left(\frac{V_1 - V_0}{R} \right) + \left(\frac{V_1 - V_2}{2000} \right) - I_{d1} + I_{d2} - I_{d3} = 0$$

$$\left(\frac{V_2 - V_1}{2000} \right) + \left(\frac{V_2 - V_3}{3000} \right) + I_{d1} = 0$$


$$\left(\frac{V_3 - V_2}{3000} \right) + \left(\frac{V_3}{4000} \right) - I_{d2} = 0$$

$$\left(\frac{V_4}{5000} \right) + I_{d3} = 0$$

3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:

- $V_d = 0.7V$ $I_d > 0$
- $I_d = 0$ $V_d < 0.7V$
- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{birth date})$.

R 900 + 100*mo + day	I_{d1}	I_{d2}	I_{d3}
1414	0	1.578mA	0
V1	V2	V3	V4
7.571V	7.291V	6.871V	0V

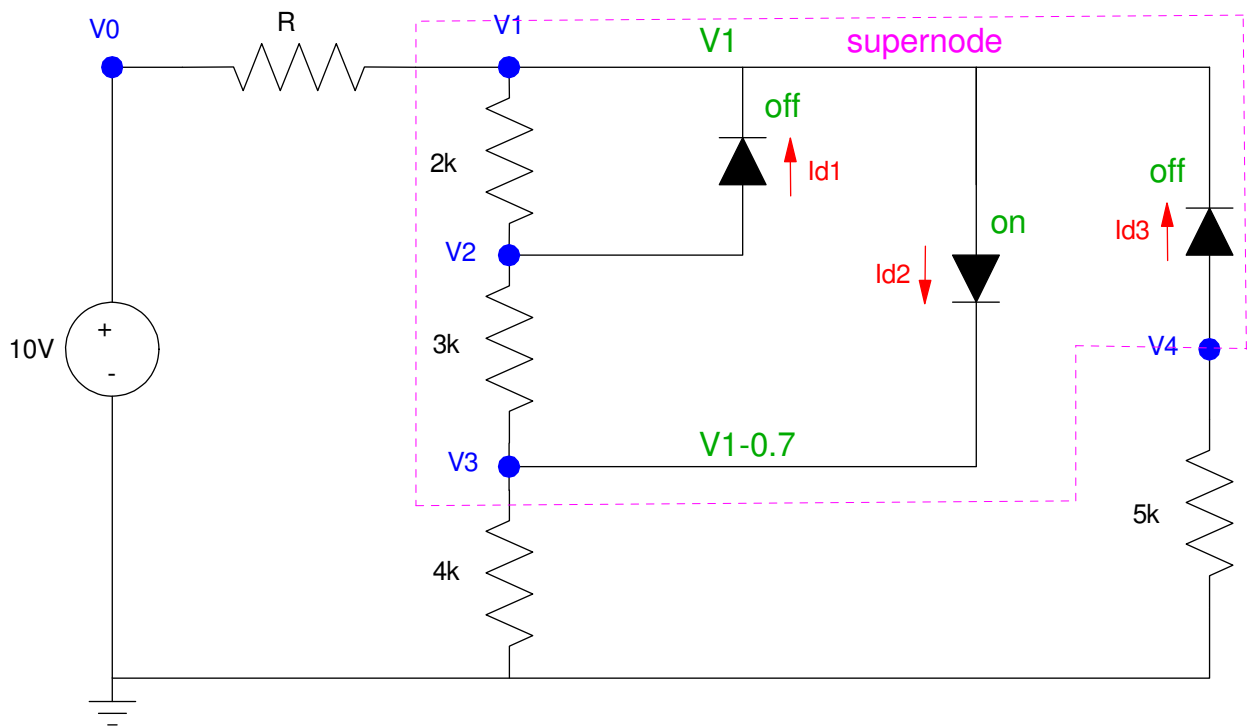

$$\left(\frac{V_1 - 10}{1414} \right) + \left(\frac{V_1 - 0.7}{4k} \right) + 0 = 0$$

$$V_1 = 7.571V$$

$$V_3 = V_1 - 0.7 = 6.871V$$


$$V_2 = \left(\frac{3}{5} \right) V_1 + \left(\frac{2}{5} \right) V_3 = 7.291V$$

$$V_4 = 0V$$

$$I_{d2} = \left(\frac{10V - V_1}{R} \right) - \left(\frac{V_1 - V_3}{5k} \right) = 1.578mA$$

4) AC to DC: Analysis: Determine V1 and V2 (both DC and AC) for the following AC to DC converter

R 900 + 100*mo + day	V1		V2	
	DC	AC	DC	AC
1414	26.07V	6.451V_{pp}	24.35V	2.791V_{pp}

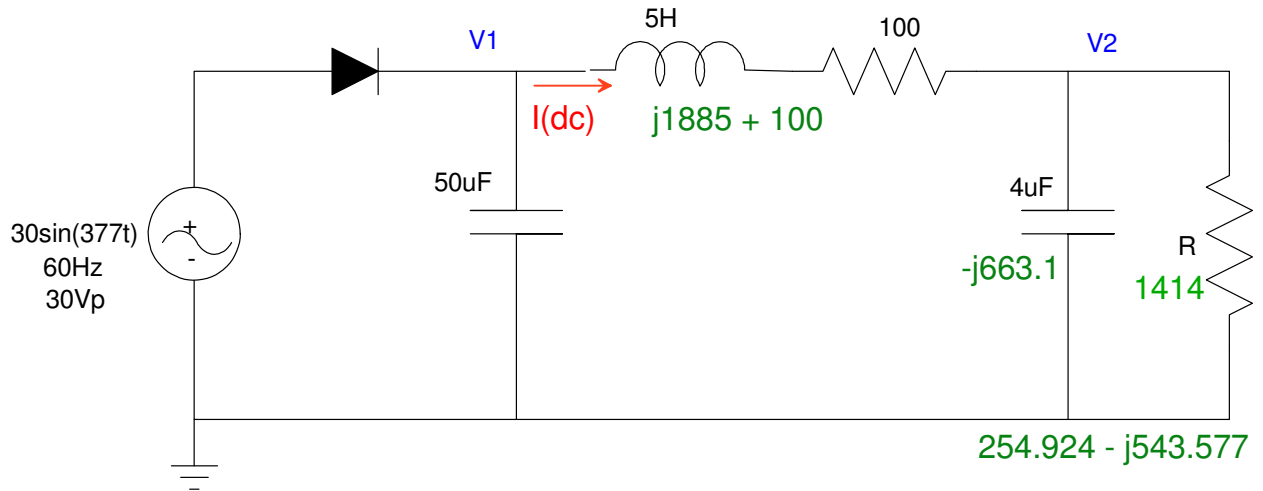

DC:

$$\max(V_1) = 29.3V$$

$$I = \frac{29.3V}{1414\Omega + 100\Omega} = 19.35mA$$

$$I = C \cdot \frac{dV}{dt}$$

$$19.35mA = 50\mu F \cdot \frac{dV}{1/60s}$$

$$dV = 6.451V_{pp}$$

$$V_1(DC) = 29.3V - \frac{1}{2} \cdot 6.451V_{pp} = 26.07V$$

$$V_2(DC) = \left(\frac{1414}{1414+100} \right) 26.07V = 24.35V$$

AC:


$$V_1(AC) = 6.451V_{pp}$$

$$V_2(AC) = \left(\frac{(254.924-j543.577)}{(254.924-j543.577)+(100+j1885)} \right) \cdot 6.451V_{pp}$$


$$|V_2(AC)| = 2.791V_{pp}$$

- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{birth date})$

R 900 + 100*mo day	R0	R1	Vz1	R2	Vz2
1414	4k	428.5	5V	150.0	8V

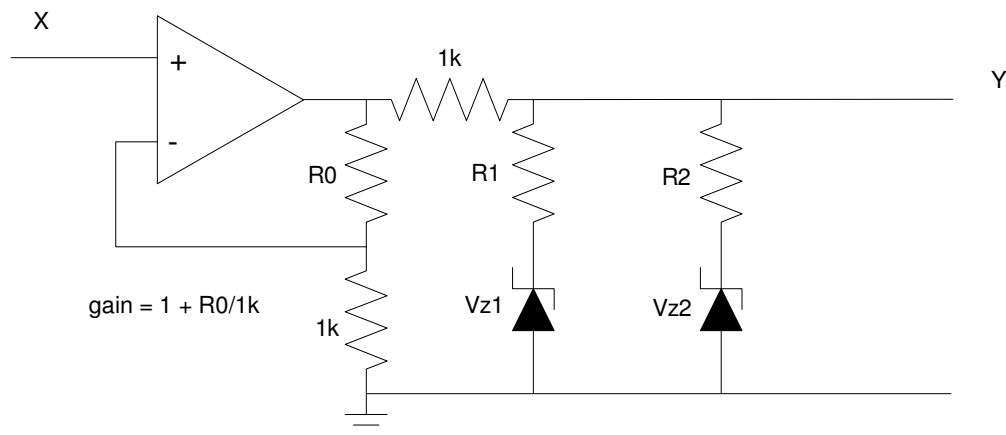

$$R_{12} = R_1 || R_2 \quad \Rightarrow R_2 = 150.0\Omega$$

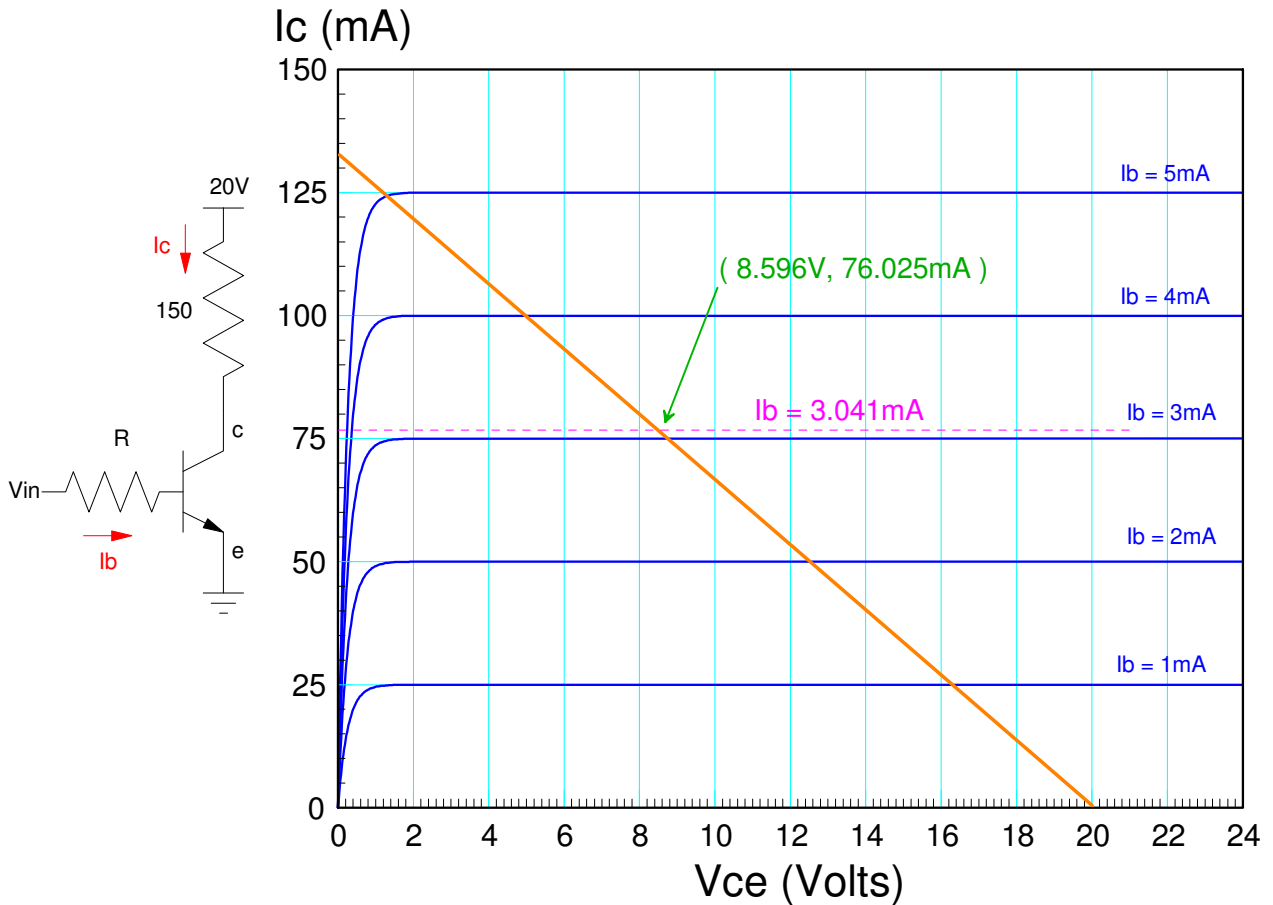


7) Design a Schmitt Trigger & transistor switch so that

- Turns on the LED at 50mA when $R_t < 2000$ Ohms
- Turns off the LED when $R_t > 2200$ Ohms

Assume

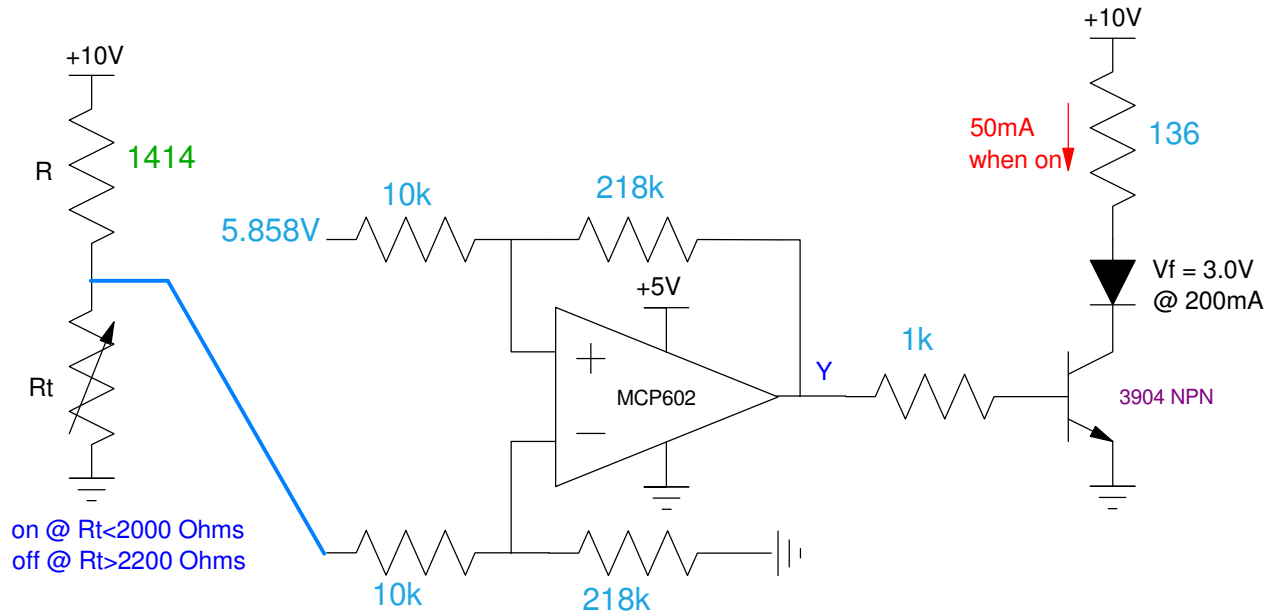- $R = 900 + 100 * (\text{your birth month}) + (\text{your birth date})$
- $V_{ce(sat)} = 0.2V$
- Current gain (β) = 100



$R_t = 2000$:

- $X = 5.858V$
- $Y = 5V$

$R_t = 2200$

- $X = 6.087V$
- $Y = 0V$

Connect to the minus input ($V(\text{on}) < V(\text{off})$)

Make the offset 5.858V (where Y goes high)

Make the gain

$$\text{gain} = \left(\frac{5V - 0V}{6.087V - 5.858V} \right) = 21.81$$

For $I_c = 50mA$

$$R_c = \frac{10V - 3V - 0.2V}{50mA} = 136\Omega$$


To saturate the transistor, $I_b > 0.5mA$. Let $I_b = 4.3mA$

$$R_b = 1000$$

8) DTL Logic: Determine the voltages and currents for the following DTL logic gage. Assume

- $R = 900 + 100 \cdot (\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 100$)


R 900 + 100*mo + da	V1	V2	V3	I4	I5	I6
1414	0.2V saturated	9.021V off	0.2V saturated	2.051mA	0 off	4.895mA

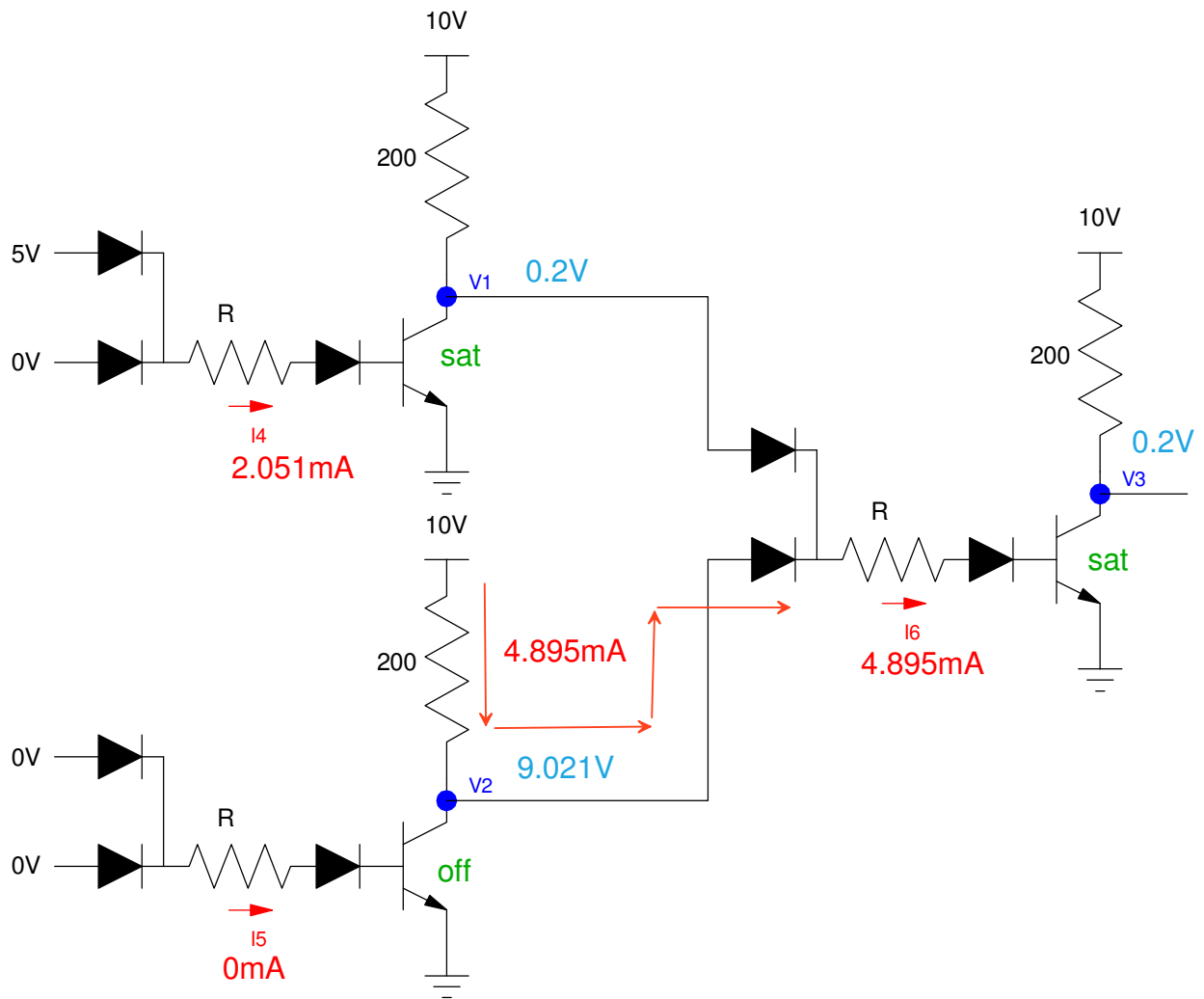

9) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line (x and y intercept), and
- Determine $\{V_{ds}, I_{ds}\}$ when $V_g = 7V$

k_n transconductance gain	Load Line x=intercept	Load Line y intercept	V_{ds} $V_g = 7V$	I_{ds} $V_g = 7V$	Operating Region off / active / ohmic
0.015 A/V²	10V	222.2 mA	4.6V	120mA	saturated

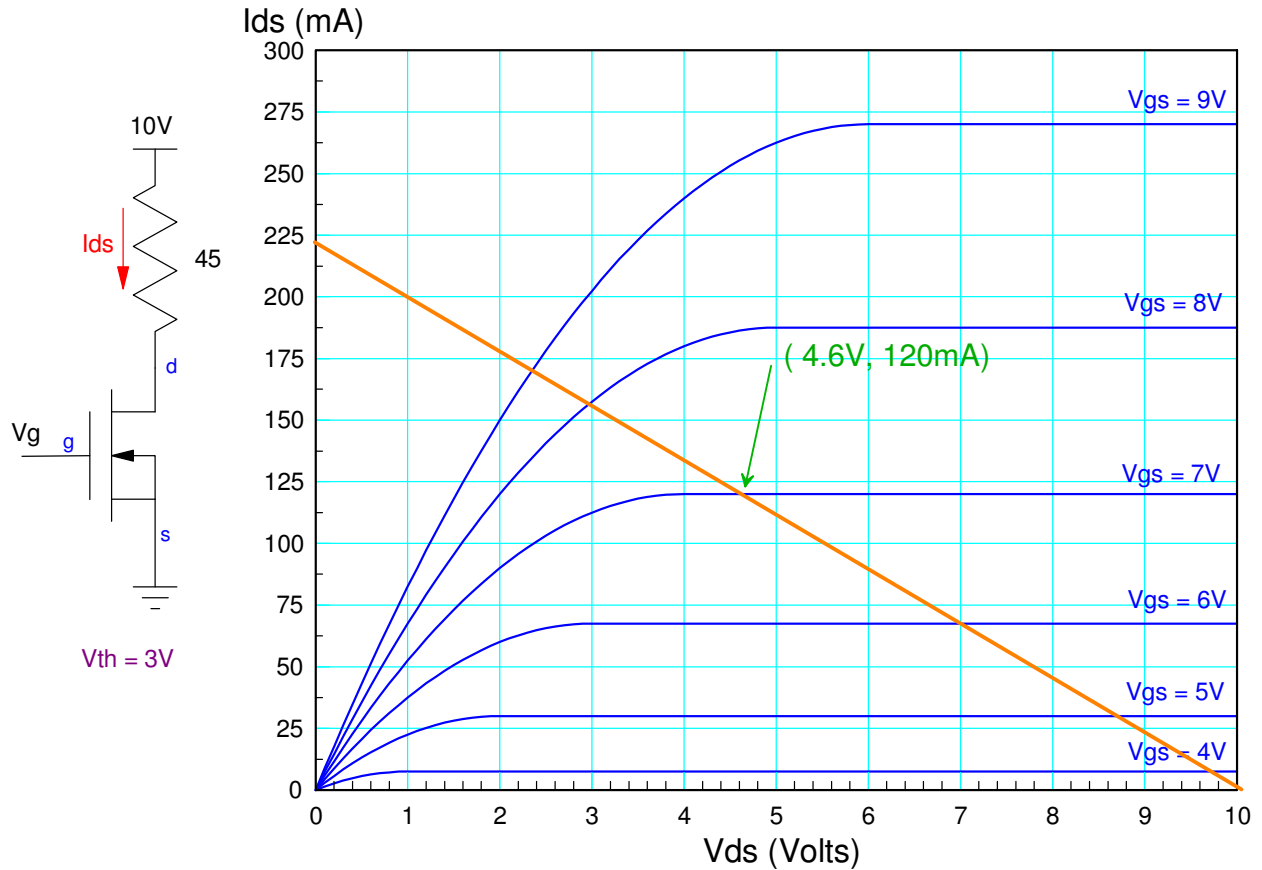

$$270mA = \frac{k_n}{2}(9V - 3V)^2$$

$$k_n = 0.015 \frac{A}{V^2}$$

10) CMOS Logic

a) Design a CMOS logic gate to implement $Y=f(A,B,C,D)$

		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	x	0	x	0
	11	0	x	x	0
	10	1	1	0	0

$$\bar{Y} = B + \bar{A}\bar{C} + AC$$

