


ECE 320 - Quiz #3 - Name _____

Ideal Diodes, LEDs, AC to DC Converters - Spring 2022

1) Determine the voltages and currents for the following circuit. Assume

- R is $900 + 100 * (\text{your birth month}) + (\text{your birthday})$. For example, May 14 = 1414 Ohms)

R 900 + 100*mo + day	V1	I2	I3	I4	I5
1414	0.7V	6.577mA	0	0	6.577mA

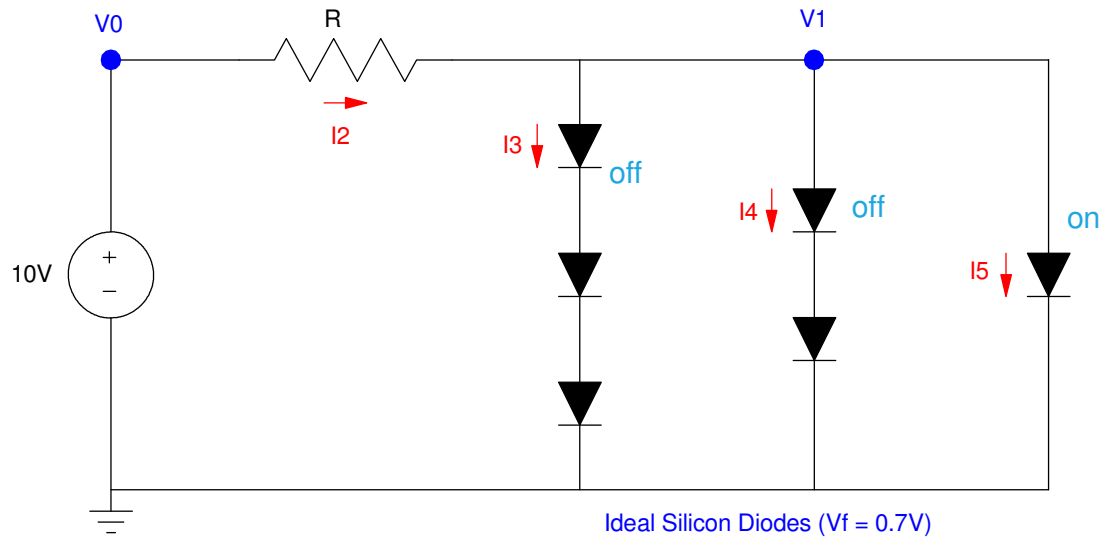


$$I_2 = \left(\frac{10V - 0.7V}{1414\Omega} \right) = 6.577mA$$

2) Determine the voltages and currents for the following circuit. Assume

- Ideal green LEDs ($V_f = 3.0V$).
- R is $900 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$.

V1	V2	V3	Id1	Id2	Id3
4.555V	1.555V	3.0V	0.778mA	0	1.555mA

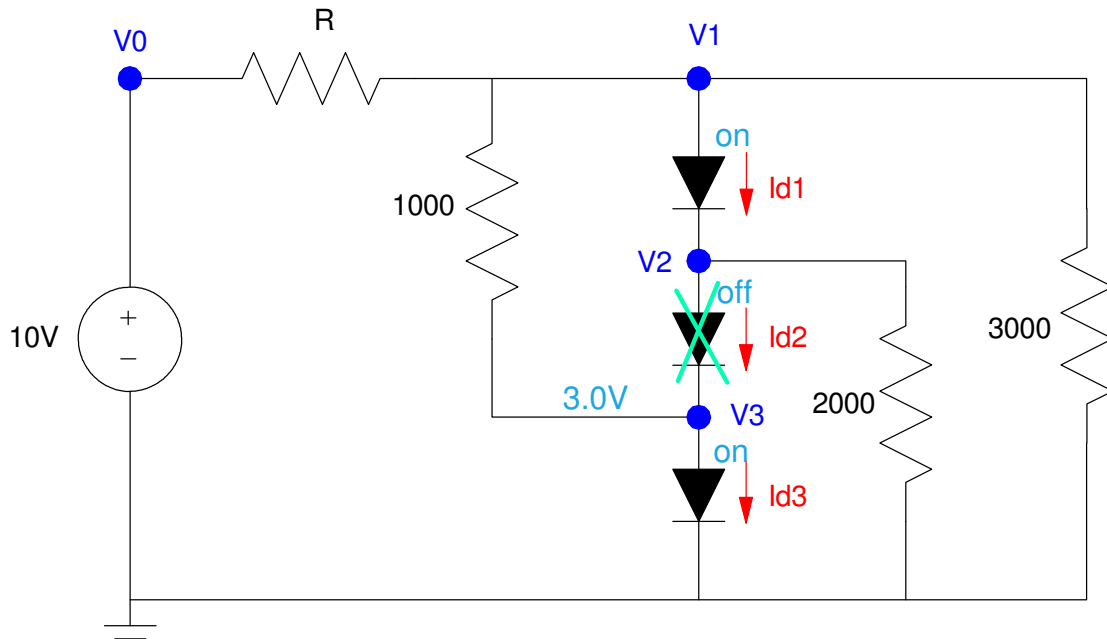

If all three diodes are on

$$V_3 = 3V, V_2 = 6V, V_1 = 9V$$

Current in doesn't match current out

$$\text{Current in} = \left(\frac{10V - 9V}{1414\Omega} \right) = 707\mu A$$

$$\text{Current Out} = \left(\frac{9V}{3k\Omega} \right) + \dots = 3mA + \dots$$

At least one diode is off.

- If $V_0 = 0V$, all three diodes are off
- Once V_1 rises above $3V$, Diode 1 turns on and Diode 3 turns on
- Assume diodes 1 and 3 are on

V_1 is then


$$\left(\frac{V_1 - 10}{1414} \right) + \left(\frac{V_1 - 3}{1000} \right) + \left(\frac{V_1}{3000} \right) + \left(\frac{V_1 - 3}{2000} \right) = 0$$

$$V_1 = 4.555V$$

3) A green and white LED are connected to a 10V source. Determine the current and brightness of each LED.
Assume

- R is $900 + 100 \cdot (\text{your birth month}) + (\text{your birthday})$.
- 3W LED: $V_f = 3.6V$ @ 750mA 180 Lumens @ 750mA
- 10W LED: $V_f = 11.0V$ @ 1000mA 650 Lumens @ 1000mA

R 900 + 100*mo + day	3W LED		10W LED	
	I _a	Lumens	I _b	Lumens
1414	8.568mA	2.056	3.728mA	2.423

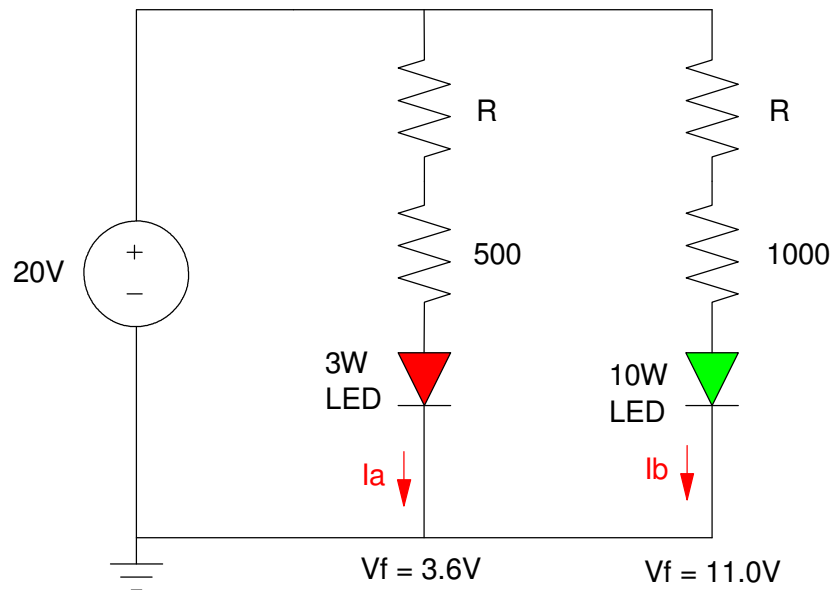

$$I_a = \left(\frac{20 - 3.6}{1414 + 500} \right) = 8.568mA$$


$$\left(\frac{8.568mA}{750mA} \right) 180 \text{ Lumens} = 2.056 \text{ Lumens}$$

$$I_b = \left(\frac{20V - 11.0V}{1414\Omega + 1000\Omega} \right) = 3.728mA$$

$$\left(\frac{3.728mA}{1000mA} \right) 650 \text{ Lumens} = 2.423 \text{ Lumens}$$

4) The following waveform is found using CircuitLab for an AC to DC converter. Determine the following

Frequency (Hz)	V2	
	DC (average)	AC (Vpp)
400 Hz	13.87V	370mVpp

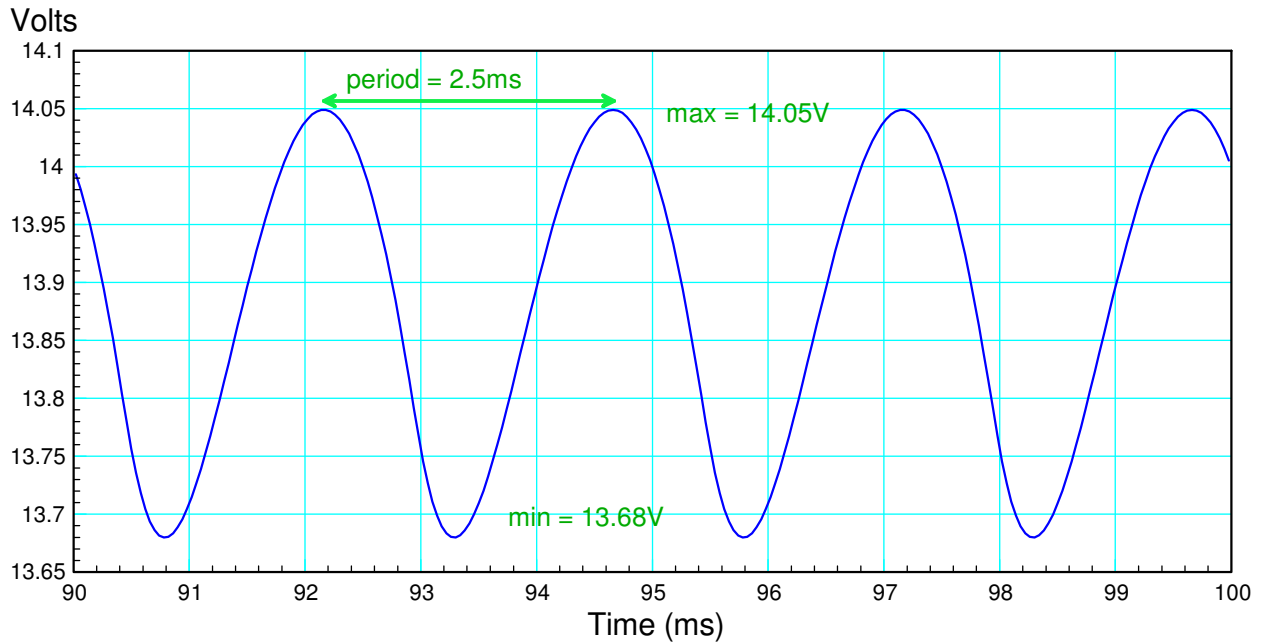

$$f = \frac{1}{\text{period}} = \frac{1}{2.5\text{ms}} = 400\text{Hz}$$


$$AC = \text{max} - \text{min} = 370\text{mV}_{pp}$$

$$DC \approx \left(\frac{\text{max} + \text{min}}{2} \right) = 13.87\text{V}$$

5) Determine the voltages V1 and V2 (both DC and AC). Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $C1 = (900 + 100 \cdot (\text{your birth month}) + (\text{your birthday})) \mu F$.

C1 (μF) 900 + 100*mo + day	V1		V2	
	DC	AC (V_{1pp})	DC	AC (V_{2pp})
1414μF	17.68V	3.250Vpp	15.154V	0.606Vpp

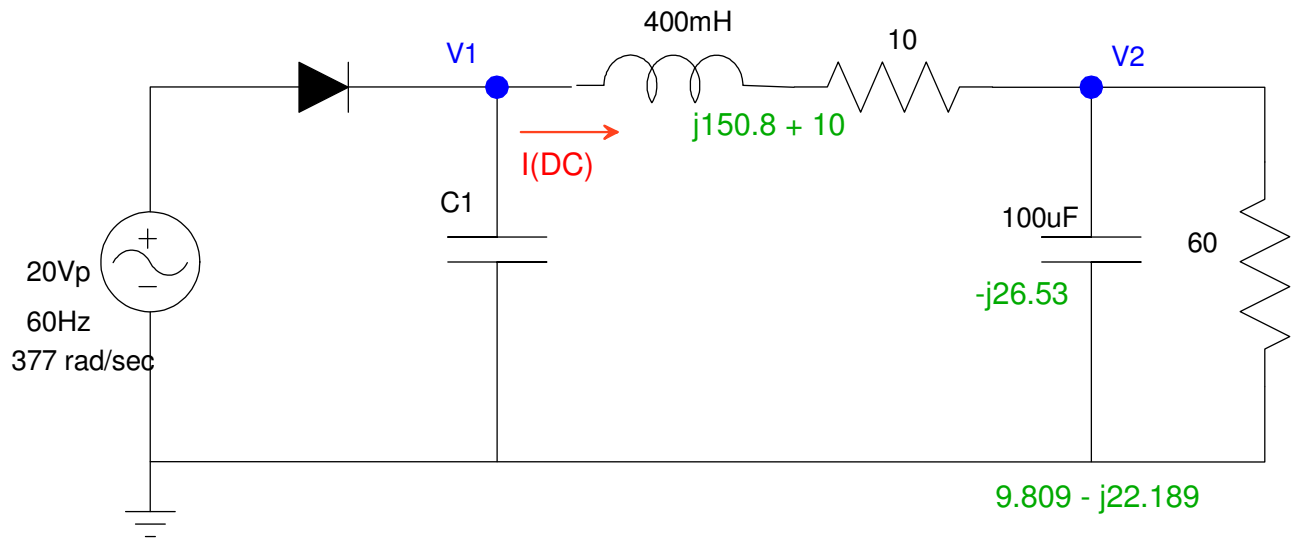

$$\max(V_1) = 19.3V$$

$$I \approx \left(\frac{19.3V}{70\Omega} \right) = 275.7mA \quad \text{worst case}$$

$$I = C \cdot \frac{dV}{dt}$$

$$275.7mA = 1414\mu F \cdot \frac{dV}{1/60s}$$

$$dV = 3.250V_{pp} = V_1(AC)$$

$$V_1(DC) = 19.3V - \frac{1}{2}V_1(AC) = 17.68V$$

$$V_2(DC) = \left(\frac{60}{60+10} \right) V_1(DC) = 15.154V$$


$$V_2(AC) = \left(\frac{(9.809-j22.189)}{(9.809-j22.189)+(10+j150.8)} \right) V_1(AC)$$

$$V_2(AC) = 0.606V_{pp}$$

6) Determine C1, and C2 so that

- The ripple at V1 is 4Vpp and
- The ripple at V2 = 500mVpp

C1	C2
1030uF	127.6uF

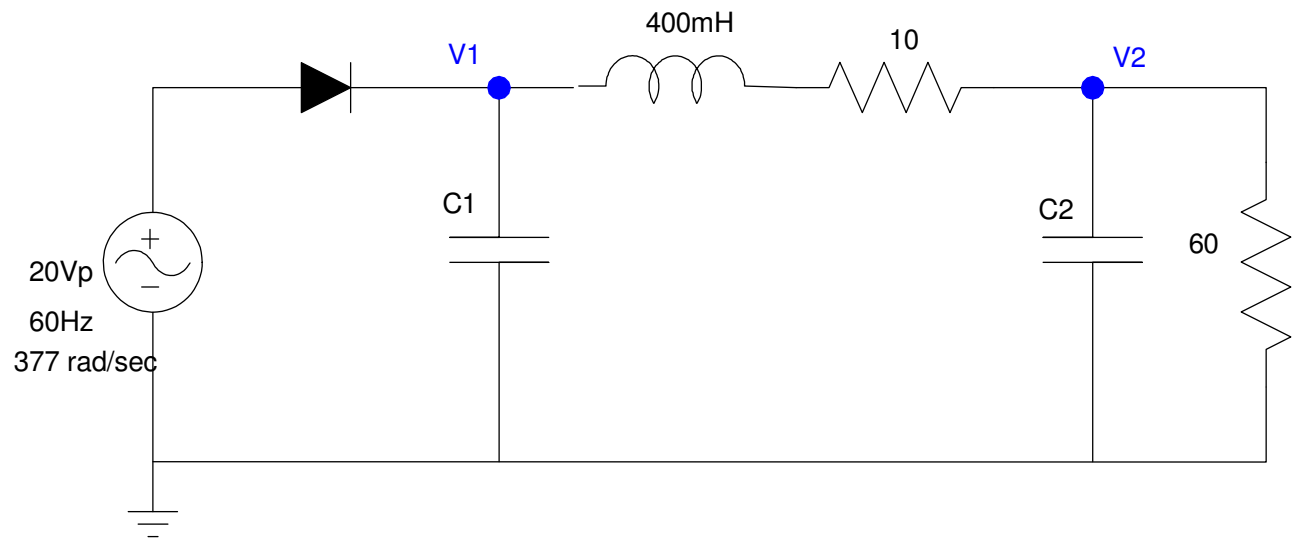

$$V_1(DC) = 19.3V - \frac{1}{2} \cdot 4V_{pp} = 17.3V$$

$$I = \left(\frac{17.3V}{70\Omega} \right) = 247mA$$

$$247mA = C_1 \cdot \frac{4V}{1/60s}$$

$$C_1 = 1030\mu F$$

Assume C2 = 0

$$V_2(AC) = \left(\frac{60}{60 + (10 + j150.8)} \right) 4V_{pp} = 1.444V_{pp}$$

$$\left| \frac{1}{j\omega C_2} \right| = \left(\frac{0.5V_{pp}}{1.444V_{pp}} \right) 60\Omega = 20.782\Omega$$

$$C_2 = 127.6\mu F$$