

ECE 320 - Quiz #8 - Name _____


Boolean Logic, DTL, TTL Logic, MOSFETs.

Boolean Logic

1) Design a circuit using NAND gates to implement the following logic

f(A,B,C,D)		CD			
		00	01	11	10
AB	00	x	x	x	1
	01	0	0	0	x
	11	0	1	1	1
	10	1	x	x	x

$$f = \bar{B} + AD + C\bar{D}$$

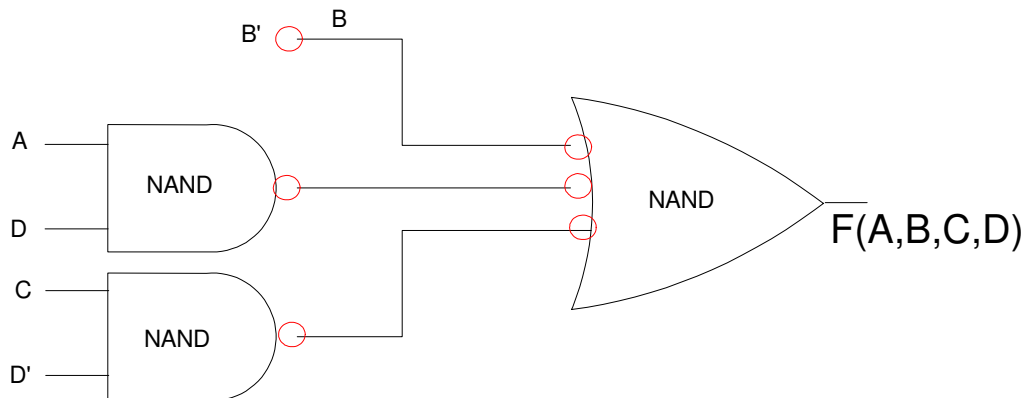


2) Design a circuit using NOR gates to implement the following logic:

Y(A,B,C,D)

		CD			
		00	01	11	10
AB	00	x	x	x	1
	01	0	0	0	x
	11	0	1	1	1
	10	1	x	x	x

$$\bar{Y} = B\bar{C}\bar{D} + \bar{A}D$$

$$Y = (\bar{B} + C + D)(A + \bar{D})$$

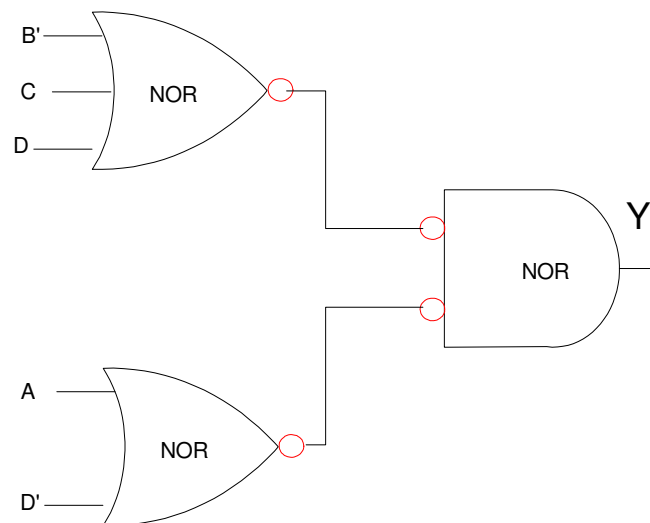


DTL: 10V Logic Logic

3) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 900 + 100*mo +day	V1	I2	V3	I4	V5
1414	1.3..1.4V floating	0	7.827V	1.537mA	0.2V

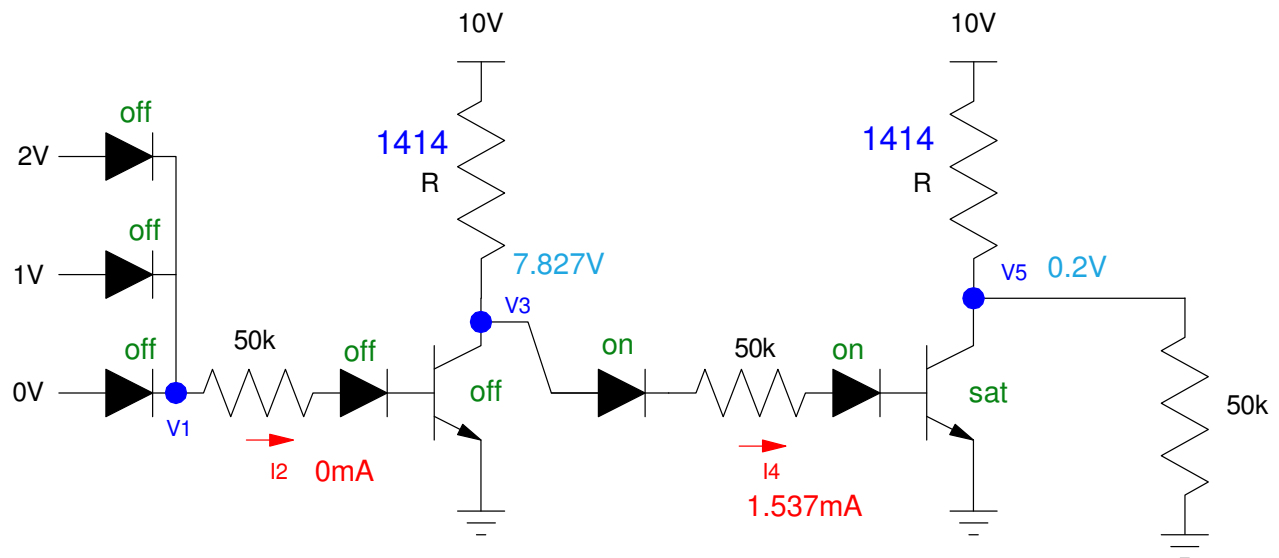

$$I_4 = \left(\frac{10V - 2.1V}{50k + 1414} \right) = 1.537mA$$

$$V_3 = 10V - 1414 \cdot 1.537mA$$


$$V_3 = 7.827V$$

DTL 10V Logic Gate:

4) Determine the voltages and currents for the following DTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 900 + 100*mo + day	V1	I2	V3	I4	V5
1414	9.30V	158uA	0.2V	0	9.725V

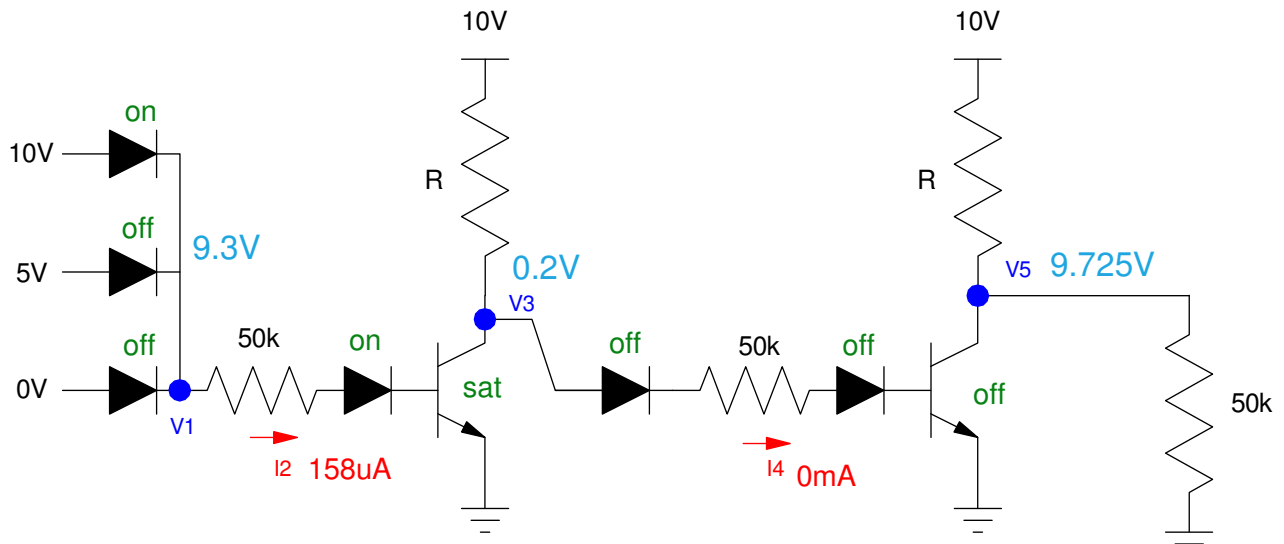

$$I_2 = \left(\frac{10V - 2.1V}{50k} \right) = 158\mu A$$


$$V_5 = \left(\frac{50k}{50k + 1414} \right) 10V = 9.725V$$

10V Open Collector Logic

5) Determine the voltages and currents for the following circuit. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $V_{be} = 0.7V$
- $\beta = 100$
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 900 + 100*mo +day	I1	I2	I3	V4
1414	0	172uA	172uA	0.2V

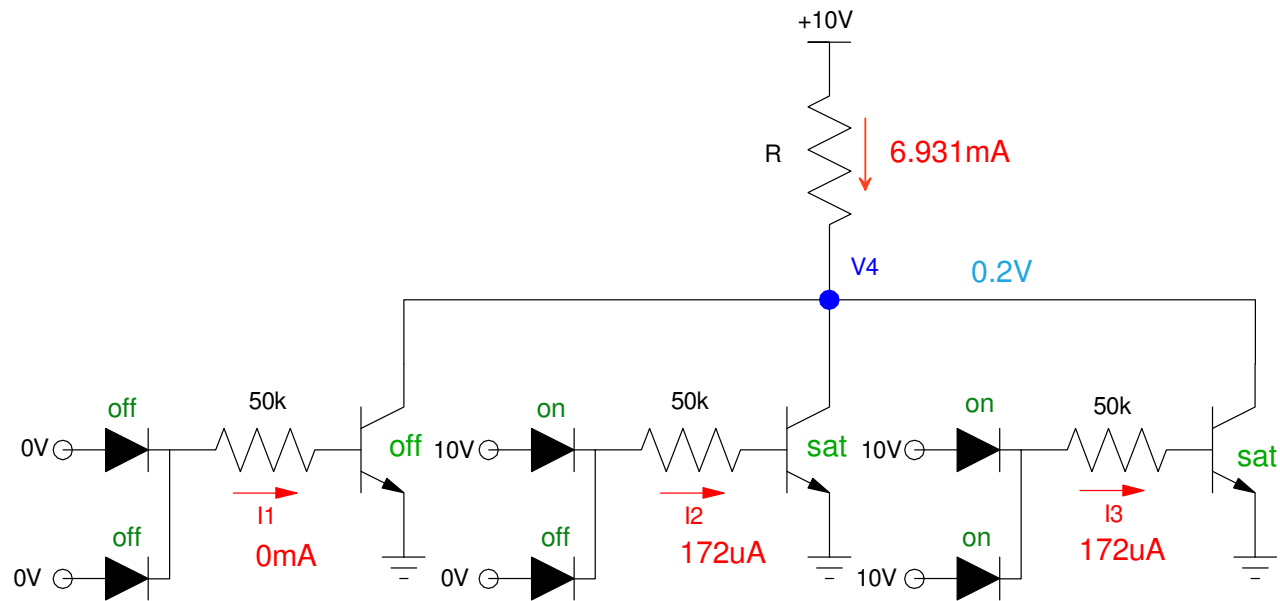

TTL Logic

6) Determine the voltages and currents for the following TTL gate. Assume

- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 100$)
- $R = 900 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 900 + 100*mo +day	V1	V2	V3	I4
1414	0.7V	0V .. 0.7V floating	9.861V	0mA

