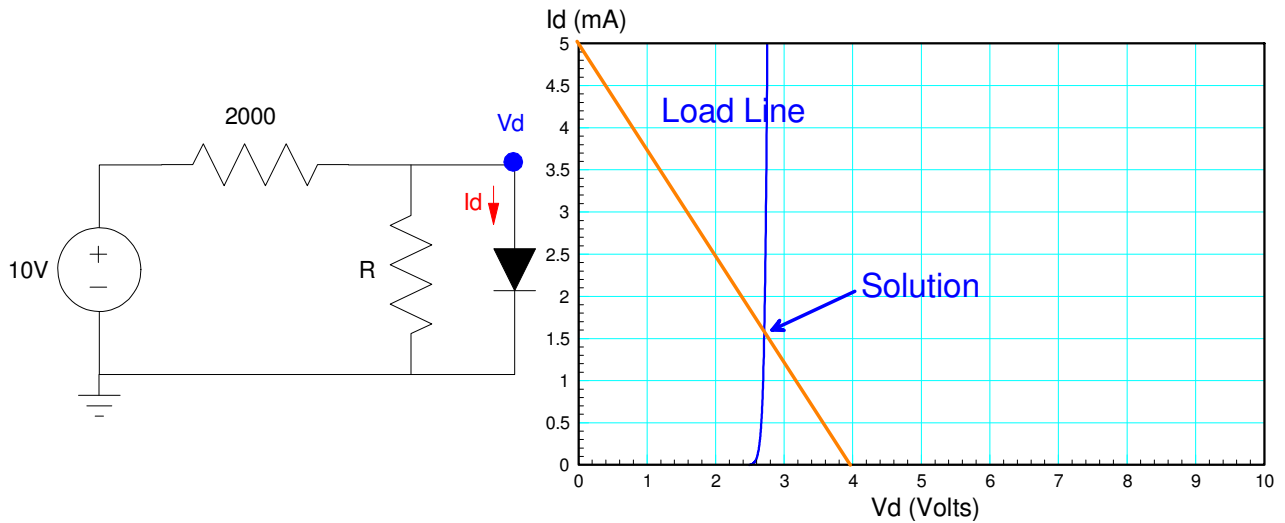


ECE 320 - Final (pt 1) - Name _____

Semiconductors & Diodes - Spring 2023

1) Load Lines: Assume the VI characteristics for the diode is as shown in the graph. Draw the load line for the following circuit and determine I_d and V_d . Assume $R = 800 + 100 * (\text{your birth month}) + (\text{your birth date})$.



R 800 + 100*mo + day	Load Line x-intercept (volts)	Load Line y-intercept (mA)	V_d Volts	I_d mA
1314	3.965V	5.00mA	2.7V	1.6mA

Convert to a Thevenin equivalent:

$$V_{th} = \left(\frac{1314}{1314 + 2000} \right) 10V = 3.965V$$

$$R_{th} = 2000 \parallel 1314 = 793.0\Omega$$

The load line is then

$$X_{int} = V_{th} = 3.965V$$

$$Y_{int} = V_{th} / R_{th} = 5.00mA$$


2) Nonlinear equations: Diode circuit

Assume the VI characteristics for the diodes shown below are

$$V_d = 0.038 \ln(10^{11} \cdot I_d + 1) \quad I_d = 10^{-11} \cdot \left(\exp\left(\frac{V_d}{0.038}\right) - 1 \right)$$

Write 6 equations to solve for 6 unknowns: $\{V_1, V_2, V_3, V_4, I_{d1}, I_{d2}, I_{d3}\}$.

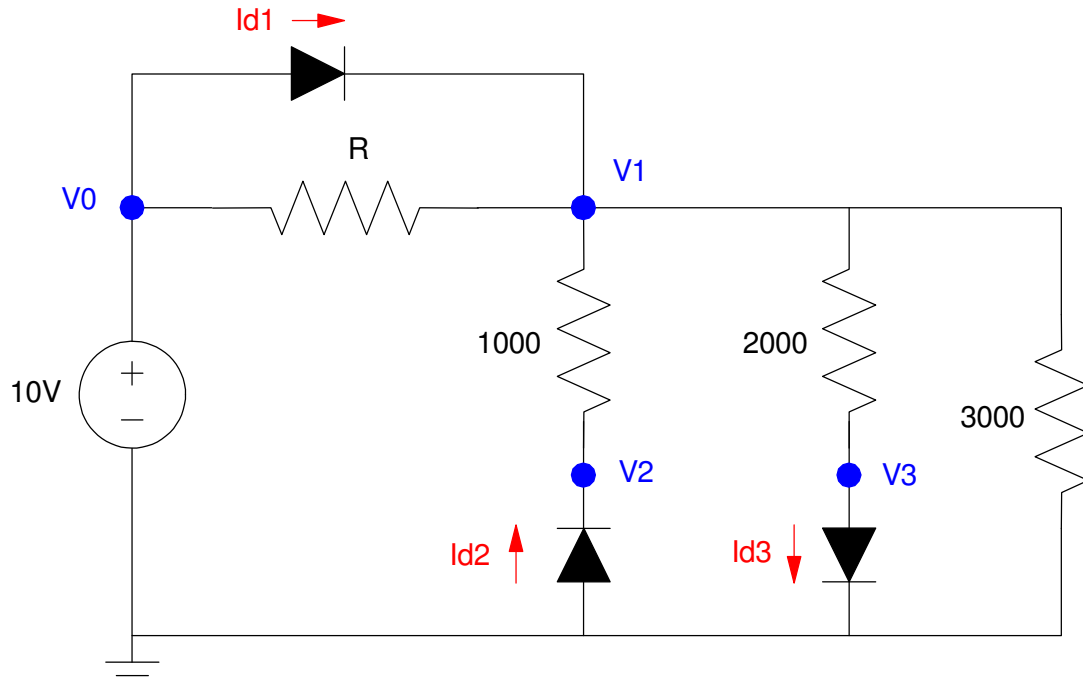- Note: you do not need to solve.
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{birth date})$.



Start with the diode equations

$$I_{d1} = 10^{-11} \cdot \left(\exp\left(\frac{V_0 - V_1}{0.038}\right) - 1 \right)$$

$$I_{d2} = 10^{-11} \cdot \left(\exp\left(\frac{0 - V_2}{0.038}\right) - 1 \right)$$

$$I_{d3} = 10^{-11} \cdot \left(\exp\left(\frac{V_3 - 0}{0.038}\right) - 1 \right)$$

$$V_0 = 10$$


$$-I_{d1} + \left(\frac{V_1 - V_0}{1314} \right) + \left(\frac{V_1 - V_2}{1000} \right) + \left(\frac{V_1 - V_3}{2000} \right) + \left(\frac{V_1}{3000} \right) = 0$$

$$\left(\frac{V_2 - V_1}{1000} \right) - I_{d2} = 0$$

$$\left(\frac{V_3 - V_1}{2000} \right) + I_{d3} = 0$$

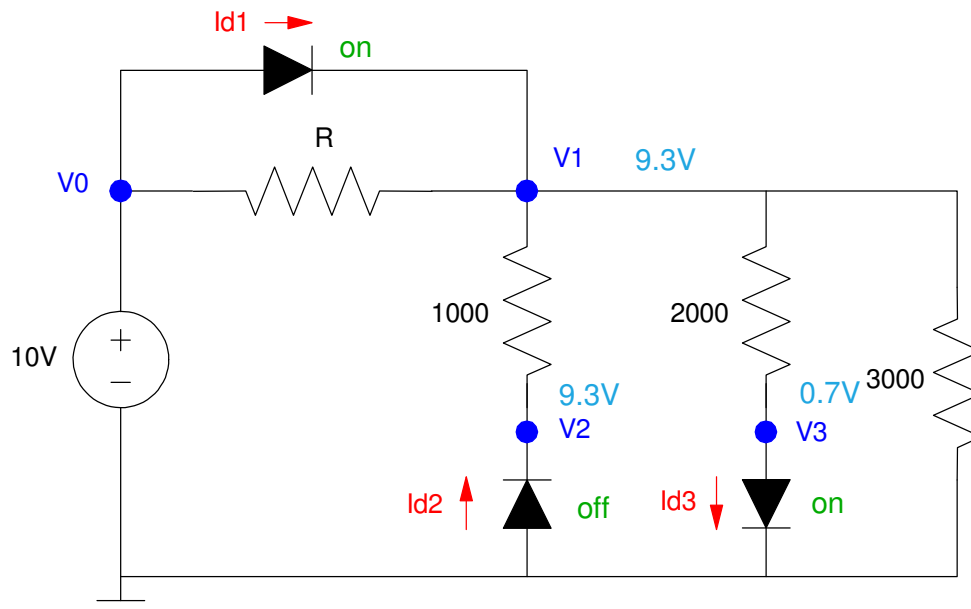3) Ideal Silicon Diodes. Assume the diodes in this circuit are ideal silicon diodes:

- $V_d = 0.7V$ $I_d > 0$
- $I_d = 0$ $V_d < 0.7V$
- $R = 800 + 100 * (\text{your birth month}) + (\text{birth date})$.




R 800 + 100*mo + day	I_{d1}	I_{d2}	I_{d3}
1314	6.867mA	0mA	4.30mA
	V_1	V_2	V_3
	9.30V	9.30V	0.70V

I_{d1} : Current In = Current Out

$$I_{d1} = \left(\frac{V_1 - V_0}{1314} \right) + 0 + \left(\frac{V_1 - V_3}{2000} \right) + \left(\frac{V_1}{3000} \right)$$

$$I_{d1} = 6.867mA$$

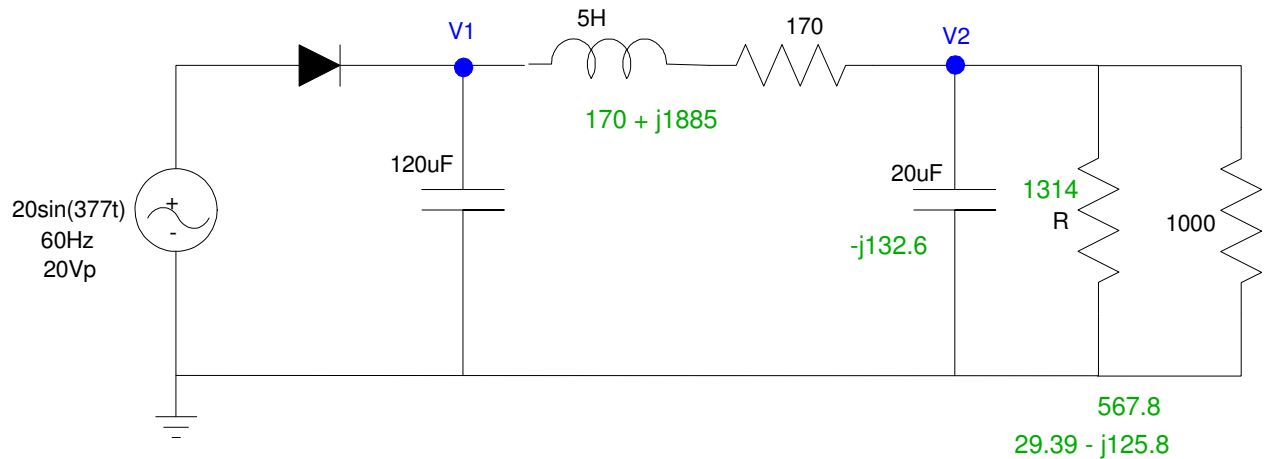4) AC to DC: Analysis: Determine V1 and V2 (both DC and AC) for the following AC to DC converter



R 800 + 100*mo + day	V1		V2	
	DC	AC	DC	AC
1314	17.48V	3.633Vpp	13.46V	0.265Vpp

$$I \approx \left(\frac{19.3V}{170+567.8} \right) = 26.16mA$$

$$I = C \frac{dV}{dt}$$

$$26.16mA = 120\mu F \cdot \frac{dV}{1/60s}$$

$$dV = V_1(AC) = 3.633V_{pp}$$

$$V_1(DC) = 19.3V - \frac{1}{2}V_{1pp} = 17.48V$$


$$V_2(DC) = \left(\frac{567.8}{567.8+170} \right) V_1(DC) = 13.46V$$

$$V_2(AC) = \left(\frac{(29.39-j125.8)}{(29.39-j125.8)+(170+j1885)} \right) V_1(AC)$$

$$|V_1(AC)| = 0.265V_{pp}$$

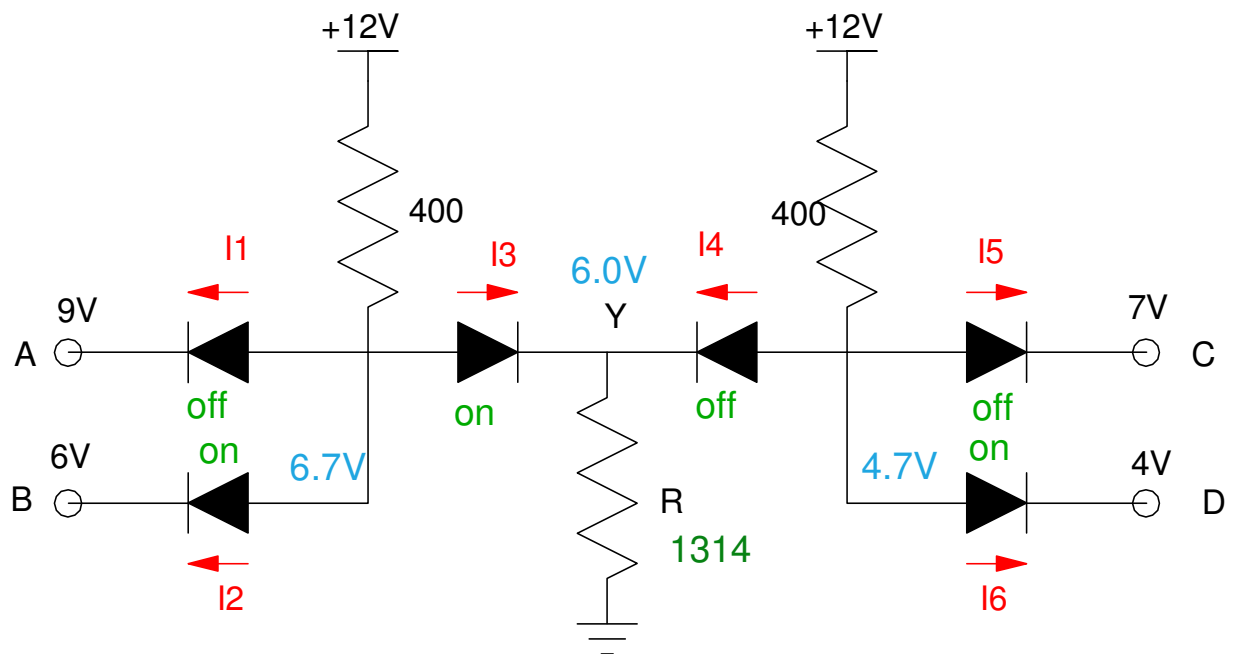5) Max/Min Circuits. Determine the currents $I_1 \dots I_6$. Assume

- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{birth date})$




R	I_1	I_2	I_3	I_4	I_5	I_6
$800 + 100 \cdot \text{mo day}$						
1314	0mA	8.684mA	4.566mA	0mA	0mA	18.25mA

$$I_6 = \left(\frac{12V - 4.7V}{400\Omega} \right) = 18.25mA$$

$$I_3 = \left(\frac{6V}{1314\Omega} \right) = 8.684mA$$

$$I_2 + I_3 = \left(\frac{12V - 6.7V}{400\Omega} \right) = 13.25mA$$

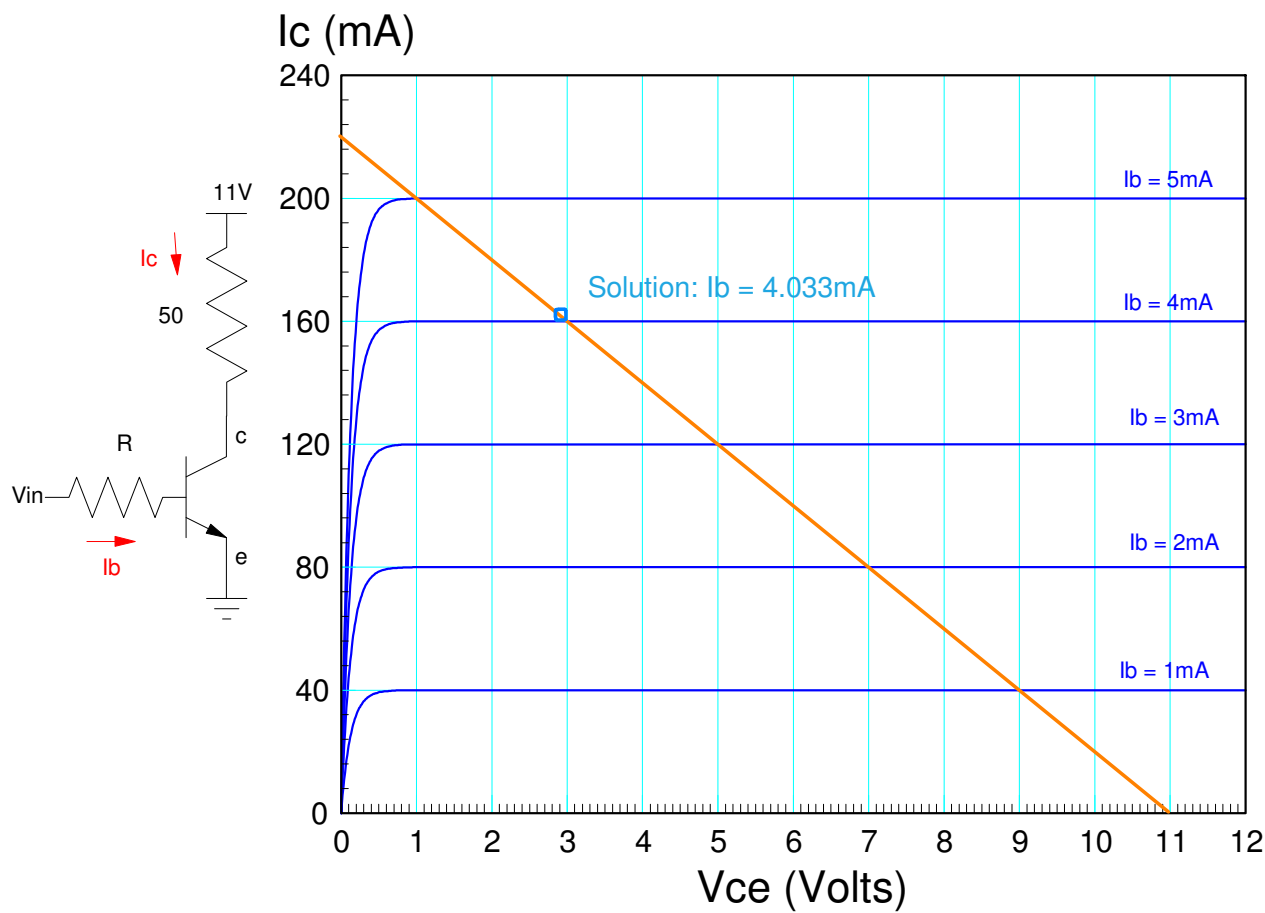6) Determine the current gain, β . Also draw the load line and determine the operating point when $V_{in} = 6V$




R 800 + 100*Mo + Day	Current Gain hfe = beta	Load Line x-intercept (Volts)	Load Line y-intercept (mA)	Vce Vin = 6V	Ic Vin = 6V
1314	40	11V	220mA	2.933V	161.33mA

7) Design a Schmitt Trigger & transistor switch so that

- Turns on the LED at 100mA when $R_t > 1500$ Ohms
- Turns off the LED when $R_t < 1300$ Ohms

Assume

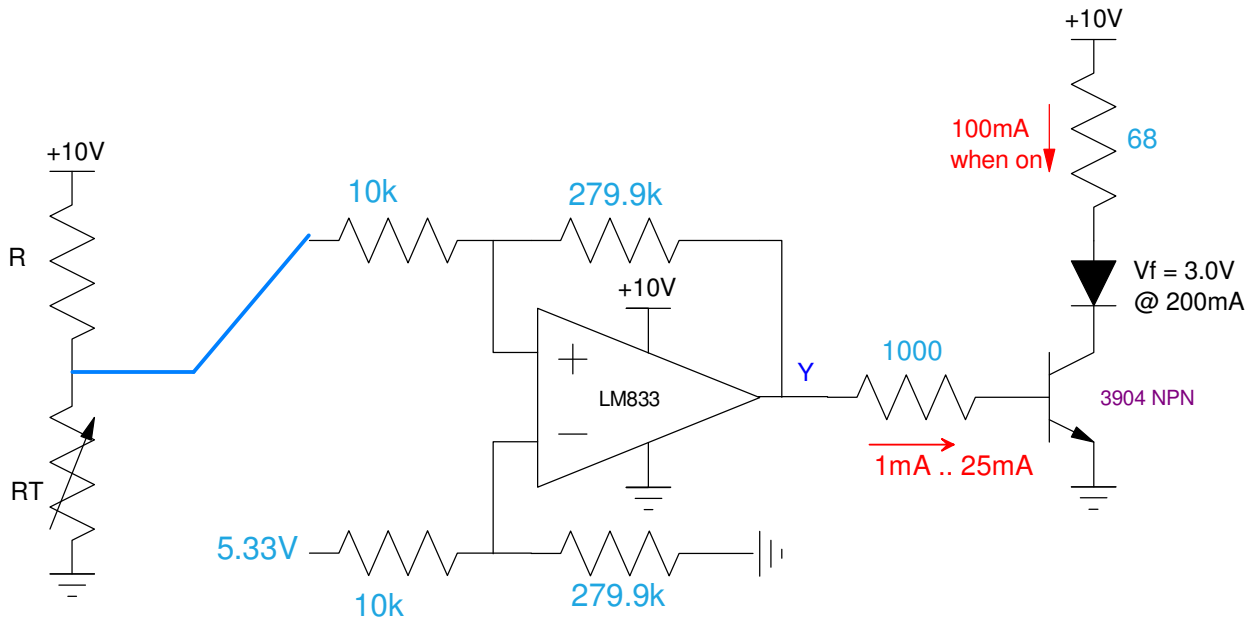- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$
- $V_{ce(sat)} = 0.2V$
- Current gain (β) = 100



$R_t = 1500$ (on)

$$V_a = \left(\frac{1500}{1500 + 1314} \right) 10V = 5.33V$$

$R_t = 1300$ (off)

$$V_a = \left(\frac{1300}{1300 + 1314} \right) 10V = 4.793V$$

$V(\text{on}) > V(\text{off})$

- connect to the plus input

$V(\text{on}) = 5.33V$

- offset = 5.33V

Gain:

$$\text{gain} = \left(\frac{10V - 0V}{5.33V - 4.793V} \right) = 27.99$$


R_c :

$$I_c = 100mA = \left(\frac{10V - 3.0V - 0.2V}{R_c} \right)$$

$$R_c = 68\Omega$$

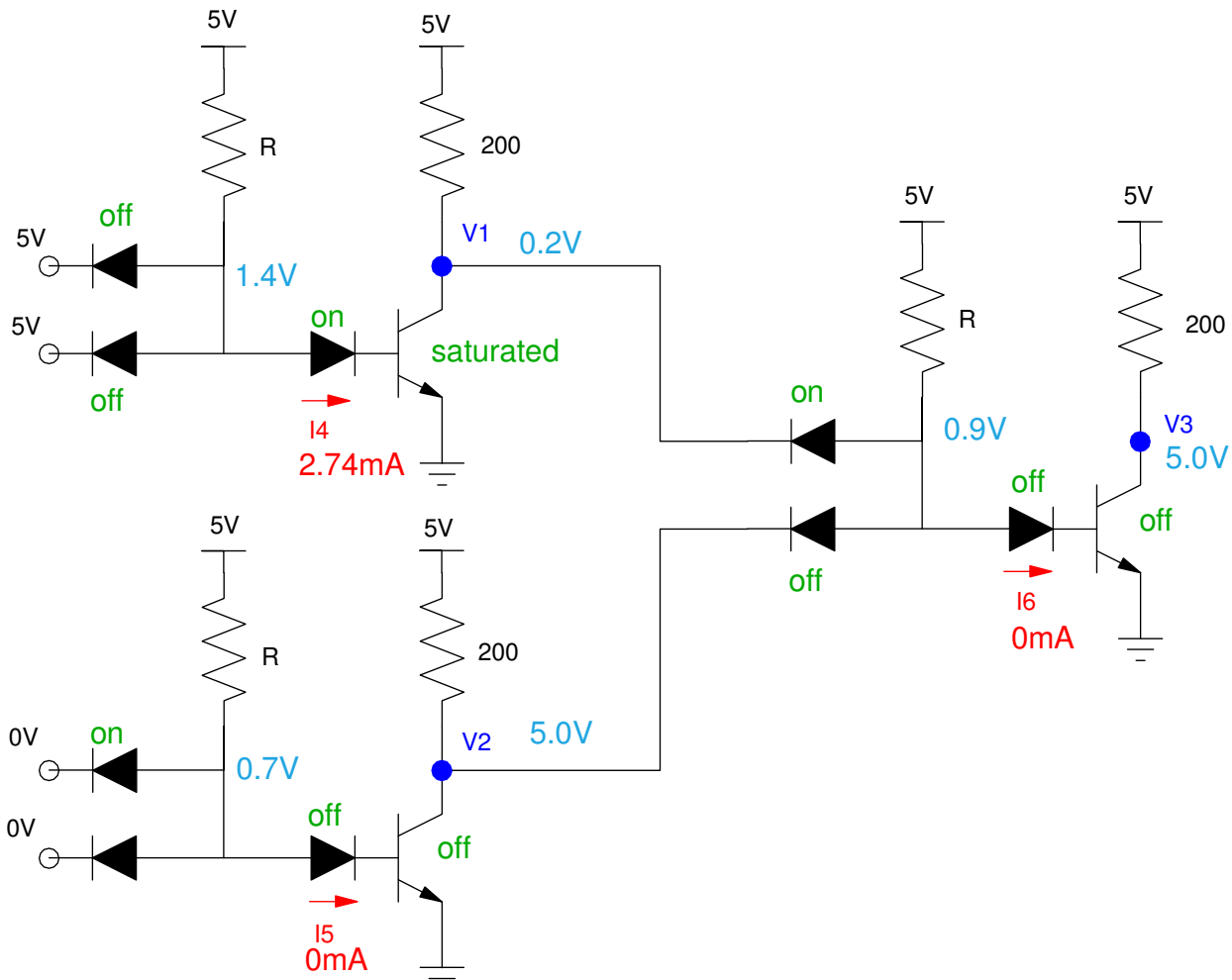8) DTL Logic: Determine the voltages and currents for the following DTL logic gage. Assume


- $R = 800 + 100 \cdot (\text{your birth month}) + (\text{birth day})$
- Ideal silicon diodes ($V_f = 0.7V$), and
- Ideal 3904 transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, $\beta = 100$)



R 800 + 100*mo + da	V1	V2	V3	I4	I5	I6
1314	0.2V	5.0V	5.0V	2.74mA	0mA	0mA

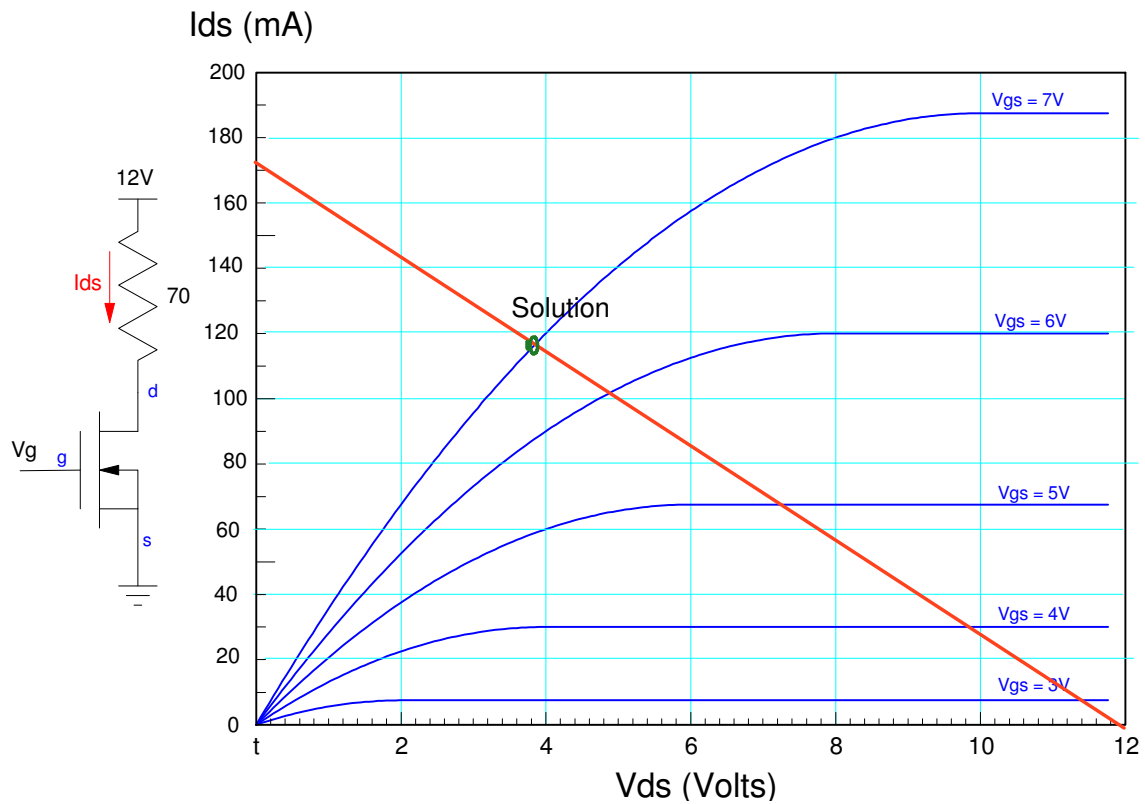9) MOSFET Load Line: For the following MOSFET circuit

- Determine the transconductance gain, k_n ,
- Draw the load line (x and y intercept), and
- Determine $\{V_{ds}, I_{ds}\}$ when $V_g = 7V$. (note: $V_{th} = 2V$)



k_n transconductance gain	Load Line x=intercept	Load Line y intercept	V_{ds} $V_g = 7V$	I_{ds} $V_g = 7V$	Operating Region off / active / ohmic
15.2 mA/V²	12V	171mA	3.8V	115mA	Ohmic

In the saturated region

$$I_{ds} = \frac{k_n}{2}(V_{gs} - V_{th})^2$$

$$190mA = \frac{k_n}{2}(7V - 2V)^2$$

$$k_n = 15.2 \frac{mA}{V^2}$$

10) CMOS Logic

Design a CMOS logic gate to implement $Y=f(A,B,C,D)$

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	x	0	x	1
	11	1	0	0	x
	10	1	1	0	0

Circle the zeros:

$$\bar{Y} = AC + BD + \bar{A}\bar{C}D$$

Using DeMorgan's Law

$$Y = (\bar{A} + \bar{C})(\bar{B} + \bar{D})(A + C + \bar{D})$$

