

ECE 320 - Quiz #5 - Name _____

555 Timers, Transistor Switch, Comparitors, Schmitt Triggers - Spring 2023


1) 555 Timers. Determine R1, R2, and C so that the 555 timer outputs a 20% duty cycle 220Hz square wave:

$$t_{on} = (R_1 + R_2) \cdot C \cdot \ln(2) = 2.000ms$$

$$t_{off} = R_2 \cdot C \cdot \ln(2) = 8.000ms$$

Let R1 be your birthday day (800 + 100*Month + Day)

R1 800 + 100*Month + Day	R2	C 800 + 100*Month + Day (uF)
-6.5876 Ohms or not possible with this circuit	8.7835	1314 uF

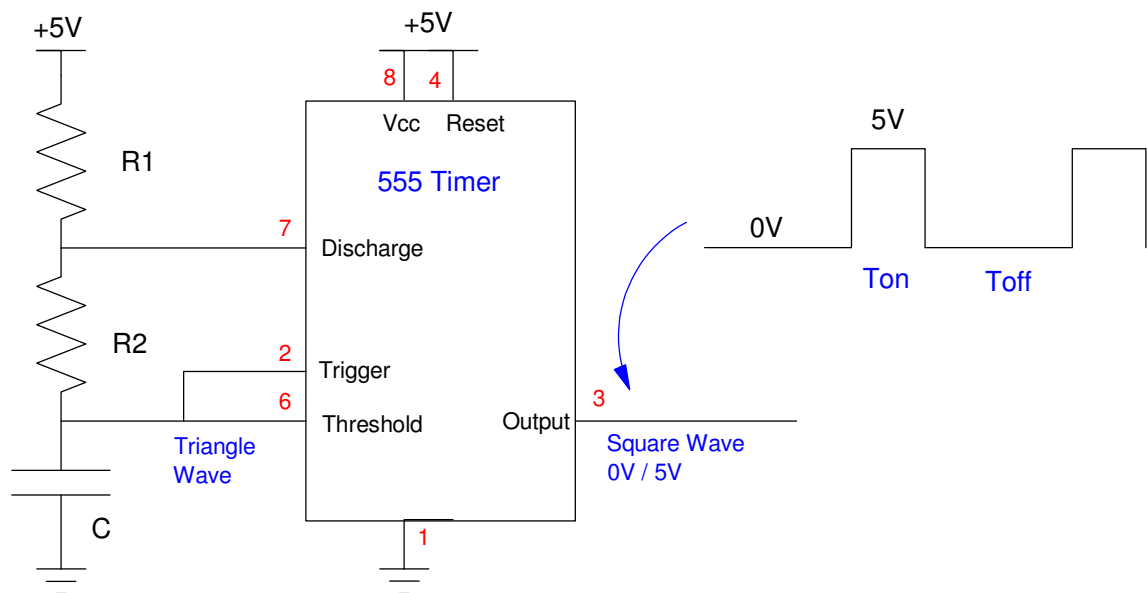

$$R_2 \cdot C \cdot \ln(2) = 8.000ms$$

$$R_2 = 8.7835\Omega$$

$$(R_1 + R_2) \cdot C \cdot \ln(2) = 2.000ms$$

$$R_1 + R_2 = 2.1959\Omega$$


2) Transistor Switch: Design. Specify R1 and R2 so that when $V_{in} = 5.00V$,

- $I_c = (800 + 100 \cdot \text{Birth Month} + \text{Birth Day}) \text{ mA}$.
- The transistor is saturated, and
- $I_b < 25\text{mA}$ (the maximum output of a 555 timer)

Assume 6144 transistors

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$ when saturated
- $\beta = 200$

$I_c \text{ (mA)}$ $800 + 100 \cdot (\text{Mo}) + (\text{Day})$	R_c	min value of R_b	max value of R_b
1314 mA	8.9802 Ohms	172 Ohms	654.49 Ohms

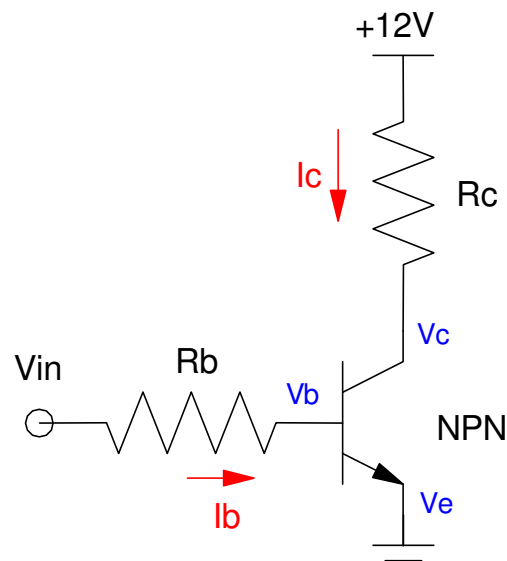

$$R_c = \left(\frac{12V - 0.2V}{1314mA} \right) = 8.9802\Omega$$

$$\min(I_b) = \left(\frac{I_c}{\beta} \right) = \left(\frac{1314mA}{200} \right) = 6.57mA$$

$$R_b = \left(\frac{5V - 0.7V}{6.57mA} \right) = 654.49\Omega$$

$$\max(I_b) = 25mA$$

$$R_b = \left(\frac{5V - 0.7V}{25mA} \right) = 172\Omega$$

3) Darlington Pair (analysis). Assume two 6144 NPN transistors are connected as a Darlington pair.

- $|V_{be}| = 0.7V$
- $|V_{ce}| = 0.2V$ when saturated
- $\beta = 200$

Let R_b be $800 + 100(\text{Birth Month}) + \text{Birth Day}$. Find the currents and voltages.

R_b 800 + 100*Mo + Day	I_1	I_2	I_3
1314 Ohms	2.7397mA	6.9166mA	1.3833A
	V_1	V_2	V_3
	1.4V	0.7V	0.9V

$$I_1 = \left(\frac{5V-1.4}{1314\Omega}\right) = 2.7397mA$$

$$I_3 + I_5 = I_4 = \left(\frac{12V-0.9V}{8\Omega}\right) = 1.3875A$$


$$I_2 = I_1 + I_5$$

$$I_3 = 200I_2$$

Solving

$$I_2 = 6.9166mA$$


$$I_3 = 1.3833A$$

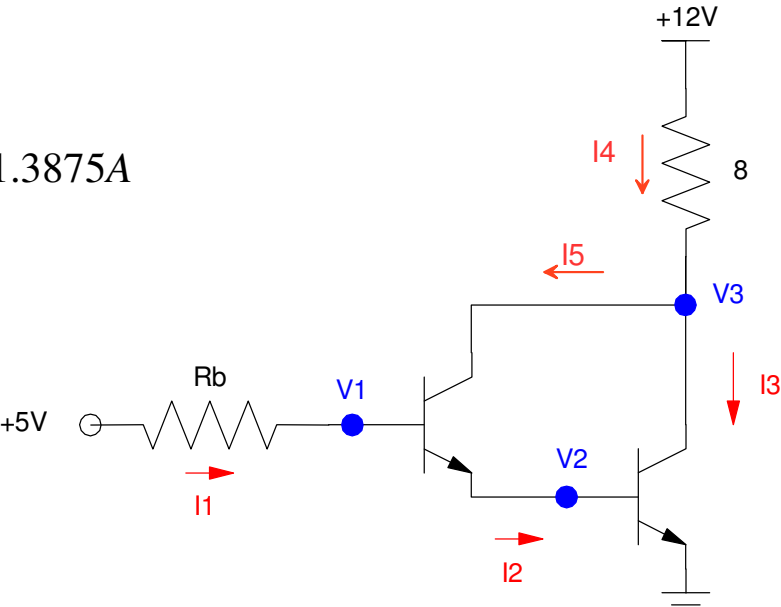

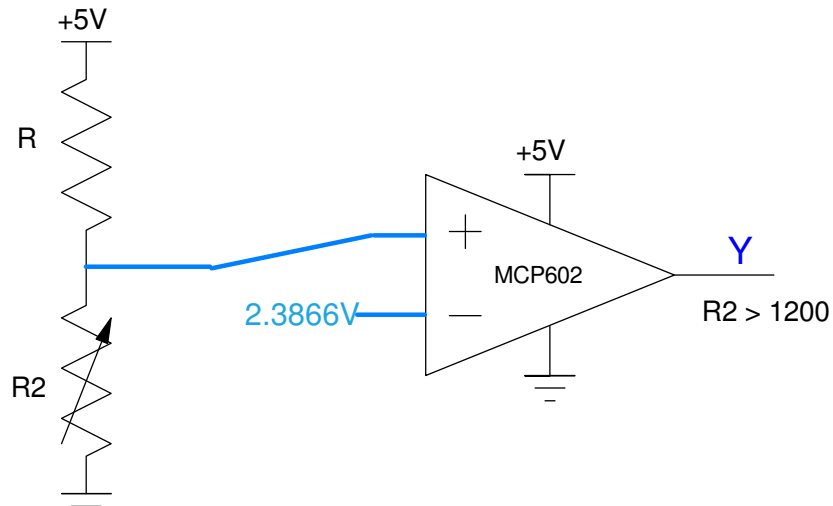4) Comparitor: Design a circuit which output

- 5V when $R2 > 1200$ Ohms
- 0V when $R2 < 1200$ Ohms

where R is $800 + 100 * (\text{Birth Month}) + (\text{Birth Day})$.



$R = 1314$ Ohms

$$V = \left(\frac{1200}{1200 + 1314} \right) 5V = 2.3866V$$

For $R2 = \text{large}$ (1M Ohm)


- V goes to 5V
- Y = 5V

Connect to the plus input

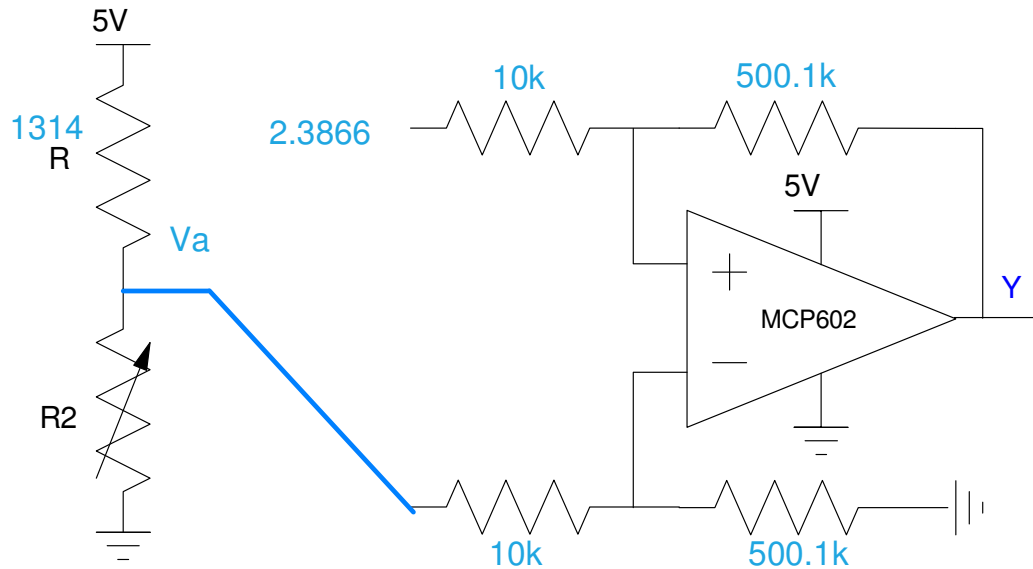5) Schmitt Trigger: Design a circuit which output

- 5V when $R < 1200$ Ohms
- 0V when $R > 1300$ Ohms
- No change for $1200 < R < 1300$ Ohms

Let R be $800 + 100(\text{Birth Month}) + (\text{Birth Date})$.



$R = 1314$ Ohms

$R2 = 1200$ Ohms ($Y = 5V$)

$$V_a = \left(\frac{1200}{1200+1314} \right) 5V = 2.3866V$$

$R2 = 1300$ Ohms ($Y = 0V$)

$$V_a = \left(\frac{1300}{1300+1314} \right) 5V = 2.4866V$$

$V(\text{on}) < V(\text{off})$

connect to the minus input

$V(\text{on}) = 2.3866V$


offset = 2.4866V

Gain:

$$\text{gain} = \left(\frac{5V-0V}{2.4866V-2.3866V} \right) = 50.01$$

6) Schmitt Trigger: Analysis. Determine the voltages and resistance where the following Schmitt trigger turns on and off. Assume Rx is $800 + 10 \cdot (\text{Birth Month}) + (\text{Birth Day})$.

R $800 + 100 \cdot \text{Mo} + \text{Day}$	On ($V_2 = +5V$)		Off ($V_2 = 0V$)	
1314	V1	R2	V1	R2
	3.2V	2336 Ohms	4.2V	6898 Ohms

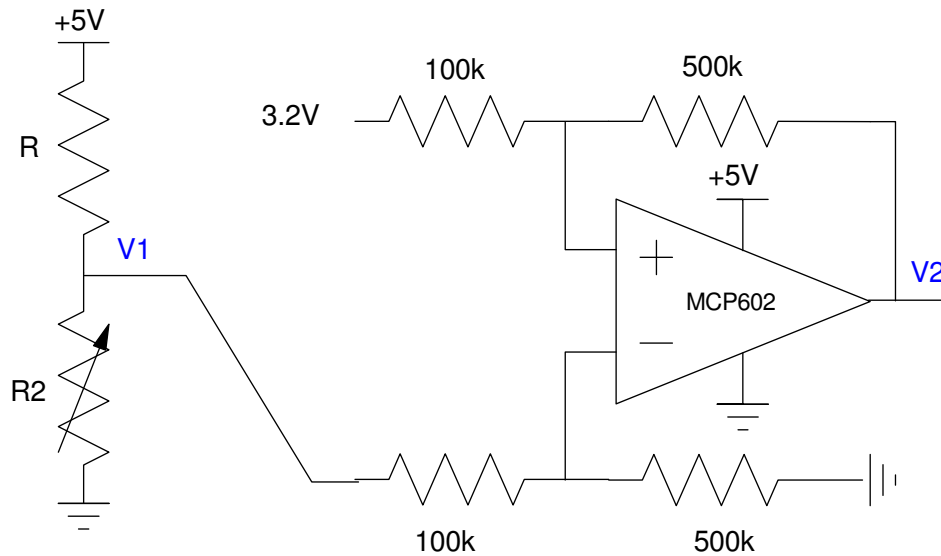

$$V(\text{on}) = 3.2V$$

Offset is the on-voltage

$$3.2V = \left(\frac{R_2}{R_2 + 1314} \right) 5V$$

$$R_2 = 2336.0\Omega$$

$$V(\text{off}) = 4.2V$$

$V(\text{on}) < V(\text{off})$ when connected to the minus input

$$\text{gain} = 5 = \left(\frac{5V - 0V}{V(\text{off}) - 3.2V} \right)$$

$$4.2V = \left(\frac{R_2}{R_2 + 1314} \right) 5V$$

$$R_2 = 6898.5\Omega$$