

ECE 320 - Quiz #7 - Name _____


DTL, TTL Logic - Spring 2023

DTL: 10V Logic Logic

1) Determine the voltages and currents for the following DTL gate. Assume

- Ideal transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 800 + 100*mo +day	V1	I2	V3	I4	V5

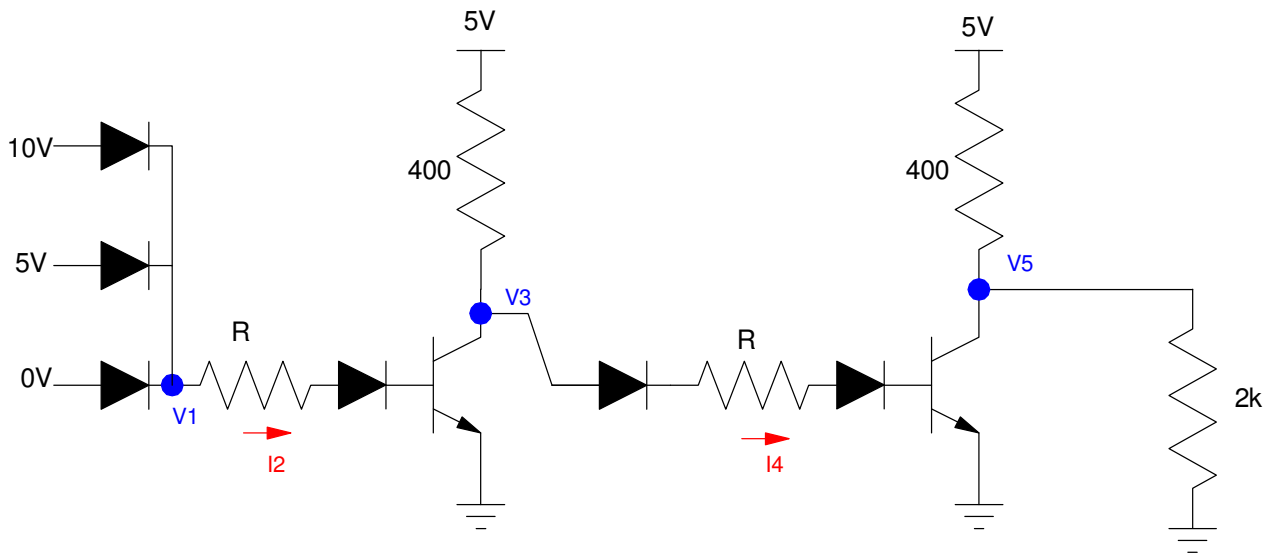


DTL 10V Logic Gate:

2) Determine the voltges and currents for the following DTL gate. Assume

- Ideal transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 800 + 100*mo +day	V1	I2	V3	I4	V5

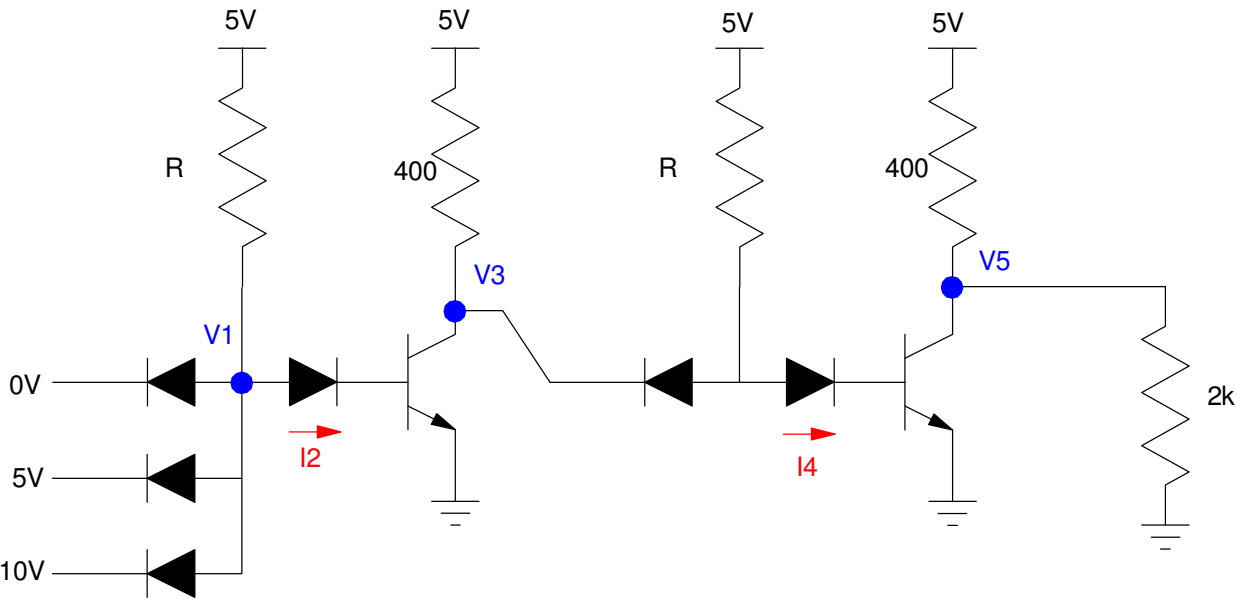


10V Open Collector Logic

3) Determine the voltages and currents for the following circuit. Assume

- Ideal transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 800 + 100*mo +day	I1	I2	I3	V4

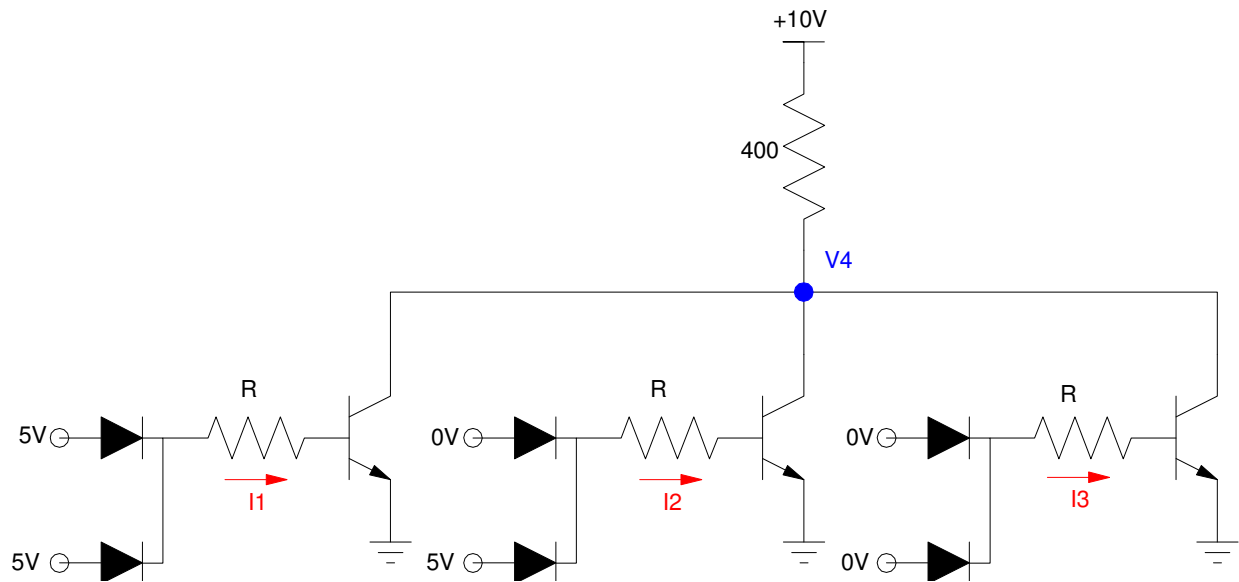


TTL Logic

4) Determine the voltges and currents for the following TTL gate. Assume

- Ideal transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R 800 + 100*mo +day	V1	V2	V3	I4

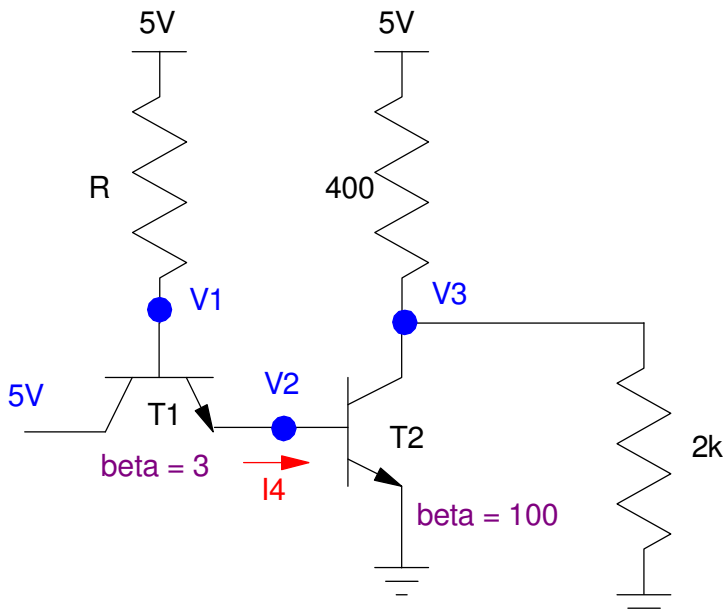


DTL Logic

5) Determine the voltages and currents when $V_0 = 4V$. Assume

- Ideal transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
- Ideal silicon diodes ($V_f = 0.7V$)
- $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R	V1	V2	V3	I4	I5
800 + 100*mo +day					

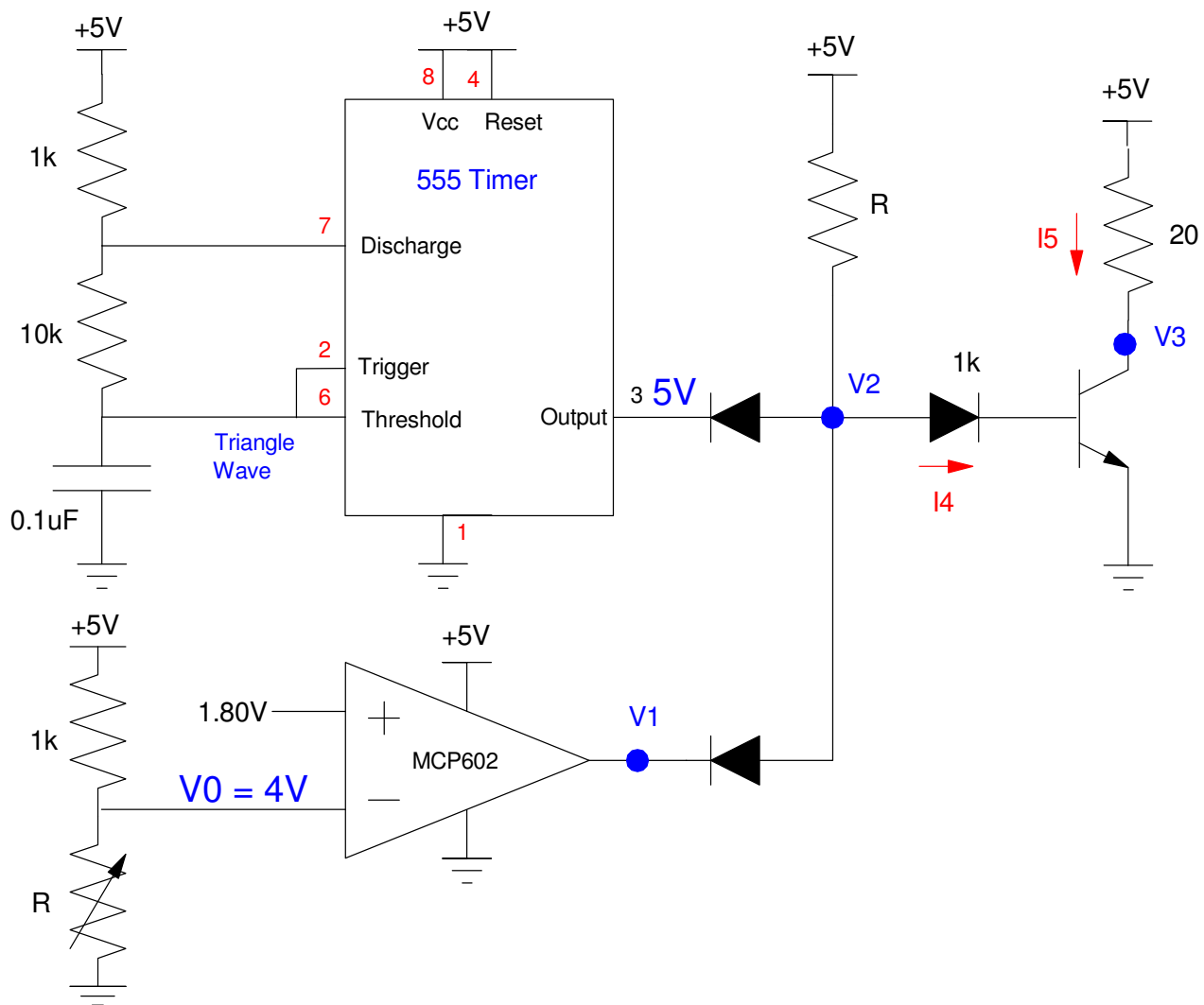

DTL Logic

- 6) Determine the voltages and currents when $V_0 = 1V$. Assume
- Ideal transistors ($V_{be} = 0.7V$, $V_{ce(sat)} = 0.2V$, gain = 100)
 - Ideal silicon diodes ($V_f = 0.7V$)
 - $R = 800 + 100(\text{Birth Month}) + (\text{Birth Day})$.

R	V1	V2	V3	I4	I5
800 + 100*mo +day					

