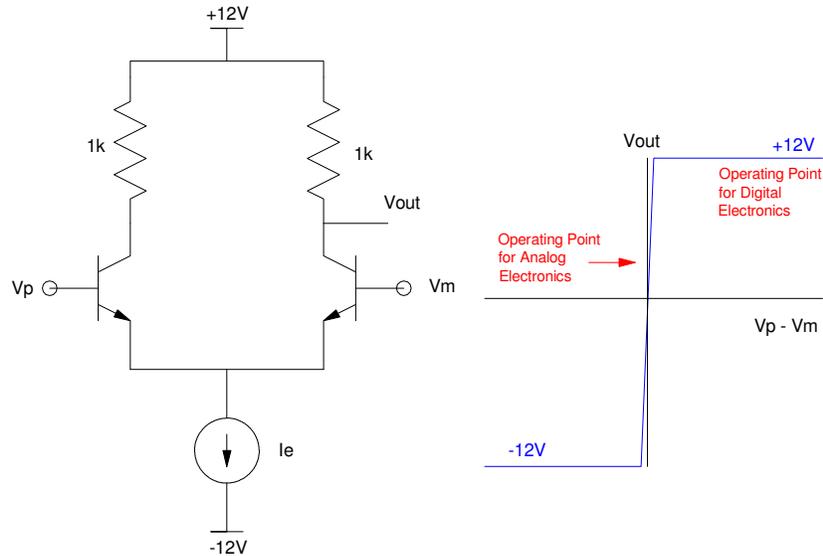


Operational Amplifiers

Operational Amplifiers (Op-Amps) are high gain differential amplifiers. The heart of an op-amp is a pair of transistors implementing emitter-coupled logic:




In ECE 320, we wanted binary outputs: a motor is either 100% on or 0% on (i.e. off). Likewise, we operated the transistors at the rails: either $+5V$ for logic 1 or $0V$ for logic 0. Towards this end, the transistors we used were always off or saturated.

In ECE 321, we want analog outputs: a motor can be 30% on or we could apply a sine wave to a speaker (as opposed to a square wave). To do this, we will be using transistor in the active region and using op-amps in the high-gain region (where $V_p - V_m \approx 0V$).

When operating in the high-gain region, an op-amp can be modeled as a 2-input device with

$$V_o \approx k(V^+ - V^-)$$

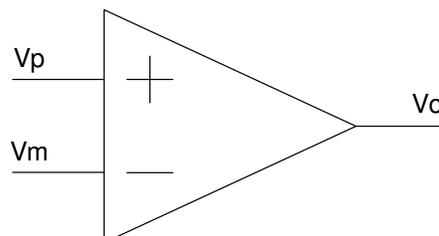where k is a large number. For short, the following symbol is used for an differential amplifier:




Symbol for an operational amplifier (op-amp)

Operational Amplifier Characteristics

Op-Amps usually come in two packages:

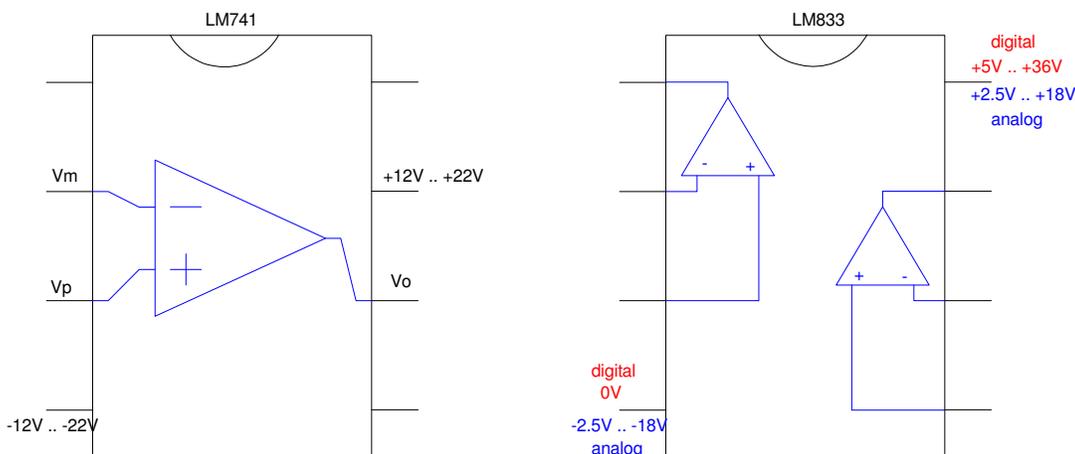- A single op-amp per package (left), or
- Two op-amps per package



Pin Layout for two common op-amps: LM741 and LM833
 The LM833 works for both digital electronics and analog electronics.

If you look up the data sheets for these, you get something like the following:

	LM741	LM833 use this one	Ideal
Input Resistance	2M Ohms	1G Ohm	infinite
Current Out (max)	25mA	50mA	infinite
Operating Voltage	+/- 12V .. +/- 22V	+/- 2.5V .. +/- 15V	any
Differential Mode Gain	200,000	310,000	infinite
Common Mode Rejection Ratio	90dB	100dB	common mode gain = 0
Slew Rate	0.5V/us	7V/us	infinite
Gain Bandwidth Product	1.5MHz	15MHz	infinite
Price (qty 100)	\$0.35	\$0.52	-

Input resistance: The input of the op-amp does draw some current. If you keep the currents involved much larger (meaning at 1V, resistors are less than 50M Ohm), you can ignore the current into V+ and V-.

Current Out (max): These op-amps can drive 1k Ohms at 10V (10mA), but they can't drive an 8-Ohms speaker (too much current).

Operating Voltage: Options for the power supply.

- LM741 op-amps need +12V and -12V to operate (they don't work for digital electronics)
- LM833 op-amps can operate single sided (0..5V, 0..10V) for digital electronics or dual power supplies (-5V..+5V, or -10V to +10V) for analog electronics.

Differential Mode Gain: The gain from $(V_+ - V_-)$ to the output

Common Mode Rejection Ratio: The gain from $(V_+ + V_-)$ is this much less than the differential mode gain. Note that

$$dB = 20 \cdot \log_{10}(\text{gain})$$

Slew Rate: The output can't change from $-10V$ to $+10V$ in zero time. It can only ramp up this fast.


Gain Bandwidth Product: The gain times the bandwidth is this number. For an LM833 (15MHz), you can have a

- Gain of 1.00 out to 15MHz
- Gain of 100.0 out to 150kHz

Note that this means for audio applications (20-20kHz) you need to keep the gain of each op-amp less than 750.

Operational Amplifier Circuit Analysis

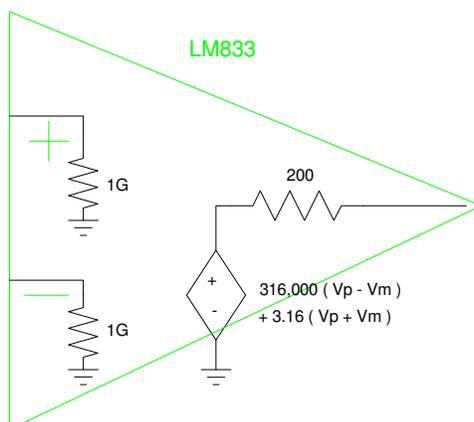
When you have an op-amp in a circuit, you essentially have a voltage controlled voltage source. For an LM833 op-amp, for example, it's circuit model is:



Circuit Model for an LM833.


Using this model, you can determine the voltages for an op-amp circuit.

Example: Determine the voltages for the following op-amp circuit.

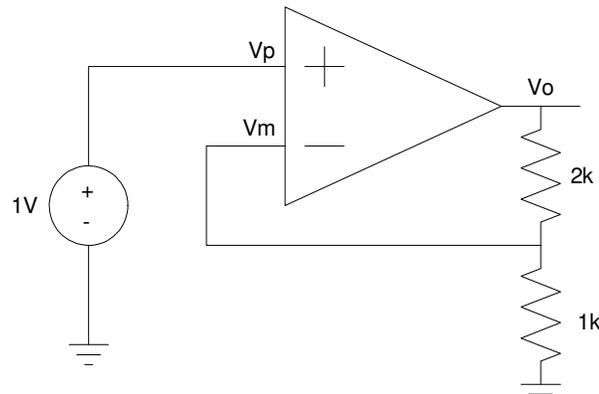

Case 1: LM833 Op-Amp.

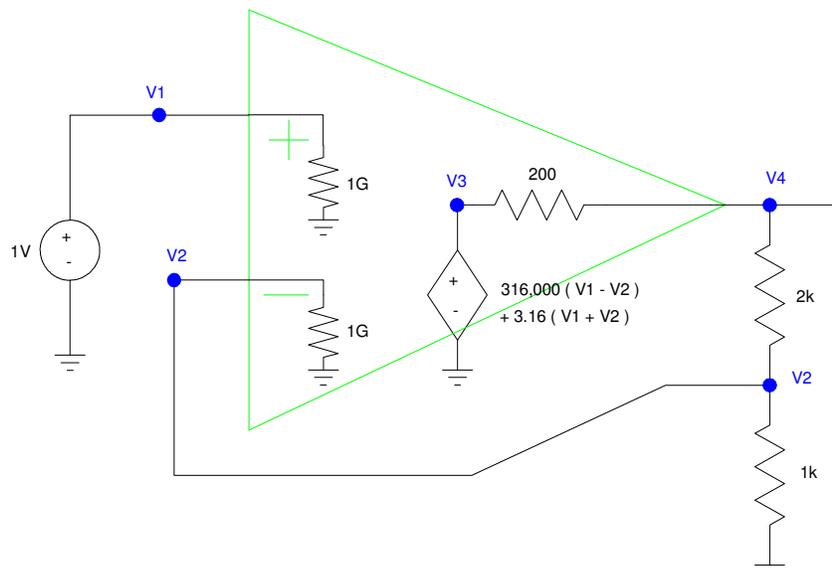Replace the op-amp with its circuit model



Write the voltage node equations:

$$V_1 = 1$$

$$\left(\frac{V_2}{1G}\right) + \left(\frac{V_2 - V_4}{2k}\right) + \left(\frac{V_2}{1k}\right) = 0$$

$$V_3 = 316,000(V_1 - V_2) + 3.16(V_1 + V_2)$$

$$\left(\frac{V_4 - V_3}{200}\right) + \left(\frac{V_4 - V_2}{2000}\right) = 0$$

Solve in Matlab:

```
A = [1, 0, 0, 0; 0, 1/1e9+1/2000+1/1000, 0, -1/2000 ;
316003.16, -316003.16, -1, 0; 0, -1/2000, -1/200, 1/2000+1/200]
```

```
1.      0.      0.      0.
0.      0.0015000  0.      - 0.0005
316003.16  - 316003.16  - 1.      0.
0.      - 0.0005  - 0.005  0.0055
```

```
B = [1; 0; 0; 0]
```

```
1.
0.
0.
0.
```

```
V = inv(A)*B
```

```
V1      1.
V2      0.9999899
V3      3.1999698
V4      2.9999716
```

Case 2: Ideal Op-Amp

Note that

$$V_o = 316,000(V_p - V_m)$$


Assuming the output is finite, this means that

$$V_p \approx V_m.$$

In the case where the gain goes to infinity (ideal op-amp), you get

$$V_p = V_m.$$

Also, the 1G Ohm input impedance is so large that the current to the + and - inputs is negligible.

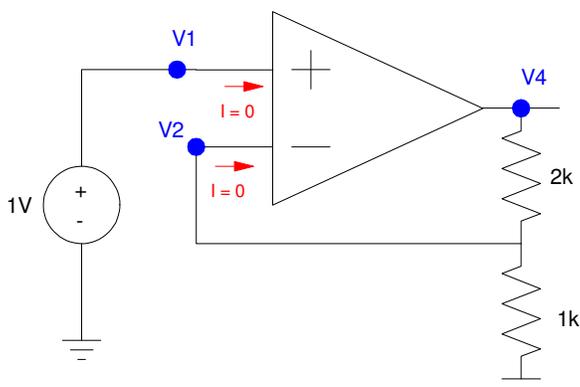

Case 2: Replace the op-amp with an ideal op-amp

Assuming an ideal op-amp, the voltage node equations become:

$$V_1 = 1$$

$$V_1 = V_2$$

$$\left(\frac{V_2}{1k}\right) + \left(\frac{V_2-V_4}{2k}\right) = 0$$

Solving results in

	Ideal OpAmp	LM833
V1	1.	1.
V2	1.	0.9999899
V3	n/a	3.1999698
V4	3.000000	2.9999716

Note:

- The results are almost identical. You have to go out to the 6th decimal place to see the difference.
- It's a *lot* easier to use the ideal op-amp model.
- If you use a different op-amp, the results will be about the same. The ideal op-amp model is a close approximation for an op-amp under most conditions.

note: "Most" means

- *You keep impedances less than 10M Ohms (so you can ignore the 1G input impedance), and*
- *You keep impedances more than 200 Ohms (so you draw less than 50mA)*

Likewise, from here on, we'll be assuming ideal op-amps. If your results are slightly different from what CircuitLab gives you, it's because CircuitLab uses the model for an LM833 (or whatever op-amp you're using).

Voltage Nodes with Op-Amps

With op-amp circuits, you almost always use voltage nodes. With voltage nodes, you write N equations for N unknowns. The trick with op-amps is the voltage node equation at the output is


- $V_p = V_m$

You do this for two reasons:

- (1) If you have negative feedback (i.e. are analyzing an amplifier as opposed to a Schmitt trigger), the high gain will force V_m to be close to V_p . Otherwise, the output would rail at the power supply.
- (2) You can't write the voltage node equation at V_o . The op-amp is an active device and will source or sink as much current as needed to force V_m to match V_p . If you try to write the voltage node equation at V_o , the current from the op-amp is "as much as needed." That doesn't help when writing voltage node equations.

Example 2: Assume ideal op-amps

- Write the voltage node equations for the following op-amp circuit
- Find the voltages

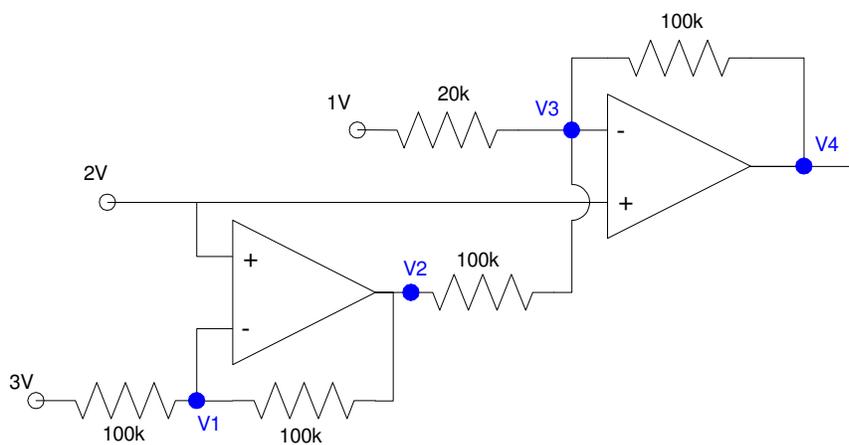

Example 2: Find the voltages

There are four unknown voltage nodes. We need to write 4 equations to solve for 4 unknowns. Start with the easy ones. For ideal op-amps with negative feedback

$$V_p = V_m$$

meaning

$$V_1 = 2V \quad (1)$$

$$V_3 = 2V \quad (2)$$

Now write two more equations. It's tempting, but you can't write the node equations at V_2 or V_4

- Equation (1) and (2) *are* the node equations at the outputs - you've already done that.
- You don't know the current from the op-amp - meaning you can't sum the currents to zero.

Instead, find two mode nodes where you *can* sum the currents to zero: nodes V1 and V3.

$$\left(\frac{V_1-3}{100k}\right) + \left(\frac{V_1-V_2}{100k}\right) = 0 \quad (3) \quad * 100k \text{ to clear the denominator}$$

$$\left(\frac{V_3-V_2}{100k}\right) + \left(\frac{V_3-1}{20k}\right) + \left(\frac{V_3-V_4}{100k}\right) = 0 \quad (4) \quad * 100k \text{ to clear the denominator}$$

Solving

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 2 & -1 & 0 & 0 \\ 0 & -1 & 7 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 2 \\ 2 \\ 3 \\ 5 \end{bmatrix}$$

In Matlab:

```
>> A = [1,0,0,0 ; 0,0,1,0 ; 2,-1,0,0 ; 0,-1,7,-1]
```

```

1      0      0      0
0      0      1      0
2     -1      0      0
0     -1      7     -1
```

```
>> B = [2;2;3;5]
```

```

2
2
3
5
```


```
>> V = inv(A)*B
```

```

V1      2
V2      1
V3      2
V4      8
```

This checks with the CircuitLab

V(V1)	2.000 V		
V(V2)	1.000 V		
V(V3)	2.000 V		
V(V4)	8.000 V		

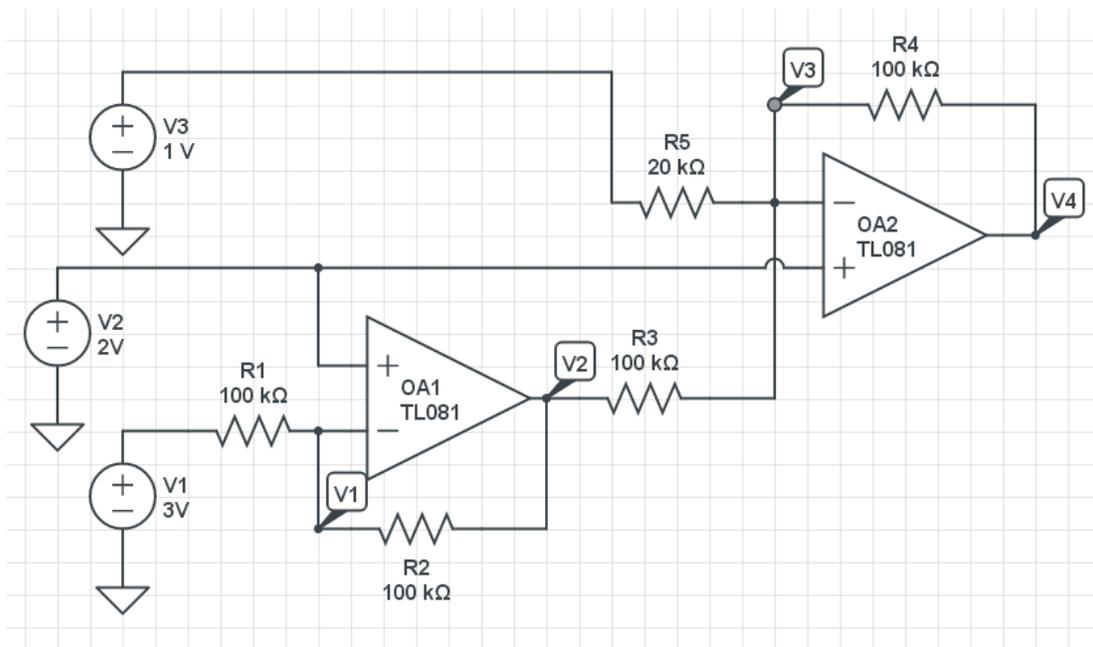


CircuitLab results for example 2: The voltagess match our computations.

Note the following:

- You don't need to use the op-amps with the +/- power supplies. For analog circuits, the output should be finite (i.e. a voltage in the range of -10V to +10V). As long as the power supply allows this (i.e you're using enough voltage to drive the output), the power supply doesn't matter.
- Using the wrong op-amp (TL081 instead of an LM833) is also OK. They both behave like an ideal op-amp (and likewise have almost identical results).

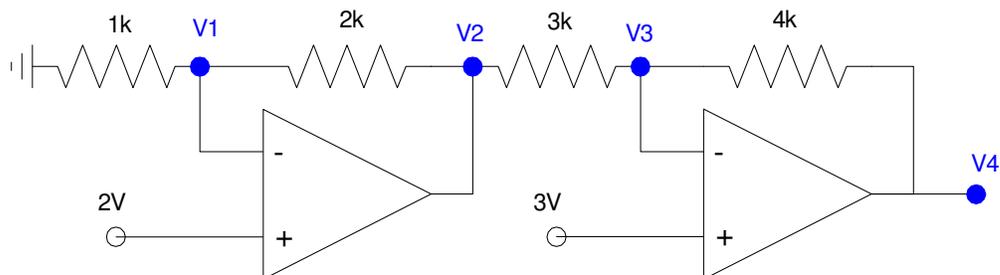Example 3: Assume ideal op-amps. Find the node voltages.



There are four unknown voltages, so we need to write 4 equations to solve for 4 unknowns.

Start with the easy ones: at the output of each op-amp, $V_+ = V_-$

$$V_1 = 2 \quad (1)$$

$$V_3 = 3 \quad (2)$$

Sum the currents to zero at nodes 1 and 3 for the remaining two equations

$$\left(\frac{V_1}{1k}\right) + \left(\frac{V_1 - V_2}{2k}\right) = 0 \quad (3)$$

$$\left(\frac{V_3 - V_2}{3k}\right) + \left(\frac{V_3 - V_4}{4k}\right) = 0 \quad (4)$$

In matrix form:

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ \left(\frac{1}{1k} + \frac{1}{2k}\right) & \left(\frac{-1}{2k}\right) & 0 & 0 \\ 0 & \left(\frac{-1}{3k}\right) & \left(\frac{1}{3k} + \frac{1}{4k}\right) & \left(\frac{-1}{4k}\right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 2 \\ 3 \\ 0 \\ 0 \end{bmatrix}$$

Solving:

```
>> A = [1,0,0,0 ; 0,0,1,0 ; 1/1000+1/2000, -1/2000, 0, 0 ; 0,-1/3000, 1/3000+1/4000,-1/4000]
```

```
1.0000      0      0      0
      0      0      1.0000      0
0.0015 -0.0005      0      0
      0 -0.0003      0.0006 -0.0003
```

```
>> B = [2;3;0;0];
```

```
>> V = inv(A)*B
```

```
V1      2.0000
V2      6.0000
V3      3.0000
V4     -1.0000
```

Checking in CircuitLab

V(V1)	2.000 V		
V(V2)	4.000 V		
V(V3)	3.000 V		
V(V4)	2.000 V		

