

ECE 376 - Homework #3

Binary Inputs, Binary Outputs, and Timing. Due Monday, September 15th

Solder your PIC board (50pt)

Demonstrate that your PIC board works

- In person, video, demo during Zoom office hours
- 50pt: Board you built powers up & you're able to download code
- 25pt: Board you built is soldered but not working (swap for a working board)
- note: If your board doesn't work, we have working boards we can swap with you. You'll need a working board for the rest of the course.

Binary Inputs

A thermistor has the following temperature - resistance relationship:

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{278}\right) \Omega$$

where T is the temperature in degrees C.

1) Design a circuit which outputs

- 0V when $T < 5C$
- 5V when $T > 5C$

2) Design a circuit which outputs

- 0V when $T < 0C$
- 5V when $T > 5C$
- No change for $0C < T < 5C$

Binary Outputs

3) Design a circuit which allows your PIC board to turn on and off an RGB Piranha LED at 0mA (off) and 20mA (on). Assume the specifications for the LEDs are:

| Color | Vf @ 20mA | mcd @ 20mA |
|-------|-----------|------------|
| red | 2.0V | 10,000 |
| green | 3.2V | 10,000 |
| blue | 3.2V | 10,000 |

1W Star LED

4) The star LED in your lab kit is a 1W white LED with a 6.8 Ohm resistor attached.

- $V_f = 3.0V @ 330mA$
- 200LM @ 330mA

a) Set up the following circuit so your PIC board can turn the LED on/off

- The 200 Ohm resistor limits the current (200 to 1k works)

b) Compute the

- Current to the LED
- The brightness of the LED

c) Build this circuit and measure

- I_d (hint: measure V_r and compute the current)
- V_f (the voltage drop across the LED)



5) Use a 6144 NPN transistor as an electronic switch to turn on and off the LED (and amplify current).

- $I_c(\max) = 3A$ ($I_b(\max) = 25mA$ - the max output of a PIC)
- $h_{fe} (\beta) > 200$


a) Set up the following circuit so that your PIC board can turn on and off the LED

b) Compute


- The currents I_b and I_c and
- The brightness of the LED

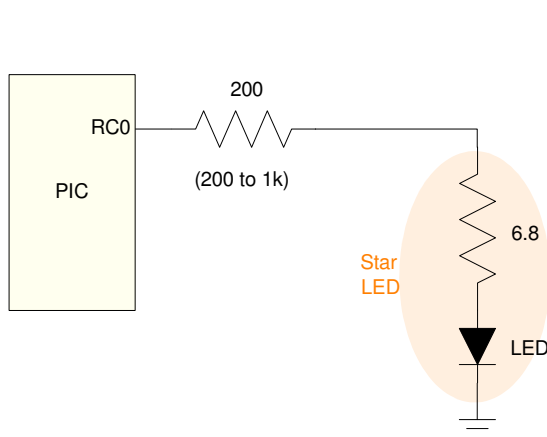c) Build this circuit and measure

- I_d (hint: measure the voltage across the 6.8 Ohm resistor on the LED)
- V_f (the voltage drop across the LED)



Problem #4

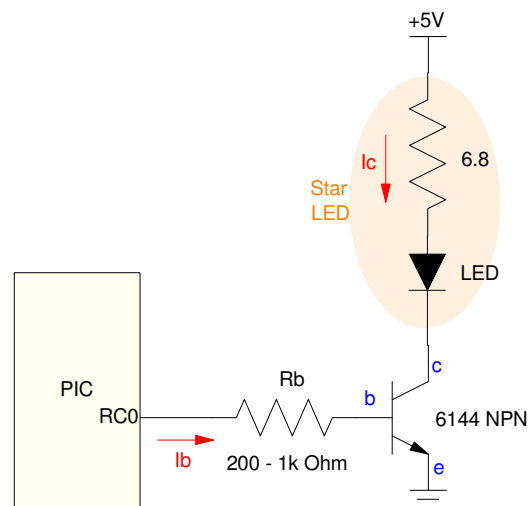

Problem #5

Timing:

- 6) Write a program which outputs the music note G2 (98.00 Hz)
 - Verify the frequency of the square wave you generate
 - (Pano Tuner app on you cell phone works well for this)

4-Key Piano:

Design an embedded system to play four notes:

- Inputs: Buttons on RB0 / RB1 / RB2 / RB3
- Outputs: RC0
- Relationship: Output a square wave on RC0 based upon the button pressed:
 - RB0 F#3 185.00 Hz
 - RB1 G#3 207.65 Hz
 - RB2 A#3 223.08 Hz
 - RB3 C#4 277.18 Hz

- 7) Give a flow chart for your program
- 8) Give an assembler program for the 4-key piano.
 - Include computations for the wait loops
- 9) Validation: Collect data in the lab to verify your code works.
 - Are the frequencies correct?
- 10) Demonstration: Demonstrate that your embedded system works (either in person or with a video)