ECE 376 - Homework #1

PIC Background. Due Monday, August 30th, 2021

 1) A PIC processor can drive up to 25mA on its I/O pins. Assuming the output is 5V, what is the smallest resistance you can connect to an output pin? i.e. how small can R2 be (figure next page) 	200 Ohms
A PIC can measure voltage to 4.88mV. To give an idea of how small this is	
2) What is the smallest change in R1 a PIC can measure if R1 = 2000 Ohms nominally?	8.81 Ohms
$V = \left(\frac{R_1}{1000 + R_1}\right) \cdot 5V$	
A PIC can measure time to 100ns. To give an idea of how small 100ns is	
3) The X-man <i>Quicksilver</i> can run 2050 miles per second. How far can <i>Quicksilver</i> go in 100ns?	330mm
4) Due to relativity, time slows down the faster you go. How fast do you have to travel for time to slow down by 100ns over the span of one year?	53.42 mph
5) A 555 timer (next page) outputs a square wave with the period of T = (R1 + 2R2) * C * ln(2) seconds What frequency does the 555 timer output if R1 = 1k, R2 = 10k, C = 10uF?	6.87Hz
6) What is the smallest change in frequency a PIC can detect?i.e. how much does the frequency have to change for the period to change by 100ns?	0.00000472 Hz
 7) With this circuit, you can build an ohm-meter: by mesuring the period, you can compute the resistance. • What is the smallest change in R2 a PIC can detect? • i.e. how much does R2 have to change for the period to change by 100ns? 	0.0072 Ohms
 8) With this circuit, you can build a temperature sensor: by mesuring the period, you can compute the resistance and from that determine the temperature. • What is the smallest change in temperature a PIC can detect? • i.e. how much does R2 have to change for the period to change by 100ns? Assume the temperature - resistance relationship of R2 is as follows where T is the 	0.00016 degrees C
temperature in degrees C. Also assume the temperature is 25C (R2 = 10k Ohms) $R_2 = 10,000 \cdot \exp\left(\frac{3905}{T + 273} - \frac{3905}{298}\right) \Omega$	


A PIC processor can drive up to 25mA on its I/O pins. Assuming the output is 5V, what is the smallest resistance you can connect to an output pin?

$$R_2 = \left(\frac{5V}{25mA}\right) = 200\Omega$$

You need to make sure the load is at least 200 Ohms to avoid overloading (and possibly harming) the PIC processor

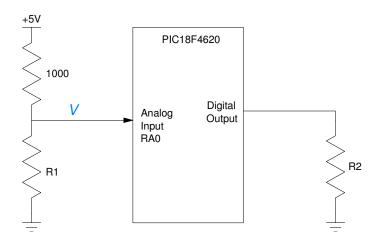Problem 2

What is the smallest change in R1 a PIC can measure if R1 = 2000 Ohms nominally?



When R1 = 2000 Ohms

$$V = \left(\frac{2000}{2000 + 1000}\right) 5V = 3.333V$$

The smallest voltage change a PIC can detect is 4.88mV. Adding this to V gives

$$V = 3.382V$$

Solving for R1

$$3.382V = \left(\frac{R_1}{R_1 + 1000}\right) 5V$$

$$R_1 = \left(\frac{3.382V}{5V - 3.382V}\right) 1000\Omega$$

$$R_1 = 2008.810\Omega$$

If you use the A/D input, the smallest change in resistance you can detect is 8.81 Ohms

The X-man Quicksilver can run 2050 miles per second. How far can Quicksilver go in 100ns?

1 mile = 1609.344 meters

$$\left(2050\frac{miles}{s}\right)\left(\frac{1609.344m}{mile}\right)(100ns) = 0.330m$$

Quicksilver can only go 330mm in 100ns

Problem 4

4) Due to relativity, time slows down the faster you go. How fast do you have to travel for time to slow down by 100ns over the span of one year?

This uses the Lorenz equation (wikipedia)

$$\Delta t' = \frac{\Delta t}{\sqrt{1 - \frac{v^2}{c^2}}}$$
Doing a Taylor's series expansion

$$\Delta t' \approx \frac{\Delta t}{\left(1 - \frac{1}{2}\left(\frac{v^2}{c^2}\right)\right)} \approx \Delta t \left(1 + \frac{1}{2}\left(\frac{v^2}{c^2}\right)\right)$$

$$(\Delta t' - \Delta t) \approx \Delta t \left(\frac{1}{2} \frac{v^2}{c^2}\right)$$

$$100ns = (31, 563, 000s) \left(\frac{1}{2} \frac{v^2}{c^2}\right)$$

$$v = 23.881 \frac{m}{s}$$

which is 53.42 mph


5) A 555 timer (next page) outputs a square wave with the period of

$$T = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$

What frequency does the 555 timer output if R1 = 1k, R2 = 10k, C = 10uF?

$$T = 0.146s$$

$$f = \frac{1}{T} = 6.870Hz$$

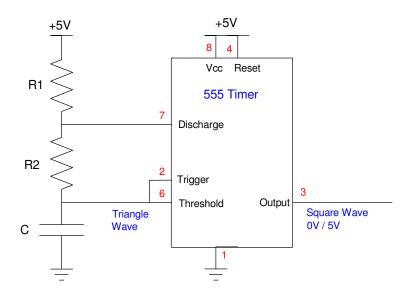

Problem 6

Problem 6) What is the smallest change in frequency a PIC can detect?

• i.e. how much does the frequency have to change for the period to change by 100ns? Carrying it out to lots of decimal places

$$T0 = 0.145560908$$
 seconds

$$f0 = 6.869976385 Hz$$

add 100ns

$$T1 = T0 + 100$$
ns

$$T1 = 0.145561008$$
 seconds

The difference in frequency is

$$f1 - f0 = 0.000004720$$
Hz

The smallest change in frequency a PIC can detect is 0.000 004 72 Hz

- 7) With this circuit, you can build an ohm-meter: by mesuring the period, you can compute the resistance.
- What is the smallest change in R2 a PIC can detect? i.e. how much does R2 have to change for the period to change by 100ns?

The period is related to R1, R2, and C by

$$T = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$

$$0.145561008 = (1000 + 2R_2) \cdot 10\mu F \cdot \ln(2)$$

$$R_2 = 10,000.00721\Omega$$

The smallest change in resistance you can detect is 0.00721 Ohms

Problem 8

- 8) With this circuit, you can build a temperature sensor: by mesuring the period, you can compute the resistance and from that determine the temperature.
 - What is the smallest change in temperature a PIC can detect?
 - i.e. how much does R2 have to change for the period to change by 100ns?

Assume the temperature - resistance relationship of R2 is as follows where T is the temperature in degrees C. Also assume the temperature is 25C (R2 = 10k Ohms)

Plugging in 10.00000721 k Ohms for R2 gives

$$R_2 = 10k \cdot \exp\left(\frac{3905}{T + 273} - \frac{3905}{298}\right)\Omega$$

$$T = 24.999836^{\circ}C$$

The change in temperature is 0.00016 degrees C