

ECE 376 - Homework #3

Binary Inputs

A thermistor has the following temperature - resistance relationship:

$$R = 1000 \cdot \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

where T is the temperature in degrees C.

1) Design a circuit which outputs

- 0V when $T < 5C$
- 5V when $T > 5C$

First, compute the resistance at 5C

$$R = 2566.99 \Omega$$


Next, pick your favorite voltage divider. Assume a 2.2k resistor and a 5V source

$$V_{in} = \left(\frac{R}{R+2000}\right) 5V$$

$$V_{in} = 2.6925V$$

Finally, connect this to a comparator. For the plus/minus inputs, pick whichever one results in $T > 5C$ (rather than $T < 5C$). This works out to the minus input

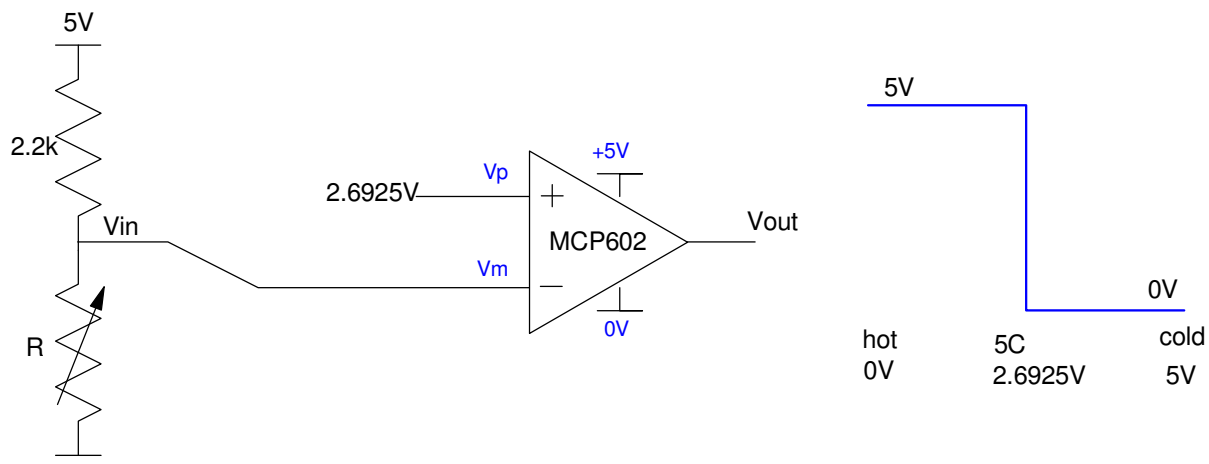- As T goes to infinity, R goes to zero
- V_{in} goes to zero
- V_{out} goes to 5V



2) Design a circuit which outputs

- 0V when $T < 0C$
- 5V when $T > 5C$
- No change for $0C < T < 5C$

At 0C

- $R = 3320.12 \text{ Ohms}$
- $V_{in} = 3.0073V$ $V(off)$
- $V_{out} = 0V$

At 5C

- $R = 2566.99 \text{ Ohms}$
- $V_{in} = 2.6925V$ $V(on)$
- $V_{out} = 5V$

$V(on) < V(off)$ so connect to the minus input

$V(on) = 2.6925V$



The gain required is

$$gain = \left(\frac{\text{change in output}}{\text{change in input}} \right)$$

$$gain = \left(\frac{5V - 0V}{3.0073V - 2.6925V} \right)$$

$$gain = 15.88$$

Set the resistor ratio to 15.88 : 1

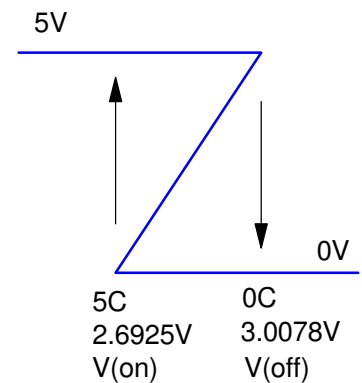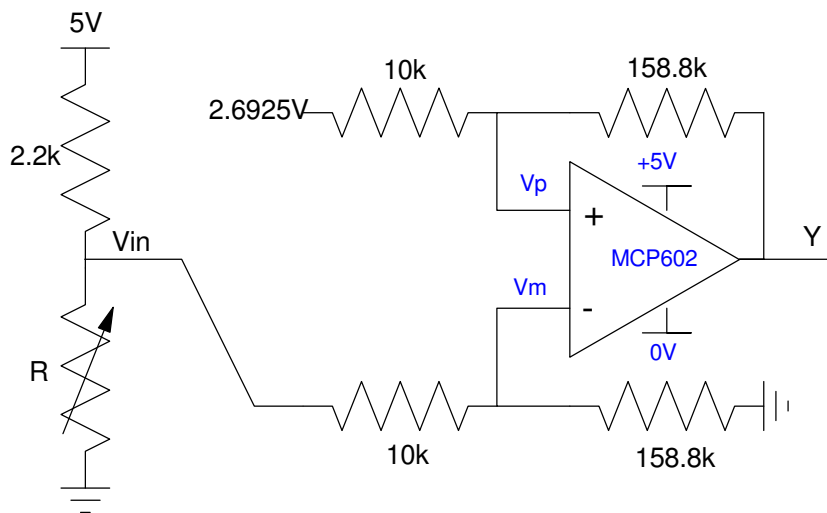

Binary Outputs


3) Design a circuit which allows your PIC board to turn on and off an RGB Piranah LED at 0mA (off) and 20mA (on). Assume the specifications for the LEDs are:

Color	Vf @ 20mA	mcd @ 20mA
red	2.0V	10,000
green	3.2V	10,000
blue	3.2V	10,000

$$R_r = \left(\frac{5V - 2.0V}{20mA} \right) = 150\Omega$$

$$R_g = \left(\frac{5V - 3.2V}{20mA} \right) = 90\Omega$$
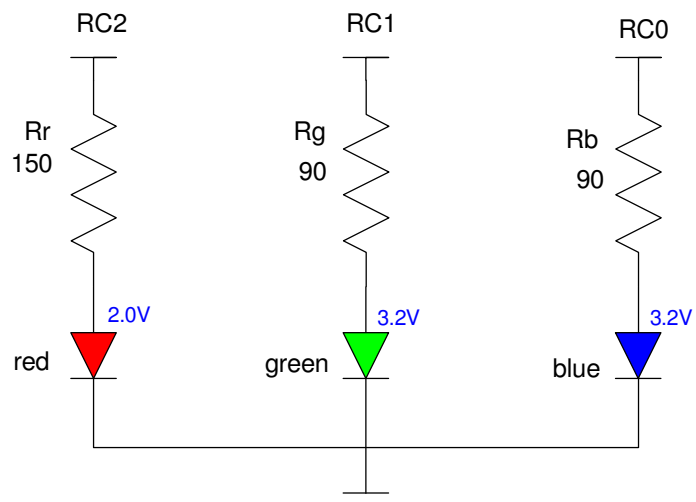
$$R_b = \left(\frac{5V - 3.2V}{20mA} \right) = 90\Omega$$



1W Star LED

4) The star LED in your lab kit is a 1W white LED in series with 6.8 Ohms.

- $V_f = 3.0V$ @ 330mA
- 200LM @ 330mA

a) Set up the following circuit so your PIC board can turn the LED on/off


- The 200 Ohm resistor limits the current (200 to 1k works)

b) Compute the

- Current to the LED
- The brightness of the LED

$$I_b = \left(\frac{5V - 3.0V}{1k + 6.8} \right) = 1.986mA$$
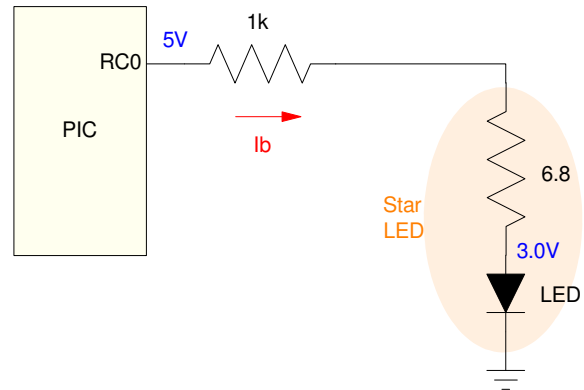
$$Light = \left(\frac{1.986mA}{330mA} \right) 200LM = 1.2 \text{ lumens}$$




c) Build this circuit and measure

I_d (the current through the LED)

- $I(1k) = 2.438V$
- $I_d = 2.439mA$
- LED is on but dim

V_f (the voltage drop across the LED):

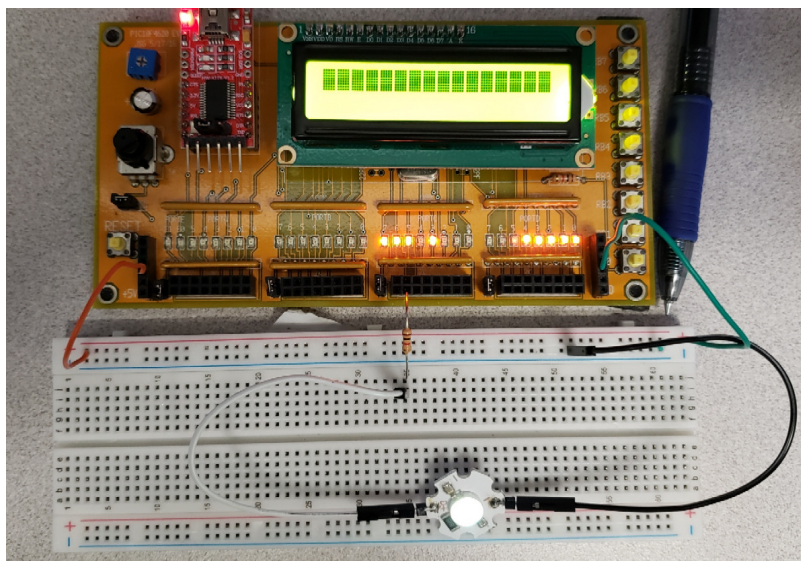- Measured across the LED
- $V_f = 2.623V$
- (slightly less than the 3.00V @ 330mA from the data sheets. V_f changes slightly with current)



5) Use a 6144 NPN transistor as an electronic switch to turn on and off the LED (and amplify current).

- $I_c(\text{max}) = 3\text{A}$ ($I_b(\text{max}) = 25\text{mA}$ - the max output of a PIC)
- $h_{fe}() > 200$

a) Set up the following circuit so that your PIC board can turn on and off the LED

b) Compute

- The currents I_b and I_c and
- The brightness of the LED

$$I_b = \left(\frac{5V - 0.7V}{1k} \right) = 4.3\text{mA}$$

$$I_c = \left(\frac{5V - 3.0V - 0.2V}{6.8\Omega} \right) = 264.7\text{mA}$$

Is is saturated?


$$\beta I_b > I_c$$

$$200 \cdot 4.3\text{mA} > 264.7\text{mA}$$

$$860\text{mA} > 24.7\text{mA}$$

Yes, the transistor is saturated (meaning $V_{ce} = 0.2\text{V}$ (ish))
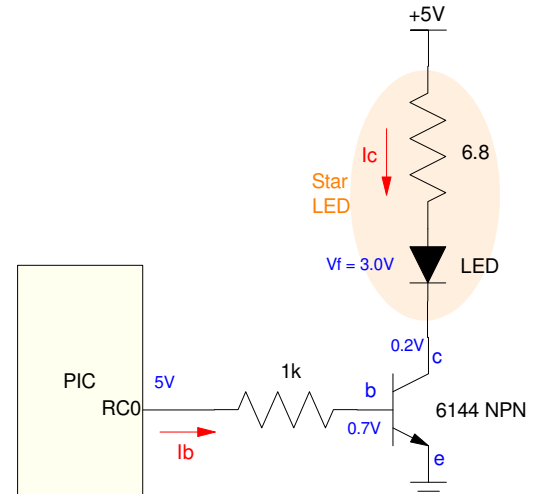
$$L = \left(\frac{264.4\text{mA}}{330\text{mA}} \right) 2000\text{LM} = 160.4 \text{ lumens}$$




c) Build ths circuit and measure

Id (hint: measure the voltage across the 6.8 Ohm resistor on the LED)

- $V_r = 1.566\text{V}$
- $I_r = V_r / 6.8 = 230.3\text{mA}$ (really bright)

V_f (the voltage drop across the LED)

- 3.138V

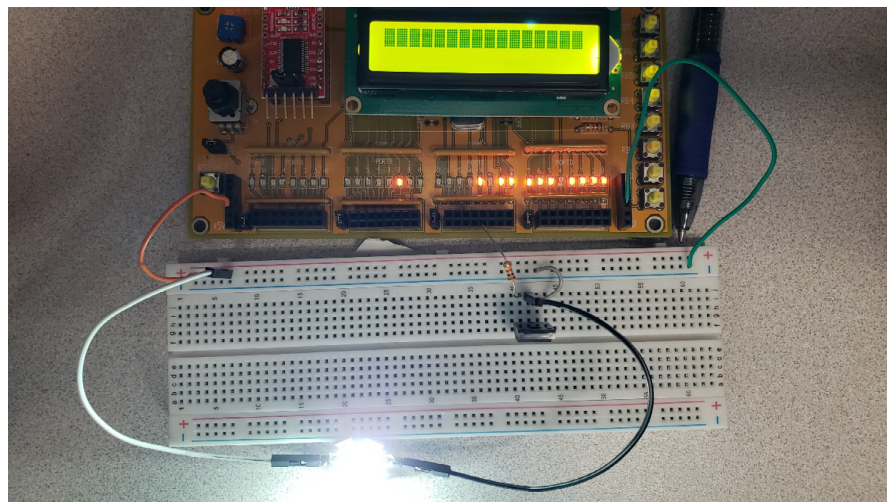

Timing:

5) Write a program which outputs the music note G2 (98.00 Hz)

- Verify the frequency of the square wave you generate
- (Pano Tuner app on you cell phone works well for this)

98 Hz gives a wait loop of

$$N = \left(\frac{10,000,000}{2 \cdot \text{Hz}} \right) = 51,020.04 \text{ clocks}$$

```
#include <p18f4620.inc>

; Variables
CNT0 EQU 1
CNT1 EQU 2

; Program
    org 0x800
    call Init
Loop:
    incf PORTC,F
    call Wait
    goto Loop

; --- Subroutines ---

Init:
    clrf TRISA
    clrf TRISB
    clrf TRISC
    clrf TRISD
    clrf TRISE
    movlw 0x0F
    movwf ADCON1
    return

; Wait 51,020 clocks (actual wait time is 51,260 clocks)
Wait:
    movlw 51
    movwf CNT1
W1:
    movlw 100
    movwf CNT0
W0:
    nop
    nop
    nop
    nop
    nop
    nop
    nop
    decfsz CNT0, F
    goto W0
    decfsz CNT1, F
    goto W1
    return

end
```

Using Pano Tuner, the actual frequency is 97.6Hz



Lab: 4 Key Sharp Piano

Requirements:

- Inputs: Buttons on RB0 / RB1 / RB2 / RB3
- Outputs: RC0
- Relationship: Output a square wave on RC0 based upon the button pressed:
 - RB0 F#3 185.00 Hz
 - RB1 G#3 207.65 Hz
 - RB2 A#3 223.08 Hz
 - RB3 C#4 277.18 Hz

6) Analysis, Code, and Flow Chart. Give computations for resistor values (if any), timing, assembler code, and a flow chart for your code

The number of clocks needed for each note are:

$$N = \left(\frac{10,000,000}{2 \cdot \text{Hz}} \right)$$

N is created using a series of loops:

$$N = 5AB + 5B + 5 + 13 \quad (\text{main routine} = 13 \text{ clocks})$$

185Hz:

- $N = 27,027$
- $A = 36, B = 146, N = 27028$

207.65 Hz:

- $N = 24,079$
- $A = 28, B = 166, N = 24088$

233.08 Hz

- $N = 21,452$
- $A = 31, B = 134, N = 21458$

277.18 Hz

- $N = 18,038$
- $A = 16, B = 212, N = 18,038$

Code & Flow Chart

```
; Program
    org 0x800
    call Init
Loop:
    movlw 0
    cpfseq PORTB ; if any button is pressed
    btg    PORTC,0

    btfsc PORTB,0
    call   B0
    btfsc PORTB,1
    call   B1
    btfsc PORTB,2
    call   B2
    btfsc PORTB,3
    call   B3

    goto Loop

; --- Subroutines ---

Init:
    clrf TRISA      ;PORTA is output
    movlw 0xFF
    movwf TRISB     ;PORTB is input
    clrf TRISC      ;PORTC is output
    clrf TRISD      ;PORTD is output
    clrf TRISE      ;PORTE is output
    movlw 0x0F
    movwf ADCON1     ;everyone is binary
    return

B0:
    movlw 21
    movwf CNT1
B0a:
    movlw 164
    movwf CNT0
B0b:
    nop
    nop
    decfsz CNT0, F
    goto B0b
    decfsz CNT1, F
    goto B0a
    return

B1:
    movlw 28
    movwf CNT1
B1a:
    movlw 166
    movwf CNT0
B1b:
    nop
    nop
    decfsz CNT0, F
    goto B1b
    decfsz CNT1, F
    goto B1a
    return

B2:
    movlw 31
```

```
    movwf CNT1
B2a:    movlw 134
        movwf CNT0
B2b:    nop
        nop
        decfsz CNT0, F
        goto B2b
        decfsz CNT1, F
        goto B2a
        return

B3:    movlw 16
        movwf CNT1
B3a:    movlw 212
        movwf CNT07
B3b:    nop
        nop
        decfsz CNT0, F
        goto B3b
        decfsz CNT1, F
        goto B3a
        return

end
```

8) Validation: Collect data in the lab to verify your code works.

- For a binary clock, is it counting once per second?
- For the dice, are the results random? Is the beep 220Hz? Is it 1 second?
- For the piano, is each note correct in frequency?



Frequency	Hz	Measured	Error (%)
F#3	185.00 Hz	185.3Hz	+0.162%
G#3	207.65 Hz	207.9Hz	+0.120%
A#3	223.08 Hz	233.4Hz	+0.137%
C#4	277.18 Hz	277.4Hz	+0.079%

9) Demonstration: Demonstrate that your embedded system works (either in person or with a video)