


ECE 376 - Test #1: Name _____

1) **Digital Inputs.** Design a circuit which outputs

- 0V when $R > 2500$ Ohms
- 5V when $R < 2000$ Ohms

Assume

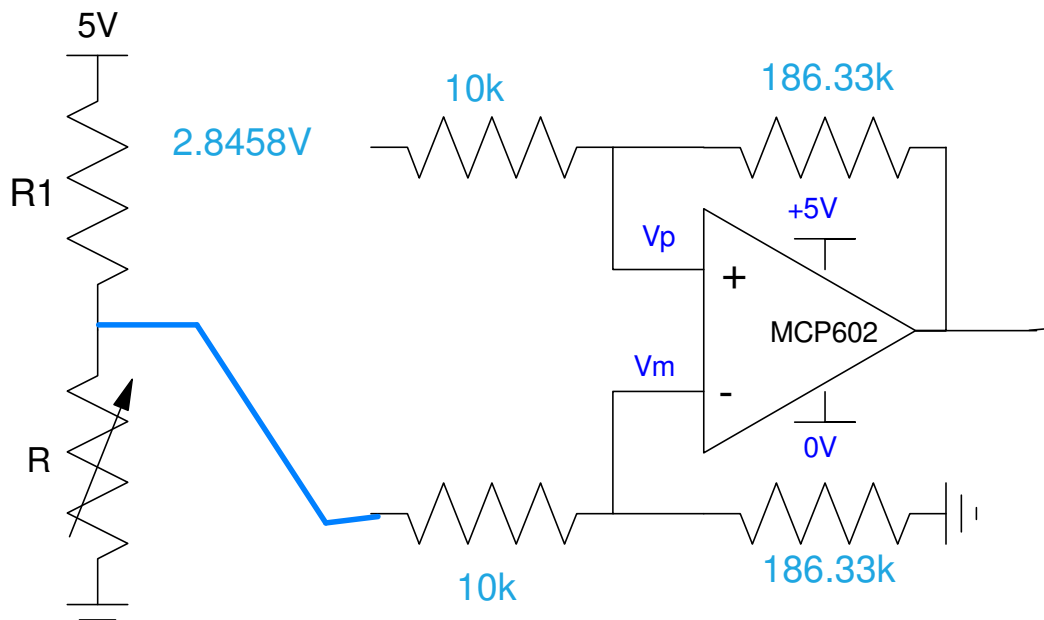- $R1 = 900 + 100 \cdot (\text{your birth month}) + (\text{your birth date})$.
- May 14th, for example, gives $R1 = 1414$ Ohms



Let $R1 = 1514$ Ohms

$R = 2000$ Ohms (on)

$$V = \left(\frac{2000}{2000 + 1514} \right) 5V = 2.8458V$$

$R = 2500$ Ohms (off)

$$V = \left(\frac{2500}{2500 + 1514} \right) 5V = 3.1141V$$

$V(\text{on}) < V(\text{off})$

- connect to the minus input

$V(\text{on}) = 2.8458V$

- Make the offset 2.8458V

$$\text{gain} = \left(\frac{\text{change in output}}{\text{change in input}} \right) = \left(\frac{5V - 0V}{3.1141V - 2.8458V} \right) = 18.633$$

2) Digital Outputs: Design a circuit which allows your PIC to turn on and off a 20W LED at N Lumens

- $N = 900 + 100 * (\text{your birth month}) + (\text{your birth date})$
- $N = 1414$ Lumens for May 14th, for example


Assume a 20W LED has the following characteristics

- $V_f = 36V$ @ $600mA$
- 1800 Lumens @ $600mA$

Assume a 6144 NPN transistor

- $V_{be} = 700mV$
- $V_{ce(sat)} = 360mV$
- Current gain = $\beta = 200$

Lumens $900 + 100 * \text{Month} + \text{Day}$	I_c (mA)	R_b	R_c
1514 Lumens	504.67mA	430 Ohms	27.03 Ohms

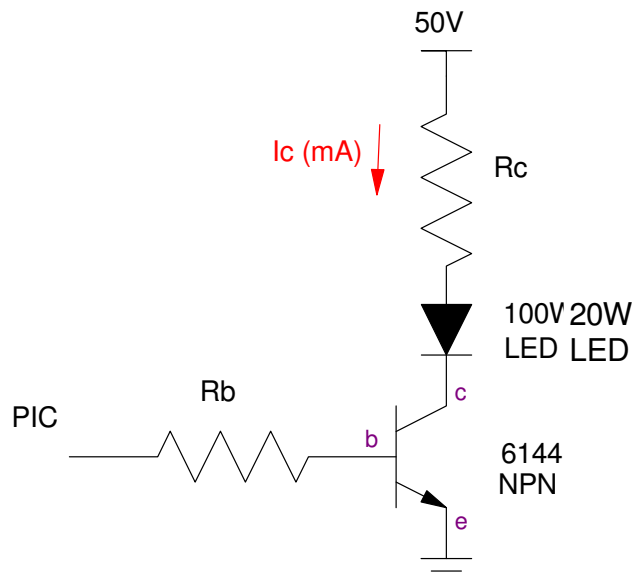

$$I_c = \left(\frac{1514 \text{ Lumens}}{1800 \text{ Lumens}} \right) 600mA = 504.67mA$$

$$R_c = \left(\frac{50V - 36V - 0.36V}{504.67mA} \right) = 27.03\Omega$$

To saturate the transistor

$$I_b > \left(\frac{I_c}{\beta} \right) = \left(\frac{504.67mA}{200} \right) = 2.52mA$$

Let $I_b = 10mA$

$$R_b = \left(\frac{5V - 0.7V}{10mA} \right) = 430\Omega$$

3) **Assembler:** Determine the contents of the W, PORTB, and PORTC registers after each operation.
Assume

- PORTB and PORTC are output.
- Default is decimal

	W	PORTB	PORTC
Start:	Birth Month (1..12) 5	Birth Date (1..31) 14	15
incf PORTB,F	5	15	15
decf PORTC,W	14	15	15
addwf PORTB,F	14	29	15
andlw 7	6	29	15
bsf PORTB,4	6	29	15
bcf PORTC,2	6	29	11
movlw 7	7	29	11
addwf PORTB,F	7	36	11
subwf PORTC,F	7	36	4
clrf PORTB	7	0	4

4) Assembler & Timing:

a) Convert the following C code to assembler.

- Assume A, B, and C are 8-bit numbers

b) How long does your program take to execute?

Clocks =

```
unsigned char A, B, C;
```

```
if (A > B)
    C = A;
else
    C = B;
```

```
A    equ    0
B    equ    1
C    equ    2

    movf     B,W
    cmpfsgt  A
    goto     PickB
PickA:
    movff    A,C
    goto     end
PickB:
    movff    B,C
end:
    nop
```

Number of Clocks:

- if (A > B) it takes 7 clocks to execute
- otherwise, it takes 6 clocks to execute

5) Assembler & Flow Charts. Write an assembler program that corresponds to the following flow chart. This program turns your PIC processor a 6 and 10 sided die:

- When RB0 is pressed and released
- PORTC displays a random number from 1..6 (six-sided die)
- PORTD displays a random number from 1..10 (ten-sided die)
- d6 and d10 are 8-bit variables in RAM

Test #1: (due Friday) Write the assembler code

Bonus (due Monday): Demonstrate your program on your PIC board

```
#include <p18f4620.inc>
```

```
d6 equ 0
d10 equ 1
```

```
; Start of Program
org 0x800
```

```
L1:
    movlw 0xFF
    movwf TRISB
    clrf TRISC
    clrf TRISD

L2:
    btfss PORTB,0
    goto L2

L3:
    incf d6,F

L4:
    movlw 6
    cmpfsgt d6
    goto L6

L5:
    movlw 1
    movwf d6

L6:
    incf d10,F

L7:
    movlw 10
    cmpfsgt d10
    goto L9

L8:
    movlw 1
    movwf d10

L9:
    movff d6,PORTC
    movff d10,PORTD

L10:
    btfsc PORTB,0
    goto L3
    goto L2
```

