

---

# Binary Outputs: LEDs

**ECE 376 Embedded Systems**

**Jake Glower - Lecture #6**

Please visit [Bison Academy](#) for corresponding lecture notes, homework sets, and solutions

---

# Binary Outputs: LEDs

## Light Emitting Diodes ( LED's )

- Are diodes, allowing current to only flow in one direction,
- They convert current to light.(light is proportional to current flow), and
- They are *very* fast, capable of  $> 100\text{MHz}$  flashes per second, and
- They are a simple way to output binary data (light on / light off)




# LED VI Characteristics

Exponential in nature

- Makes analysis hard

Ideal Diode

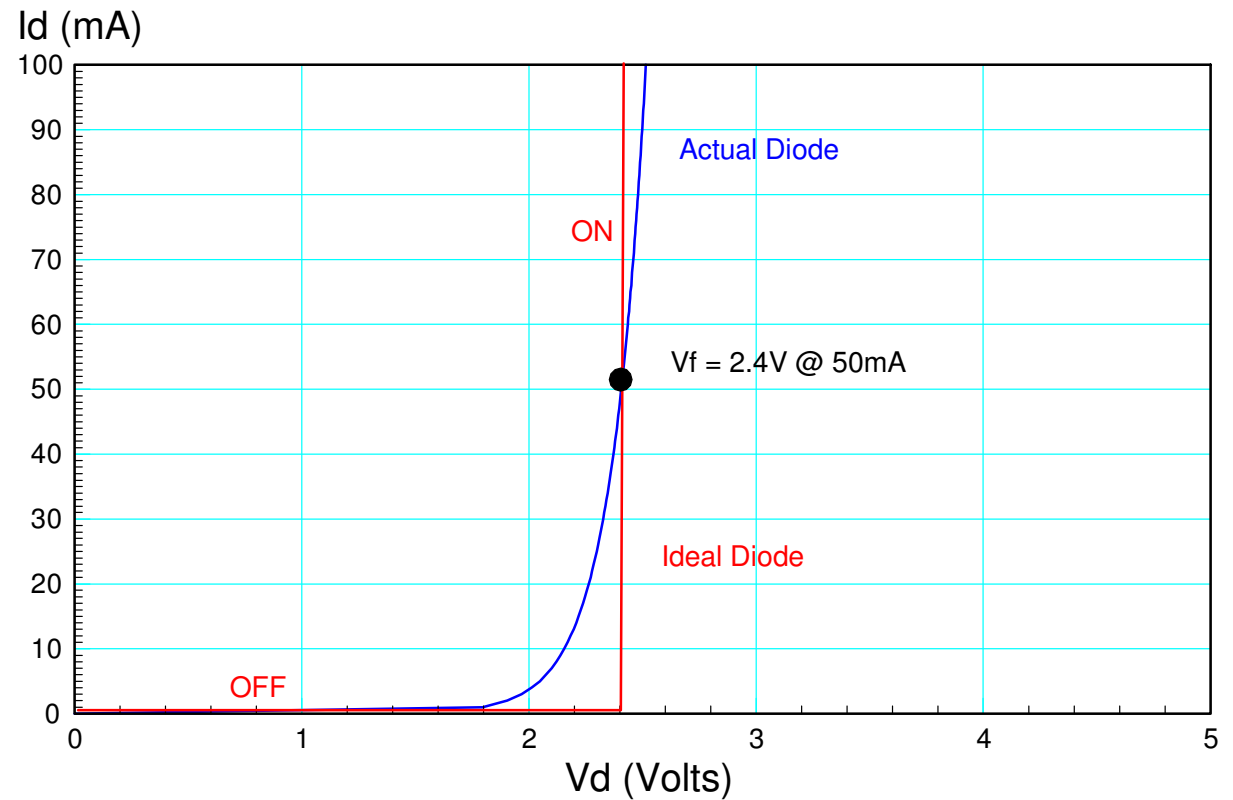- $V_d = \text{constant}$  when  $I_d > 0$
- Slightly wrong but often times close enough



---

## Diode Specifications

- Vf:  $V_d$  when  $I_d > 0$ 
  - Ideal diode approximation
- mcd: Light output in millicandles
  - One beeswax candle = 1000 mcd
- lux: Light output in lux
  - 100W light bulb = 1000 lux
- Color: Nonscientific term
- Wavelength: More accurate color

LED	Color	Current	Typical Vf	Typical mcd	Wavelength (nm)	Price ea
1W White Star LED		350mA	3.4V	100 lm	n/a	\$1.55
0.5W 10mm White LED		100mA	3.3V	25 lm	n/a	\$0.30
Piranah RGB LED	Red	20mA	1.8V	8000 mcd	630 nm	\$0.31
	Green	20mA	3.0V	8000 mcd	525 nm	
	Blue	20mA	3.0V	8000 mcd	470 nm	


---

# Diode Circuits


Case 1: Connect with a resistor

- $V_f < 5V$
- $I_d < 25mA$

Case 2: Connect with a transistor

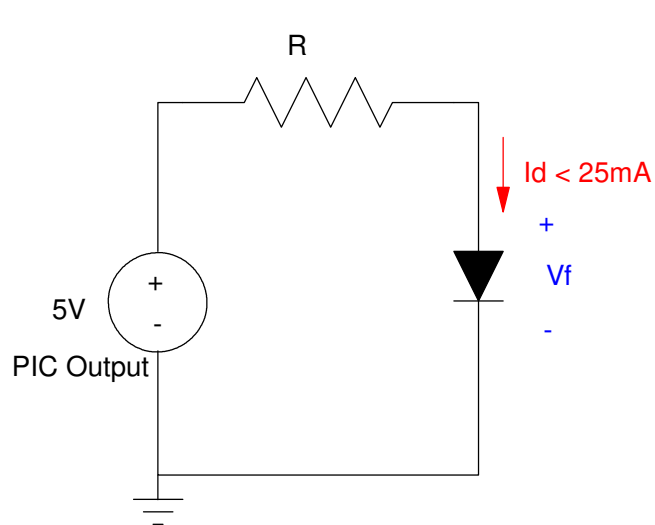

Case 1:  $I_d < 25mA$

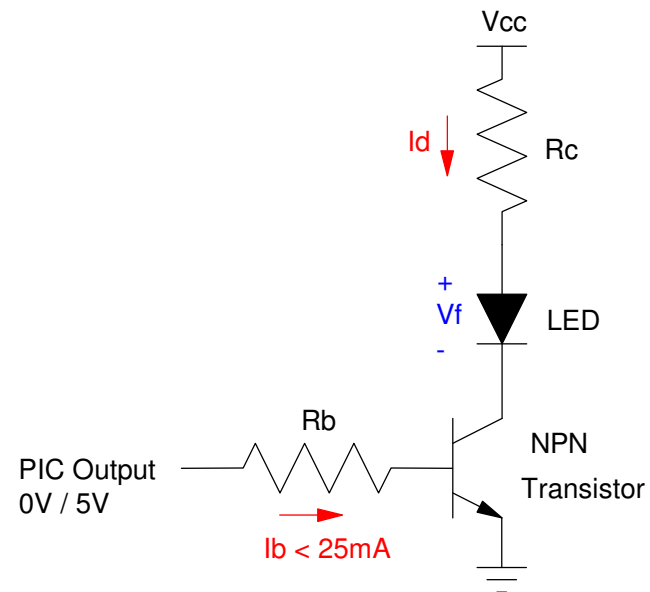

Case 2:  $I_d > 25mA$

## Case 1: $V_d < 5V$ , $I_d < 25mA$


Connect a red LED to a PIC. Set light level to 5000mcd

- $V_f = 1.8V$  @  $20mA$ , 8,000mcd @  $20mA$

Solution: Light is proportional to current

$$I_d = \left( \frac{5000mcd}{8000mcd} \right) \cdot 20mA = 12.5mA$$
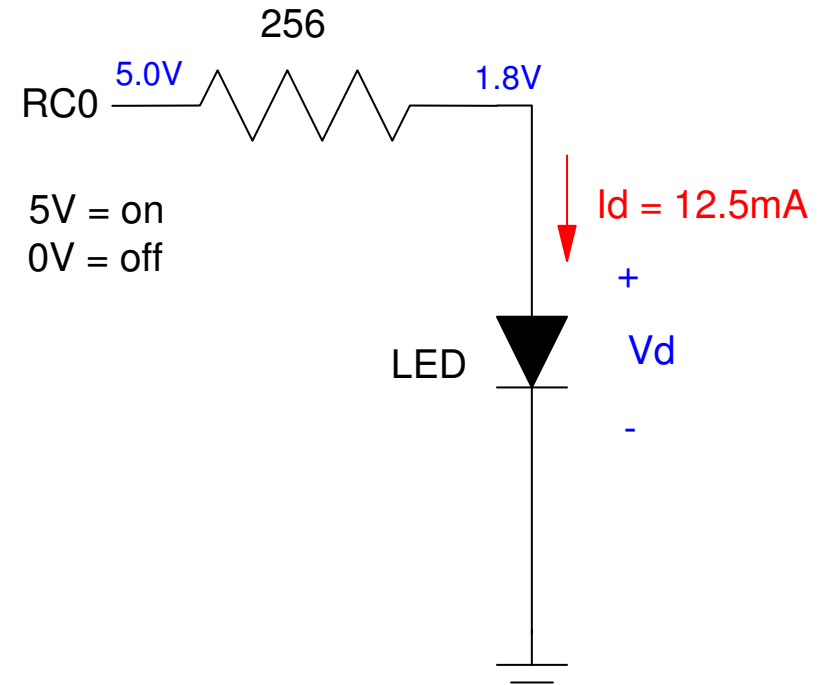
$$R_r = \left( \frac{5V - 1.8V}{12.5mA} \right) = 256\Omega$$



## Case 2: $I_d > 25\text{mA}$

Option #1: Use a solid state relay (\$7 solution from [www.mpja.com](http://www.mpja.com))

- Input: 3 - 32V DC @  $< 10\text{mA}$
- Output: 5 - 60VDC @ 10A max

Also available for up to 480VAC, 40A

### 10A DC Solid State Relay. DC Control Input



Stock No: 33980 RL



Be the first to review this item

**\$6.95**

Availability: **In Stock** Units: **32**

Quantity

**ADD TO CART**


**Add To Wish List**

---
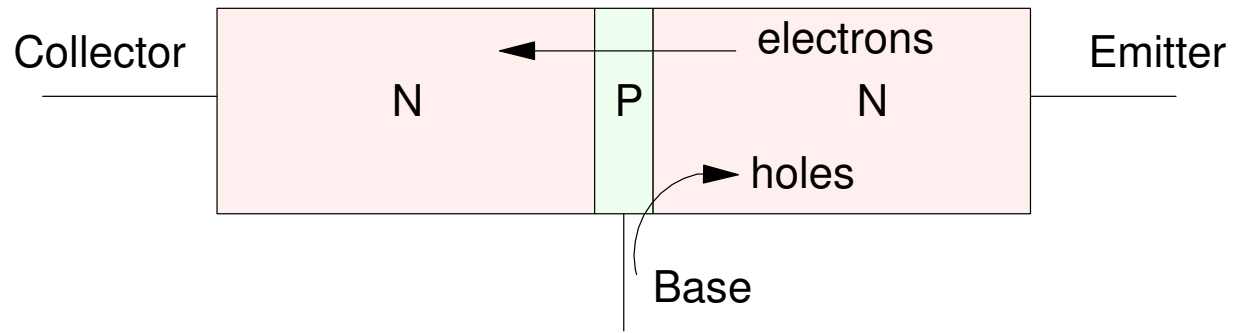
## Case 2: $I_d > 25\text{mA}$

Option #2: BJT Transistor (\$0.53 solution)

- NPN semiconductor
- Base current can turn on / off the current
  - Saturated (on) when  $\beta I_b > I_c$




NPN Transistor: The base current controls the current from collector to emitter

---



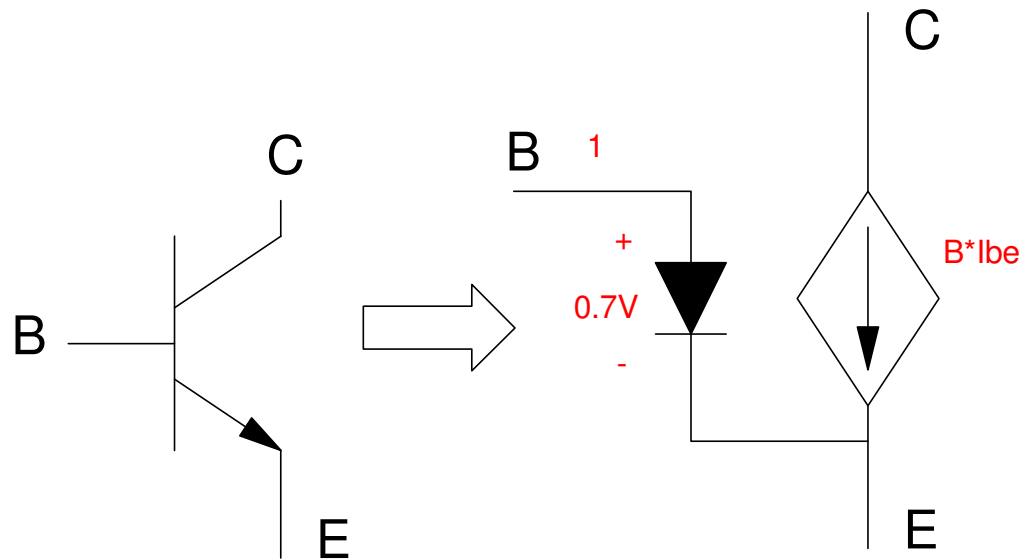
# Transistor Model

- Between the base and the emitter is a diode. It takes 0.7V to turn on a Silicon diode.
- Between the collector and the emitter is a current-controlled current source. The current flow amplifies the base to emitter current.



Symbol and Circuit Model for an NPN Transistor: The arrow indicates a diode from base to emitter.

# Transistor Specifications

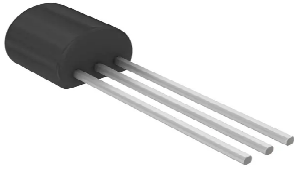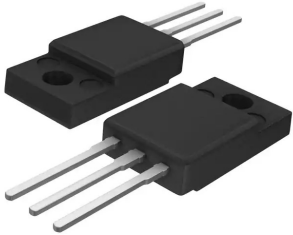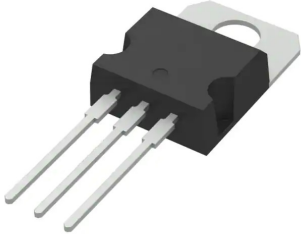	3904	6144	TIP112
Type	NPN	NPN	NPN
Current Gain	100	200	1,000
max(Ic)	200mA	10A	4A
max(Vce)	40V	50V	40V
Vce(sat)	300mV	360mV	900mV
Vbe	0.7V	0.7V	1.4V
price	\$0.037	\$0.53	\$0.59
Image			

# Using a Transistor as a Switch

- Turn on and off a 1W White LED @ 100mA
  - $V_f = 3.0V$  @ 350mA
- Use a 6144 NPN transistor

Pick  $I_c$  to set the current

$$R_c = \left( \frac{10V - 3.0V - 0.36V}{100mA} \right) = 66.4\Omega$$

Pick  $I_b$  so that  $\beta I_b > I_c$


$$I_b > \frac{I_c}{\beta} = \frac{100mA}{200} = 0.5mA$$

Let  $I_b = 2mA$

$$R_b = \left( \frac{5V - 0.7V}{2mA} \right) = 2150\Omega$$


note:  $R_b$  is somewhat arbitrary

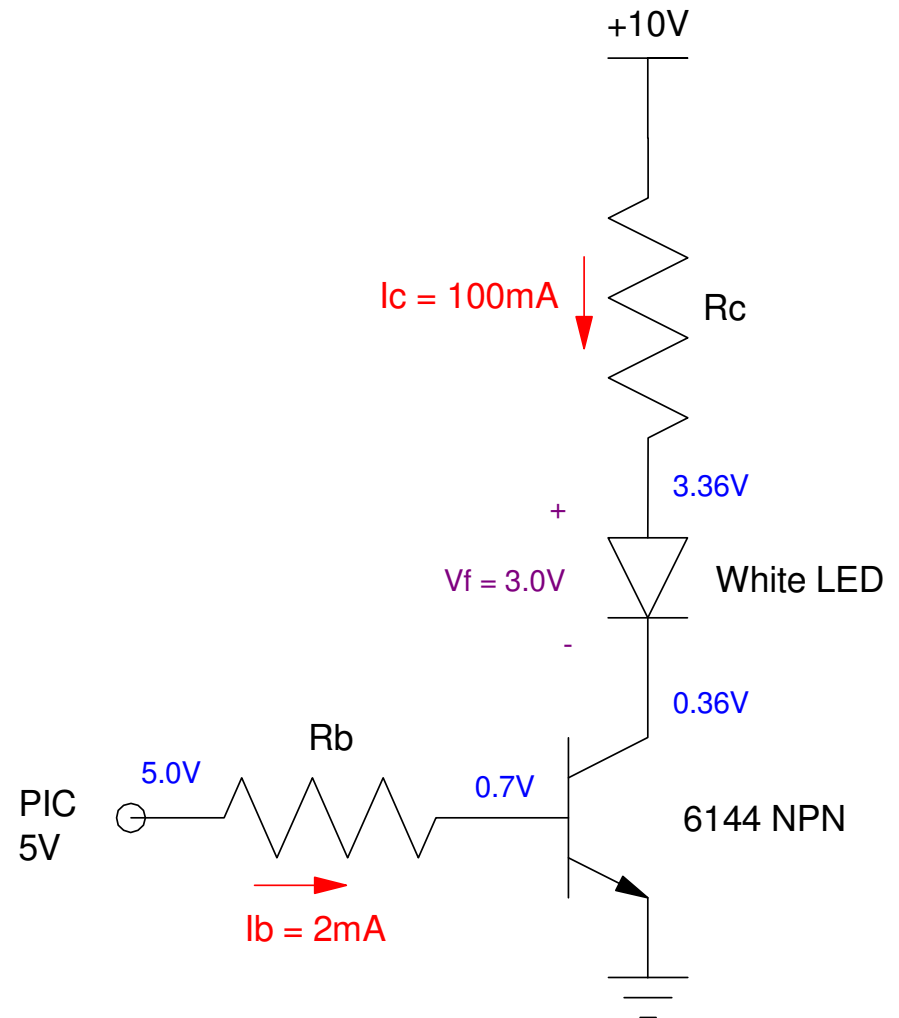- $R_b > \left( \frac{5V - 0.7V}{25mA} \right) = 172\Omega$
- $R_b < \left( \frac{5V - 0.7V}{0.5mA} \right) = 8600\Omega$



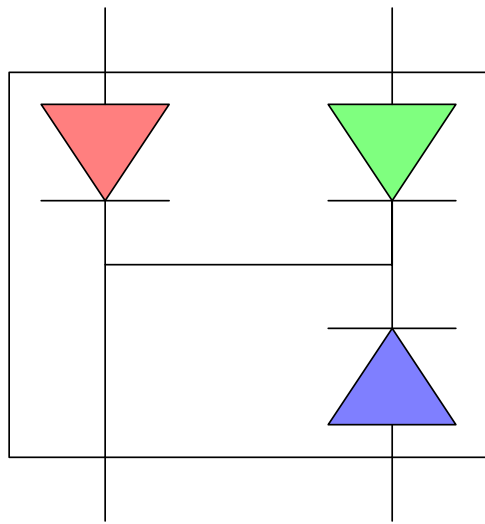
# Fun with RGB LEDs

- You can make any color by mixing red + green + blue
- Piranha LED's combine three colors in one LED
- Single pixel in a scoreboard



Piranah Package

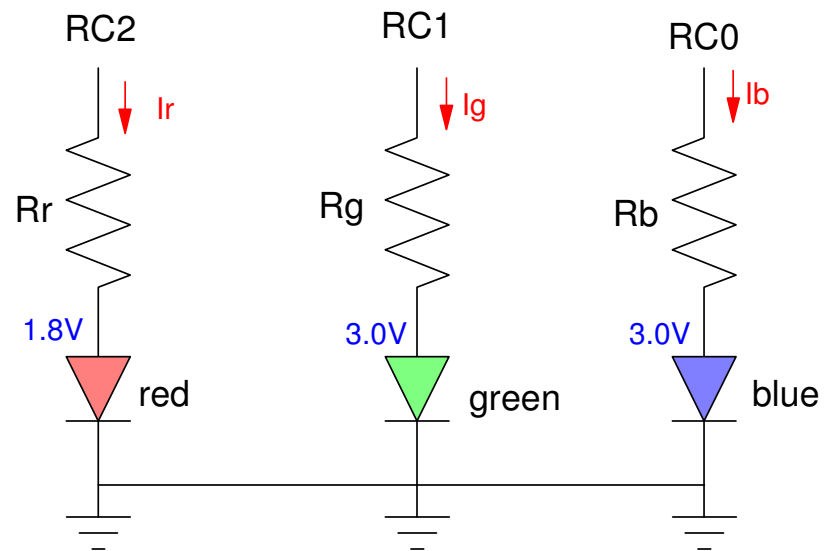

Connection to a PIC

---

# LED Flashlight

Build an LED flashlight with the following functions:

- RB0                All lights off
- RB1                Red light on
- RB2                Green light on
- RB3                Blue light on

Define "on" to be 20mA.

Hardware Solution: Previous figure with

$$R_r = \left( \frac{5V - 1.8V}{20mA} \right) = 160\Omega$$

$$R_g = \left( \frac{5V - 3.0V}{20mA} \right) = 100\Omega$$

$$R_b = \left( \frac{5V - 3.0V}{20mA} \right) = 100\Omega$$

---

---

## Option 1: Lights on while button is pressed


- No Buttons: LEDs off
- RB0: Turn on Red
- RB1: Turn on Green
- RB2: Turn on Blue

Code:

```
Init:
    movlw 0xFF
    movwf TRISB
    clrf  TRISC
    movlw 0x0F
    movwf ADCON1

Loop:
    movff PORTB, PORTC
    goto  Loop

end
```

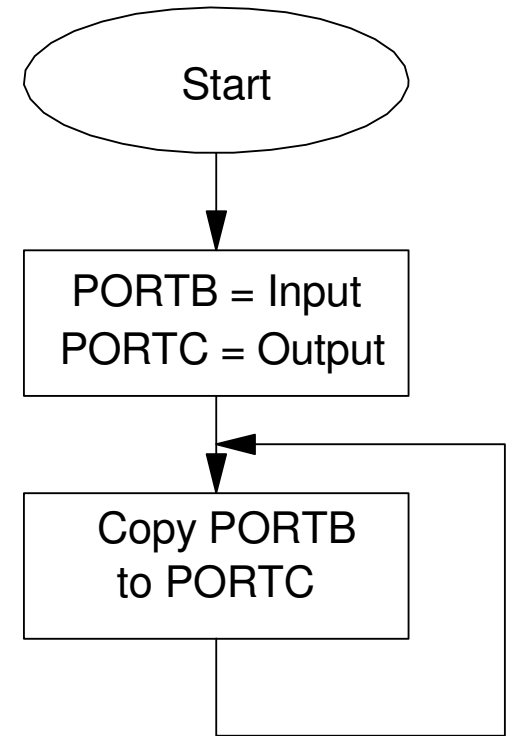

note: Code is a lot more complicated if the hardware shuffles the pins to the LED

---

## Option 2: Lights Remain On

```
COLOR equ 0
```

```
#include <p18f4620.inc>
```


```
org 0x800  
call Init
```

Loop:

```
movf COLOR,W  
btfsc PORTB,0  
movlw 0  
btfsc PORTB,1  
movlw 1  
btfsc PORTB,2  
movlw 2  
btfsc PORTB,3  
movlw 4  
movwf COLOR  
movff COLOR, PORTC
```

```
call Wait
```

```
goto Loop
```

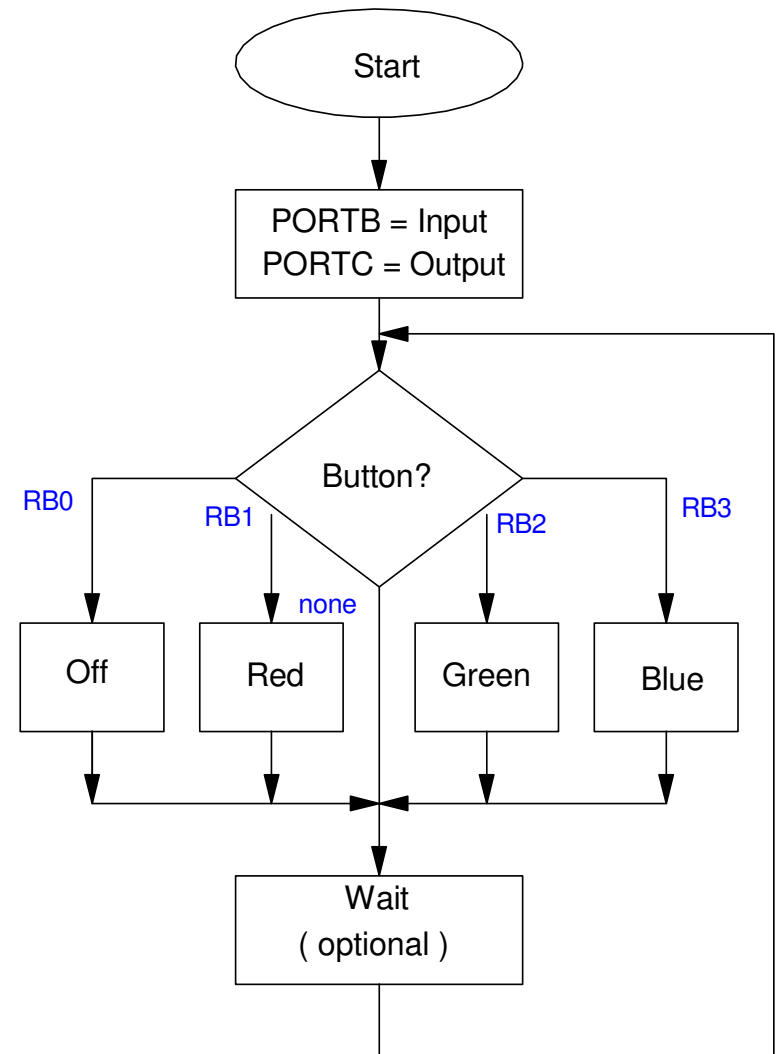

## Option 3: Change the brightness to 1600mcd (20%)


- Hardware: Change R
- Software: Make the duty cycle 20%

Loop:

```
    clrf    PORTC
    call    Wait
    call    Wait
    call    Wait


    movf    COLOR,W
    btfsc   PORTB,0
    movlw   0
    btfsc   PORTB,1
    movlw   1
    btfsc   PORTB,2
    movlw   2
    btfsc   PORTB,3
    movlw   4
    movwf   COLOR
    movff   COLOR, PORTC
    call    Wait

    goto    Loop
```

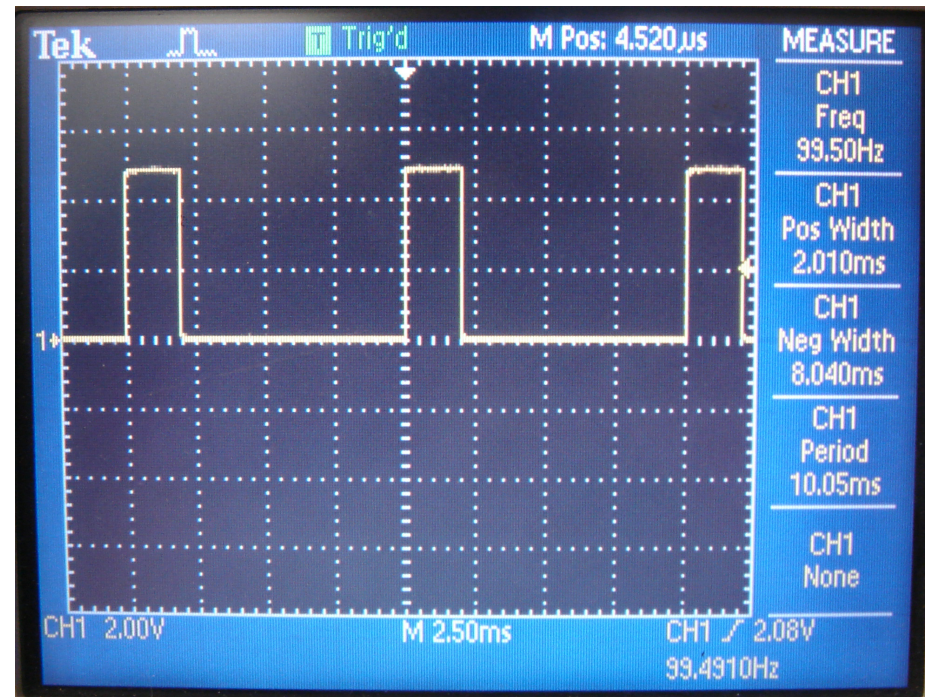


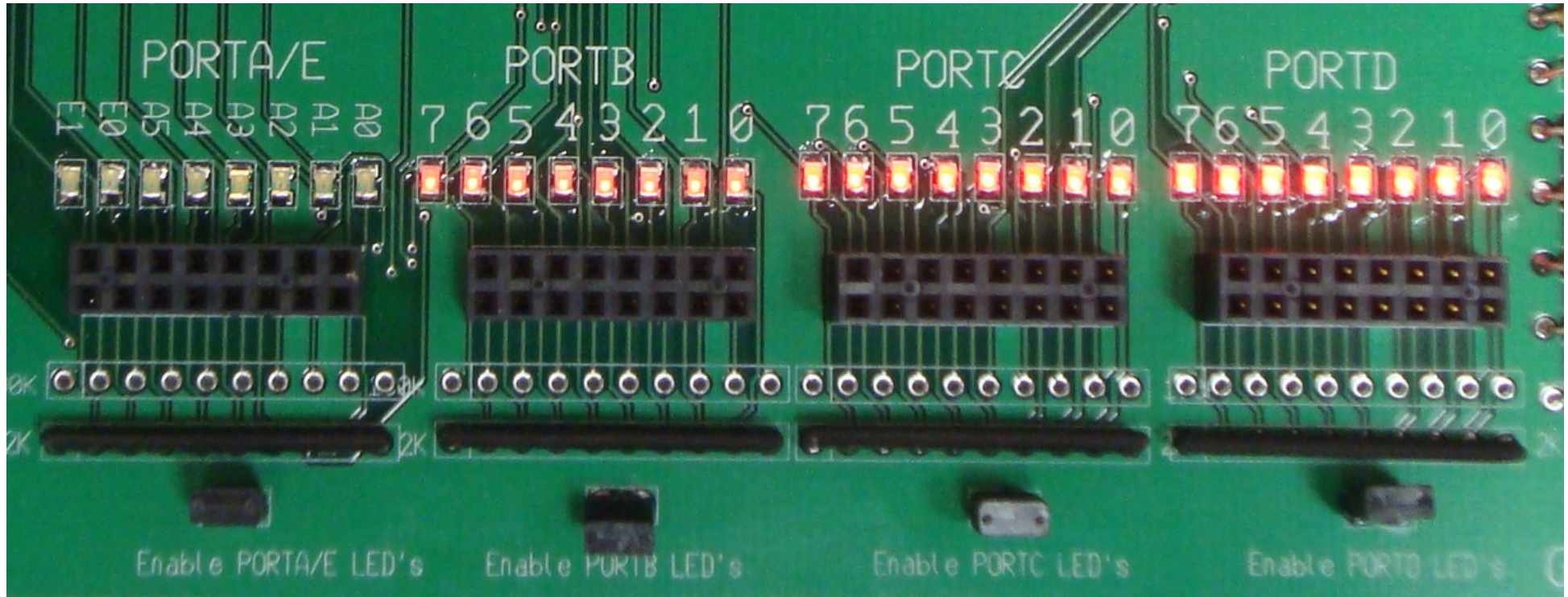
# Pulse Width Modulation

- Changing the duty cycle allows you to adjust how bright the LEDs are via software
- 5% (PORTB), 20% (PORTC), 90% (PORTD)


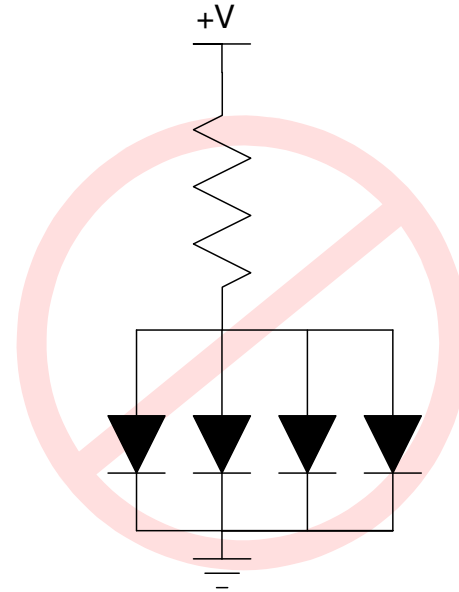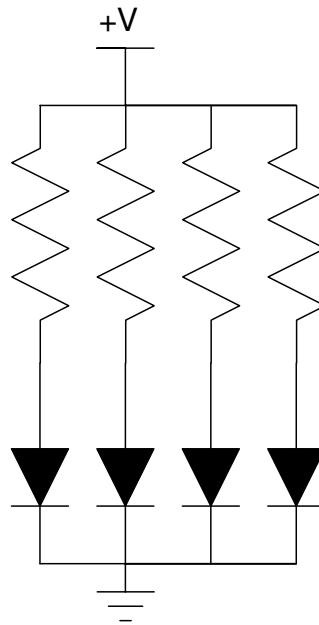
# Powering Multiple LEDs

- Placing in series works
- Placing in parallel with separate resistors works
- Placing in parallel does not work
  - The LED with the lowest  $V_d$  takes most of the load and burns out



---

## 1000W LED (90,000 lumens)

- When 900 Watts isn't enough
- <https://youtu.be/-JVqRy0sWWY>




---
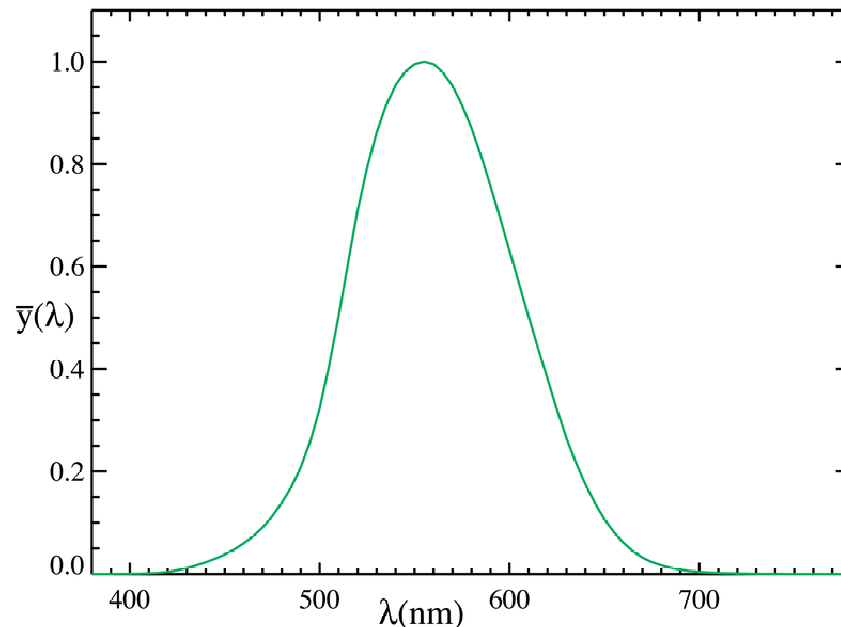
## Sidelight: What's the efficiency of LED light bulbs?

Depends upon how you define 100% efficient.

- The human eye is most sensitive to green light.
  - If you limit yourself to green light, 100% efficiency is 683 lm/W.
- If you want white light, that depends upon how much energy goes into each color.
  - Assume an ideal black body radiating at 5800K, band limited to (400nm - 700nm).
  - 215 lm / W = 100%



Sensitivity of the human eye to light: ([www.wikipedia.com](http://www.wikipedia.com))

---

---

# Efficiency of Light Bulbs

- 2021 numbers

	W, Lumens	Price		lm / W	eff
		new	@ 1000 hr		
Incandescent (c. 2000)	60W / 300 Lm	-	\$7.20	5.27	2.1%
Incandescent: GE 66247	43W / 620 Lm	\$1.36	\$6.52	14.4	5.7%
Halogen: Phillips 60W	43W / 750 Lm	\$1.46	\$6.62	17.4	6.9%
CFL: Philips 823031 CFL	13W / 860Lm	\$3.50	\$5.06	66.2	26.4%
LED: Sylvania 74765	8.5W / 800 Lm	\$0.83	\$1.85	94.1	37.5%
Street Lights:					
Mercury: GE 175W Street	175W / 7850 Lm	\$11.29		36	14%
Sodium: BulBrite	70W / 6000 Lm	\$8.95		86	34%
100W LED	100W / 9000 Lm	\$8.29		90	36%
LED Light (theory)				201	80%
Ideal Black Body	-	-		251	100%

---

---

## Implications:

- 1990: About 20% of the electricity produced in the U.S. went to lighting
- 2021: About 5% of the electricity produced in the U.S. goes to lighting.

This reduction means

- Less coal needs to be burned and less CO<sub>2</sub> is put into the atmosphere,
- Fewer power plants need to be built,
- Older, less efficient power plants can be retired, and
- Brown outs and blackouts are avoided - situations where energy demand exceeds supply.

This is why the less efficient lights were banned in Europe. You can still buy them in the U.S.

---

(1) [www.lighting.sandia.gov](http://www.lighting.sandia.gov)

(2) <https://www.eia.gov/tools/faqs/faq.php?id=99&t=3>

---

---

## Summary: LEDs

LEDs are

- Easy to connect to a PIC board
- Easy to turn on and off
- Very fast
  - > 100MHz very common
  - Must faster than a PIC

Hardware:

- If you need less than 5V and 25mA, use a resistor to connect an LED to the PIC board
- If you need more than 5V or more than 25mA, use a transistor

Software:

- Logic 0 (0V) turns off the LED
  - Logic 1 (5V) turns on the LED
  - PWM allows you to vary the brightness from 0% to 100% in software
  - note: you can change this in hardware if you want
-