## **Soldering LAB Worksheet for SD401**

Name
Group#
Date
Use the Digi-key.com website to answer the following questions using Datasheets
LED's
On your Soldering Board are two discrete LEDs, assuming a Red LED was used and the manufactures part# is WP7113SRD/J4 for this device and 20mA of forward current is being used as a reference.
What is the typical Vf of this device?
What is the Typical Luminous Intensity of the LED in milli candles?
What is the Max DC Forward current this device is rated for?
What is the Dominant Wavelength of this device?
What is the cost to purchase this LED in 1 lot vs 10 lot pricing?
Price of LED's x 1 lot = \$ Price of LED's x 10 lot = \$ Cost differential of the total =\$ (how much to save buying in quantity)
IC Packages
Using a PIC Microcontroller in SD401 required a PIC18F2620-I/SP be used
What is the Digi-key part#?
How many I/O ports does this microcontroller have?
How many 10-Bit A/D (ch) does this I.C. have?
How many leads (Pins) are on this package?
What page of the datasheet will you find the Package outline dimensions/ pitch etc.
Page #

## Soldering with Unleaded Solder

This lab project required Soldering and Leaded Solder was used, part# KE11	16-ND
What does 1 # of solder (Leaded) Cost \$	
What is its composition?	
What does the first number of the composition stand for?	
What does the second number of the composition stand for?	
What is the melting point of this solder in degrees Celsius?	
What is the shelf life of this Solder?	
Trace width Calculations Using Digi-keys Conversion Calculator for length and trace widt following	th answer the
Calculate the required trace width in mils of a trace 2121 mils lo 650mA of current	ong carrying
with a thickness of 1 oz/ft2 and a temperature rise of 20 deg F f room temperature of 68 deg F. the External Required Trace width would be?	
With the same information, use copper thickness of 0.5oz/ft2	
The External Required trace width would be?	mils
With the same information, use copper thickness of 2oz/ft2	
The External Required Trace width would be?	mils


Once the Through Hole PCB Soldering Kit has been completed

The Kit and the worksheet should be turned in to Dr. Glower or Jeff Erickson before Week 12

(1 Worksheet + 1 Practice Solder Board per Student) You may keep the Boards once graded
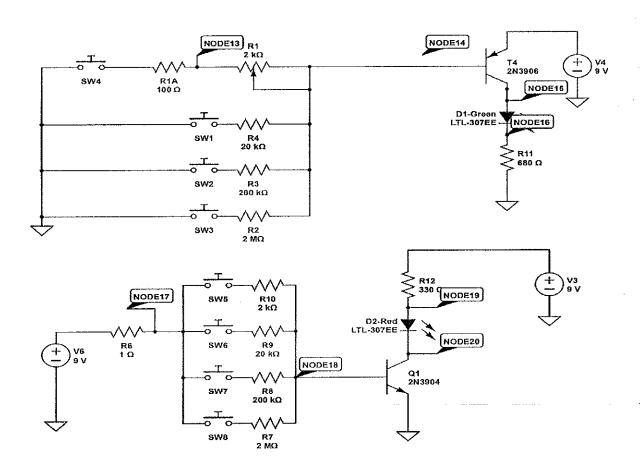
## Soldering LAB Worksheet for SD401

Using the Following Schematic, add the following through hole components and solder the board using unleaded (60/40 or 63/37 rosin core solder).



With SW8 Closed, will Q1 be in the

Cutoff region?

Saturation region?

Active Region?

With SW5 Closed, will Q1 be in the

Cutoff region?

Saturation Region?

Active Region?

With SW1 Closed, will T4 be in the

With SW2 Closed, will T4 be in the

Cutoff region?

Cutoff region?

Saturation region?

Saturation Region?

Active Region?

Active Region?

If Q1 is Saturated (on) the Voltage drop from Vce should be (circle one) 9V  $\,$  5V  $\,$  2V  $\,$  0.7 V  $\,$  0.2V  $\,$  0V

If Q1 is Saturated the Voltage drop from Base to Emitter (Vbe) should be 9V 5V 2V 0.7 V 0.2V 0V

If T4 is in the Cutoff region the voltage measured at the Collector should be (circle one) 9V 5V 2V 0.7V 0.2V 0V

If the LED D1 green was designed for 10mA, but measured 6mA, how would you increase the current to designed specifications (10mA)?

If T4 is in the Active region (voltage measured is 5.2V), would the LED still be on?

