
CircuitLab, Diodes, & Transistors

ECE 401 Senior Design I

Week #3

Please visit Bison Academy for corresponding lecture notes,
homework sets, and videos
www.BisonAcademy.com

Introduction

In ECE 401, you can choose from a dozen different circuits to build.

Regardless of which one you select, your overall design:


- Must operate at 5VDC
- Must have LEDs operating at 20mA +/- 5mA
- Must have one NPN and one PNP transistor (or more), capable of driving a 100mA load
- Must have at least one IC (PIC18F2620, MCP602 op-amp, 555 timer)

This lecture covers:

- Analysis and design of LED circuits,
 - Analysis and design of NPN and PNP electronic switches,
-

CircuitLab

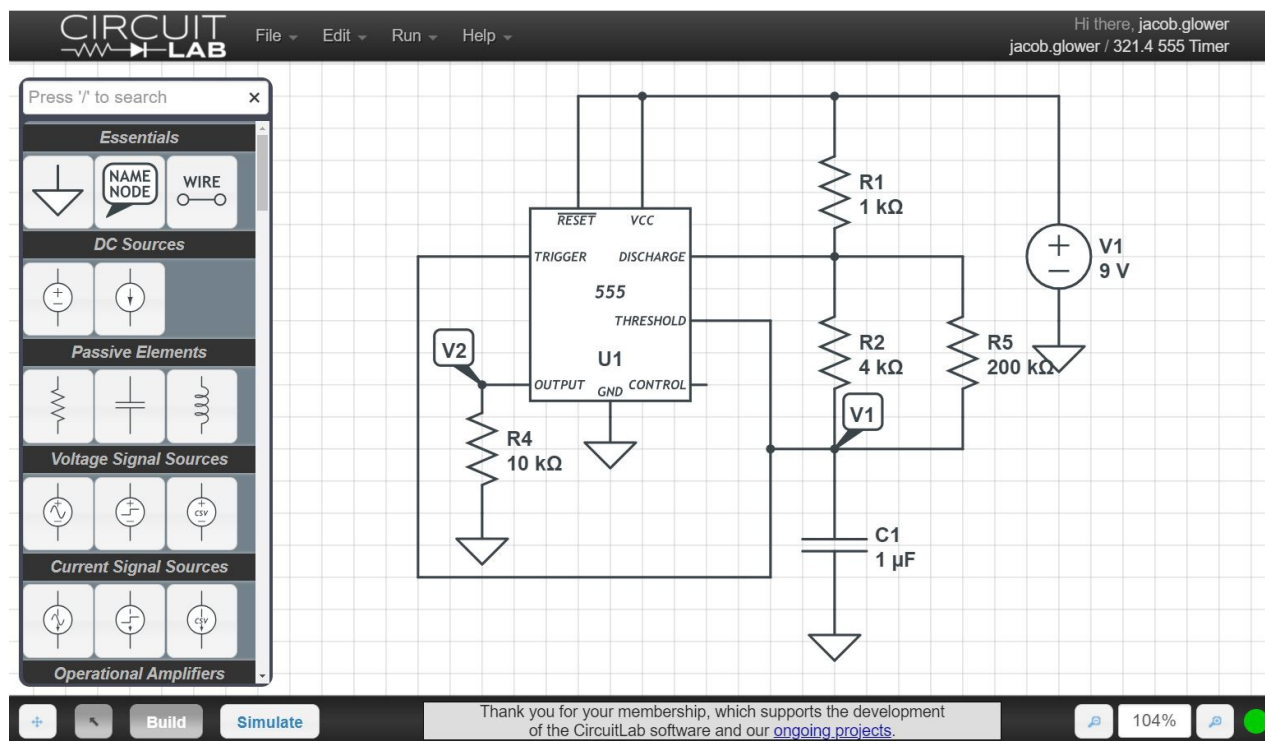CircuitLab is a circuit simulator, which is very similar to SPICE or PSpice, and has a graphical front end. The graphical front end makes CircuitLab very easy to use.



What CircuitLab Does

Lets you check your design using a nonlinear circuit simulator.

- Hand Calculations: Usually make approximations
 - Ideal Diode
 - $V_{ce(sat)} = 0.2V$
- CircuitLab: More accurate, nonlinear models

Lets you adjust your circuit if necessary

- Tweak to set the current through the diodes to 10mA
- Tweak to set the duty cycle to 50%
- etc.

Once your design is finalized, you can build it on a breadboard

Classes where CircuitLab is Useful

Circuits I and II

- Linear Circuits

Electronics I and II

- Nonlinear Circuits

Digital Systems

- Boolean Logic
- Controls Systems
- Dynamic Systems

Likewise, CircuitLab is pretty useful



Signing Up for CircuitLab

There are several ways you can use CircuitLab:

- **Trial Version:** If you don't register or sign in, you're using the trial version. This limits you to 1/2 hour per session and you cannot save your work.
 - **Free Version:** Register with CircuitLab using your NDSU email address (@ndsu.edu). The ECE department pays for a site license - so all NDSU students can use CircuitLab for free. There is no time limit and you can save your work.
 - **Personal Version:** Sign up with your personal email account at a cost of \$24/year. Again, there is no time limit and you can save your work. Plus, you still have your work after you graduate.
-



Diodes

- Covered in ECE 320 Electronics I.

Diodes act as valves:

- Current allow current to flow from the anode to the cathode,
- Current block current from flowing the other way.

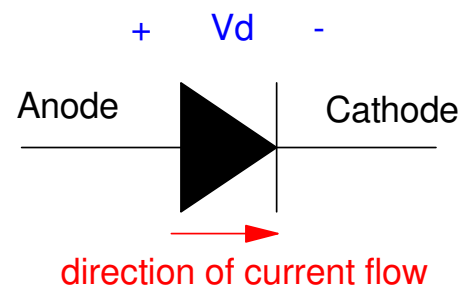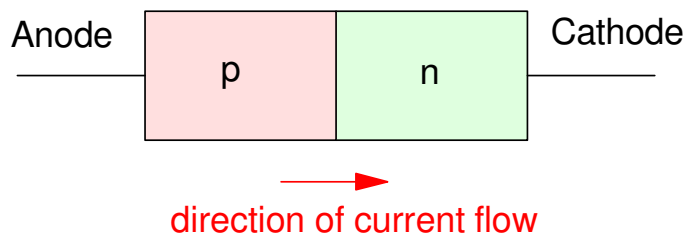Because of this, the symbol for a diode looks like an arrow: this arrow serves as a reminder for which way the current can flow.



Symbol for a diode: Diodes only allow current to flow from the anode to the cathode

Diode VI Characteristics

Diodes are nonlinear devices


- This makes analysis of diode circuits difficult

Ideal Diode

- Simplified model of a diode
- $I_d = 0$ when $V_d < V_f$
- $V_d = V_f$ when $I_d > 0$

Not perfect, but usually good enough

- Use CircuitLab to get better answers

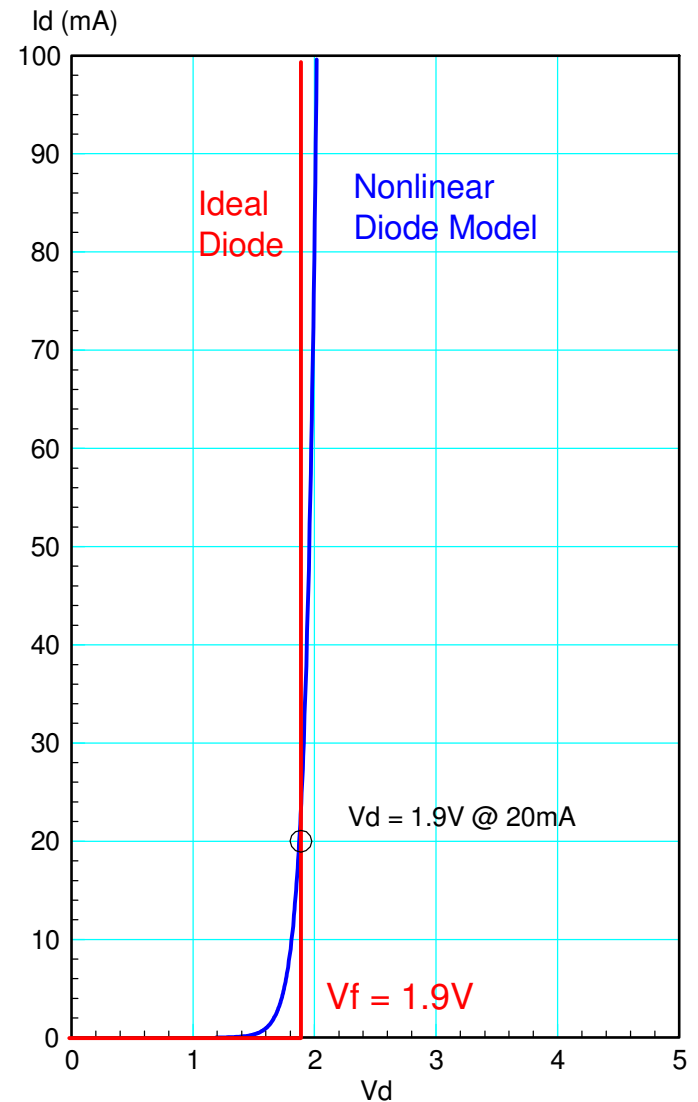


Ideal Diode Model

V_f acts like a turn-on voltage:

- Diode turns on if you apply more than V_f
- Diode turns off if you apply less than V_f

V_f depends upon the diode

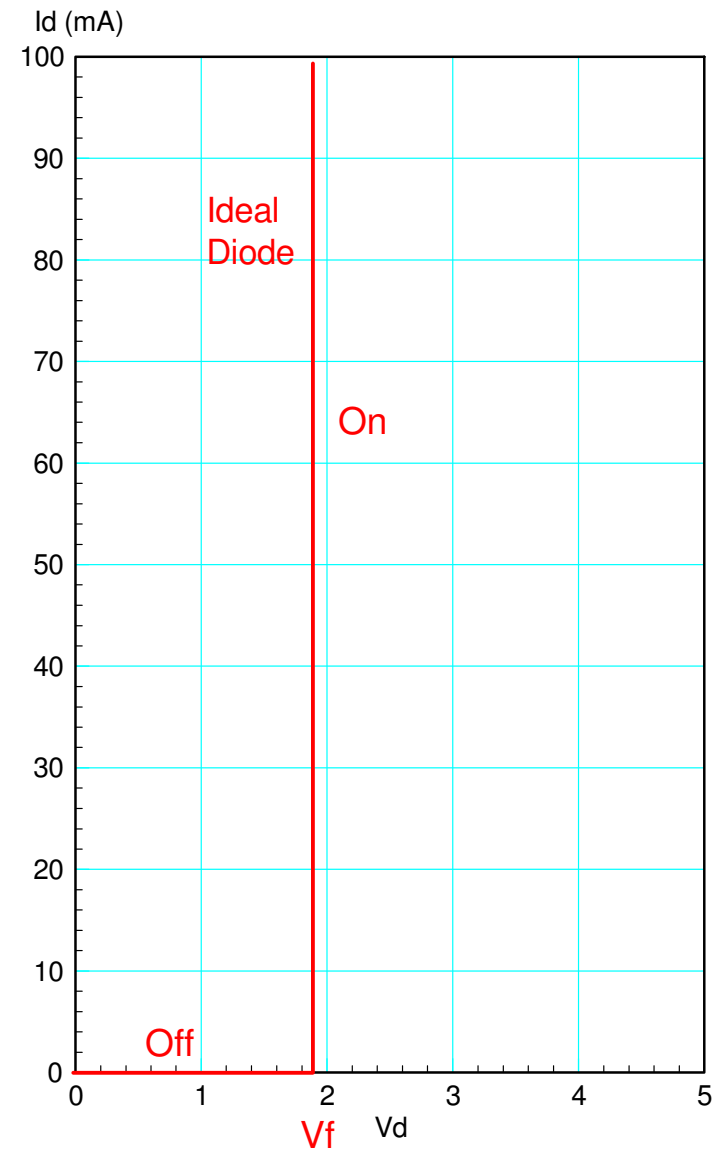- Germanium: $V_f = 0.3V$
- Silicon: $V_f = 0.7V$
- Red LED: $V_f = 1.9V$
- Yellow LED: $V_f = 2.0V$
- Green LED: $V_f = 2.0V$



Diode Example (CircuitLab)

In CircuitLab, you can build this circuit through drag and drop.

- R rotates the element
- Double Click to change values
- k = 1000
- M = million
- m = milli
- u = micro



Make sure you have a ground (CircuitLab insists on this)

The screenshot displays the CircuitLab interface. On the left, a vertical toolbar contains various components: Essentials (arrow, NAME NODE, WIRE), DC Sources (two diodes), Passive Elements (resistor, capacitor, inductor), and Voltage Signal Sources (AC, DC, CSV). The main workspace shows a circuit diagram with a sine wave source labeled 'V1 sine 1 kHz' connected to a diode labeled 'D1 1N4004'. A ground symbol is connected to the bottom terminal of the diode. On the right, a panel titled 'My Device Models' shows a list of diode models (1N4001 to 1N4005) with 'Buy' buttons. Below this list is a 'View All Diodes In Stock' button. To the right of the list is a detailed configuration panel for the selected diode (D1, Part#: 1N4004), showing parameters like I_S, R_S, C_J0, and M_J, along with 'Save Custom Device Model' and 'Import SPICE Model' buttons.

Once completed, you can determine the voltages and currents by

- Clicking on Add Expression and then click on the voltage node to see that voltage
- Click on one side of a resistor to see the current through that resistor

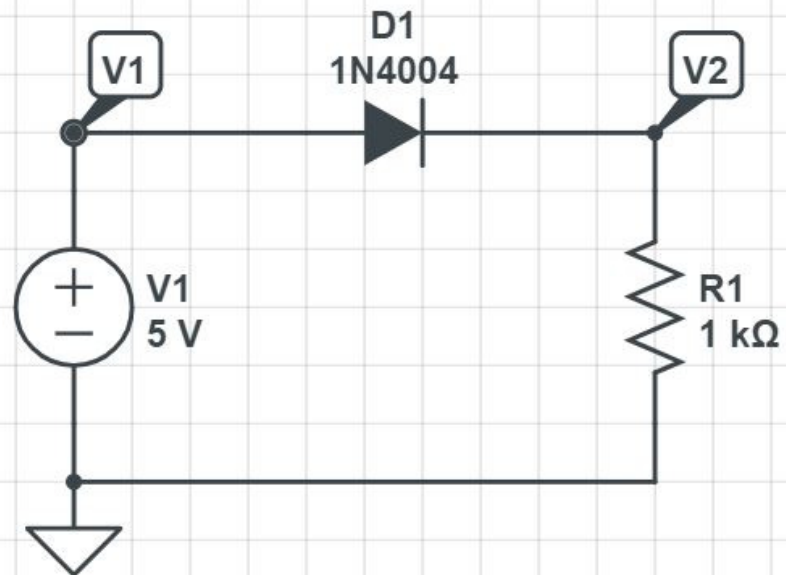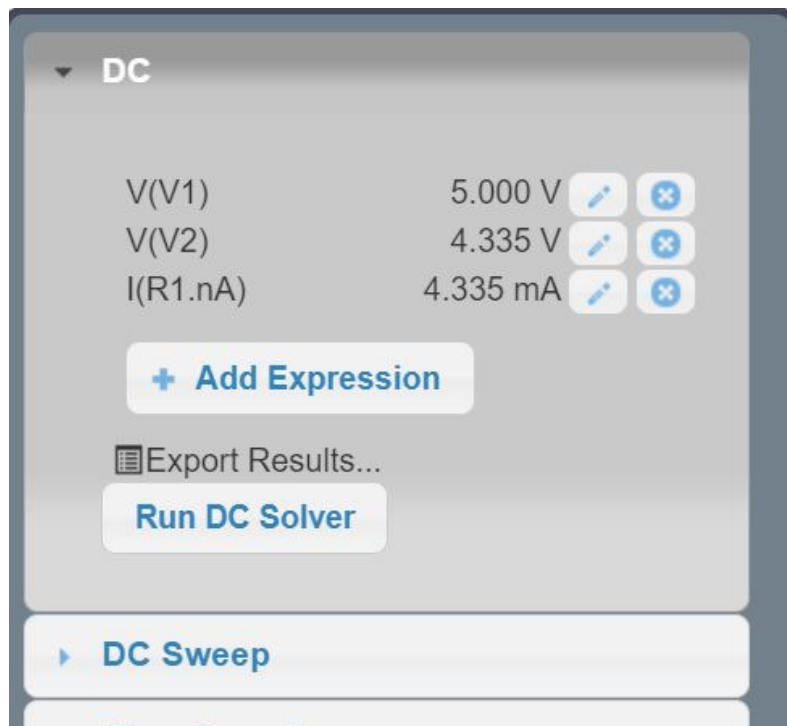
When the diode is turned on ($I_d > 0$), the voltage drop is 0.7V (ish)



When you try to push current backwards, the diode turns off


- $I_d = 0$ (ideal diode)
- $I_d = -76.90\text{pA}$ (CircuitLab)

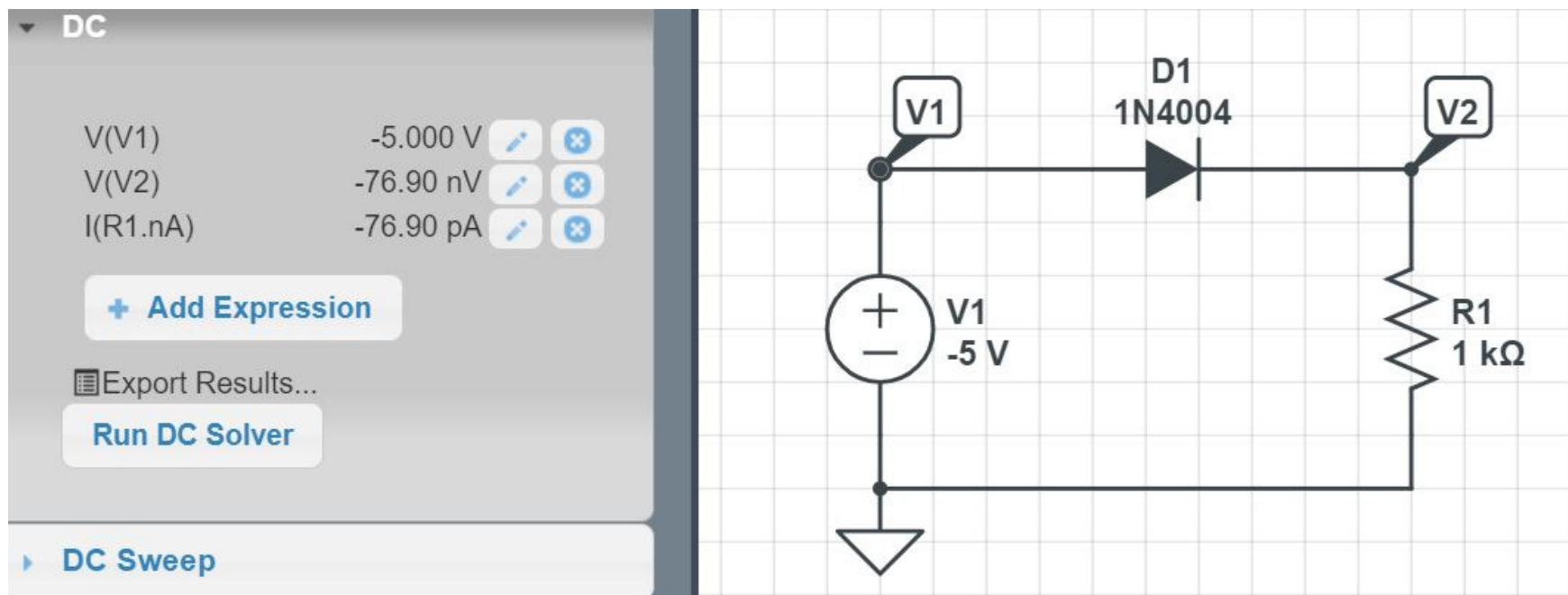Diodes *do* conduct current when reverse biased, but it's really small




CircuitLab & Time Domain Simulations

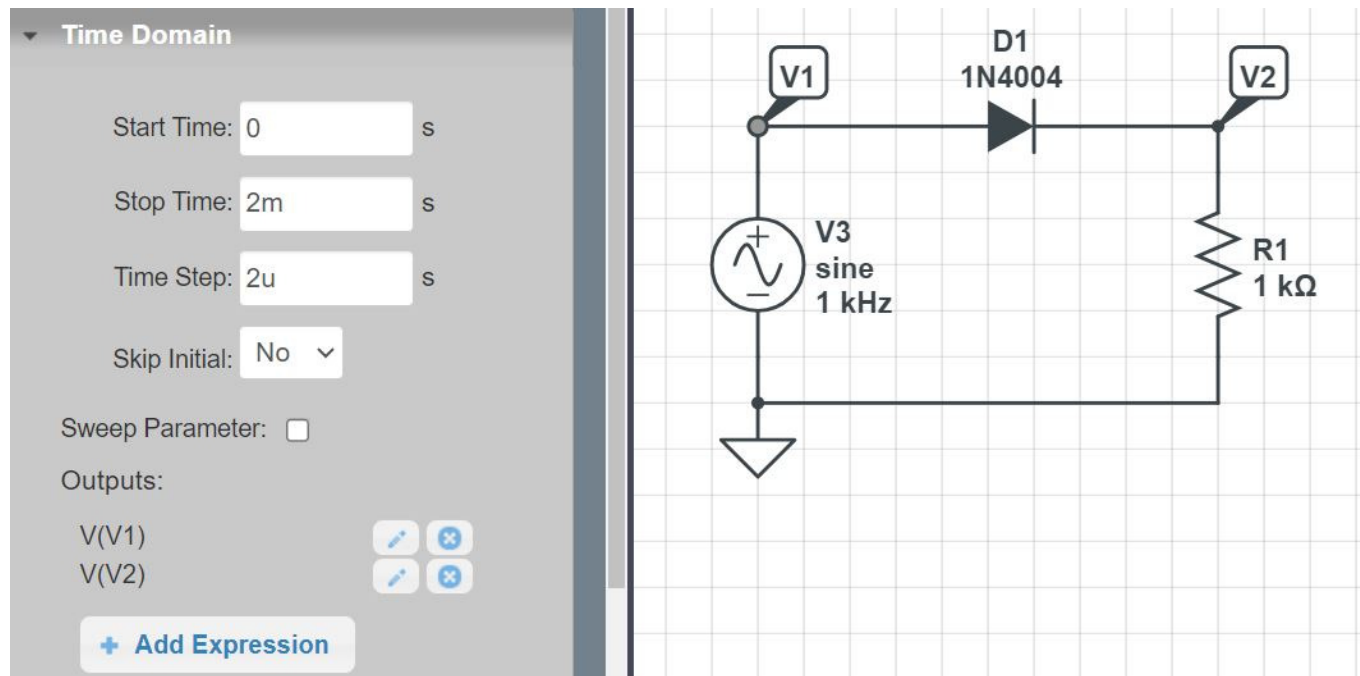- Similar to an oscilloscope
- Apply a sine wave for V3
- Run the simulation for 2-3 cycles
- Set the sampling rate 1000x smaller (gives 1000 points on the graph)



Resulting Waveform:

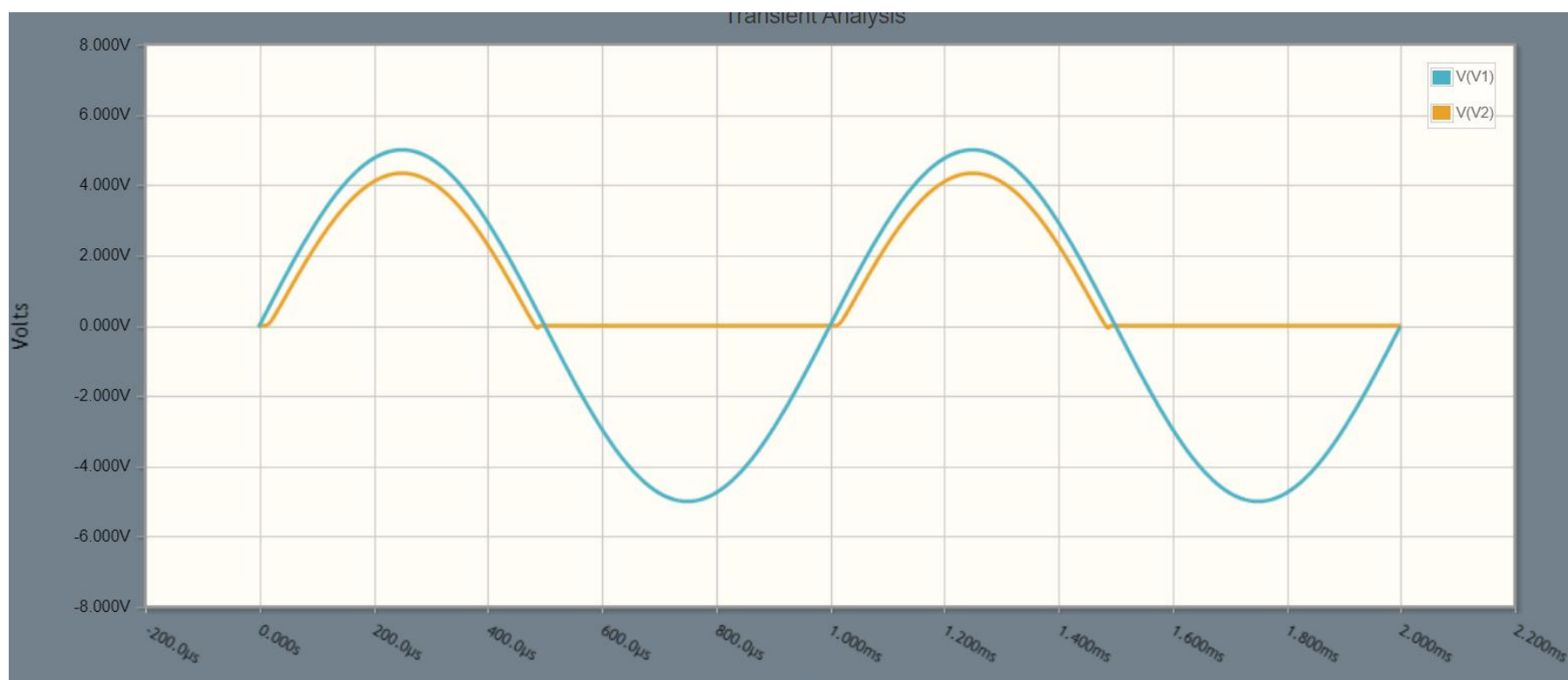- When $V_{in} > 0.7V$, the diode turns on
 - $V_{out} = V_{in} - 0.7V$ (ish)
- When $V_{in} < 0.7V$, the diode turns off
 - $V_{out} = 0V$



Diode Circuit Analysis:


- Determine which diodes are on and off
 - Not always that easy
- Replace with the ideal diode model
- Determine voltages and currents

Calculations:

$$I_1 = \left(\frac{5V - 0.7V}{1k} \right) = 4.3mA$$

$$I_2 = \left(\frac{5V - 1.9V}{2k} \right) = 1.55mA$$
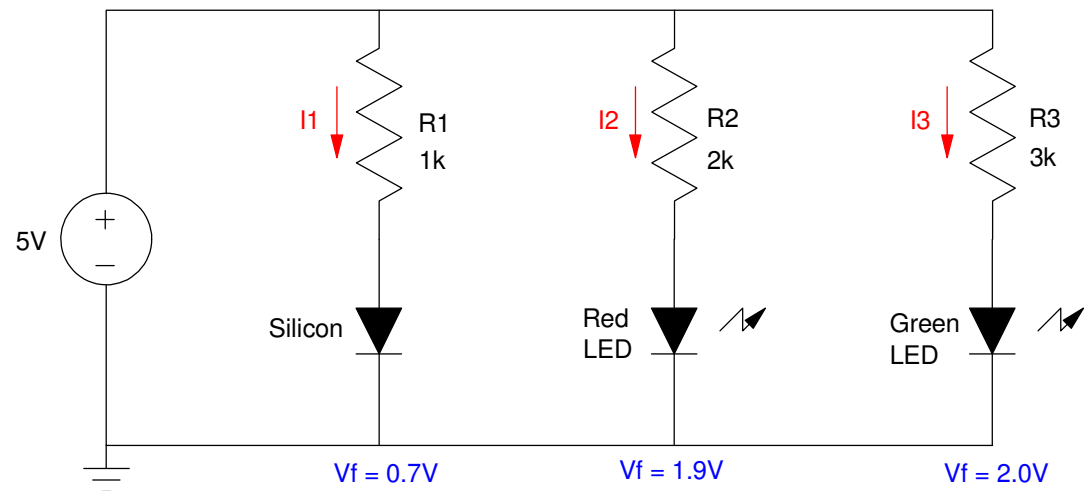
$$I_3 = \left(\frac{5V - 2.0V}{3k} \right) = 1.00mA$$



Diode Circuit Design:


- Pick the current desired
 - Light is proportional to current
- Calculate the resistance needed

Example: Set $I_d = 20\text{mA}$

$$R_1 = \left(\frac{5\text{V} - 0.7\text{V}}{20\text{mA}} \right) = 215\Omega$$

$$R_2 = \left(\frac{5\text{V} - 1.9\text{V}}{20\text{mA}} \right) = 155\Omega$$
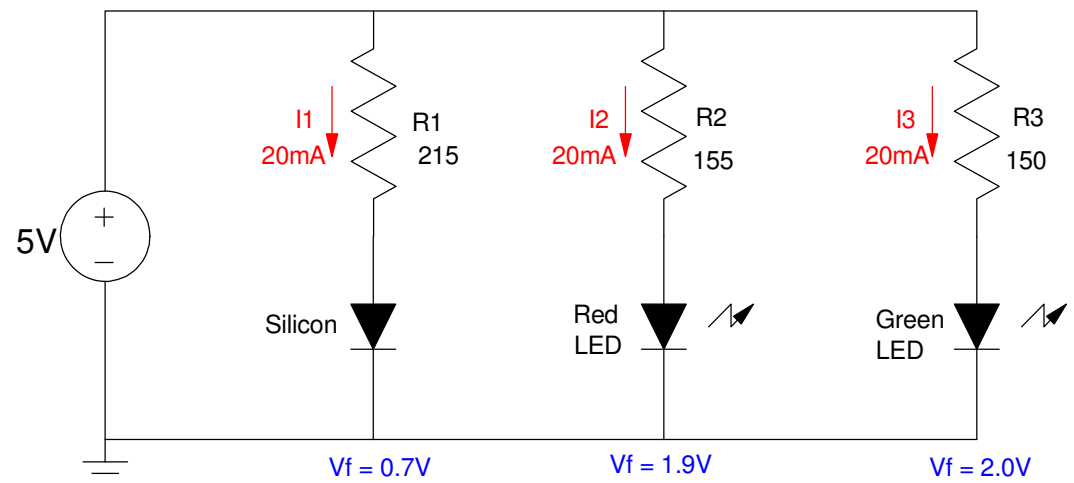
$$R_3 = \left(\frac{5\text{V} - 2.0\text{V}}{20\text{mA}} \right) = 150\Omega$$



Light Emitting Diodes (LEDs)

LEDs are nothing more than diodes - except that they produce light proportional to the current flowing through them. As diodes, they can be approximated with an ideal-diode model:

- $I_d = 0$ if $V_d < V_f$
- $V_d = V_f$ if $I_d > 0$

The on-voltage (V_f) depends upon the diode and is usually specified in the diode's data sheets:

LED	V_f	mcd	Wavelength	Cost	Digikey PN
Red	1.9V @ 20mA	30mcd @ 20mA	645nm	\$0.13	732-5016-ND
Yellow	2.0V @ 20mA	450mcd @ 20mA	592nm	\$0.18	732-5018-ND
Green	2.1V @ 20mA	140mcd @ 20mA	572nm	\$0.21	732-5017-ND


With LEDs, brightness is proportional to current

Assuming a 9V source (the kit assume you're using a 9V battery). the current and brightness of the first diode (330 Ohms) is:

$$I = \left(\frac{9V - 2.0V}{330\Omega} \right) = 21.21mA$$

The brightness is then proportional to this current where 20mA = 450mcd:
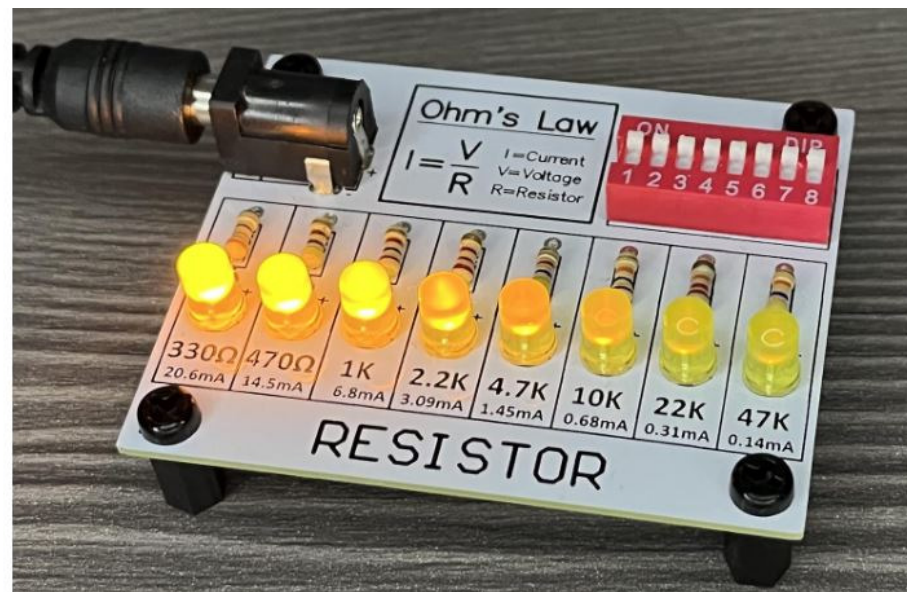
$$\left(\frac{21.21mA}{20mA} \right) 450mcd = 477.2mcd$$





Voltage Regulation

In ECE 401,

- Power to your PCB comes from a 9V battery, while
- Your components on your PCB operate off of 5VDC.

Solution: Use a LM7805 regulator

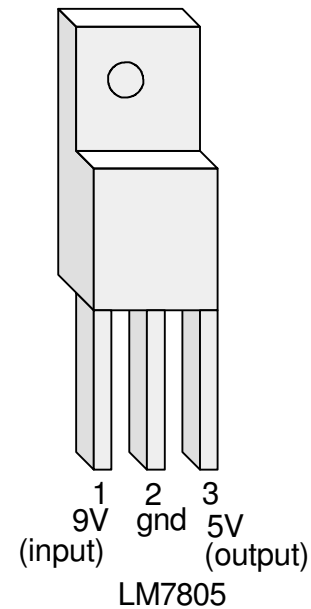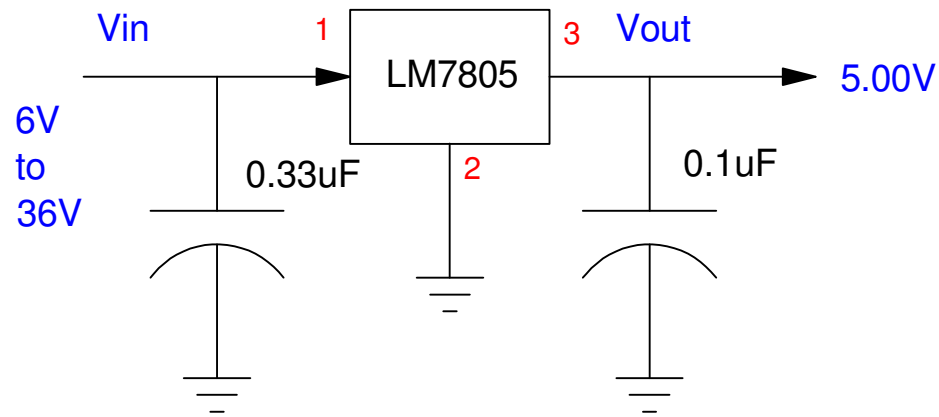- Pro: Simple circuit
- Con: Efficiency = 55% @ 9V




Example:

- Convert 9V down to 5V, and
- Drive an LED at 10mA from the 5V source

Assuming a red LED

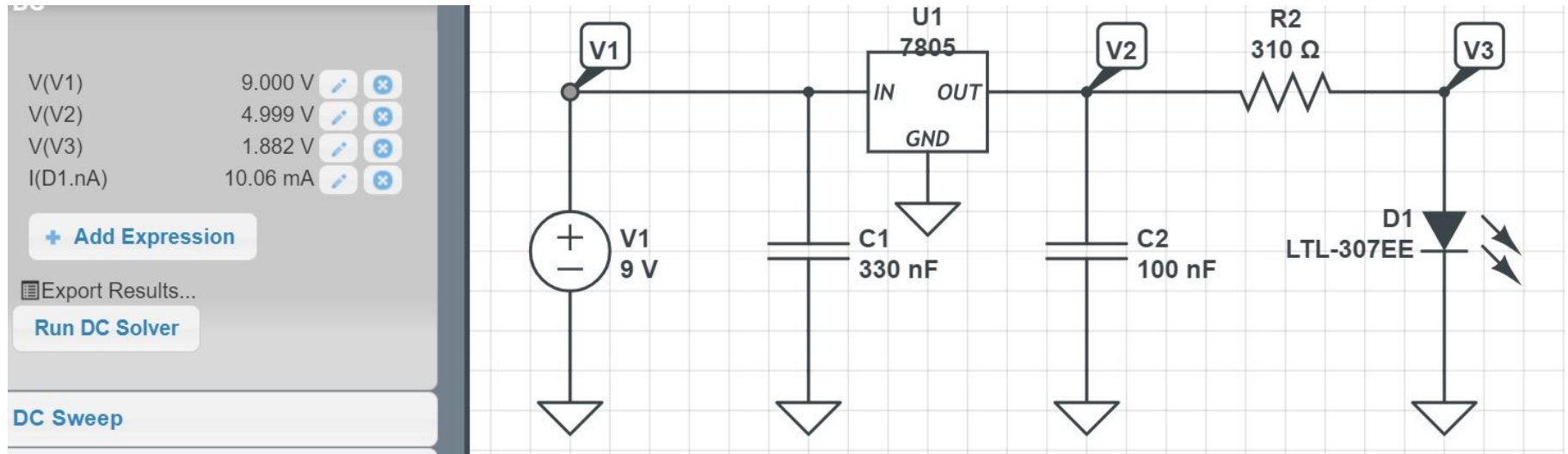
$$R = \left(\frac{5V - 1.9V}{10mA} \right) = 310\Omega$$



Interpreting the Results:

- $V2 = 5V$ (close)
 - The 7805 is doing its job
- $V3 = 1.9V$ (close)
 - The red LED is on
- $I3 = 10mA$ (close)
 - $R2$ is correct

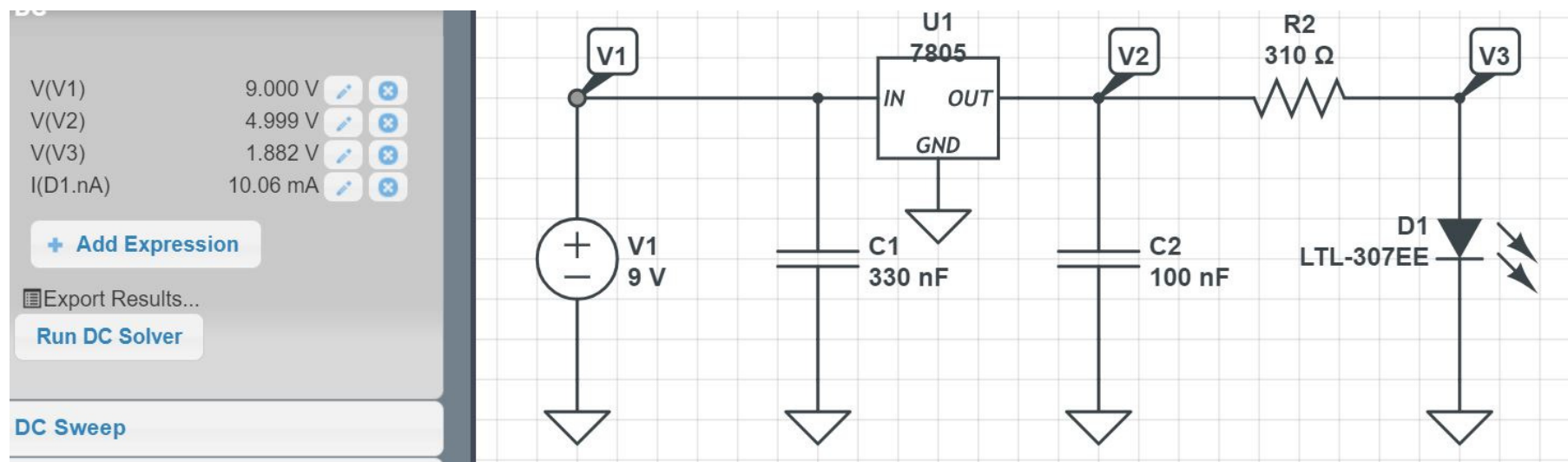You could find tune $R2$ if you really want 10.00mA exactly.



Reverse Polarity Protection & Overcurrent Protection

Another requirement for your PCB in ECE 401 is to add

- Reverse polarity protection
 - connecting 9V to your PCB backwards will not fry your PCB
- Overcurrent protection
 - if your circuit draws too much current, a fuse blows.


There are several ways to do this.

Method #1: Diode + Fuse.

- Diodes do not allow current to flow backwards
 - Blocks current if the 9V battery is inserted backwards
- Fuse blows if the load is too much
 - 1 Ohm resistor replaces the fuse for ECE 401 (2 cents)

Problem:


- Drops 0.7V through the diode

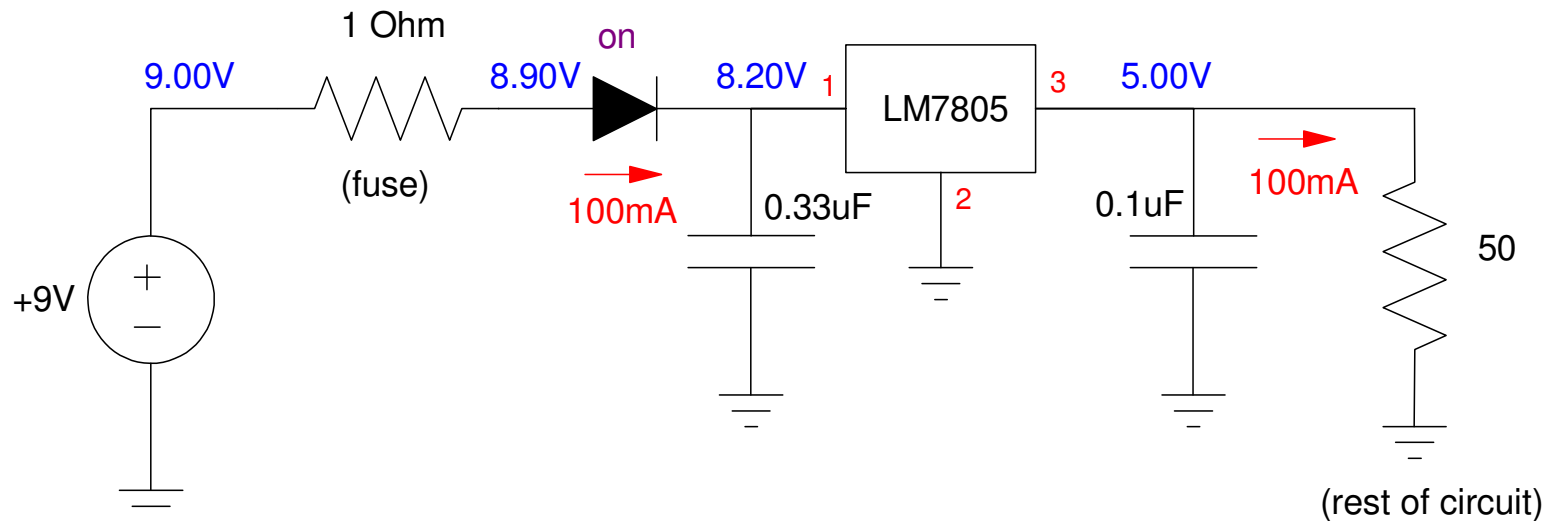

Method #2: Fuse + Diode.

Add a reverse biased diode to ground

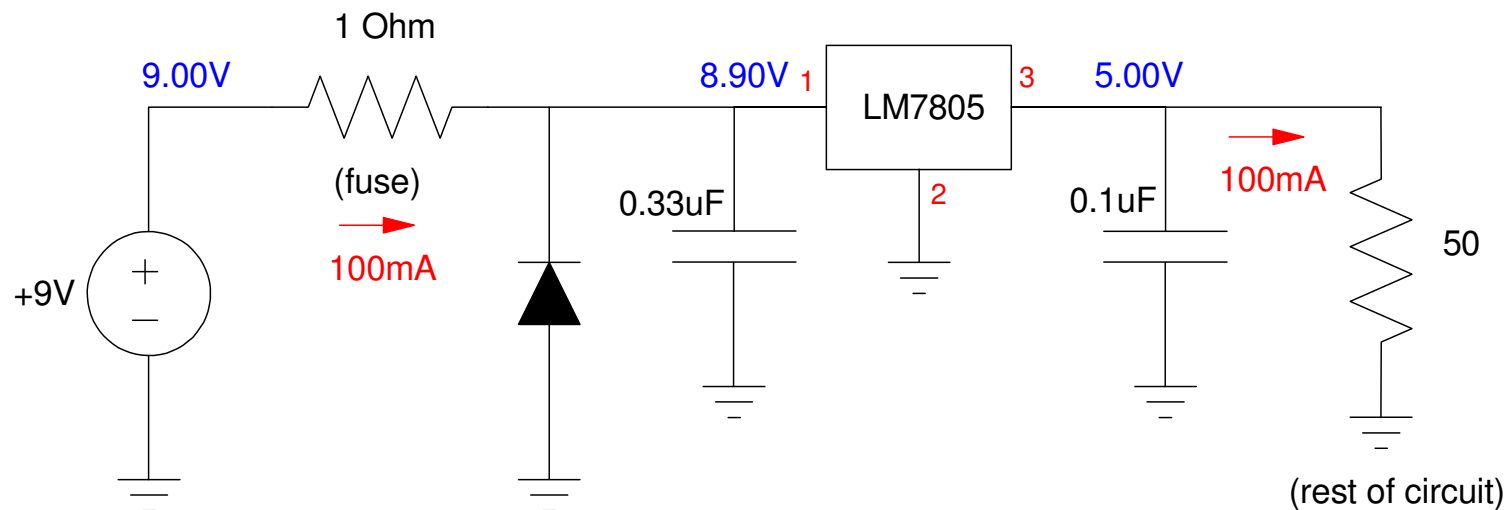- If the 9V battery is connected correctly, the diode remains off.
- If the 9V battery is reversed,
 - The diode turns on, limiting the voltage to the LM7805 to $-0.7V$,
 - The current through the fuse becomes large (9A), blowing the fuse.



BJT Transistors

Bipolar Junction Transistors

- Electronic switches (you can turn a device on and off using 0V & 5V),
- Which amplify current (1mA can turn on and off a device which draws 100mA)

The current amplification and the maximum current a given BJT transistor can handle depends upon which transistor you're using.



Spec	3904 NPN	3906 PNP
Current Gain (min)	100	100
Max Current	200mA	200mA
V _{be} (on)	0.7V	0.7V
V _{ce} (sat)	0.2V	0.2V
Cost (ea)	\$0.11	\$0.11

NPN and PNP Transistors

Two types of BJT transistors exist:

- PNP: an electronic switch which connects your device to +5V, or
- NPN: an electronic switch which connects your device to ground.

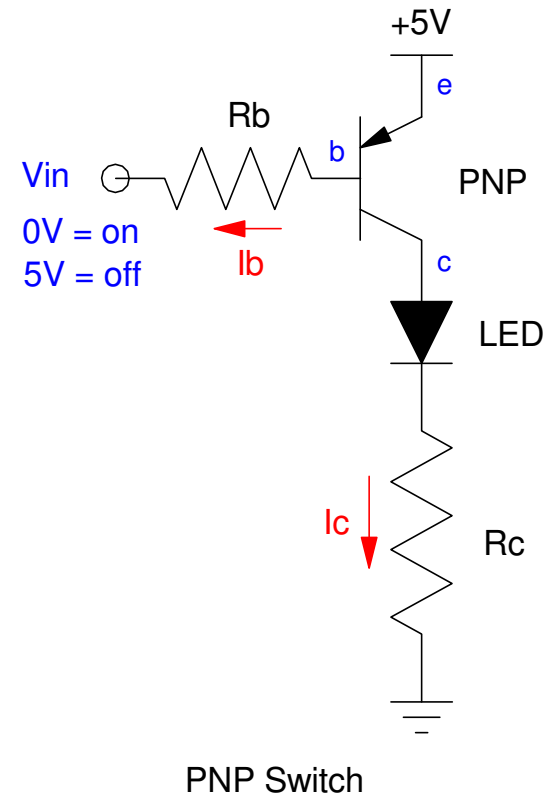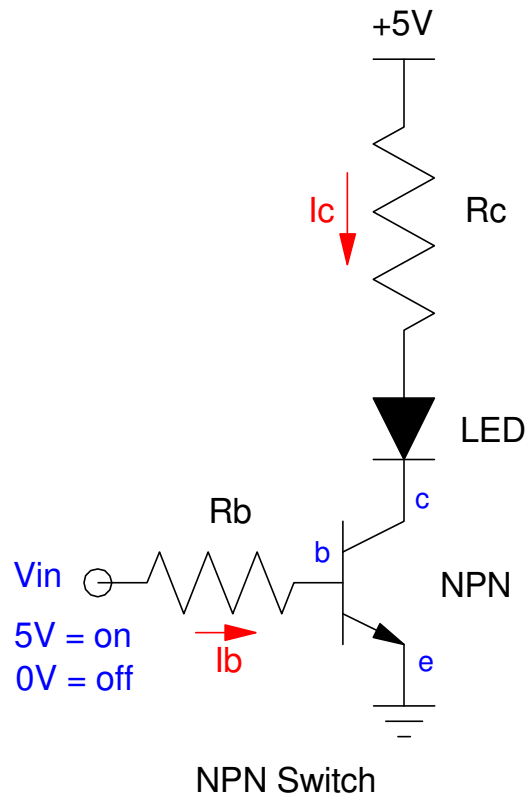The basic circuit for each of these are as follows:



Diode from Base to Emitter

The arrow going between the base and the emitter is all important:


- It represents a diode (a pn junction)
- It tells you the direction current flows
- The base current controls the collector current

I_b limits the collector current

$$I_c = \beta I_b = 100 I_b$$

It does this by dumping voltage

- Whatever it takes to set I_c

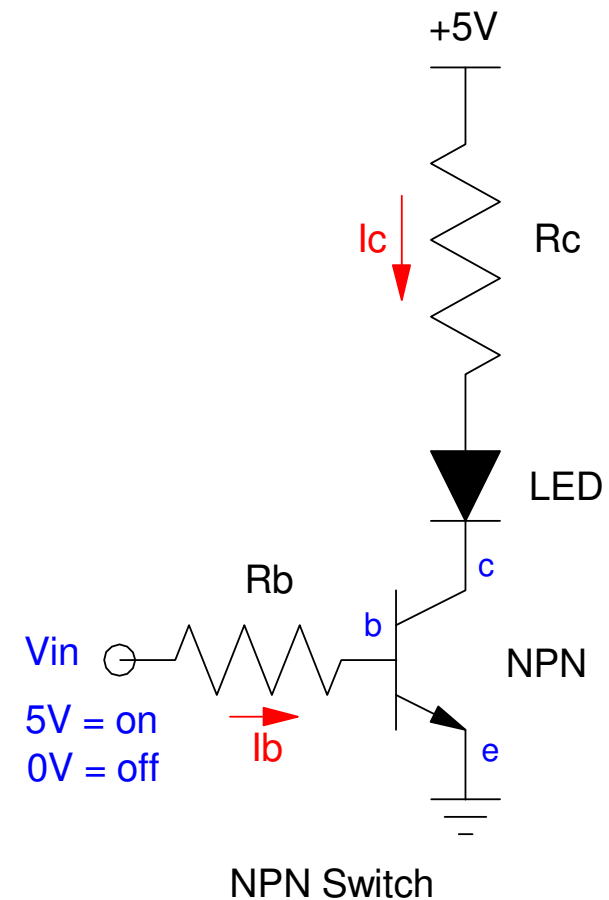


Load Lines

A good way to see how a transistor switch operates

- When $I_c = 0\text{mA}$, $V_{ce} = 5\text{V}$
 - the x-axis intercept
- When $V_{ce} = 0\text{V}$, $I_c = 20\text{mA}$
 - the y-axis intercept

The line connecting these two points is called *the load line*.

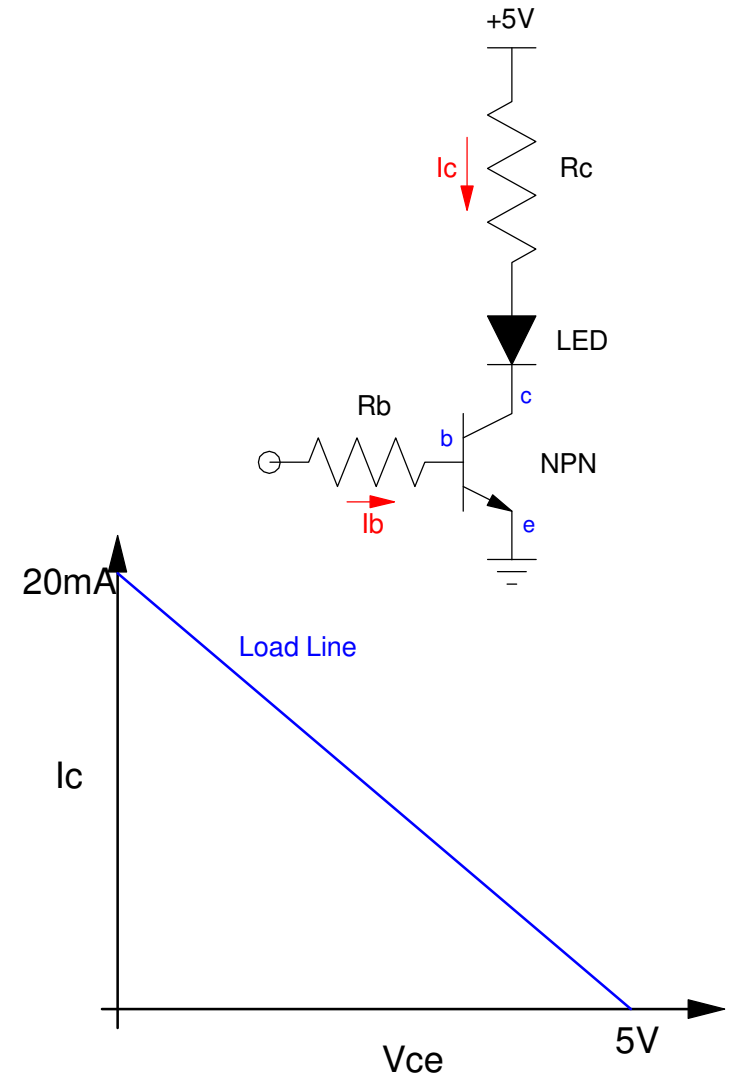Any solution has to be on the load line somewhere.



Off State:


- $I_b = 0$
- $I_c = 100 \cdot I_b = 0$
- $V_{ce} = 5V$

Active Region

- $0mA < I_b < 20mA$
- $5V > V_{ce} > 0.2V$
- $I_c = 100 \cdot I_b$

On State

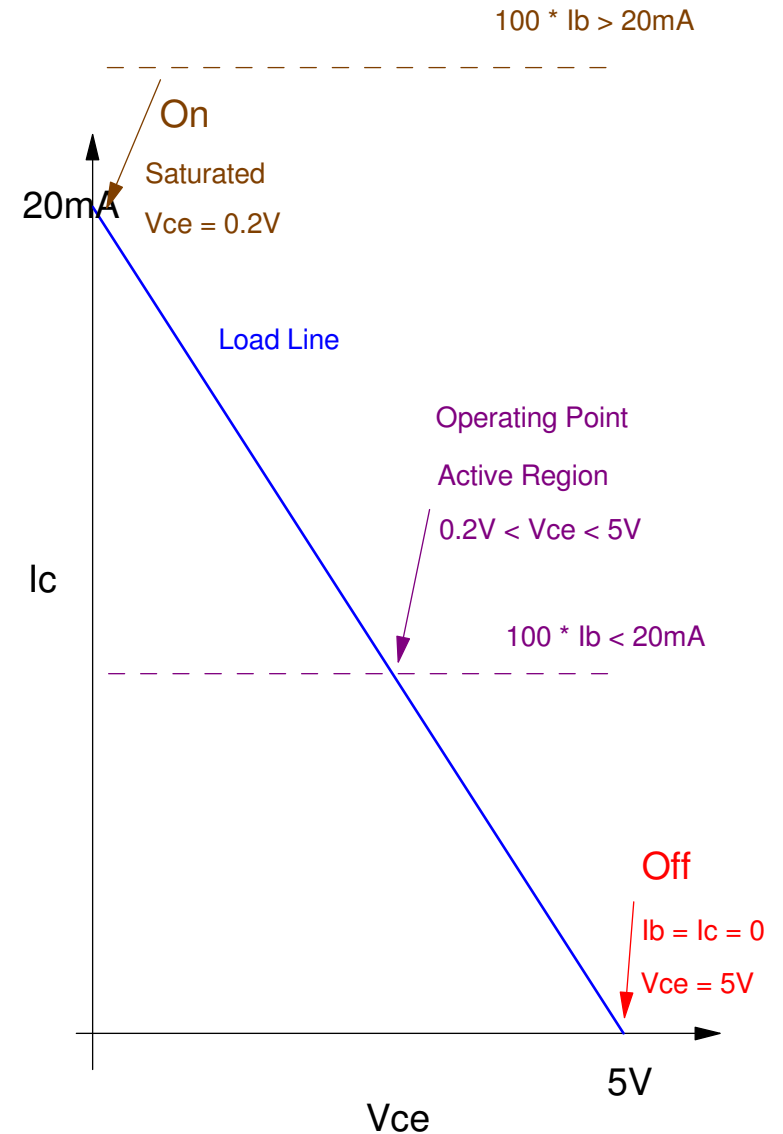- Saturated Region
- $100 \cdot I_b > 20mA$
- $V_{ce} = 0.2V$



The Active Region is Bad

You want to operate in the ON and OFF state

Off State


- $I = 0$
- $P = V * I = 0$

On State

- $V = 0.2V$ (almost zero)
- $I = 20mA$
- $P = 4mW$ (almost zero)

Active Region

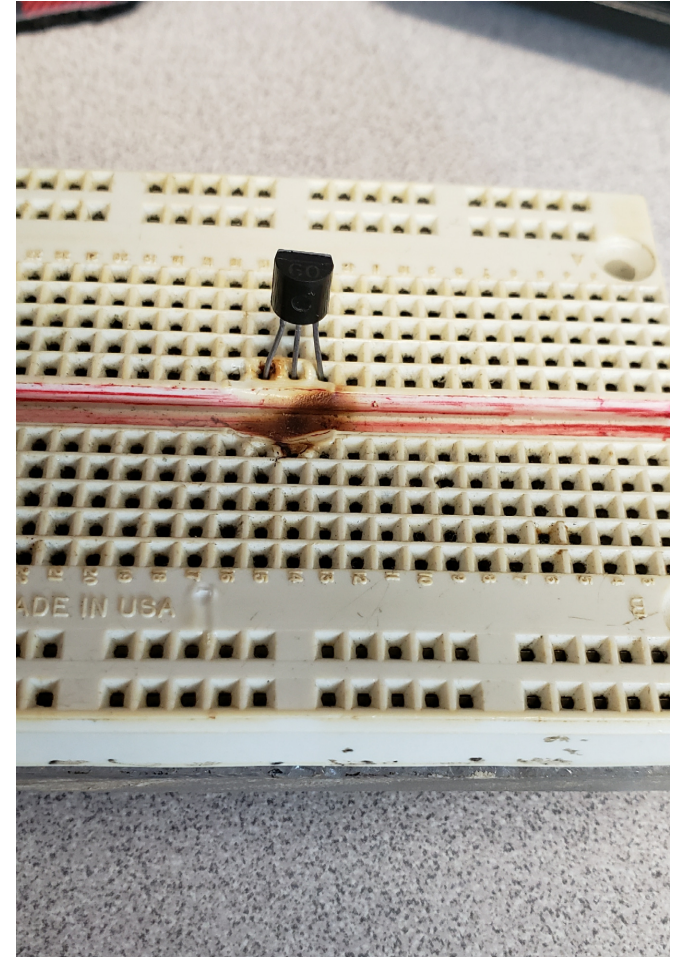- $P = V * I$
- The transistor gets hot
- You start to melt your breadboard



Analysis of Transistor Switches:

- Same equations for PNP and NPN

Off State

- Easy: $I_b = I_c = 0$

On State:

$$V_{ce} = 200mV$$


$$I_c = \left(\frac{5V - V_f - V_{ce}}{R_c} \right)$$

$$I_b = \left(\frac{5V - 0.7V}{R_b} \right)$$

Check that you're saturated:

$$\beta I_b > I_c$$

$$I_b > \left(\frac{I_c}{100} \right)$$

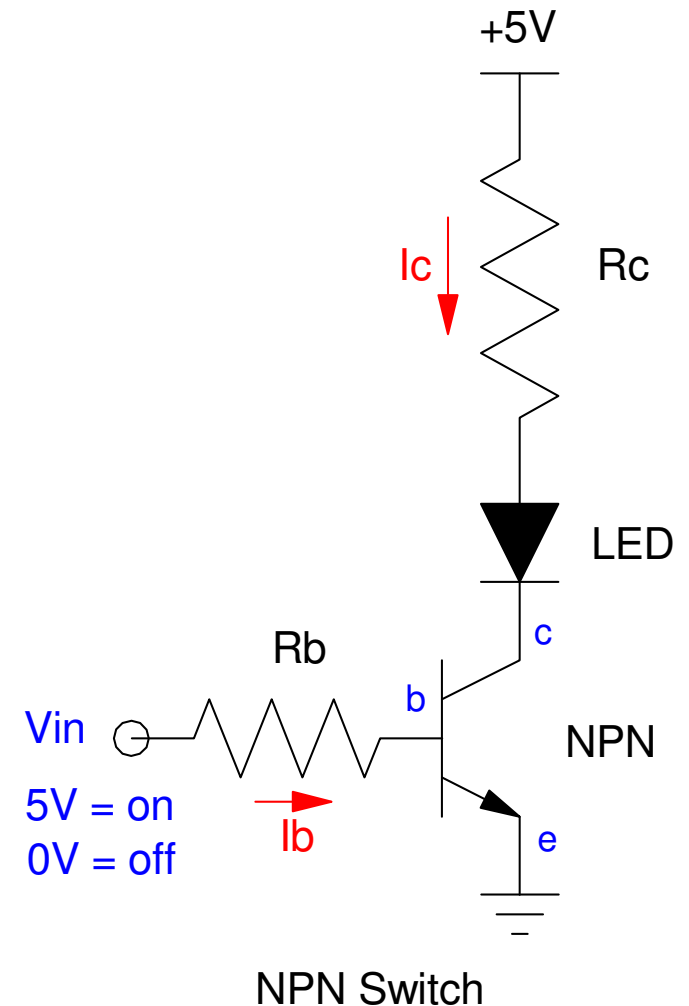

BJT Switch Example


Assume

- $R_c = 50 \text{ Ohms}$
- $R_b = 1k \text{ Ohms}$
- $V_f = 1.9V$ (red LED)
- 3904 NPN transistor with a current gain of 100

What you expect when $V_{in} = 5V$ is


- $V_b = 0.7V$ *the drop across a silicon diode*
- $V_c = 0.2V$ *saturated*
- $I_c = 58.0mA$
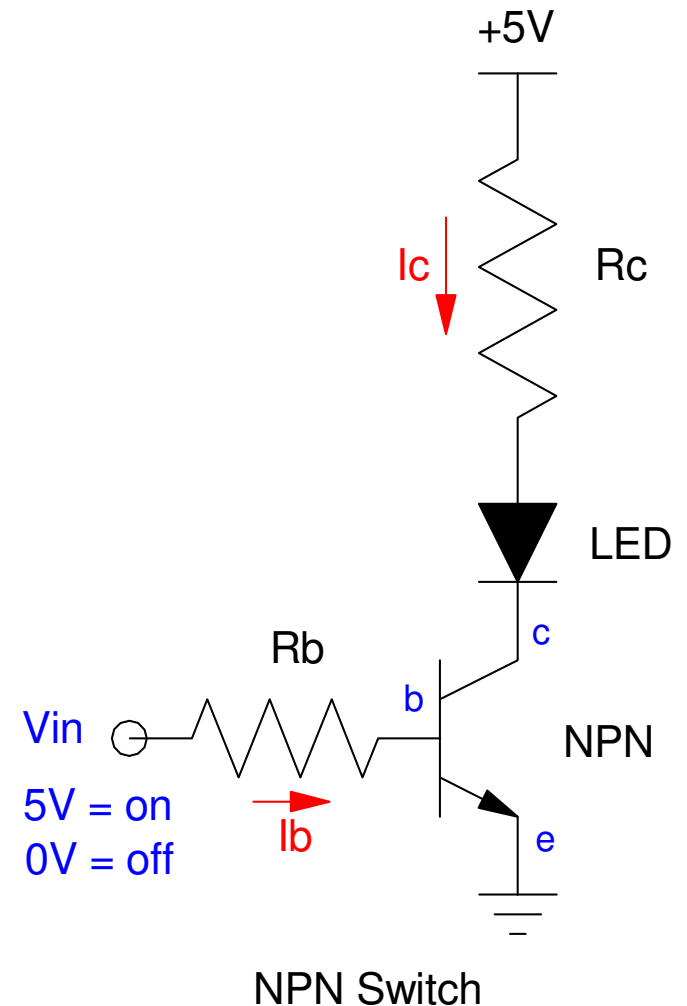
$$I_c = \left(\frac{5V - 1.9V - 0.2V}{50\Omega} \right) = 58.0mA$$



In CircuitLab, what you get is close but slightly different:

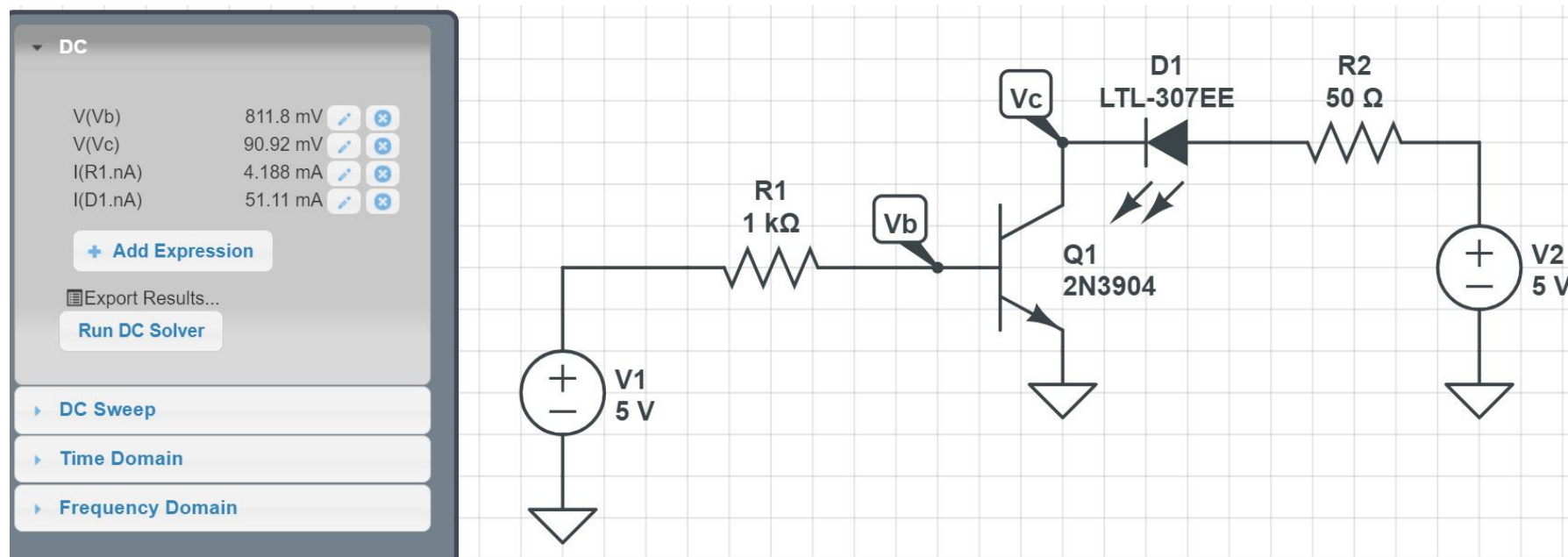- $V_b = 0.8118V$
 - calculated = $0.7V$ (ideal diode)
- $V_c = 0.0909V$
 - calculated = $0.2V$
- $I(D1) = 51.11mA$
 - Close to $58.0mA$




Operation in the Active Region

If I_b is too small, then the transistor enters the active region (bad)

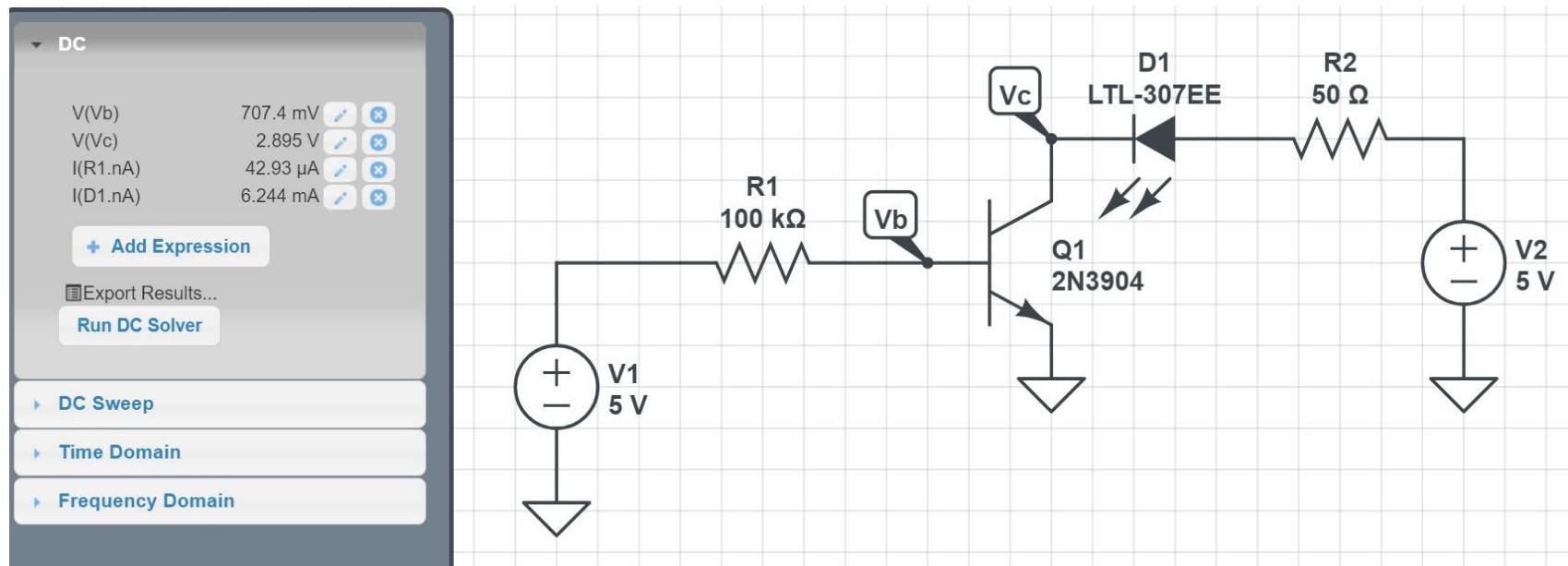Example: Increase R_b to 100k

- $I_b = 42.93\mu\text{A}$
- $I_c = \min(\beta I_b, \max(I_c)) = 6.21\text{mA}$
- $V_{ce} = 2.85\text{V}$ (active region)




What happens when you operate in the active region?

- $I_c < 58\text{mA}$
- The transistor gets hot
 - and can melt the breadboard

Avoid operating in the active region when using a transistor as a switch

- Keep $V_{ce} = 0.2\text{V}$ (ish)

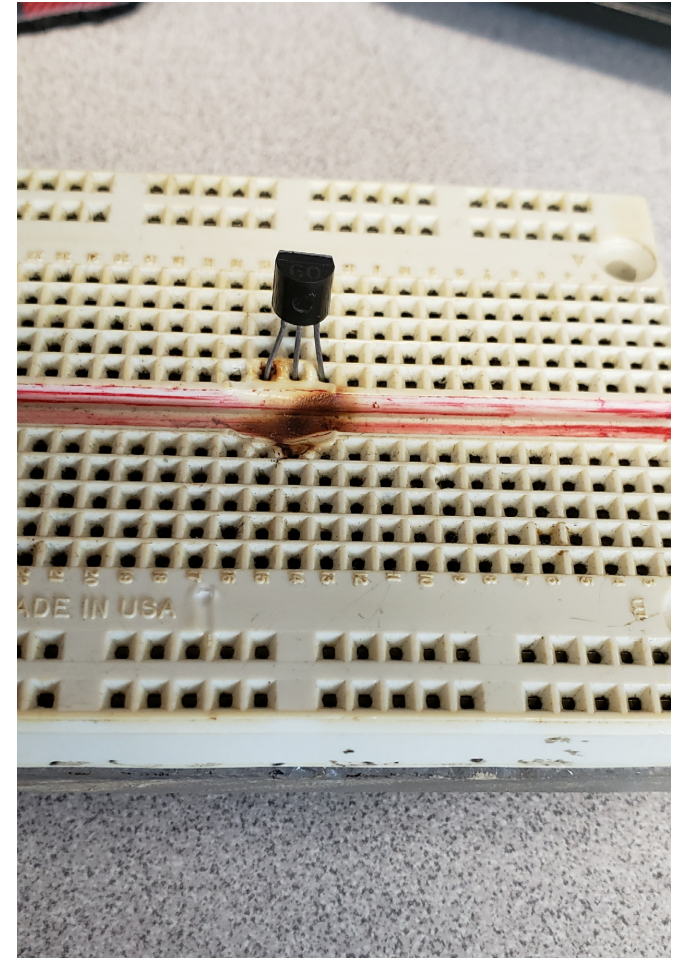


Design of Transistor Switches:

- Pick R_c to set the desired current
- Pick R_b to saturate the transistor
 - $I_b > I_c/100$

For example, design a circuit

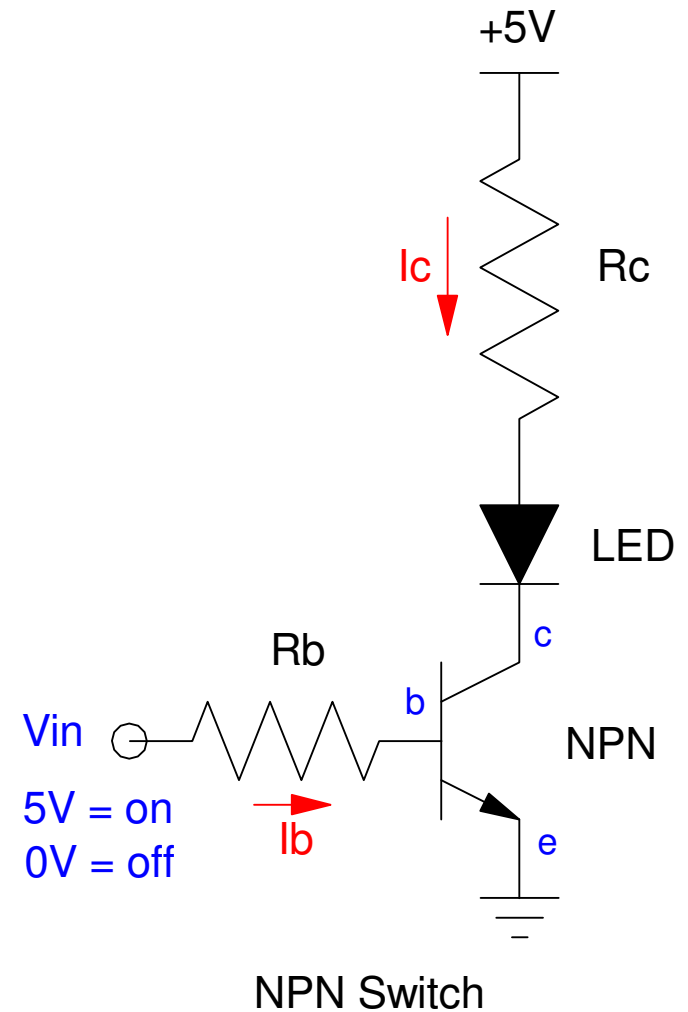- To turn on and off a red LED
- At 20mA when on,
- Using a 0V/5V input capable of driving at most 5mA.



Solution:

First pick R_c to set the current to 20mA

$$R_c = \left(\frac{5V - 1.9V - 0.2V}{20mA} \right) = 145\Omega$$

Next, pick I_b so that the transistor is saturated


$$I_b > \left(\frac{I_c}{100} \right) = 0.2mA$$

Let $I_b = 1mA$



$$R_b = \left(\frac{5V - 0.7V}{1mA} \right) = 4.3k\Omega$$

Same equations for a PNP switch

Resulting Circuit

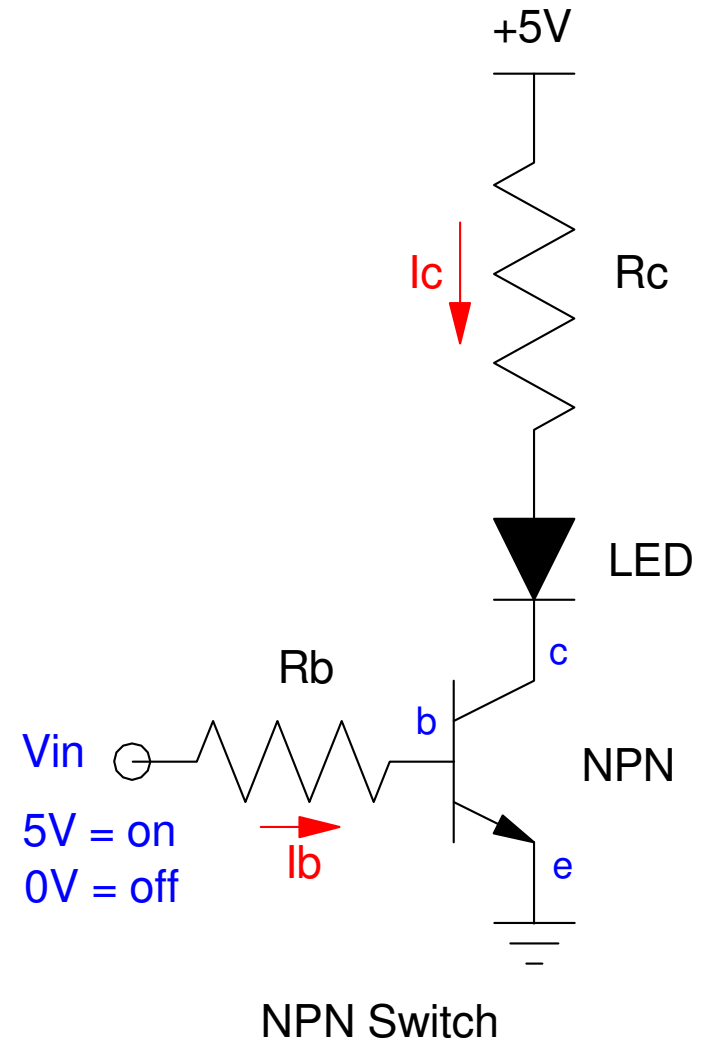

NPN & PNP Switch

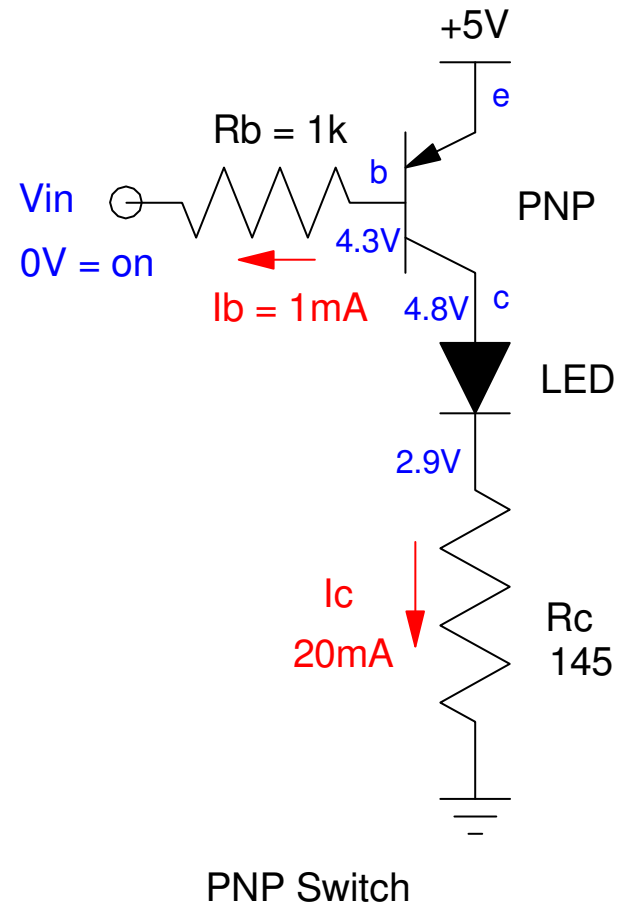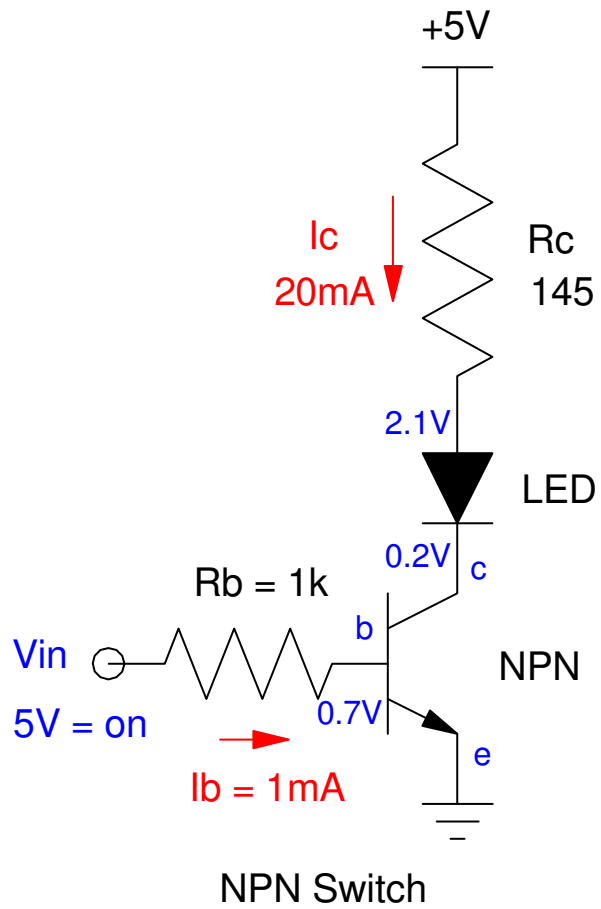

Homework #3:

Fill In Section #2: Requirements

- Engineering Requirements
- Gantt Chart

Engineering Requirements (partial list):

- Must operate off of 5VDC
- Must include at least one integrated circuit
- Must include at least one LED with $I_d = 20\text{mA} \pm 5\text{mA}$
- Must include at least one NPN and one PNP transistor
 - Base current allows 100mA
- Power supply = 9V battery (mark +/- polarity)
 - use a LM7805 regulator to drop 9V to 5V
- Must have a reverse-polarity protection diode
- Must have a 1/4 Watt 1-Ohm resistor in series with the power supply

(continued next page)

Update Section #3: Paper Design in your OneNote document

Include:

- Your circuit schematics
- Calculations for R's and C's
- Calculations for voltages you expect to see.

Note: If you're using a microprocessor, assume the output pins are either 0V or 5V.
