
Op-Amps & 555 Timers

ECE 401 Senior Design I

Week #4

Please visit Bison Academy for corresponding lecture notes,
homework sets, and videos
www.BisonAcademy.com



Operational Amplifiers (Op-Amps)

One of the requirements for your 401 project is it must include an integrated circuit (IC). Usually, this is an op-amp, a 555 timer, or a PIC processor.

Op-amps are really useful devices that can do all sorts of things. With op-amps, you can build

- Comparitors
- Schmitt Triggers
- Half-wave and full-wave rectifiers,
- Envelope detectors
- Amplifiers
- Filters

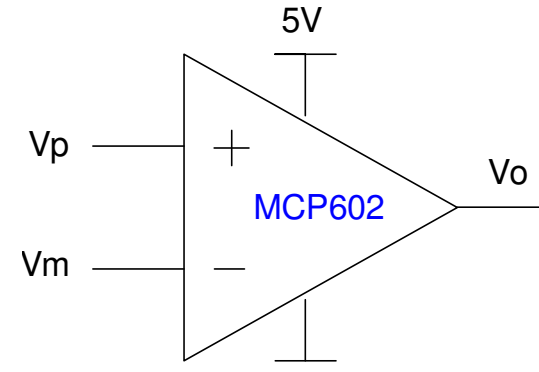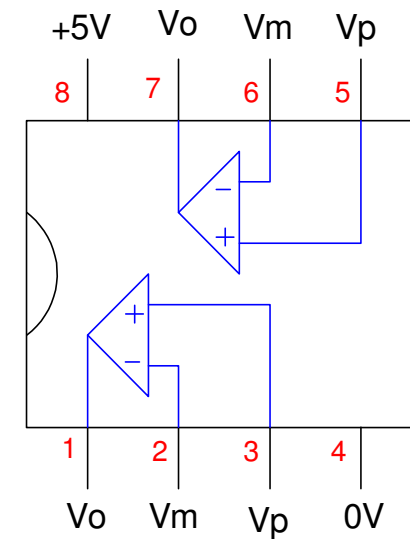to name just a few. Op-amps are just darn useful.



Op-Amps in CircuitLab

Two types of op-amps are available

- No power supply
 - Use for analog circuits (filters, amplifiers, etc)
- +/- Power Supply
 - Use for digital circuits (Comparitors, Schmitt Triggers)

The image shows the CircuitLab interface with a component library on the left and a configuration panel on the right. The library includes sections for Current Signal Sources, Operational Amplifiers, and Diodes. Two op-amp symbols are placed on a grid: a black triangle labeled 'OA1 LM741' and a red triangle labeled 'OA2 MCP602'. The configuration panel for the selected component (MCP602) is open, showing a list of op-amp models with 'MCP602' selected. The configuration fields are as follows:

Field	Value	Unit
name:	OA2	
Part#:	MCP602	
A_OL:	500e3	
GBW:	2.8e6	Hz
R_O:	30	Ω
I_B:	1p	A
R_IN:	1e13	Ω
SR:	2.3e6	V/s



Buttons for 'Save Custom Device Model', 'View All Op-Amps In Stock', 'Datasheet', and 'Buy' are also visible.

MCP602 Op-Amp

- The heart of a comparitor

Use an MCP602:

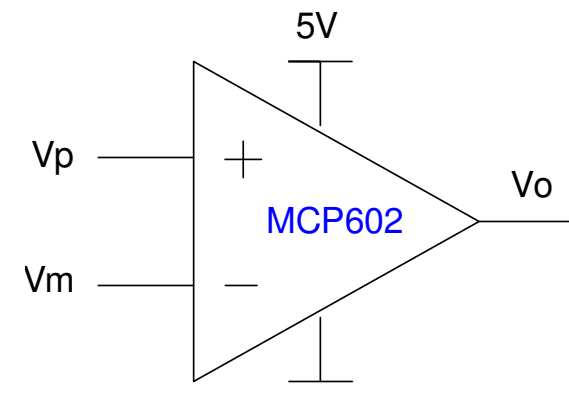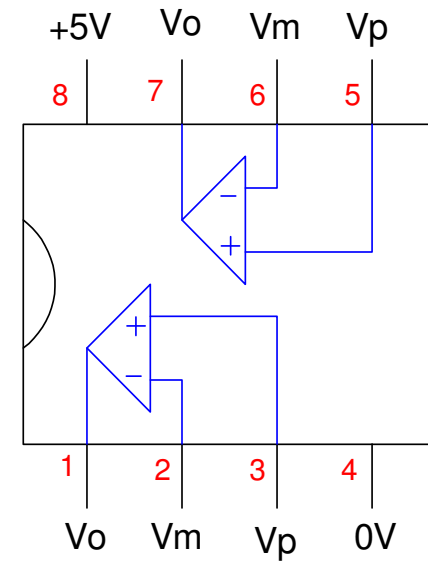- It can operate from a single 5V power supply
 - range is 3V to 6V
- It's a rail-to-rail op-amp.
 - Output can go all the way up to 5.00V
 - Output can go all the way down to 0.00V
- It's a dual op-amp
 - you get two op-amps in each IC




The MCP602 is a high-gain differential amplifier,
where

$$V_o = 200,000(V_p - V_m)$$

What this means is

- $V_p > V_m$
 - The output rails at the upper power supply (5V)
- $V_p < V_m$
 - The output rails at the lower power supply (0V)

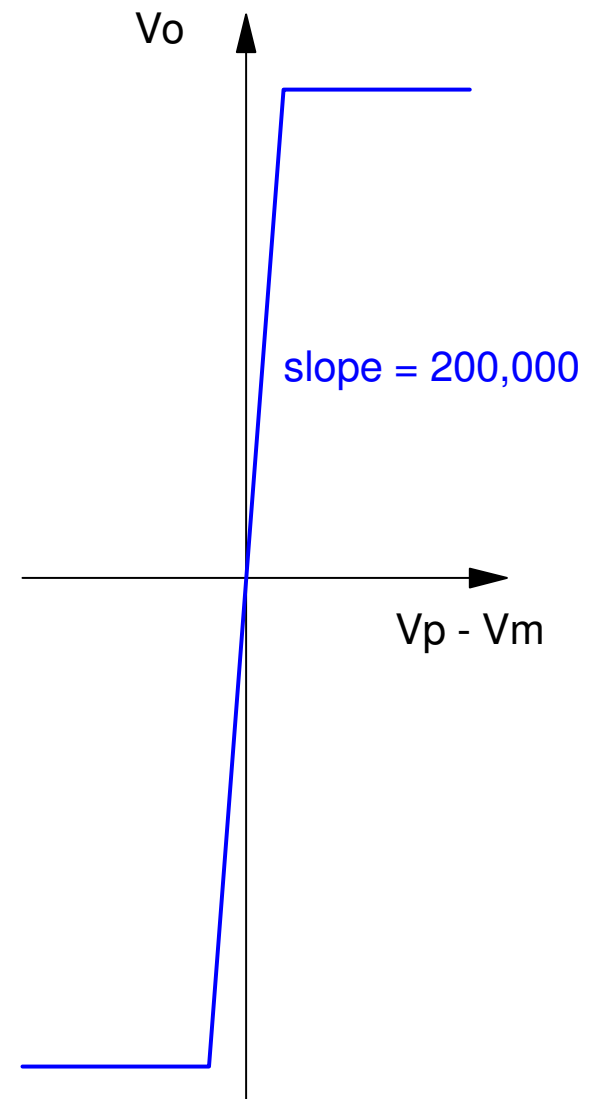This allows you to build several different circuits.




Comparator: $Y = (V_{in} > 2.3V)$

Turn on an LED when $V_{in} > 2.3V$


- Connect V_{in} to V_p
- Connect $2.3V$ to V_m
- This produces the function: $Y = V_{in} > 2.3V$

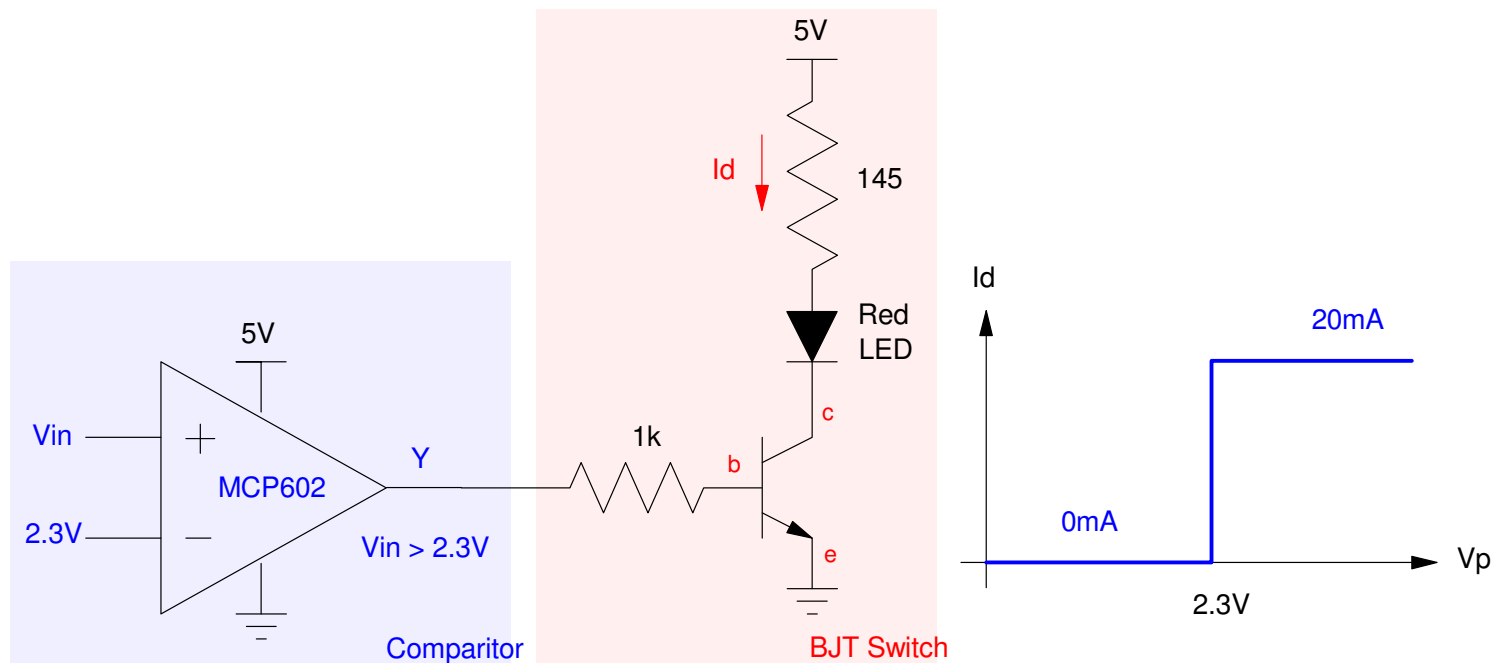If you swap V_p and V_m , you get the opposite ($V_{in} < 2.3V$)



Checking in CircuitLab

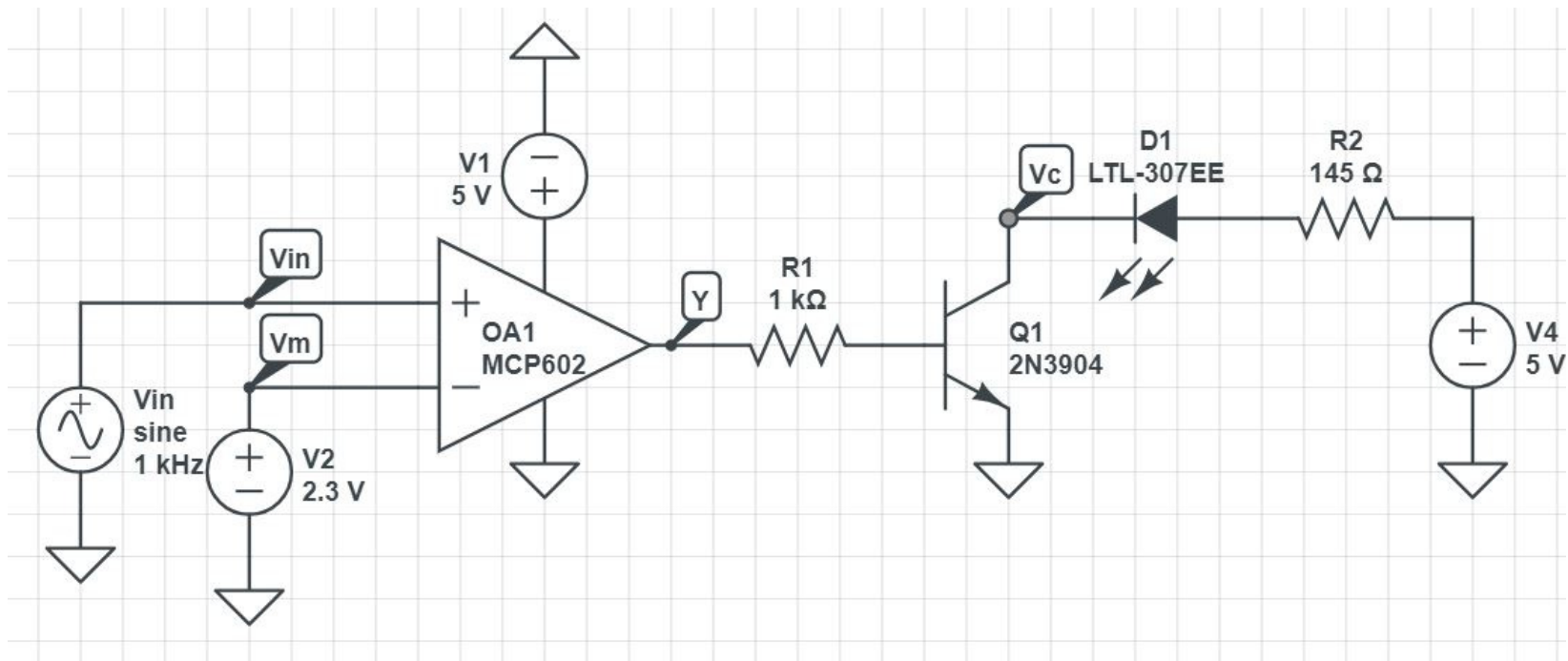- Use an op-amp with the voltage inputs
 - Tells CircuitLab what is logic 1 (5V) and 0 (0V).
- Use an AC input for V_{in} .
 - When $V_{in} > 2.3V$, Y slams to 5V.
 - When $V_{in} < 2.3V$, Y slams to 0V




Time-Domain Simulation

When $V_{in} > 2.3V$

- $V(Y) = 5V$ (on)
- $V_c = 0.2V$ (the transistor is saturated)

When $V_{in} < 2.3V$

- $V(Y) = 0V$ (off)
- $V_c = 5V$ (off)

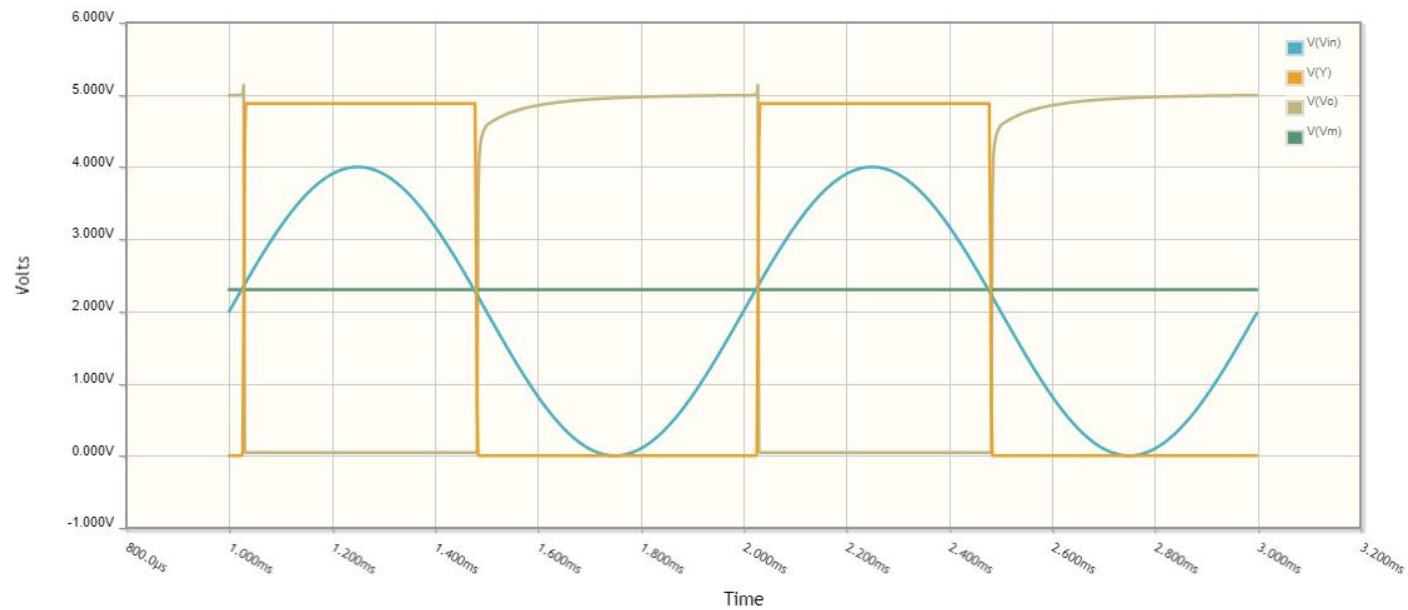

Comparitor: $Y = (T > 20C)$

First, convert temperature to resistance

$$R = 1000 \cdot \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

Convert resistance to voltage


$$V_x = \left(\frac{R}{R+1000}\right) 5V$$

Connect V_x to V_m

- As T goes up
- R goes down
- V_x goes down
- Y goes up


Connect V_p to $V_x(20C)$

- $R = 1250.59$ Ohms
- $V_x = 2.778V$

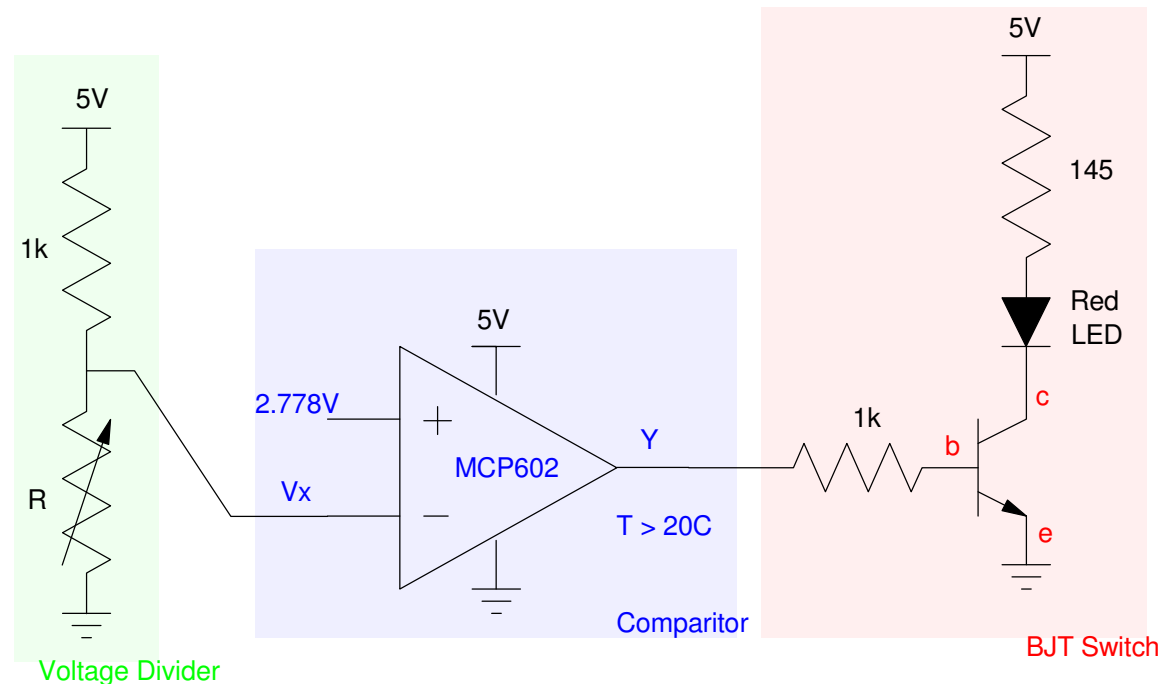

Note

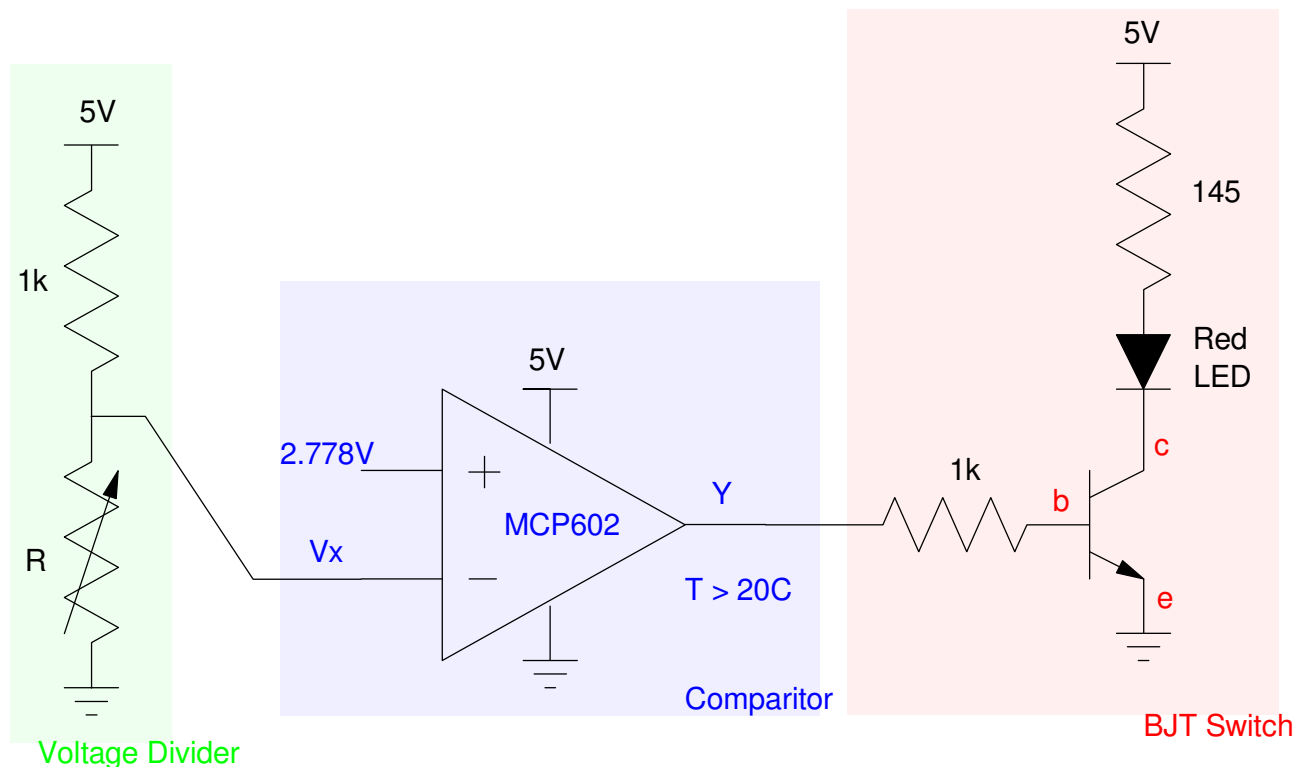- If you swap V_p and V_m , you get the opposite (light is on when $T < 20C$).
- If you change R to a light sensor, the LED turns on and off with light level
- If you change R to a magnetic field sensor, the LED turns on and off with magnetic field strength




Schmitt Triggers

Add hysteresis to avoid chatter

- Add positive feedback


$V(\text{on}) > V(\text{off})$

- Connect V_{in} to the plus input

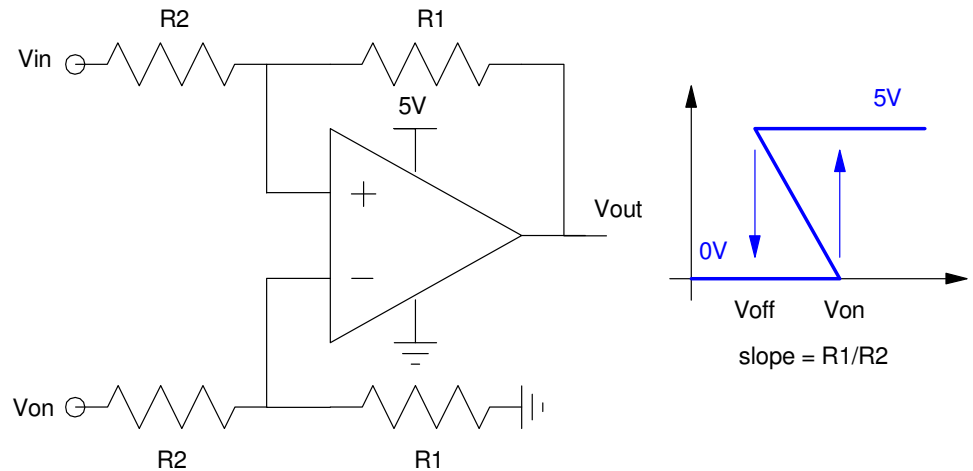

$V(\text{on}) < V(\text{off})$

- Connect V_{in} to the minus input

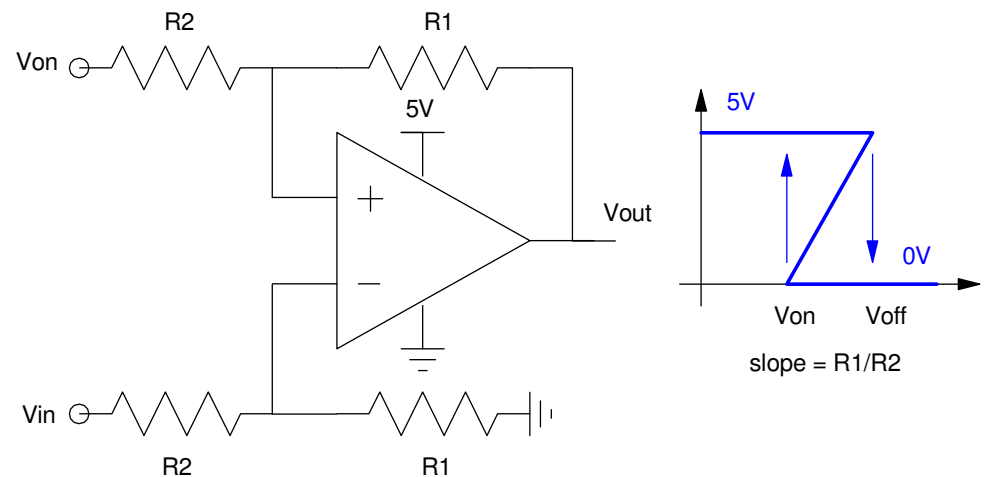

The offset is $V(\text{on})$ in both cases

Example: design a circuit which turns an LED

- On when $T > 25\text{C}$ and
- Off when $T < 20\text{C}$

When $20\text{C} < T < 25\text{C}$, the LED remains unchanged (on or off).

Step 1: Convert temperature to resistance

- Use a thermistor

$$R = 1000 \exp\left(\frac{3905}{T+273} - \frac{3905}{298}\right) \Omega$$

Step 2: Convert resistance to voltage

- Use a voltage divider with a 1k resistor


$$V_x = \left(\frac{R}{R+1000}\right) 5V$$

20C	25C
$R = 1250$	$R = 1000$
$V_x = V_{\text{off}} = 2.778V$	$V_x = V_{\text{on}} = 2.500V$

Since $V_{on} < V_{off}$, connect to the minus input

$$gain = \left(\frac{\text{change in output}}{\text{change in input}} \right)$$
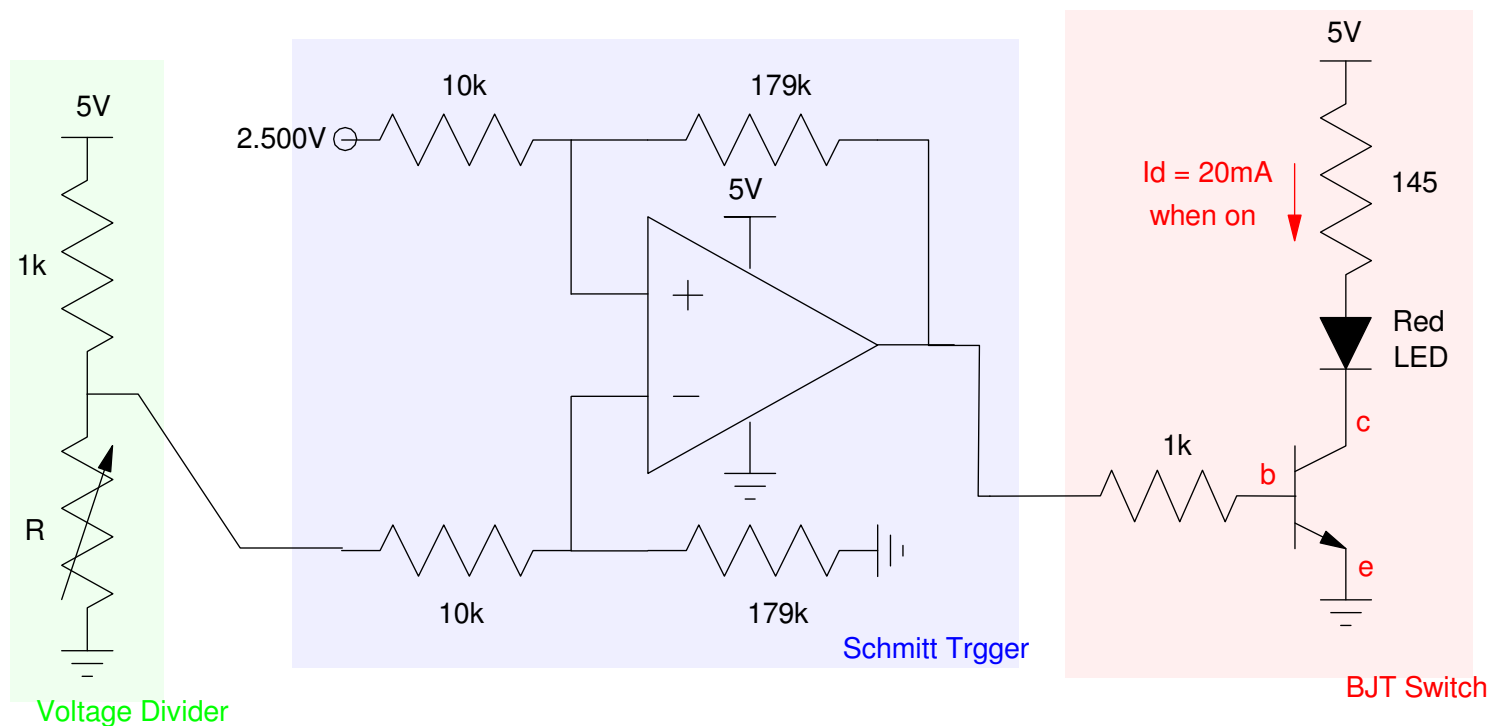
$$gain = \left(\frac{5V - 0V}{2.778V - 2.500V} \right) = 17.96$$




555 Timers

Really useful IC that can make

- An oscillator
 - Keep track of time, make lights blink, etc.
- An light controlled oscillator
 - Frequency varies with light level
 - Or temperature, magnetic field strength, etc.
- A voltage-controlled oscillator
 - Allowing you to make siren noises, and
- A one-shot
 - Output a single pulse

This course looks at an oscillator

- See ECE 320 for other circuits

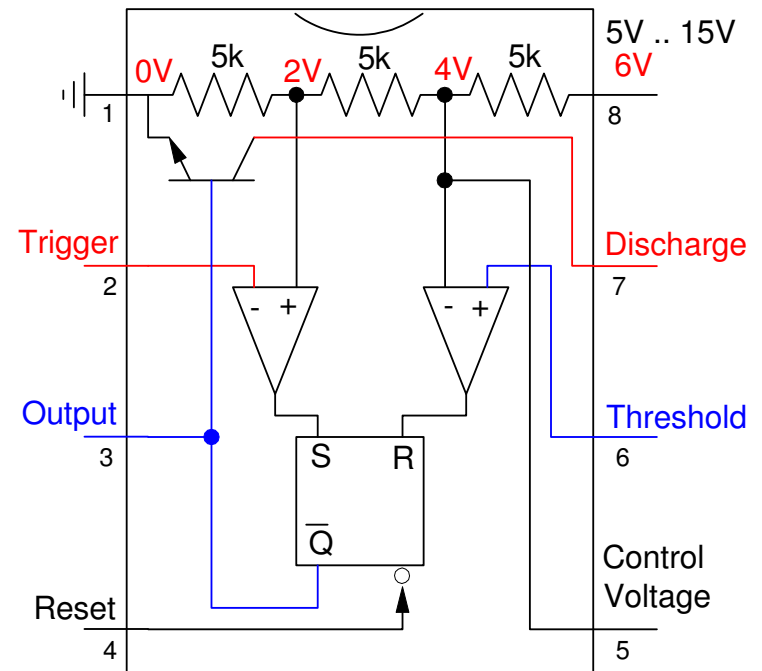


555 Timer:

Name comes from three 5k resistors

Function of Pins:

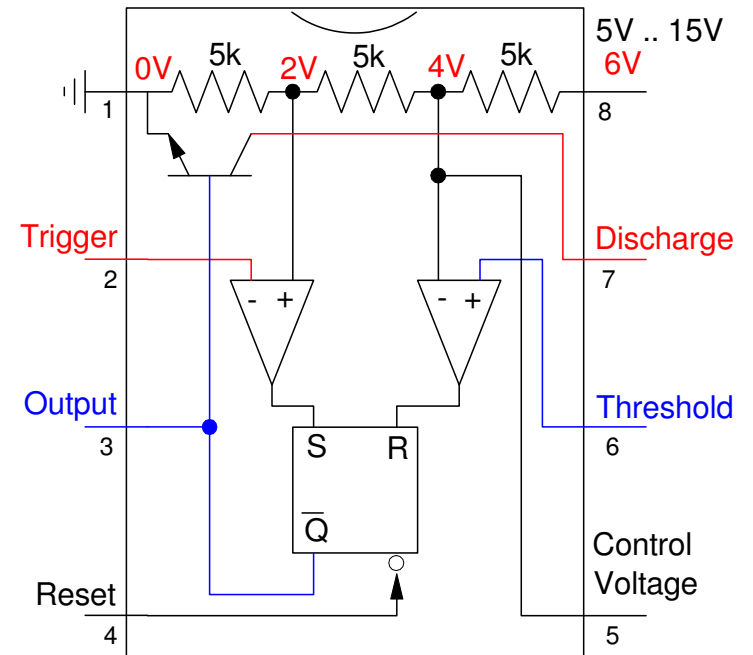- Power and Ground: 0V and 5V
- Trigger: Set the SR flip-flop $> 2V$
- Threshold: Clear the SR flip-flop when $> 4V$
- Control Voltage: Change the threshold voltage
- Discharge:
 - When the output is low, Discharge is shorted to ground through a transistor.
 - Otherwise, Discharge is a floating pin.



555 Oscillator (take 1):



When V_2 reaches $1/3$ of $5V$

- Discharge is floating,
- C charges up to $2/3$ of $5V$ through $R1$ and $R2$.

When V_2 reaches $2/3$ of $5V$

- Discharge is grounded
- C discharges down to $1/3$ of $5V$ through $R2$

Repeat

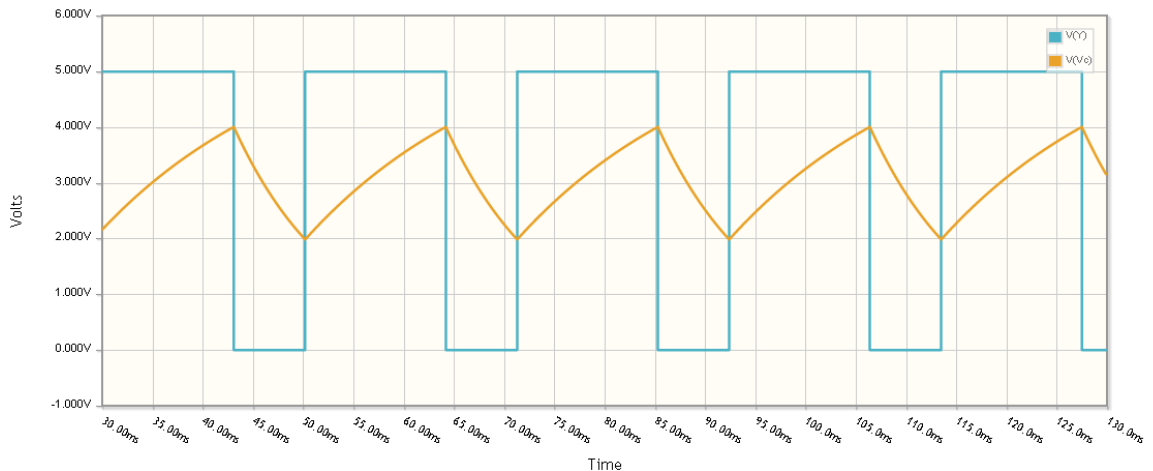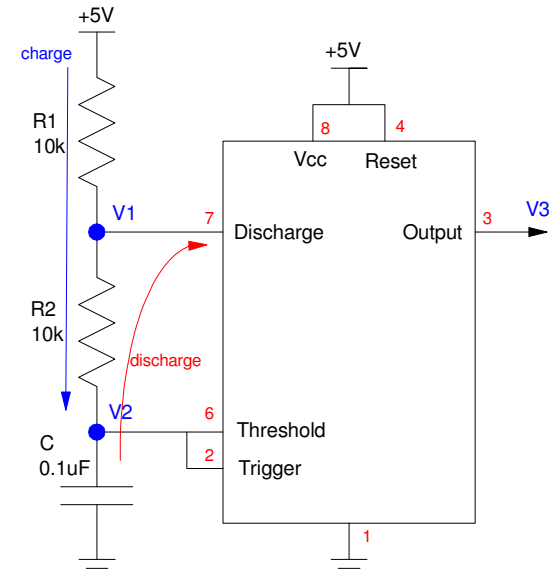

Calculations:

$$T_{on} = (R_1 + R_2) \cdot C \cdot \ln(2)$$

$$T_{off} = R_2 \cdot C \cdot \ln(2)$$

$$T = \text{Period} = T_{on} + T_{off} = (R_1 + 2R_2) \cdot C \cdot \ln(2)$$


For the values given, this works out to

$$T_{on} = 1.386ms$$

$$T_{off} = 0.693ms$$


$$T = \text{Period} = 2.079ms$$

$$f = \frac{1}{T} = 480.9Hz$$

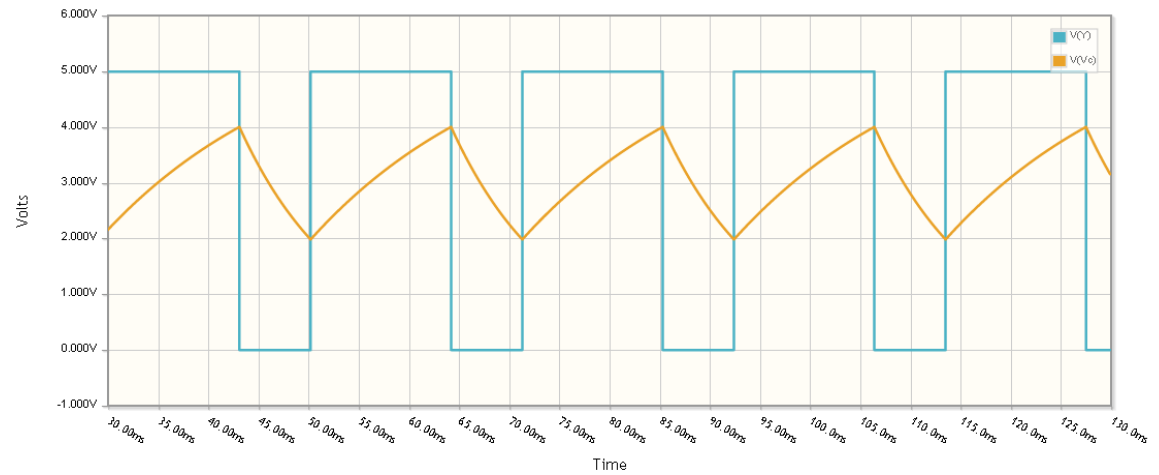

Note

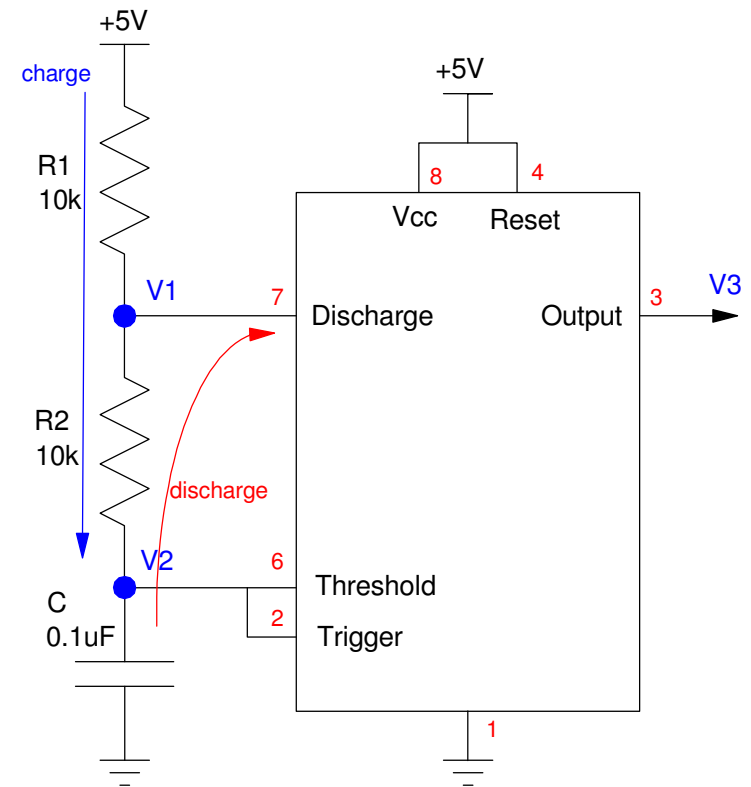
- The on time is twice as large as the off time. This is due to C charging through R1 and R2, while discharging through R2.
- If you replace either resistor with a thermistor or a photo-resistor, the period (and frequency) will change with temperature or light.



555 Oscillator (take 2):

A slight improvement is to add a diode as follows. This results in

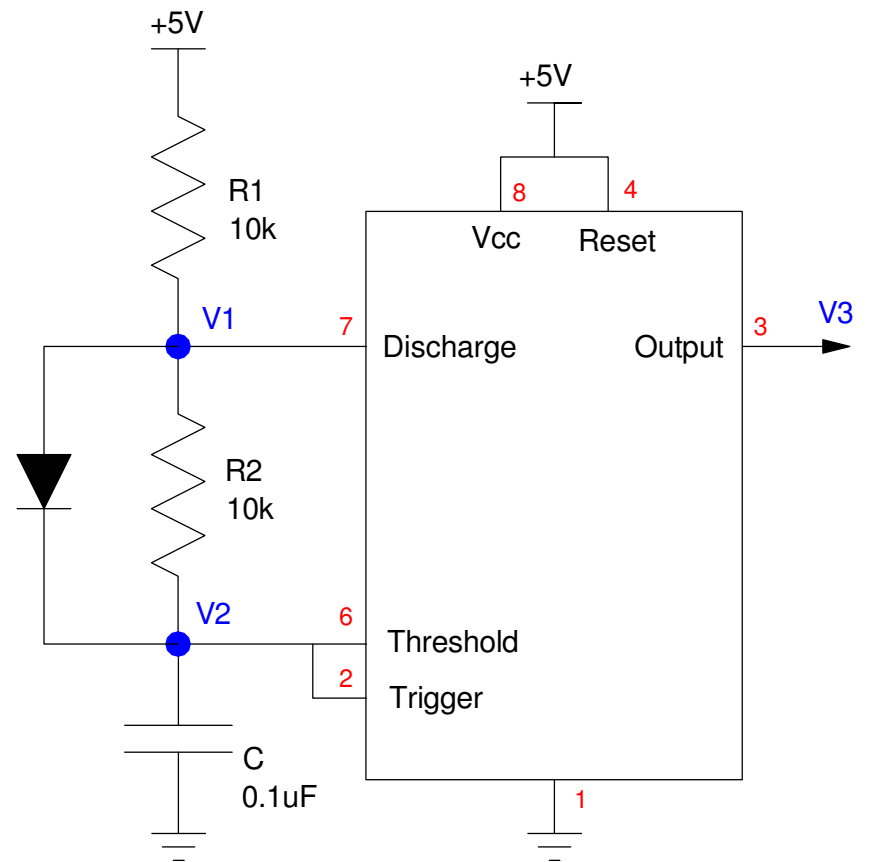- C charging through R1 (R2 is bypassed by the diode), and
- C discharging through R2 (when pin 7 of the 555 timer is grounded).



Calculations

$$T_{on} \approx R_1 \cdot C \cdot \ln(2)$$

$$T_{off} = R_2 \cdot C \cdot \ln(2)$$

If $R_1 = R_2 = 10k$


$$T_{on} \approx 0.693ms$$

$$T_{off} = 0.693ms$$

$$T = T_{on} + T_{off} = 1.386ms$$


$$f = \frac{1}{T} = 721.3Hz$$

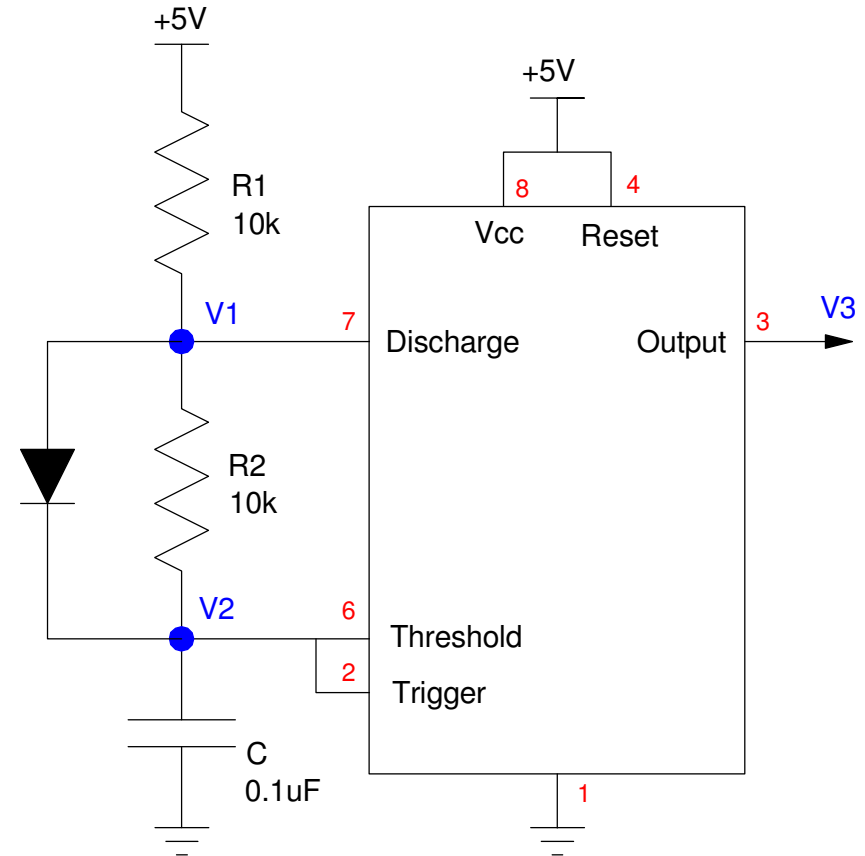note: $T(on)$ is approximate due to ignoring V_d in the calculations for T_{on}




Checking in CircuitLab

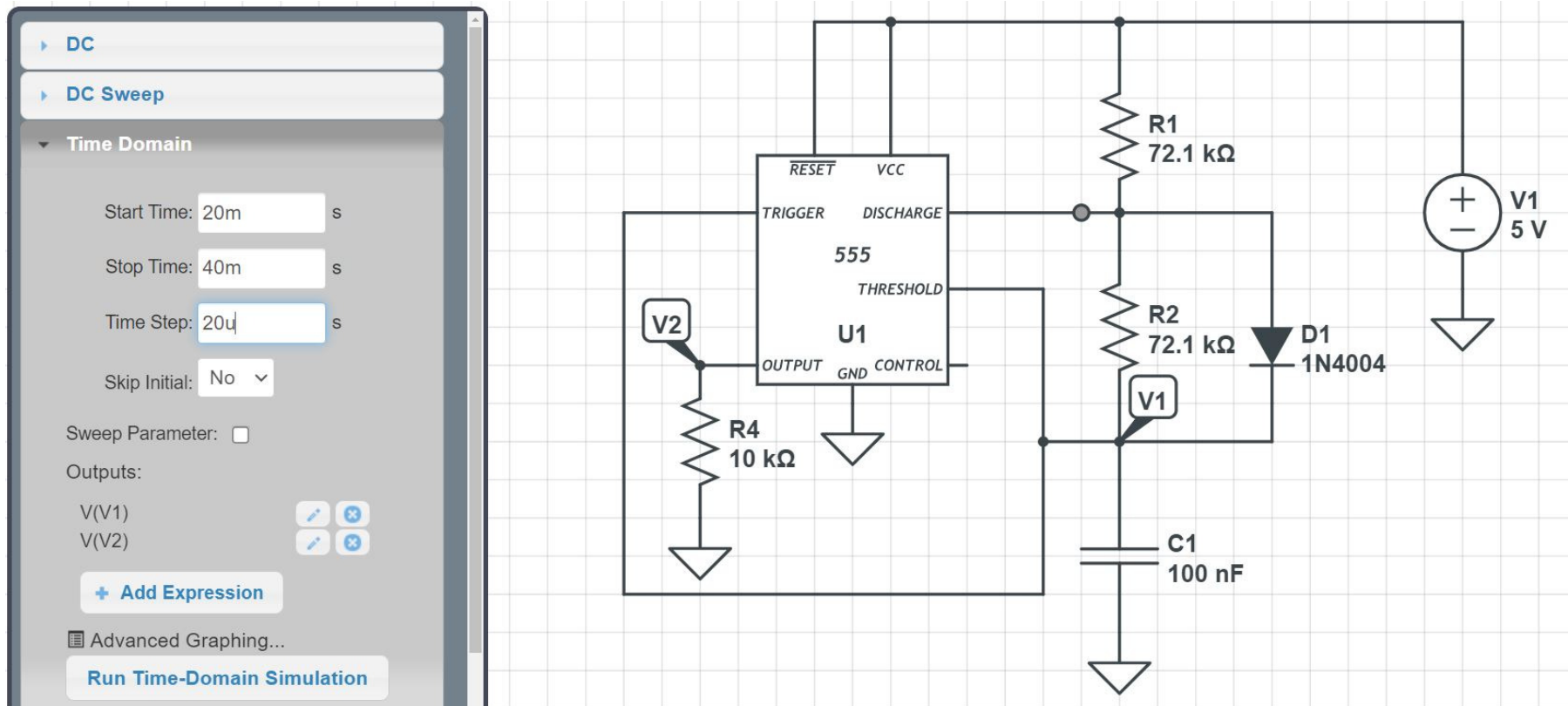Build the circuit and do a time-domain simulation:



Measure the on/off times

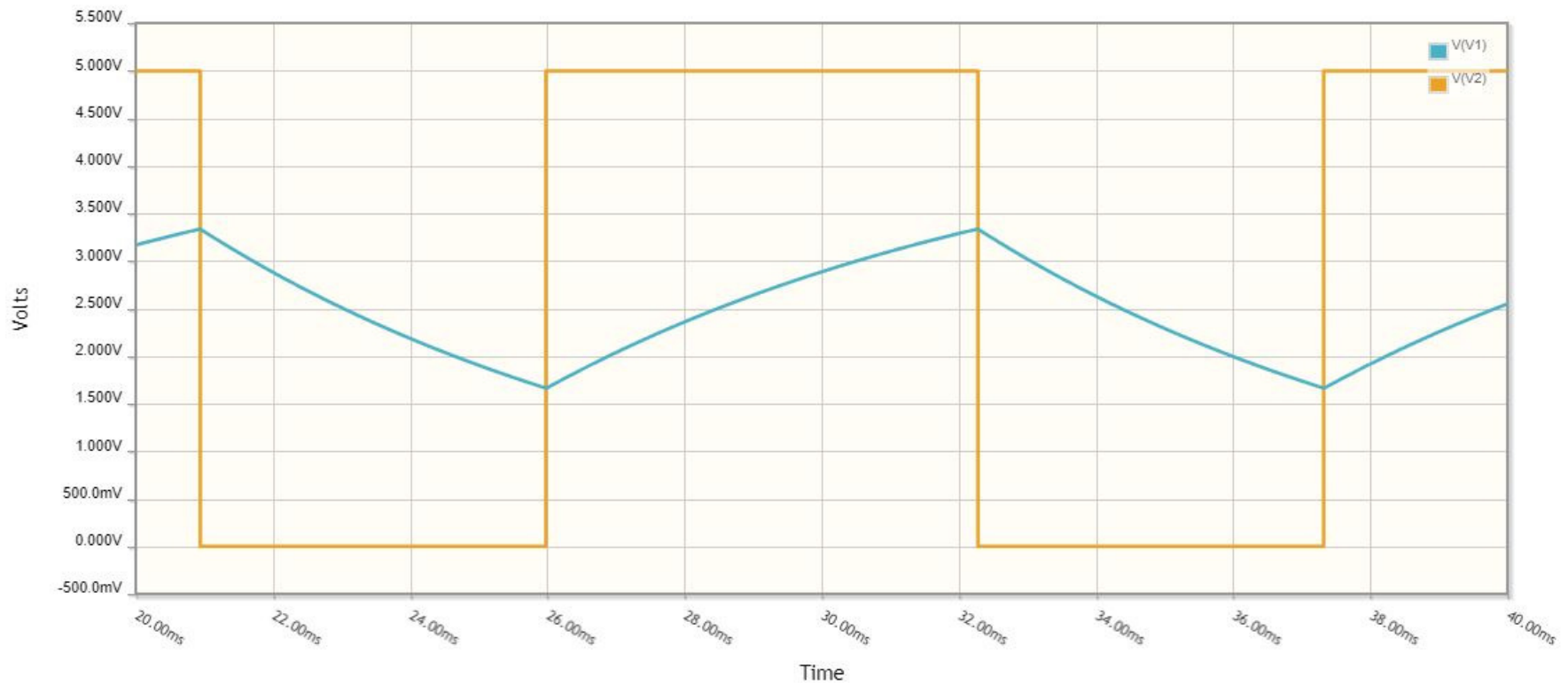- $T(\text{on}) = 6.824\text{ms}$
- $T(\text{off}) = 5.04\text{ms}$
- Not quite 5.00ms due to the diode when charging (T_{on})



Adjust R1 to bring T(on) to 5.00ms

Iteration #1

$$R_1 \rightarrow \left(\frac{5ms}{6.824ms} \right) 72.13k = 52.85k\Omega$$

Rerun the simulation and you get T(on) = 4.64ms. Iterate again...


$$R_1 \rightarrow \left(\frac{5ms}{4.64ms} \right) 52.85k\Omega = 56.95k\Omega$$

T(on) = 5.04ms

- C = 0.1uF
- R1 = 56.95k
- R2 = 72.13k

Note:

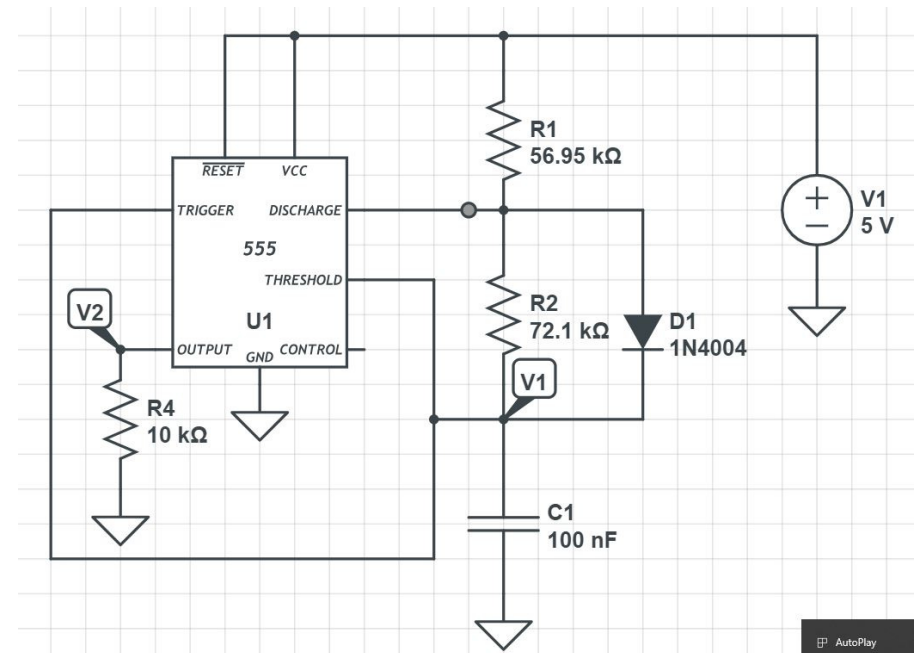- Calculations get you close
- You may need to tweak values



LED Brightness Control

Vary R1 and R2 to change the on / off times

- Replace R1 and R2 with a potentiometer allows adjustment of the duty cycle

