

ECE 463/663 - Homework #2

State-Space, Eigenvalues, Eigenvectors. Due Monday, Jan 22nd

1) For the following RLC circuit


- Specify the dynamics for the system (write N coupled differential equations)
- Express these dynamics in state-space form
- Determine the transfer function from V_0 to V_2

2) For the transfer function from V_0 to V_2

- Determine a 1st or 2nd-order approximation for this transfer function
- Plot the step response of the actual 5th-order system and its approximation

3) For this circuit


- What initial condition will the energy in the system decay as slowly as possible?
- What initial condition will the energy in the system decay as fast as possible?

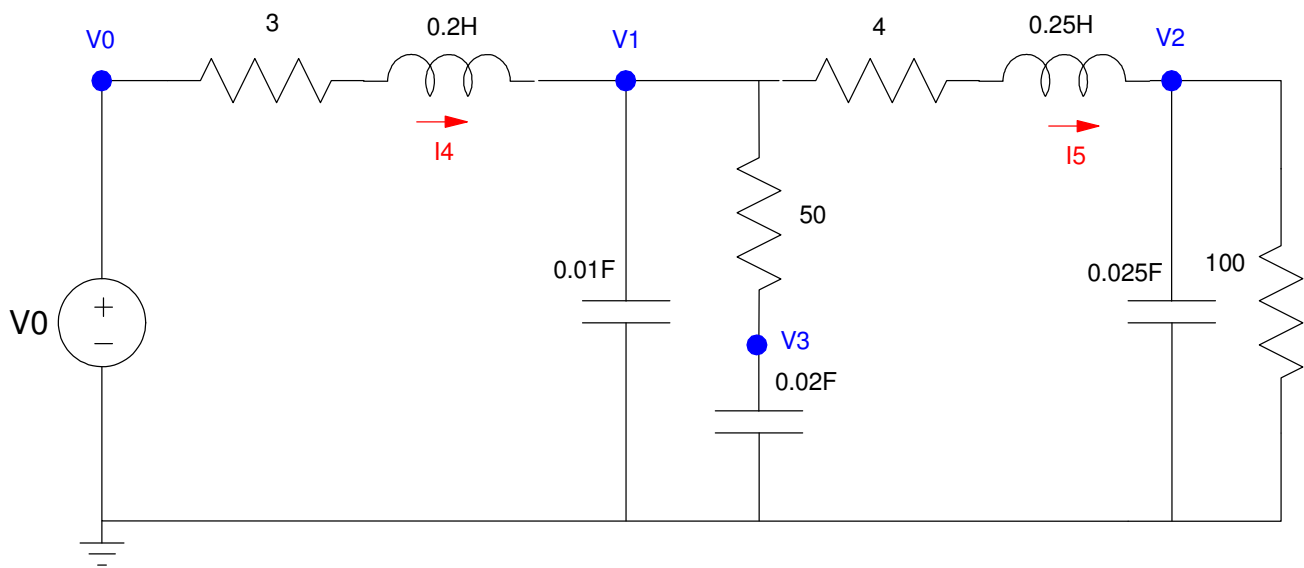

Problem 1 - 3

Problem 4 - 7 (over)

Problem 4-7: 10-Stage RC Filter.

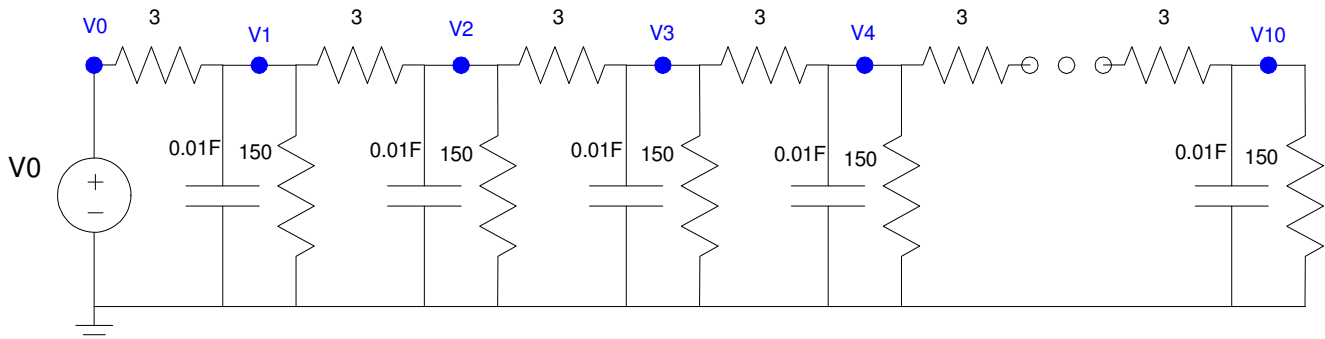

Problems 4-7

4) For the 10-stage RC circuit

- Specify the dynamics for the system (write N coupled differential equations)
 - note: Nodes 1..9 have the same form. Just write the node equation for node 1 and node 10.
- Express these dynamics in state-space form
- Determine the transfer function from V0 to V10

5) For the transfer function for problem #4

- Determine a 2nd-order approximation for this transfer function
- Plot the step response of the actual 10th-order system and its 2nd-order approximation

6) For the circuit for problem #4

- What initial condition will decay as slowly as possible?
- What initial condition will decay as fast as possible?

7) Modify the program *heat.m* to match the dynamics you calculated for this problem.

- Give the program listing
- Give the response for $V_{in} = 0$ and the initial conditions being
 - The slowest eigenvector
 - The fastest eigenvector
 - A random set of voltages